

B.Tech III Year II Semester (R13) Regular & Supplementary Examinations May/June 2017

POWER SEMICONDUCTOR DRIVES

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- Draw the speed Vs torque and power characteristics of a separately excited DC motor.
 - Mention the two drawbacks if armature current in a DC motor is discontinuous.
 - When do you use controlled converter in the armature circuit and fixed excitation voltage in field winding?
 - Mention the two methods of chopper control.
 - Mention the two advantages of AC drives.
 - What condition to be satisfied to work a DC motor in regenerative braking mode?
 - Mention the two methods which are applicable for speed control of squirrel cage I.M.
 - What is the need of v/f control in an I.M?
 - What is the effect on p.f at starting and power input to the motor when an IM is operated with reduced voltage and frequency operation?
 - What are the two possible modes of operation is possible through cycloconverters?

PART – B
(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- 2 With relevant circuit diagram, explain the principle of operation of 3 ϕ Full Converter fed DC drive.

OR

- 3 A separately excited DC motor, operating from a 1 ϕ half controlled converter at a speed of 140 rpm, has an input voltage of $330 \sin 314t$ and a back emf 80 V. The SCR's are fired symmetrically at $\alpha = 30^\circ$ in every half cycle and the armature has a resistance of 4 Ω . Calculate the average armature current and the motor torque.

UNIT – II

- 4 With necessary diagram, explain the four quadrant operation of a DC drive and mention the conditions to be satisfied in each quadrant.

OR

- 5 With relevant circuit and operating characteristics, explain the operation of 1 ϕ dual converter fed DC drive.

UNIT – III

- 6 With relevant circuit and waveforms, explain the motoring control of DC chopper fed series motor drive.

OR

- 7 A DC chopper is used for regenerative braking of a separately excited DC motor. The supply input voltage is 400 V, $R_a = 0.2 \Omega$, $K_m = 1.2$ V-sec/rad. The average armature current during regenerative braking is kept constant at 300 A. For a duty cycle of 60% of chopper, determine the following: (i) Power returned to supply. (ii) Minimum and maximum braking speeds. (iii) Speed during regenerative braking.

UNIT – IV

- 8 With the help of block diagram, explain the closed loop operation of IM drive including both current and speed loop.

OR

- 9 With relevant circuit and characteristics, explain the operation of Static Kramer drive.

UNIT – V

- 10 Draw the circuit diagram and explain the operation of Self Controlled Synchronous motor drive employing load commutated inverter.

OR

- 11 A 6 MW, 3-phase, 11 KV, y-connected, 6-pole, 50 Hz, 0.9 leading p.f synchronous motor has $X_s = 9 \Omega$ and $R_s = 0$. Rated field current is 50 A, machine is controlled by variable frequency control at constant (v/f) ratio up to the base speed and at constant voltage above base speed. Determine torque and field current for the rated armature current at 0.8 leading p.f.
