

Code No: 07A30401

R07**Set No. 2**

II B.Tech I Semester Examinations, November 2010

PULSE AND DIGITAL CIRCUITSCommon to Electronics And Instrumentation Engineering, Electrical And
Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Define the following:
 - i. Storage time
 - ii. Delay time
 - iii. Rise time
 - iv. Fall time
- (b) Explain how a BJT can be used as a switch. Compare its performance as a switch with JFET. [8+8]
2. (a) Describe frequency division employing a transistor astable multivibrator with waveforms.
- (b) Describe frequency division employing a transistor monostable multivibrator with waveforms. [8+8]
3. (a) What is pedestal? Illustrate the effect of control voltage on gate output.
- (b) Write the advantages and disadvantages of unidirectional diode gate. [16]
4. (a) Draw the circuit diagram of diode-transistor logic NOR gate and explain its operation.
- (b) Draw the output waveform X for the given inputs figure 3b

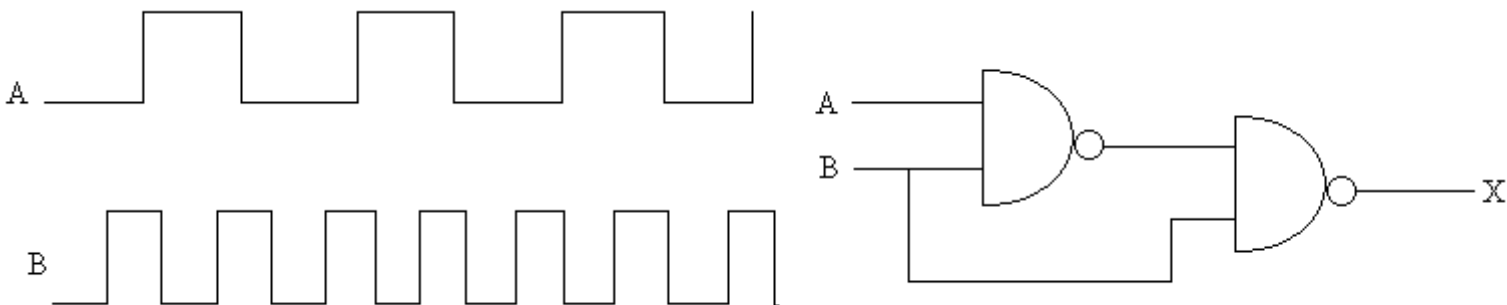


Figure 3b

5. Consider a self-biased nonsaturated flip-flop obtained from figure 2 by setting $V_{BB}=0$ and by adding a common emitter resistor R_e to ground in figure 2. The circuit has the following parameters: $V_{CC}=25V$, $V_Z=4.3V$, $h_{FE}=50$, $R_C=2.2K$, $R_1=R_2=15K$ and $R_e=470\Omega$. Neglect the voltage drop across a forward-biased junction. Verify that the transistors do not enter the saturation region. Calculate the transistor

Code No: 07A30401

R07**Set No. 2**

currents and the current in each diode.

[16]

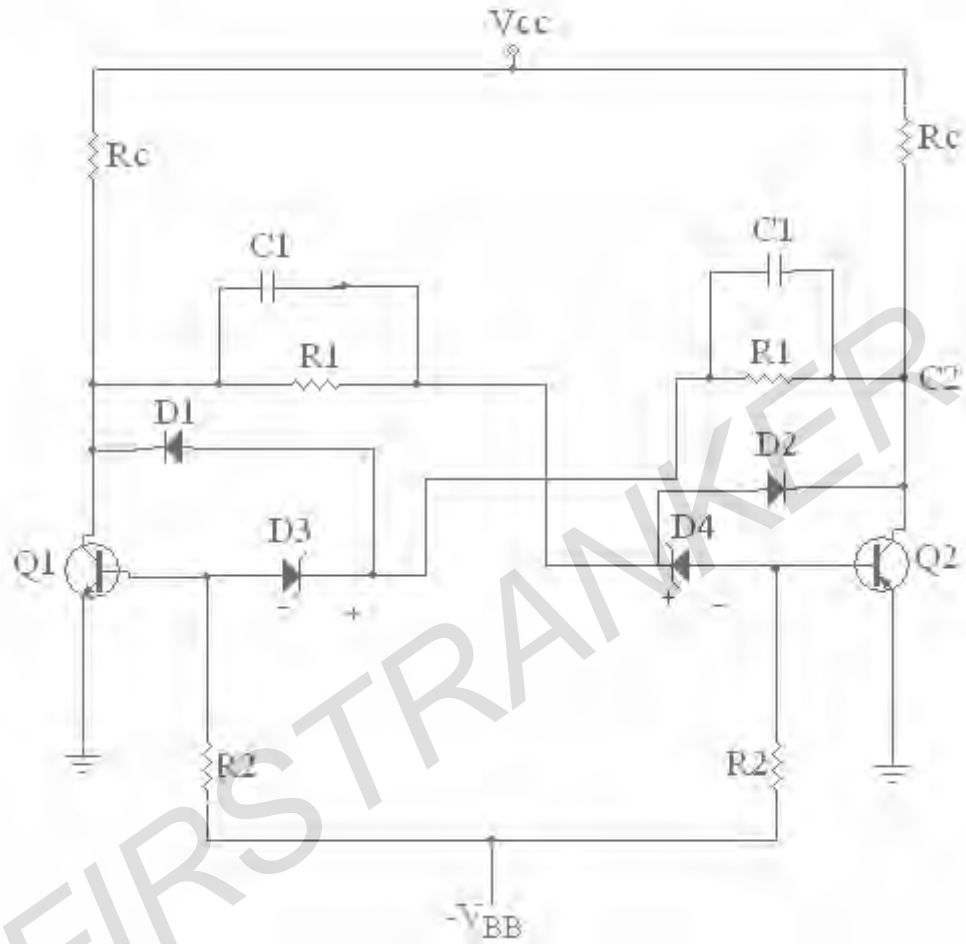


Figure 2

6. (a) Design a diode clamper to restore a d.c level of +3 Volts to an input sinusoidal signal of peak value 10Volts. Assume drop across diode is 0.6 volts as shown in the figure 4a.

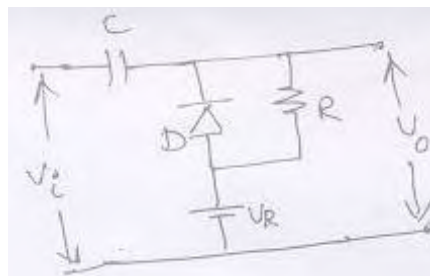


Figure 4a

- (b) Compare series diode clipper and shunt diode clipper. [8+8]
7. (a) List out the applications of sweep circuits.
- (b) Distinguish between voltage and current sweep circuits.
- (c) Draw the circuit of a linear current sweep and explain its operation with waveforms. Explain the necessity of generating trapezoidal waveform. [4+4+8]

Code No: 07A30401

R07**Set No. 2**

8. (a) Obtain the response of RC high pass circuit for an exponential i/p signal
- (b) A square wave whose peak-to-peak value is 1 V, extends $\pm 0.5V$ w.r.t. to ground. The half period is 0.1 Sec this voltage impressed upon an RC differentiating circuit whose time constant is 0.2 sec. Determine the maximum and minimum values of the o/p voltages in the steady state. [8+8]

FIRSTRANKER

Code No: 07A30401

R07**Set No. 4**

II B.Tech I Semester Examinations, November 2010

PULSE AND DIGITAL CIRCUITSCommon to Electronics And Instrumentation Engineering, Electrical And
Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Draw the circuit diagram of diode-transistor logic NOR gate and explain its operation.
- (b) Draw the output waveform X for the given inputs figure 3b

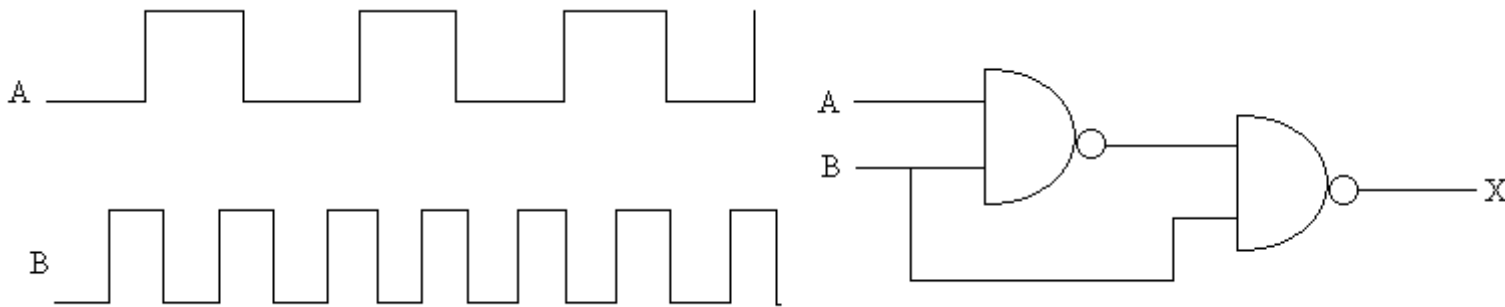


Figure 3b

2. (a) What is pedestal? Illustrate the effect of control voltage on gate output.
- (b) Write the advantages and disadvantages of unidirectional diode gate. [16]
3. (a) Describe frequency division employing a transistor astable multivibrator with waveforms.
- (b) Describe frequency division employing a transistor monostable multivibrator with waveforms. [8+8]
4. (a) Define the following:
 - i. Storage time
 - ii. Delay time
 - iii. Rise time
 - iv. Fall time
- (b) Explain how a BJT can be used as a switch. Compare its performance as a switch with JFET. [8+8]
5. (a) Obtain the response of RC high pass circuit for an exponential i/p signal
- (b) A square wave whose peak-to-peak value is 1 V, extends $\pm 0.5V$ w.r.t. to ground. The half period is 0.1 Sec this voltage impressed upon an RC differentiating circuit whose time constant is 0.2 sec. Determine the maximum and minimum values of the o/p voltages in the steady state. [8+8]

Code No: 07A30401

R07**Set No. 4**

6. Consider a self-biased nonsaturated flip-flop obtained from figure 2 by setting $V_{BB}=0$ and by adding a common emitter resistor R_e to ground in figure 2. The circuit has the following parameters: $V_{CC}=25V$, $V_Z=4.3V$, $h_{FE}=50$, $R_c=2.2K$, $R_1=R_2=15K$ and $R_e=470\Omega$. Neglect the voltage drop across a forward-biased junction. Verify that the transistors do not enter the saturation region. Calculate the transistor currents and the current in each diode. [16]

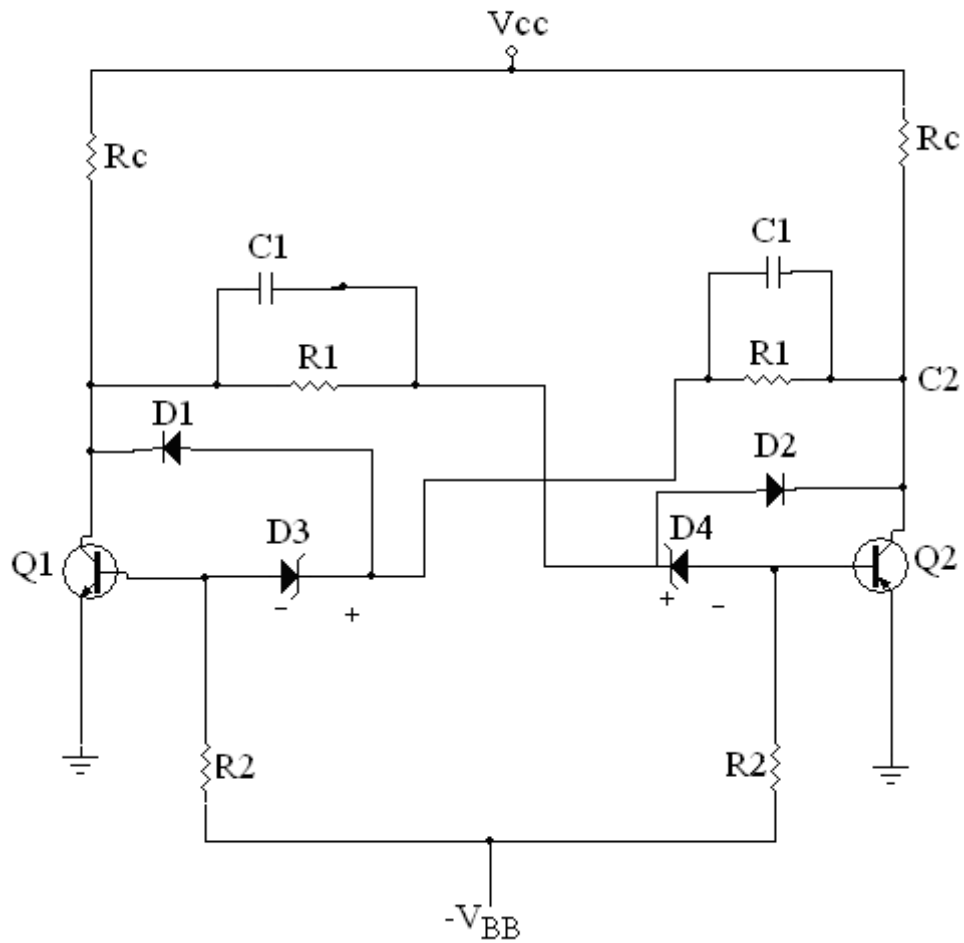


Figure 2

7. (a) Design a diode clamper to restore a d.c level of +3 Volts to an input sinusoidal signal of peak value 10Volts. Assume drop across diode is 0.6 volts as shown in the figure 4a.

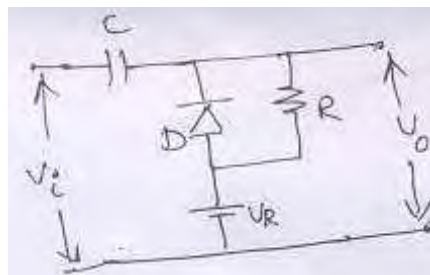


Figure 4a

- (b) Compare series diode clipper and shunt diode clipper.

[8+8]

Code No: 07A30401

R07

Set No. 4

8. (a) List out the applications of sweep circuits.
(b) Distinguish between voltage and current sweep circuits.
(c) Draw the circuit of a linear current sweep and explain its operation with waveforms. Explain the necessity of generating trapezoidal waveform. [4+4+8]

FIRSTRANKER

Code No: 07A30401

R07**Set No. 1**

II B.Tech I Semester Examinations, November 2010

PULSE AND DIGITAL CIRCUITSCommon to Electronics And Instrumentation Engineering, Electrical And
Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Obtain the response of RC high pass circuit for an exponential i/p signal
(b) A square wave whose peak-to-peak value is 1 V, extends $\pm 0.5V$ w.r.t. to ground. The half period is 0.1 Sec this voltage impressed upon an RC differentiating circuit whose time constant is 0.2 sec. Determine the maximum and minimum values of the o/p voltages in the steady state. [8+8]
2. (a) What is pedestal? Illustrate the effect of control voltage on gate output.
(b) Write the advantages and disadvantages of unidirectional diode gate. [16]
3. (a) Describe frequency division employing a transistor astable multivibrator with waveforms.
(b) Describe frequency division employing a transistor monostable multivibrator with waveforms. [8+8]
4. (a) Draw the circuit diagram of diode-transistor logic NOR gate and explain its operation.
(b) Draw the output waveform X for the given inputs figure 3b

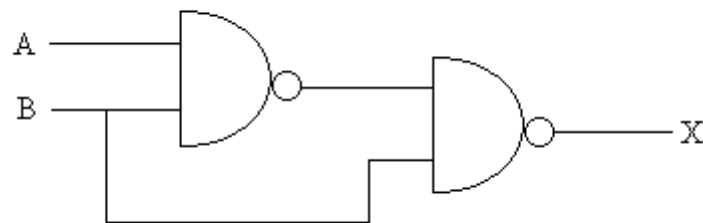
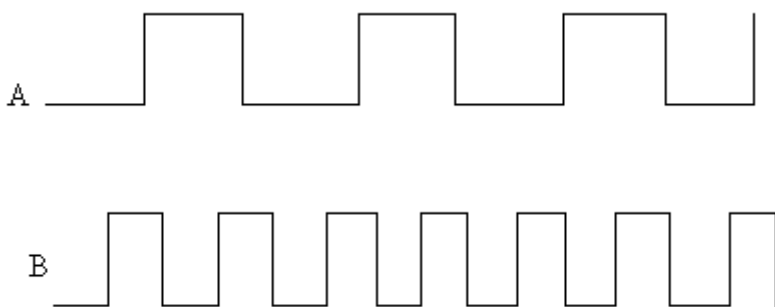


Figure 3b

5. (a) Design a diode clamper to restore a d.c level of +3 Volts to an input sinusoidal signal of peak value 10Volts. Assume drop across diode is 0.6 volts as shown in the figure 4a.

Code No: 07A30401

R07

Set No. 1

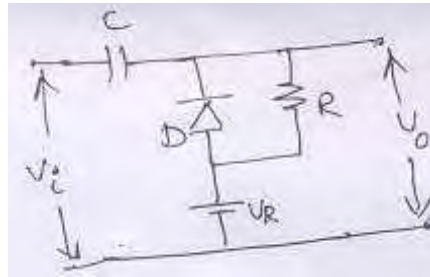


Figure 4a

- (b) Compare series diode clipper and shunt diode clipper. [8+8]
6. (a) List out the applications of sweep circuits.
 (b) Distinguish between voltage and current sweep circuits.
 (c) Draw the circuit of a linear current sweep and explain its operation with waveforms. Explain the necessity of generating trapezoidal waveform. [4+4+8]
7. (a) Define the following:
 i. Storage time
 ii. Delay time
 iii. Rise time
 iv. Fall time
 (b) Explain how a BJT can be used as a switch. Compare its performance as a switch with JFET. [8+8]
8. Consider a self-biased nonsaturated flip-flop obtained from figure 2 by setting $V_{BB}=0$ and by adding a common emitter resistor R_e to ground in figure 2. The circuit has the following parameters: $V_{CC}=25V$, $V_Z=4.3V$, $h_{FE}=50$, $R_c=2.2K$, $R_1=R_2=15K$ and $R_e=470\Omega$. Neglect the voltage drop across a forward-biased junction. Verify that the transistors do not enter the saturation region. Calculate the transistor currents and the current in each diode. [16]

Code No: 07A30401

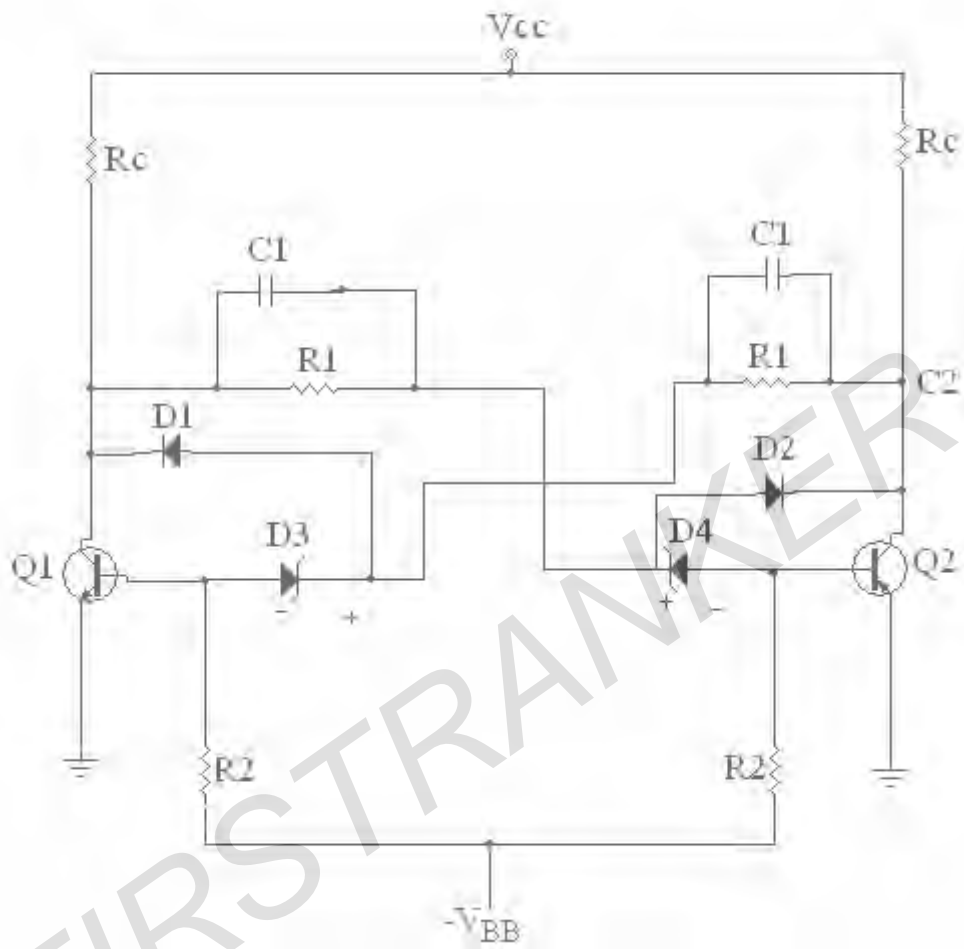
R07**Set No. 1**

Figure 2

Code No: 07A30401

R07**Set No. 3**

II B.Tech I Semester Examinations, November 2010

PULSE AND DIGITAL CIRCUITS**Common to Electronics And Instrumentation Engineering, Electrical And
Electronics Engineering****Time: 3 hours****Max Marks: 80****Answer any FIVE Questions
All Questions carry equal marks**

1. (a) Obtain the response of RC high pass circuit for an exponential i/p signal
(b) A square wave whose peak-to-peak value is 1 V, extends $\pm 0.5V$ w.r.t. to ground. The half period is 0.1 Sec this voltage impressed upon an RC differentiating circuit whose time constant is 0.2 sec. Determine the maximum and minimum values of the o/p voltages in the steady state. [8+8]
2. Consider a self-biased nonsaturated flip-flop obtained from figure 2 by setting $V_{BB}=0$ and by adding a common emitter resistor R_e to ground in figure 2. The circuit has the following parameters: $V_{CC}=25V$, $V_Z=4.3V$, $h_{FE}=50$, $R_C=2.2K$, $R_1=R_2=15K$ and $R_e=470\Omega$. Neglect the voltage drop across a forward-biased junction. Verify that the transistors do not enter the saturation region. Calculate the transistor currents and the current in each diode. [16]

Code No: 07A30401

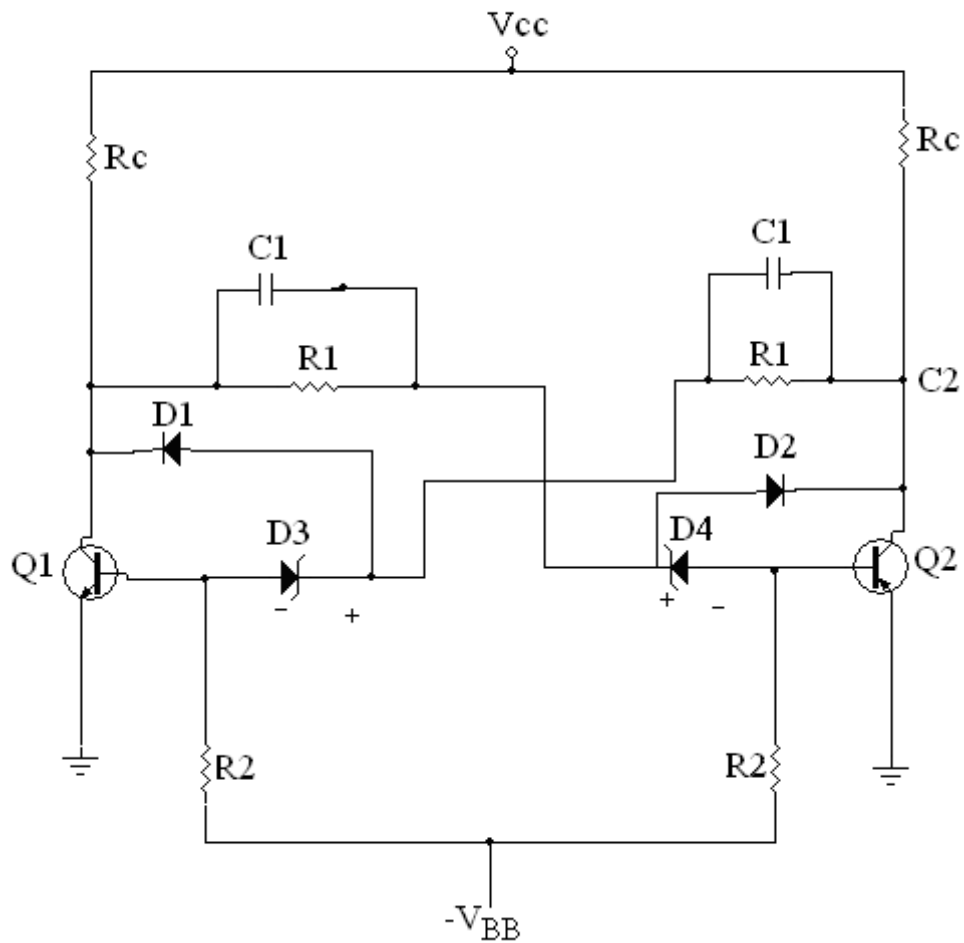
R07**Set No. 3**

Figure 2

3. (a) Draw the circuit diagram of diode-transistor logic NOR gate and explain its operation.
 (b) Draw the output waveform X for the given inputs figure 3b

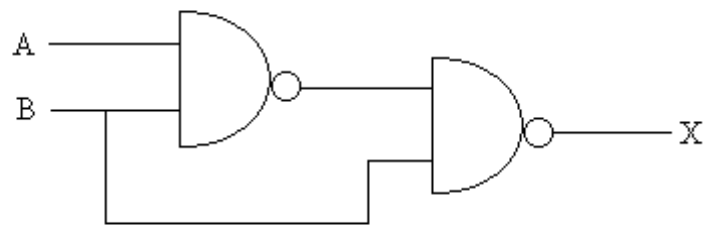
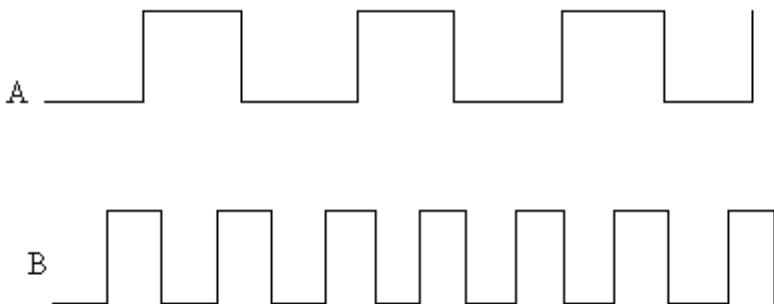


Figure 3b

4. (a) Design a diode clamper to restore a d.c level of +3 Volts to an input sinusoidal signal of peak value 10Volts. Assume drop across diode is 0.6 volts as shown in the figure 4a.

Code No: 07A30401

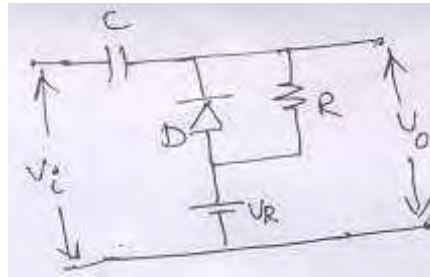
R07**Set No. 3**

Figure 4a

- (b) Compare series diode clipper and shunt diode clipper. [8+8]
5. (a) Define the following:
- Storage time
 - Delay time
 - Rise time
 - Fall time
- (b) Explain how a BJT can be used as a switch. Compare its performance as a switch with JFET. [8+8]
6. (a) List out the applications of sweep circuits.
- (b) Distinguish between voltage and current sweep circuits.
- (c) Draw the circuit of a linear current sweep and explain its operation with waveforms. Explain the necessity of generating trapezoidal waveform. [4+4+8]
7. (a) Describe frequency division employing a transistor astable multivibrator with waveforms.
- (b) Describe frequency division employing a transistor monostable multivibrator with waveforms. [8+8]
8. (a) What is pedestal? Illustrate the effect of control voltage on gate output.
- (b) Write the advantages and disadvantages of unidirectional diode gate. [16]
