

Code No: 07A3EC14

R07**Set No. 2**

II B.Tech I Semester Examinations, November 2010

ELECTRONIC CIRCUIT ANALYSISCommon to Electronics And Telematics, Electronics And Communication
Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) For a single stage transistor amplifier, $R_S = 10K$ and $R_L = 10K$. The h-parameter values are $h_{fc} = -51$, $h_{ic} = 1.1K\Omega$, $h_{rc} \approx 1$, $h_{oc} = 25 \mu A/V$. Find A_I , A_V , A_{VS} , R_i , and R_o for the CC transistor configuration.
- (b) For a single stage transistor amplifier, $R_S = 1K\Omega$, and $R_L = 10K$. The h-parameter values are $h_{fe} = 50$, $h_{ie} = 1.1K\Omega$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 25 \mu A/V$. Find A_I , A_V , A_{VS} , R_i , and R_o for the CE transistor configuration. [8+8]
2. (a) Define the terms:
 - i. Load Regulation
 - ii. Line Regulation
 - iii. Ripple Rejection
 - iv. Sense Voltage
- (b) In a zener diode regulator, $V_{i_{nom}} = 40V$, $V_{i_{min}} = 35V$, $V_{i_{max}} = 45V$, $V_z = 20V$, $r_z = 5 \text{ ohms}$, $I_{L_{min}} = 0mA$, $I_{L_{max}} = 100mA$, $I_{z_{min}} = 10mA$, $I_{z_{max}} = 400mA$. Find $P_{z_{max}}$ and load resistance. [8+8]
3. (a) The basic Switching regulator is designed to maintain a 12V dc output when the unregulated input voltage varies from 15V to 24V. When pass transistor is conducting, its collector to emitter saturation voltage is 0.5V. Assuming that the load is constant and the LC filter is ideal, find the minimum and maximum duty cycles of the pulse width modulator.
- (b) Write the Features and Applications of DC/DC converters [8+8]
4. (a) Derive the expression for the high 3-dB frequency f_h^* of n-identical non interacting stages in terms of f_H for one stage.
- (b) If four identical amplifiers are cascaded each having $f_H = 100 \text{ KHz}$, determine the overall upper 3dB frequency f_h^* . Assume non interacting stages.
- (c) Write a short note on Bootstrapped Darlington circuit. [5+5+6]
5. Draw the circuit diagram of a class-B tuned amplifier. Explain its operation with neat waveforms. Also derive the expression for percentage efficiency and maximum power dissipation. [16]
6. Draw the circuit diagram of a Double tuned amplifier and derive the expression for 3-dB bandwidth. [16]

Code No: 07A3EC14

R07

Set No. 2

7. (a) Show that in Hybrid - π model, the diffusion capacitance is proportional to the emitter bias current.
- (b) What is the frequency range to consider Giaccolletto model of a transistor at high frequencies? What is the significance of f_T in discussing the frequency range of a transistor at high frequencies? [8+8]
8. (a) Draw the circuit of class -A series fed power amplifier and derive the expression for output power P_o . [10]
- (b) Draw and discuss the operation of Class - C power amplifier. [6]

FIRSTRANKER

Code No: 07A3EC14

R07**Set No. 4**

II B.Tech I Semester Examinations, November 2010

ELECTRONIC CIRCUIT ANALYSISCommon to Electronics And Telematics, Electronics And Communication
Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. Draw the circuit diagram of a Double tuned amplifier and derive the expression for 3-dB bandwidth. [16]
2. (a) Define the terms:
 - i. Load Regulation
 - ii. Line Regulation
 - iii. Ripple Rejection
 - iv. Sense Voltage
- (b) In a zener diode regulator, $V_{i_{nom}} = 40V, V_{i_{min}} = 35V, V_{i_{max}} = 45V, V_z = 20V, r_z = 5 \text{ ohms}, I_{L_{min}} = 0mA, I_{L_{max}} = 100mA, I_{z_{min}} = 10mA, I_{z_{max}} = 400mA$. Find $P_{z_{max}}$ and load resistance. [8+8]
3. (a) The basic Switching regulator is designed to maintain a 12V dc output when the unregulated input voltage varies from 15V to 24V. When pass transistor is conducting, its collector to emitter saturation voltage is 0.5V. Assuming that the load is constant and the LC filter is ideal, find the minimum and maximum duty cycles of the pulse width modulator.
- (b) Write the Features and Applications of DC/DC converters [8+8]
4. (a) Draw the circuit of class -A series fed power amplifier and derive the expression for output power P_o . [10]
- (b) Draw and discuss the operation of Class - C power amplifier. [6]
5. (a) Show that in Hybrid - π model, the diffusion capacitance is proportional to the emitter bias current.
- (b) What is the frequency range to consider Giacolletto model of a transistor at high frequencies? What is the significance of f_T in discussing the frequency range of a transistor at high frequencies? [8+8]
6. Draw the circuit diagram of a class-B tuned amplifier. Explain its operation with neat waveforms. Also derive the expression for percentage efficiency and maximum power dissipation. [16]
7. (a) Derive the expression for the high 3-dB frequency f_h^* of n-identical non interacting stages in terms of f_H for one stage.

Code No: 07A3EC14

R07

Set No. 4

- (b) If four identical amplifiers are cascaded each having $f_H = 100$ KHz, determine the overall upper 3dB frequency f_h^* . Assume non interacting stages.
- (c) Write a short note on Bootstrapped Darlington circuit. [5+5+6]
8. (a) For a single stage transistor amplifier, $R_S = 10K$ and $R_L = 10K$. The h-parameter values are $h_{fc} = -51$, $h_{ic} = 1.1K\Omega$, $h_{rc} \approx 1$, $h_{oc} = 25 \mu A/V$ Find A_I , A_V , A_{VS} , R_i , and R_o for the CC transistor configuration.
- (b) For a single stage transistor amplifier, $R_S = 1K\Omega$, and $R_L = 10K$ The h-parameter values are $h_{fe} = 50$, $h_{ie} = 1.1K\Omega$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 25 \mu A/V$. Find A_I , A_V , A_{VS} , R_i , and R_o for the CE transistor configuration. [8+8]

FIRSTRANKER

Code No: 07A3EC14

R07**Set No. 1**

II B.Tech I Semester Examinations, November 2010

ELECTRONIC CIRCUIT ANALYSISCommon to Electronics And Telematics, Electronics And Communication
Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) The basic Switching regulator is designed to maintain a 12V dc output when the unregulated input voltage varies from 15V to 24V. When pass transistor is conducting, its collector to emitter saturation voltage is 0.5V. Assuming that the load is constant and the LC filter is ideal, find the minimum and maximum duty cycles of the pulse width modulator.
(b) Write the Features and Applications of DC/DC converters [8+8]
2. Draw the circuit diagram of a class-B tuned amplifier. Explain its operation with neat waveforms. Also derive the expression for percentage efficiency and maximum power dissipation. [16]
3. (a) Derive the expression for the high 3-dB frequency f_h^* of n-identical non interacting stages in terms of f_H for one stage.
(b) If four identical amplifiers are cascaded each having $f_H = 100$ KHz, determine the overall upper 3dB frequency f_h^* . Assume non interacting stages.
(c) Write a short note on Bootstrapped Darlington circuit. [5+5+6]
4. (a) For a single stage transistor amplifier, $R_S = 10K$ and $R_L = 10K$. The h-parameter values are $h_{fc} = -51$, $h_{ic} = 1.1K\Omega$, $h_{rc} \approx 1$, $h_{oc} = 25 \mu A/V$ Find A_I , A_V , A_{VS} , R_i , and R_o for the CC transistor configuration.
(b) For a single stage transistor amplifier, $R_S = 1K\Omega$, and $R_L = 10K$ The h-parameter values are $h_{fe} = 50$, $h_{ie} = 1.1K\Omega$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 25 \mu A/V$. Find A_I , A_V , A_{VS} , R_i , and R_o for the CE transistor configuration. [8+8]
5. (a) Define the terms:
 - i. Load Regulation
 - ii. Line Regulation
 - iii. Ripple Rejection
 - iv. Sense Voltage
 (b) In a zener diode regulator,
 $V_{i_{nom}} = 40V$, $V_{i_{min}} = 35V$, $V_{i_{max}} = 45V$, $V_z = 20V$, $r_z = 5$ ohms $I_{L_{min}} = 0mA$, $I_{L_{max}} = 100mA$, $I_{z_{min}} = 10mA$, $I_{z_{max}} = 400mA$. Find $P_{z_{max}}$ and load resistance. [8+8]
6. Draw the circuit diagram of a Double tuned amplifier and derive the expression for 3-dB bandwidth. [16]

Code No: 07A3EC14

R07

Set No. 1

7. (a) Show that in Hybrid - π model, the diffusion capacitance is proportional to the emitter bias current.
- (b) What is the frequency range to consider Giaccolletto model of a transistor at high frequencies? What is the significance of f_T in discussing the frequency range of a transistor at high frequencies? [8+8]
8. (a) Draw the circuit of class -A series fed power amplifier and derive the expression for output power P_o . [10]
- (b) Draw and discuss the operation of Class - C power amplifier. [6]

FIRSTRANKER

Code No: 07A3EC14

R07**Set No. 3**

II B.Tech I Semester Examinations, November 2010

ELECTRONIC CIRCUIT ANALYSISCommon to Electronics And Telematics, Electronics And Communication
Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) The basic Switching regulator is designed to maintain a 12V dc output when the unregulated input voltage varies from 15V to 24V. When pass transistor is conducting, its collector to emitter saturation voltage is 0.5V. Assuming that the load is constant and the LC filter is ideal, find the minimum and maximum duty cycles of the pulse width modulator.
(b) Write the Features and Applications of DC/DC converters [8+8]
2. (a) Derive the expression for the high 3-dB frequency f_h^* of n-identical non interacting stages in terms of f_H for one stage.
(b) If four identical amplifiers are cascaded each having $f_H = 100$ KHz, determine the overall upper 3dB frequency f_h^* . Assume non interacting stages.
(c) Write a short note on Bootstrapped Darlington circuit. [5+5+6]
3. Draw the circuit diagram of a Double tuned amplifier and derive the expression for 3-dB bandwidth. [16]
4. (a) Define the terms:
 - i. Load Regulation
 - ii. Line Regulation
 - iii. Ripple Rejection
 - iv. Sense Voltage
 (b) In a zener diode regulator,
 $V_{i_{nom}} = 40V, V_{i_{min}} = 35V, V_{i_{max}} = 45V, V_z = 20V, r_z = 5 \text{ ohms}, I_{L_{min}} = 0mA, I_{L_{max}} = 100mA, I_{z_{min}} = 10mA, I_{z_{max}} = 400mA.$ Find $P_{z_{max}}$ and load resistance. [8+8]
5. (a) Show that in Hybrid - π model, the diffusion capacitance is proportional to the emitter bias current.
(b) What is the frequency range to consider Giacolletto model of a transistor at high frequencies? What is the significance of f_T in discussing the frequency range of a transistor at high frequencies? [8+8]
6. (a) For a single stage transistor amplifier, $R_S = 10K$ and $R_L = 10K$. The h-parameter values are $h_{fc} = -51, h_{ic} = 1.1K\Omega, h_{rc} \approx 1, h_{oc} = 25 \mu A/V$ Find $A_I, A_V, A_{VS}, R_i,$ and R_o for the CC transistor configuration.

Code No: 07A3EC14

R07

Set No. 3

- (b) For a single stage transistor amplifier, $R_S=1K\Omega$, and $R_L= 10K$ The h-parameter values are $h_{fe} = 50$, $h_{ie} =1.1K\Omega$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 25 \mu A/V$. Find A_I , A_V , A_{VS} , R_i , and R_o for the CE transistor configuration. [8+8]
7. Draw the circuit diagram of a class-B tuned amplifier. Explain its operation with neat waveforms. Also derive the expression for percentage efficiency and maximum power dissipation. [16]
8. (a) Draw the circuit of class -A series fed power amplifier and derive the expression for output power P_o . [10]
- (b) Draw and discuss the operation of Class - C power amplifier. [6]

FIRSTRANKER