

Code.No: 07A40401

R07

SET-1

II B.TECH – II SEM EXAMINATIONS, DECEMBER - 2010
DIGITAL IC APPLICATIONS
(ELECTRONICS AND INSTRUMENTATION ENGINEERING)

Time: 3hours**Max.Marks:80**

Answer any FIVE questions
All questions carry equal marks

- - -

- 1.a) Design CMOS transistor circuit for 2-input OR gate. With the help of function table explain the circuit.
- b) Design a CMOS transistor circuit that has the functional behavior

$$f(Z) = \overline{A.(B+C)}$$
[8+8]

- 2.a) Design TTL three state NAND gate and explain the operation with the help of functional table.
- b) Explain how CMOS TTL interfacing can be achieved. Give the input and output levels of voltages. [8+8]

- 3.a) Explain the difference between function and procedure supported by VHDL. Give the necessary examples.
- b) Explain the various data types supported by VHDL. Give the necessary examples. [8+8]

4. Explain with an example the syntax and the function of the following VHDL statements.
 - a) Variable assignment statements
 - b) Next statements
 - c) Assertion statements
 - d) Report statements [4+4+4+4]

5. Design a two-digit BCD adder with logic gates. Using this logic write the VHDL Program in behavioral structural style of modeling. [16]

6. Design a 8×8 combinational multiplier and write the necessary VHDL program in structural model. [16]

- 7.a) Differentiate between Asynchronous counter and synchronous counter? Design a 4-bit counter in both modes and estimate the propagation delay.
- b) Design a modulo -100 counter using 74×163 ICs. [8+8]

- 8.a) Discuss how PROM, EPROM and EEPROM technologies differ from each other.
- b) With the help of timing waveforms, explain read and write operations of DRAM. [8+8]

Code.No: 07A40401

R07

SET-2

II B.TECH – II SEM EXAMINATIONS, DECEMBER - 2010
DIGITAL IC APPLICATIONS
(ELECTRONICS AND INSTRUMENTATION ENGINEERING)

Time: 3hours**Max.Marks:80**

Answer any FIVE questions
All questions carry equal marks

- - -

- 1.a) Design a CMOS transistor circuit that has the functional behavior
 $f(Z) = (A + B)(A + D)(B + D)$
- b) Distinguish between static and dynamic power dissipation of CMOS circuit. Derive the expression for dynamic power dissipation. [8+8]
- 2.a) Design 2-input LS-TTL NAND gate and explain its operation. Give the function table, truth table.
- b) Compare CMOS, TTL and ECL with reference to logic levels, DC noise margin, propagation delay and fan-out. [8+8]
- 3.a) Explain the difference between VHDL program structure and other procedural language program structure.
- b) Write a VHDL program to detect prime number of a 8-bit input. [8+8]
- 4.a) Design an excess-3 decimal counter using 74*163 and explain the operation with help of timing waveforms.
- b) Design an 8-bit synchronous binary counter with serial enable control. [8+8]
- 5.a) Design an 8-bit parallel-in and serial-out shift register. Explain the operation of the shift register with the help of timing diagram
- b) Difference between serial adder and parallel adder. [8+8]
- 6.a) Design sequence detector to detect the 1101 sequence using JK flip flops.
- b) Design divide by 6-counter using T-flip flop. Write state table and reduce the expression using K-map. [8+8]
- 7.a) Give the comparison between PROM, PLA and PAL.
- b) Explain how a 4×4 binary multiplier can be designed using 256×8 ROM. [8+8]
8. Explain the following terms with reference to CMOS logic.
- a) Logic Levels.
- b) Noise margin.
- c) Transition time
- d) Propagation delay [4+4+4+4]

II B.TECH – II SEM EXAMINATIONS, DECEMBER - 2010
DIGITAL IC APPLICATIONS
(ELECTRONICS AND INSTRUMENTATION ENGINEERING)

Time: 3hours

Max.Marks:80

Answer any FIVE questions
 All questions carry equal marks

- - -

- 1.a) Explain the concept of sinking and sourcing currents. How are they estimated for CMOS families?
- b) Design CMOS transistor circuit for 4-input OR-AND inverter gate. With the help of function table explain the circuit. [8+8]
- 2.a) Design 2-input LS-TTL NOR gate and explain its operation. Give the function table, truth table.
- b) Explain the behavioral difference between simple transistor logic inverter and schottkey logic inverter. [8+8]
- 3.a) Explain the time dimension and simulation in VHDL. Give the necessary examples.
- b) Explain the difference between variable data type and signal data types. Give the necessary examples. [8+8]
4. Design the logic circuit and write a data-flow style VHDL program for the following functions
 - a) $F(X) = \sum A B C D (0, 1, 2, 5, 7, 8, 10, 14, 15) + d (3, 6, 11)$
 - b) $F(Y) = \pi A B C D (1, 4, 5, 7, 9, 11, 12, 13, 15)$ [8+8]
- 5.a) Design 8-bit ALU circuit using two 74LS181 ICs.
- b) Design a 3-input 5-bit multiplexer. Write the truth table and draw the logic diagram and write VHDL program in dataflow model. [8+8]
- 6.a). Design a divide by 96-counter using 7490 ICs.
- b)
 - i) How many flip flops are required to build a binary counter that count from 0 to 1024?
 - ii) Determine the frequency at the output of last (MSB) flip flop for an input clock frequency of 2MHz.
 - iii) If the counter is initially at zero, what count it will hold after 2060clock pulses?
 - iv) Draw the block diagram for the above counter using TTL integrated circuit. [8+8]
- 7.a) How many ROM bits are required to build a 16-bit adder/ subtractor with mode control, carry input, carry output and two complement overflow output? Show the block schematic with all inputs and outputs.
- b) Design an 8*4 diode ROM using 74X138 for the following data starting from the location 1, 4, 9, B, A, O, F, C. [8+8]

- 8.a) Compare HC,HCT,VHC, and VHCT CMOS logic families with the help of output specifications with V_{cc} from 4.5 to 5.5V.
- b) Explain the following terms.
- i) Sequential Statement.
 - ii) Concurrent Statement.
- [8+4+4]

FIRSTRANKER

II B.TECH – II SEM EXAMINATIONS, DECEMBER - 2010
DIGITAL IC APPLICATIONS
(ELECTRONICS AND INSTRUMENTATION ENGINEERING)

Time: 3hours

Max.Marks:80

Answer any FIVE questions
All questions carry equal marks

- - -

- 1.a) Explain the circuit diagram of basic CMOS gate and explain its operation.
- b) Explain the electrical characteristics of CMOS of
 - i) CMOS steady state electrical behavior.
 - ii) CMOS dynamic state electrical behavior. [6+10]

- 2.a) Draw and explain the operation of transistor inverter with its transfer characteristics.
- b) What are the characteristics of TTL families? [10+6]

- 3.a) Explain the differences between variable data type and signal data types. Give the necessary examples.
- b) Design and explain 16×1 multiplexer and Write a VHDL program in data flow model. [8+8]

4. Explain with an example the syntax and the function of the following VHDL statements.
 - a) Variable assignment statements
 - b) Next statements
 - c) Assertion statements
 - d) Report statements [4+4+4+4]

- 5.a) Distinguish between latch and flip-flop. Show the logic diagram for both. Explain the operation with the help of function table
- b) Design a Modulo-12 ripple counter using 74×74? Write a VHDL program for this logic using data flow style. [8+8]

6. Write VHDL program for 8-bit comparator circuit. Using this entity write VHDL program for 24-bit comparator. Show the additional logic used for this purpose use structural style or modeling. [16]

- 7.a) Write a behavioral VHDL program to compare 16-bit signed and unsigned integers.
- b) Difference between PROM, EPROM, PAL, PLA. [8+8]

- 8.a) Draw the basic cell structure of Dynamic RAM. What is the necessity of refresh cycle Explain the necessity of two-dimensional decoding mechanism in memories.
- b) Draw MOS transistor memory cell in ROM and explain the operation. Explain the timing requirements of refresh operation. [8+8]
