

Code.No: 07A51102

R07

SET-1

III B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
LINEAR & DIGITAL IC APPLICATIONS
(COMMON TO BME, E.CONT.E, ETM, E.COMP.E)


Time: 3hours

Max.Marks:80


Answer any FIVE questions
 All questions carry equal marks

- - -

 - 1.a) What is an electrical noise? What precautions can be taken to minimize the effect of noise on an op-amp circuit?
- b) Given $R_1 = 100 \Omega$ and $R_F = 4.7k\Omega$. What is the maximum possible output offset voltage V_{oo} ? The op-amp is LM307 with $V_{io} = 10 \text{ mv}$ and supply voltage $\pm 15\text{V}$ as shown in figure. [8+8]



 - 2.a) Explain why do we use two stage op-amplifier as an instrumentation amplifier.
- b) Draw the output of the op amp as shown in figure. When $V_1 = 0\text{V}$ & $V_1 = 4\text{V}$. [4+12]



3. Draw the circuit of the second order low pass filter and derive the gain of the filter and also plot the frequency response. [16]
- 4.a) Explain the function of each pin of 555 timer.
- b) List the important features of 555 timer. [8+8]

- 5.a) Design a first -order low pass filter so that it has a cut off frequency of 2kHz and pass Band gain of '1'
b) Convert the 2 kHz low pass filter to a cut off frequency of 3kHz in part (a) [8+8]
6. Explain with suitable example how binary multiplication can be performed using shift and add method? [16]
7. Explain following terms:
a) Logic Levels
b) Speed of logic circuit
c) Power dissipation
d) Noise Margin
e) Noise immunities. [16]
8. a) With neat circuit diagram explain the working of a 4-bit odd parity generator .
b) Design a 2-digit binary multiplication circuit? [6+5+5]

--oOo--

FIRSTRANKER

Code.No: 07A51102

R07

SET-2

III B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
LINEAR & DIGITAL IC APPLICATIONS
(COMMON TO BME, E.CONT.E, ETM, E.COMP.E)


Time: 3 hours

Max.Marks:80

Answer any FIVE questions
 All questions carry equal marks

- - -

 - 1.a) List out the merits and limitations of integrated circuit technology?
 b) Explain the input offset current and input bias current with op-Amps. [8+8]
- 2.a) What are the limitations of an ordinary op-amp differentiator?
 b) The inverting amplifier with a single supply is shown in figure $R_{in} = 50\Omega$, $R_4 = 10k\Omega$, $R_2 = R_3 = R_F = 100k\Omega$ and $C_i = C_0 = 0.1\mu F$. Determine the BW of amplifier. Also determine the maximum ideal output voltage swing. [4+12]



- 3.a) Design a Band pass filter so that $f_c = 1kHz$, $Q = 3$ and $A_F = 10$.
 b) Draw the frequency response. [8+8]
- 4.a) With neat diagram explain the dual slope type A/D converter?
 b) Compare successive approximation type & single slope ADC? [8+8]
5. If $f_s = 100 KHz$, the voltage to frequency transfer coefficient of VCO, $K_v = 2mHz/v$, f_0 the VCO frequency is 5MHZ and $N=100$ in the frequency multiplier what is the dc voltage at lock? [16]
6. Implement the following functions using a multiplexer:
 a) $F(A, B, C) = \sum m(1, 3, 5, 6)$
 b) $F(A, B, C) = \sum m(0, 1, 3, 4, 8, 9, 15)$ [16]
7. Explain the MOS and CMOS logic families and different CMOS characteristics. [16]
- 8.a) With the help of logic diagram of a 4-bit adder/subtractor for adding or subtracting two numbers of arbitrary signs, using 1's complement and explain its working?
 b) Design a 4-bit parallel full adder with look ahead carry scheme? [8+8]

--oOo--

Code.No: 07A51102

R07

SET-3

III B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
LINEAR & DIGITAL IC APPLICATIONS
(COMMON TO BME, E.CONT.E, ETM, E.COMP.E)


Time: 3hours

Max.Marks:80

Answer any FIVE questions
 All questions carry equal marks

- - -

 - 1.a) Why is emitter resistor R_E replaced by a constant current bias circuit in differential amplifier stage of an op-amp?
- b) Compare and contrast the properties of ideal and practical op-amp. [8+8]
2. For the VCO determine the change in output frequency if V_c is varied between 9V and 11V. Assume that $+V = 12V$, $R_2 = 15k\Omega$, $R_3 = 100k\Omega$, $R_1 = 0.8k\Omega$, and $C_1 = 75$ Pf. Derive the equations used. [16]
- 3.a) Distinguish between single slope and dual slope type of A/D converter?
- b) What are over sampling converter? [8+8]
4. With neat circuit diagrams explain the following:
 - a) AND-OR-INVERT gates
 - b) Open collector TTL 2-input OR gate. [16]
- 5.a) With a circuit diagram and waveform explain the operation of an inverting and non-inverting comparators.
- b) For the circuit as shown in figure draw the output wave form, given $V_i = 100mV$ peak sine wave at 100Hz, $R = 1k\Omega$ and $V_r = V_z = 6.2V$ and supply voltage is $\pm 12V$. [8+8]



- 6.a) Derive the expression of the lock-in range.
- b) Derive the expression of the capture range. [8+8]
7. With the help of neat diagram and truth table explain BCD to 7-segment decoder. [16]
- 8.a) What is meant by a transparent latch?
- b) Convert a D-FF to a JK-FF, using extra NAND gates, if required.
- c) Explain the function of preset and clear inputs in flip-flop.
- d) Why $S=R=1$ not permitted in SR-Flip-Flop. [16]

--oOo--

Code.No: 07A51102

R07

SET-4

III B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
LINEAR & DIGITAL IC APPLICATIONS
(COMMON TO BME, E.CONT.E, ETM, E.COMP.E)

Time: 3hours

Max.Marks:80

Answer any FIVE questions
 All questions carry equal marks

- - -


- 1.a) How many bits are required to design a DAC, that can have a resolution of 5mv? The ladder has +8V full scale?
- b) How many resistors are required for an 8-bit weighted resistor DAC? What are the resistance values, assuming the smallest resistance is R? [16]

2. Explain the following terms:
 - a) Floating input
 - b) Active and passive pull-up
 - c) Open collector outputs
 - d) Unused points. [16]

3. Design a BCD to gray code converter using:
 - a) 8:1 multiplexer.
 - b) BCD to decimal decoder and NAND gates.
 - c) NAND gates only. [16]


4. Write short notes on the following:
 - a) Level triggering.
 - b) Edge triggering.
 - c) Pulse triggering
 - d) Explain the RS flip-flop using NAND gates? [8+8]

 - 5.a) Describe the limitations of op-amp as a comparator.
- b) In the shown in figure determine the output voltage swing and draw the output waveform given $V_i = 500\text{mV}$ peak 100Hz sine wave, $R = 100\Omega$, $V_z = 6.2$, $V_1, V_D = 0.7\text{V}$ and supply voltages = $\pm 15\text{V}$. [8+8]




- 6.a) Derive that the period of a triangular wave is $T = 4 R_1 C_1 (R_2/R_3)$.
- b) In the circuit as shown in figure $+V = +12V$, $R_2 = 1.5 \text{ k}\Omega$, $R_1 = R_3 = 10 \text{ k}\Omega$ & $C_1 = 0.001 \mu\text{f}$.
- i) Determine the nominal frequency of the output waveforms.
- ii) Draw the square wave output waveform if the modulating input is a sine wave.

[16]

 


 - 7.a) Calculate v_0/v_1 for the circuit as shown in figure.



- b) Calculate Y_{of} for the gain circuit as shown in figure $R_i = \infty$

[8+8]

 

- 8.a) A system uses a 12-bit word to represent the input signal of the maximum peak - to-peak voltage at the input is set to 5V, find the resolution of the system and the dynamic range.
- b) Explain the characteristics of an n-bit weighted resistor D/A converter? [8+8]

--oOo--