

Code No: 07A7EC32

R07**Set No. 2****IV B.Tech I Semester Examinations, NOVEMBER 2010****VLSI DESIGN****Common to Electronics And Computer Engineering, Electronics And Instrumentation Engineering****Time: 3 hours****Max Marks: 80****Answer any FIVE Questions
All Questions carry equal marks**

1. Draw the structure, explain the function and write the applications characteristics of the following programmable CMOS devices: [16]
 - (a) PLA
 - (b) PAL
 - (c) FPGA
 - (d) CPLD.
2. (a) Design a comparator using XNOR and AND gate and draw its schematic.
 (b) Design a zero/one detector and draw its schematic and also calculate its delay. [8+8]
3. (a) What are the advantages of Hardware Description Languages and Software Languages?
 (b) What are different design verification tools and explain them in brief? [8+8]
4. Compare the relative merits of three different forms of pull up for an inverter circuits. What is the best choice for realization in
 - (a) nMOS technology
 - (b) CMOS technology. [16]
5. Discuss the Gate logic with reference to the following:
 - (a) NMOS and CMOS inverters.
 - (b) NMOS- NAND and CMOS NAND gates
 - (c) NMOS- NOR and CMOS- NOR gates. [4+6+6]
6. Explain the following two oxidation methods in IC fabrication.
 - (a) High pressure oxidation
 - (b) Plasma oxidation. [8+8]
7. Briefly discuss the limits of scaling. Why scaling is necessary for VLSI circuits? [16]
8. (a) What are the different ATPG algorithms? Explain them briefly with suitable example.

Code No: 07A7EC32

R07

Set No. 2

- (b) The number of nodes in a circuit is 100 and the length of test sequence 12,000.
Find number of cycles need to be simulated? [8+8]

FIRSTRANKER

Code No: 07A7EC32

R07**Set No. 4**

IV B.Tech I Semester Examinations, NOVEMBER 2010

VLSI DESIGN

Common to Electronics And Computer Engineering, Electronics And
Instrumentation Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. Explain

- (a) Propagation delay
- (b) Wiring capacitance.

[8+8]

2. Write a syntax for the following in VHDL :

[16]

- (a) if
- (b) case
- (c) when
- (d) generic
- (e) entity
- (f) architecture
- (g) configuration
- (h) library.

3. (a) What are the reasons of malfunctioning of chip? What are the different levels of testing?

(b) Explain how a parallel scan is used for data path test.

(c) What is mean by level sensitive of logic system?

[6+6+4]

4. Explain the following terms related to the fabrication of IC

- (a) Diffusion
- (b) oxidation
- (c) Lithography
- (d) Metallization.

[4+4+4+4]

5. Explain the following

- (a) Double metal MOS process rules.
- (b) Design rules for P- well CMOS process.

[8+8]

6. (a) What are the differences between a gate array chip and standard-cell chip?
What benefits does each implementation style have?

Code No: 07A7EC32

R07

Set No. 4

- (b) Write the equations for a full adder in SOP form. Sketch a 3-input, 2- output PLA implementing this logic. [8+8]
7. (a) Draw the serial multiplier and explain how the successive addition algorithm is implemented in it.
- (b) Design a gray-coded counter in which only one bit changes on each cycle. [8+8]
8. (a) Discuss the nFET resistance with relevant equations.
- (b) Calculate the linearized drain source resistance of an nFET with following parameters. $W=8\mu\text{m}$, $L=0.5\mu\text{m}$, $k'_n=180\ \mu\text{A}/\text{V}^2$, $V_{tn}=0.7\text{V}$ and $V_{DD}=3.3\text{V}$. [8+8]

Code No: 07A7EC32

R07**Set No. 1****IV B.Tech I Semester Examinations, NOVEMBER 2010****VLSI DESIGN****Common to Electronics And Computer Engineering, Electronics And Instrumentation Engineering****Time: 3 hours****Max Marks: 80****Answer any FIVE Questions
All Questions carry equal marks**

1. (a) What are stick diagrams?
(b) Write stick encoding for
 - i. n diffusion
 - ii. Polysilicon
 - iii. Metal-1
 - iv. Contact cut.
 (c) Draw stick diagram for P-well CMOS inverter. [2+2+2+2+2+6]
2. (a) Explain the manufacturing test of a chip with suitable examples.
(b) Explain how an Ad-hoc test technique used to test long counters. [8+8]
3. (a) Why resistor pull up is not used in MOS circuits?
(b) Discuss different forms of pull up, mentioning merits and demerits of each form. [4+12]
4. (a) Write a VHDL program in behavioral modeling with concurrent signal assignment.
(b) Explain the method of switch-level simulation for CMOS circuits and name such a simulators. [8+8]
5. (a) Compare the Antifuse and Vialink programmable interconnections for PAL devices.
(b) What are different typically available SSI Standard-cell types and compare them. [8+8]
6. (a) Draw the logic and schematic diagrams for 4 bit ALU and explain how it performs both arithmetic and Boolean operations.
(b) Explain how a higher radix multipliers reduce the number of adders. [8+8]
7. Describe three sources of wiring capacitances. Explain the effect of wiring capacitance on the performance of a VLSI circuit. [16]
8. Describe the flow diagram of Berkeley N well fabrication. [16]

Code No: 07A7EC32

R07**Set No. 3**

IV B.Tech I Semester Examinations, NOVEMBER 2010

VLSI DESIGN

Common to Electronics And Computer Engineering, Electronics And
Instrumentation Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. Explain the following in brief:

(a) Chip level test techniques

(b) System level test techniques. [8+8]

2. Mention the properties of oxidation, explaining thermal oxidation technique. [16]

 
3. Calculate on resistance of the circuit shown in the figure 3 from V_{DD} to GND. If n-channel sheet resistance $R_{sn} = 10^4 \Omega$ per square and P-channel sheet resistance $R_{sp} = 3.5 \times 10^4 \Omega$ per square. [16]

Figure 3

4. (a) Explain nMOS inverter and latch up in CMOS circuits?

(b) Draw the nMOS transistor circuit model and explain various components of the model. [8+8]

5. Design a stick diagram and layout for the CMOS logic shown below.

$$Y = (AB) + (CD)$$

[16]

6. (a) Explain how an array is constructed to describe memories in VHDL.

(b) Write a VHDL module which describes a 64-word x 16-bit RAM. [8+8]

Code No: 07A7EC32

R07

Set No. 3

7. Develop a model of word line decoder delay for a RAM with 2^n rows and 2^m columns. Assume true and complementary inputs are available and that the input capacitance equals the capacitance of one of the columns of $H=2^m$. Use static CMOS gates and express result in terms of n and m . [16]
8. (a) What are the characteristics of 22V10 PAL CMOS device and draw its I/O structure.
- (b) Explain any one chip architecture that used the antifuse and give its advantages. [8+8]

FIRSTRANKER