

Code.No: A109210204


R09

SET-1

II B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010**ELECTRICAL CIRCUITS
(COMMON TO EEE, ECE, ETM)****Time: 3hours****Max.Marks:75****Answer any FIVE questions
All questions carry equal marks**


- - -

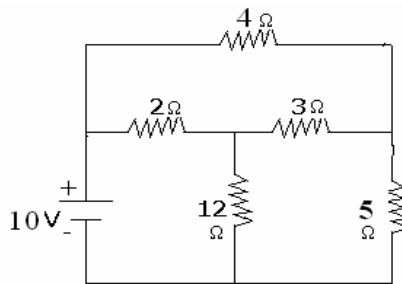- 1.a) Explain Active elements in detail.
- b) A 25 ohms resistor is connected across a voltage source $V(t) = 150 \sin \omega t$. Find the current $I(t)$ and the instantaneous power $P(t)$ and also the average power. Draw the relevant waveforms. [7+8]
- 2.a) State and explain Kirchoff's laws.
- b) Find the current supplied by 10 V battery by using Star – Delta transformation for the following network. [7+8]




- 3.a) Derive the expression for RMS value of alternating current wave $I = I_m \sin \omega t$.
- b) A coil takes a current of 1 A at 0.6 lagging power factor from a 220 V, 60 Hz single phase source. If the coil is modeled by a series RL circuit find
 - i) The complex power in the coil and
 - ii) The values of R and L. [7+8]
- 4.a) Show that the resonant frequency ω_0 of an RLC series circuit is the geometric mean of ω_1 and ω_2 , the lower and upper half power frequencies respectively.
- b) A voltage $V = 50 \angle 0^\circ$ V is applied to a series circuit consisting of fixed inductive reactance $X_L = 5$ ohms and a variable resistance R. Sketch the admittance and current locus diagrams. [7+8]
- 5.a) Obtain the expression for co-efficient of coupling.
- b) A cast steel electromagnet has an air gap length of 3 mm and an iron path of length 40 cm. Find the number of ampere turns necessary to produce a flux density of 0.7 Wb/m² in the gap. Neglect the leakage and fringing. [7+8]

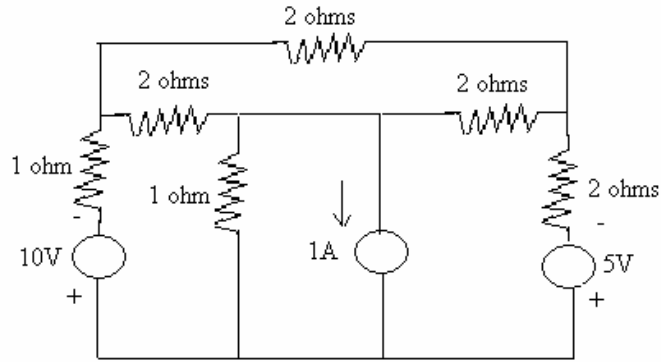
6. For the below network, draw
 i) Graph ii) Tree iii) Dual network [4+4+7]



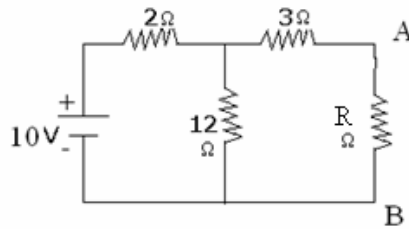- 7.a) State and explain Tellegens theorem.
 b) When the load impedance R draws the maximum power? Find the maximum power delivered to the load by using maximum power transfer theorem for the given network. [7+8]



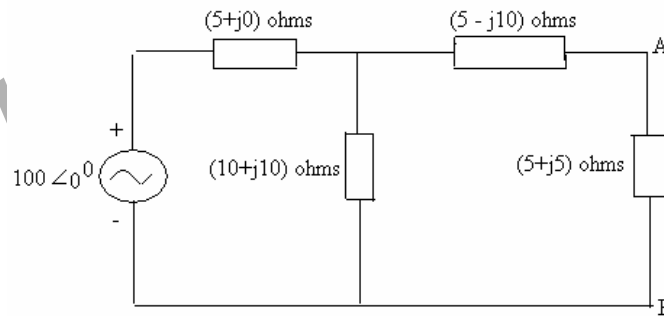- 8.a) State and explain Milleman's theorem for AC network by taking any one example.
 b) By using Norton's theorem find the current flowing through $(5+j5)$ ohms impedance [7+8]



Code.No: A109210204

R09

SET-2

II B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
ELECTRICAL CIRCUITS
(COMMON TO EEE, ECE, ETM)


Time: 3hours

Max.Marks:75


Answer any FIVE questions
All questions carry equal marks

- - -

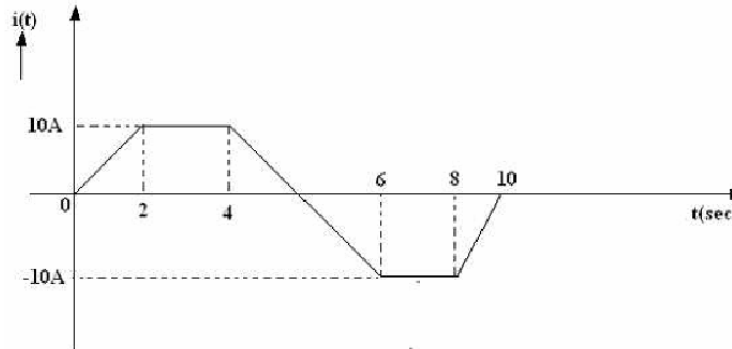- 1.a) Explain Passive elements in detail.
 b) A pure inductance of 3 mH carries a current of the wave form shown in figure. Sketch the waveform of $V(t)$ and $P(t)$. Determine the average value of power. [7+8]




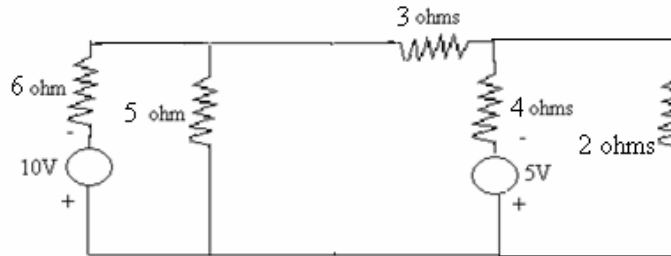- 2.a) Three resistances R_{ab} , R_{bc} and R_{ca} are connected in delta connection, Derive the expressions for equivalent star connection.
 b) By using nodal analysis find the current flowing through 3 ohms resistor. [7+8]




- 3.a) Show that power dissipated by a pure capacitor excited by a sinusoidal voltage source $V = V_m \sin \omega t$ is zero.
 b) A circuit consisting of three branches, Z_2 is in parallel with Z_3 the combination is in series with Z_1 having the values $Z_1 = 10 + j30$, $Z_2 = 5 + j10$ and $Z_3 = 4 - j16$ connected across single phase, 100 V, 50 Hz supply. Find
 i) I_1 , I_2 and I_3 ii) V_1 and V_2 [7+8]
- 4.a) Obtain the current locus of a series circuit having a fixed resistance and a variable inductance.
 b) Given a series RLC circuit with $R = 100$ ohms, $L = 0.5$ H and $C = 40 \mu F$, Calculate the resonant, lower and upper half – power frequencies. [7+8]

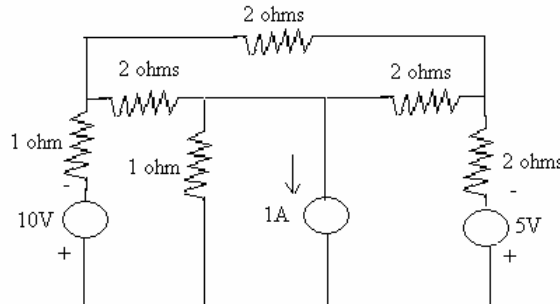- 5.a) Define and explain self – inductance and mutual – inductance.
 b) Two coupled coils of $L_1 = 0.8 \text{ H}$ and $L_2 = 0.2 \text{ H}$ have a coupling coefficient $k = 0.9$. Find the mutual inductance M .
 c) State and explain Faraday's laws of electro magnetic induction. [5+5+5]
6. Obtain the node voltages for the following network shown in figure. [15]




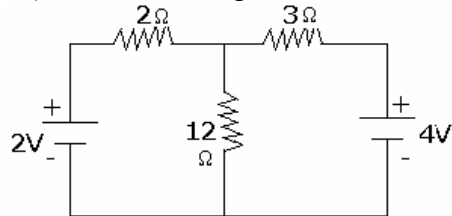- 7.a) State and explain reciprocity theorem.
 b) Using superposition theorem determine the current through 12Ω resistor (All resistances are in Ω) as shown in figure [7+8]



Figure

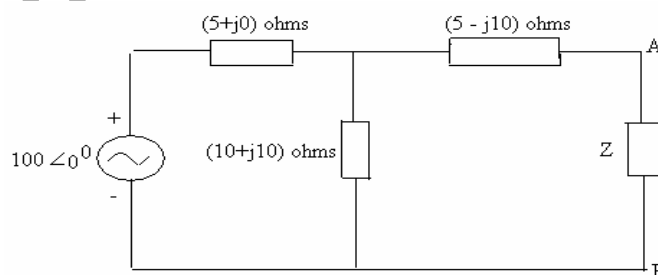- 8.a) Write down the procedure to obtain the Norton's equivalent circuit for AC network by taking any one example.
 b) When the maximum power will be flowing through the impedance Z ? And also find the maximum power delivered the load impedance Z for the following network. [7+8]



Code.No: A109210204

R09

SET-3

II B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
ELECTRICAL CIRCUITS
(COMMON TO EEE, ECE, ETM)


Time: 3hours

Max.Marks:75


Answer any FIVE questions
All questions carry equal marks

- - -

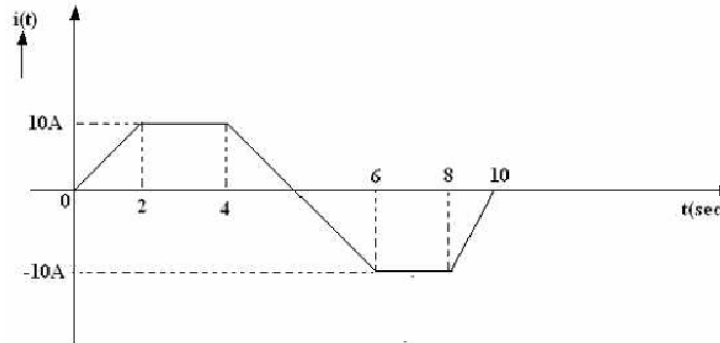- 1.a) Write short notes on source transformation.
 b) A pure inductance of 5 mH carries a current of the wave form shown in figure. Sketch the waveform of $V(t)$ and $P(t)$. Determine the average value of power. [7+8]



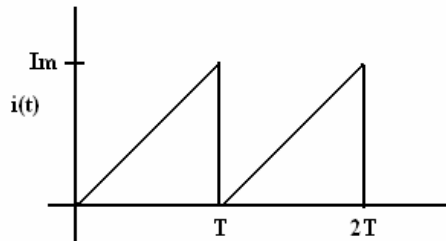
- 2.a) Write short notes on Star – Delta transformation.
 b) By taking any one example write down the procedure to obtain node voltages by using nodal analysis. [7+8]
 3.a) Find form factor of triangular waveform shown in the figure.




Figure

- b) A series circuit consisting of a 10 ohms resistor, a 100 μ F capacitance and 10 mH inductance is driven by a 50 Hz AC voltage source of maximum value 100 V. Calculate the equivalent impedance, current in the circuit, the power factor and power dissipated in the circuit. [7+8]
 4.a) Show that $Q_0 = \omega_0 L / R = f_0 / BW$ for a series RLC circuit.
 b) A voltage of $V = 50 \angle 0^\circ$ V is applied to a series circuit of fixed resistance $R = 5$ ohms and a variable capacitance C . Sketch the admittance and current locus diagrams. [7+8]

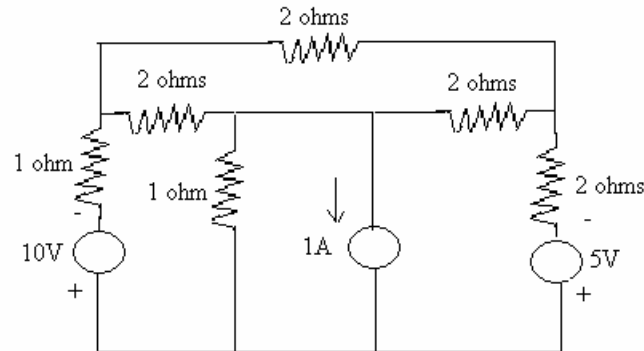- 5.a) What is an electric circuit? What is a magnetic circuit? Make a comparison between electric circuit and magnetic circuit.
- b) Coil 1 of a pair of coupled coils has a continuous current of 5 A, and the corresponding fluxes ϕ_{11} and ϕ_{12} are 0.2 and 0.4 mWb respectively. If the turns are $N_1 = 500$ and $N_2 = 1500$, find L_1 , L_2 , M and k . [7+8]
6. For the below network draw the graph and write down the procedure to obtain cut set matrix. [15]




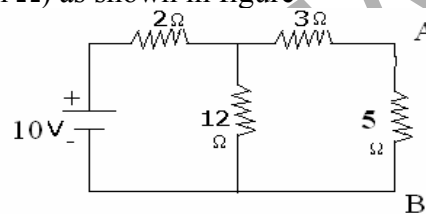- 7.a) State and explain Millman's theorem.
- b) By using Thevenin's theorem determine the current through 5Ω resistor (All resistances are in Ω) as shown in figure [7+8]



Figure

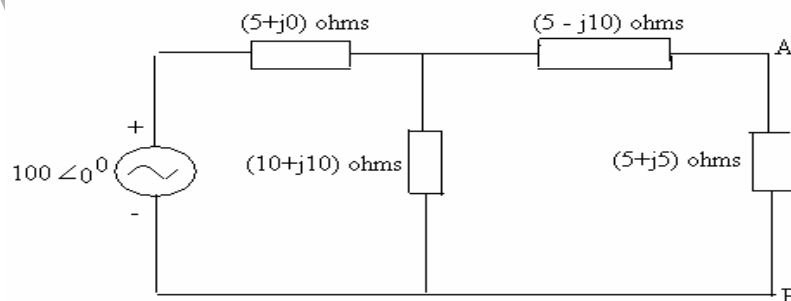- 8.a) State and explain Compensation theorem for AC network by taking any one example.
- b) By using Norton's theorem find the current flowing through $(5+j5)$ ohms impedance. [7+8]



Code.No: A109210204

R09

SET-4


II B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
ELECTRICAL CIRCUITS
(COMMON TO EEE, ECE, ETM)

Time: 3hours**Max.Marks:75**


Answer any FIVE questions
All questions carry equal marks

- - -

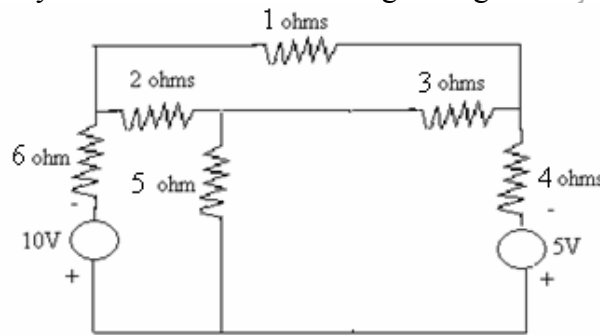- 1.a) Explain voltage - current relationship for passive elements.
- b) A 20 ohms resistor is connected across a voltage source $V(t) = 200 \sin \omega t$. Find the current $I(t)$ and the instantaneous power $P(t)$ and also the average power. Draw the relevant waveforms. [7+8]
- 2.a) State and explain Kirchoff's laws.
- b) By using loop analysis find the current flowing through 5 ohms resistor. [7+8]



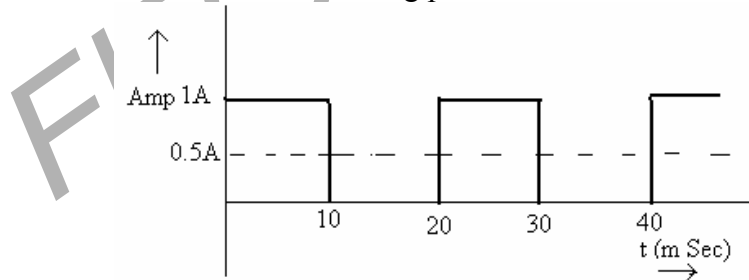- 3.a) Find form factor of a non alternating periodic waveform shown in figure.




Figure


- b) A parallel circuit having two branches, first branch consisting of 3 ohms resistor in series with 12.7 mH inductor, second branch consisting of 1 ohm resistor in series with 3.18 mH is connected across 200 V, single phase, 50 Hz supply. Calculate:
 - a) Conductance and susceptance of each branch
 - b) The resultant admittance
 - c) The current in each branch
 - d) Total current input

[7+8]

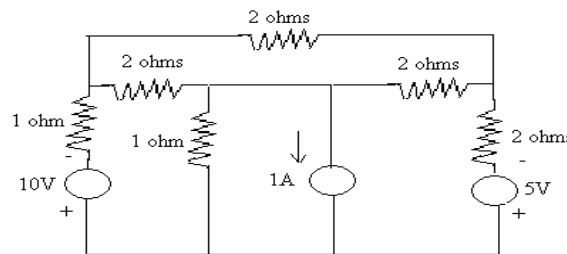- 4.a) Obtain the current locus of a fixed resistance and a variable capacitance.
 b) Given a series RLC circuit with $R = 10 \text{ ohms}$, $L = 1 \text{ mH}$ and $C = 1 \mu\text{F}$ is connected across a sinusoidal source of 20 V with variable frequency. Find
 i) The resonant frequency
 ii) Q factor of the circuit at resonant frequency
 iii) Half power frequencies. [7+8]
- 5.a) State and explain Faraday's laws of electro magnetic induction.
 b) An iron ring of mean circumference of 1 m is uniformly wound with 400 turns of wire. When a current of 1.2 A is passed through the coil, a flux density of 1.15 Wb/m^2 is produced in the iron. Find the relative permeability of the iron under these circumstances. [7+8]
6. For the above network draw the graph, Select a tree and write tie set schedule for selected tree, solve circuit. [15]



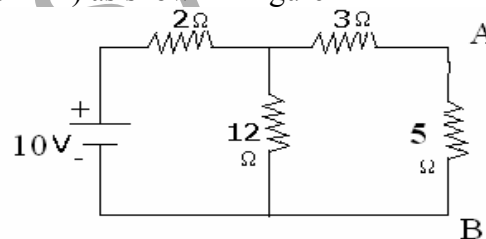- 7.a) State and explain Compensation theorem.
 b) By using Norton's theorem determine the current through 5Ω resistor (All resistances are in Ω) as shown in figure [7+8]



- 8.a) State and explain Superposition theorem for AC network by taking any one example.
 b) When the maximum power will be flowing through the impedance Z ? And also find the maximum power for the following network. [7+8]

