

Code.No: A109211402

R09

SET-1


II B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
ELECTRICAL ENGINEERING
(MECHANICAL ENGINEERING)
(MECHATRONICS)

Time: 3hours


Max.Marks:75

Answer any FIVE questions
 All questions carry equal marks

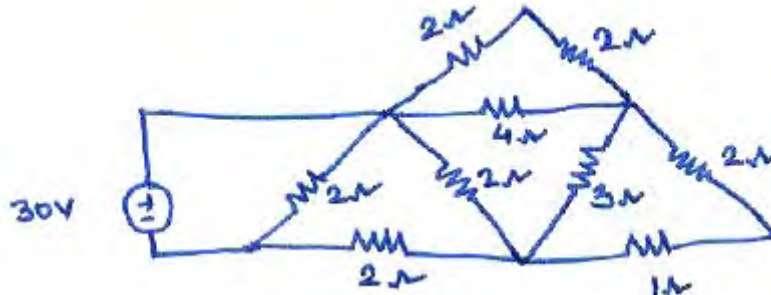
- 1.a) Determine the current delivered by the Source in the Circuit shown below.



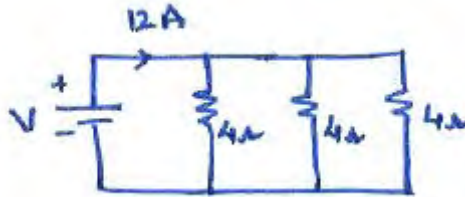
- b) Determine the current through each resistor in the circuit shown below. [8+7]



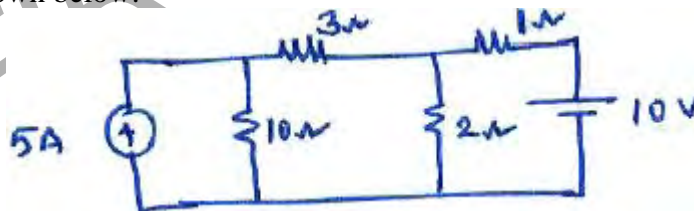
- 2.a) Write the node voltage equations and determine the current in each branch for the network shown below.



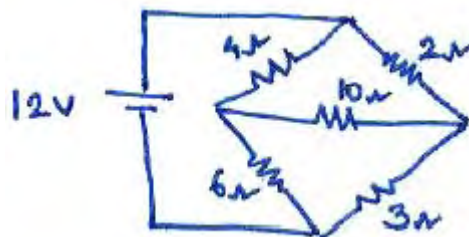- b) Use Thevenin's theorem to find current through 10Ω resistor. [7+8]



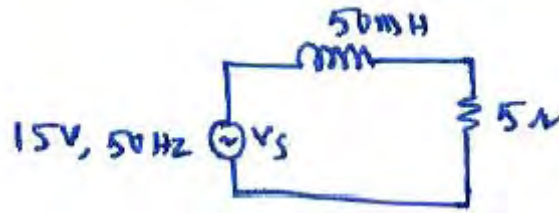- 3.a) Define RMS value, Average value, Form factor and Peak factor.
 b) For the circuit shown below, find effective voltages across resistance, inductance, and also determine the phase angle. [8+7]



- 4.a) Explain the principle and operation of a transformer.
 b) Explain how to determine the efficiency, regulation and equivalent circuit parameters of single phase transformer by conducting O.C. and S.C. tests. [6+9]
- 5.a) Explain the different methods of excitation of dc generators with suitable diagrams.
 b) A 4-pole, dc generator has a lap-wound armature having 50 slots with 18 conductors. The flux per pole is 0.005 wb. Determine the induced emf at a speed of 900 rpm. [8+7]
- 6.a) Explain the working principle of a DC motor.
 b) A 230V DC Shunt motor takes a no-load current of 2.5 A. The armature and field resistances are 0.5Ω and 150Ω respectively. Calculate the efficiency of the motor, when on full load it takes a current of 150 A. [7+8]
- 7.a) Explain the Torque – speed characteristics of 3ϕ Induction Motor.
 b) The power input to the rotor of a 440 V, 50 Hz, 4-pole, three phase induction motor 25 kw and speed is 960 rpm. Calculate the Rotor Copper losses and the mechanical power developed. [7+8]
- 8.a) Explain how the measuring instruments are classified.
 b) Explain the construction and operating principle of PMMC instruments. [7+8]


II B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
ELECTRICAL ENGINEERING
(MECHANICAL ENGINEERING)
(MECHATRONICS)

Time: 3hours


Max.Marks:75

Answer any FIVE questions
 All questions carry equal marks

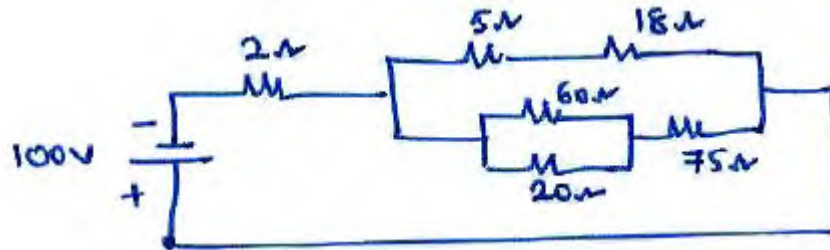
- 1.a) For the circuit shown in figure. Find the total resistance and current 'I'.



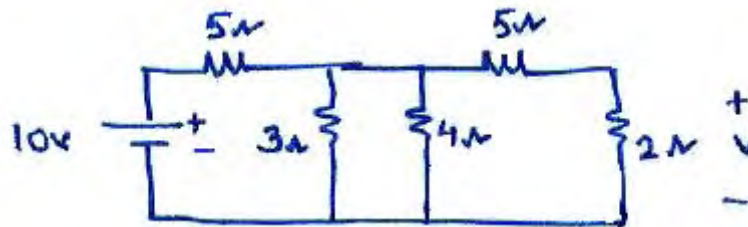
- b) Using network reduction, find the voltage 'V' in the below circuit. [7+8]



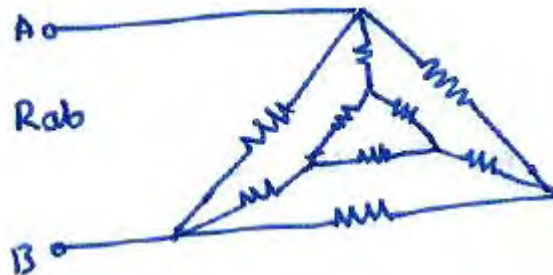- 2.a) Find R_{ab} in the below circuit, when all the resistor are having equal values.



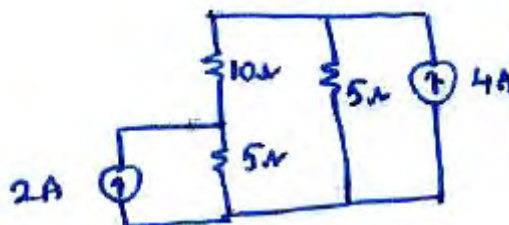- b) Find the voltages across the two current sources in the below circuit using Superposition Theorem. [8+7]



Code.No: A109211402

R09

SET-3

II B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
ELECTRICAL ENGINEERING
(MECHANICAL ENGINEERING)
(MECHATRONICS)


Time: 3hours

Max.Marks:75


Answer any FIVE questions
 All questions carry equal marks

- - -

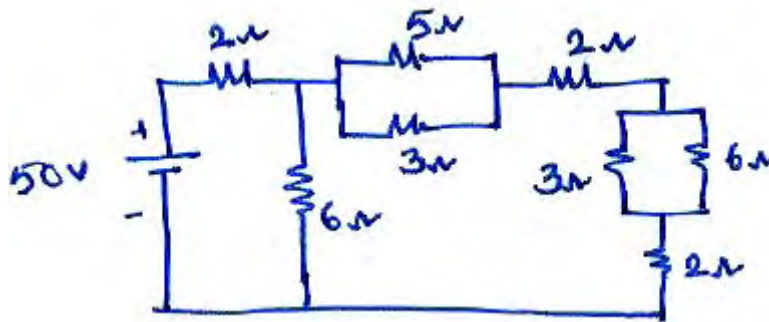
- 1.a) Find the current I in the below circuit.



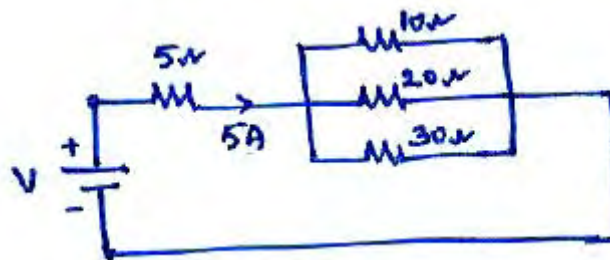- b) The current in the 5Ω resistance of the circuit shown below is $5A$. Find the current in the 10Ω resistor. Calculate the power absorbed by the 5Ω resistor. [8+7]



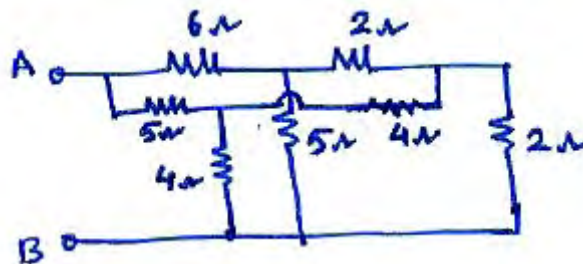
- 2.a) Determine the equivalent resistance across 'AB' terminals.




- b) State and explain maximum power transfer theorem.

[8+7]

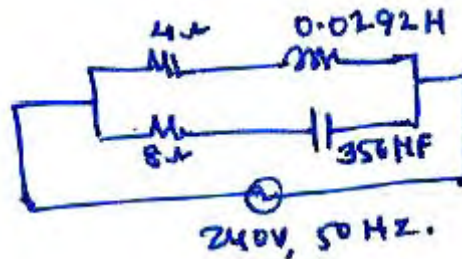- 3.a) In the below circuit, calculate the supply current, overall power factor and the total power supplied to the circuit.



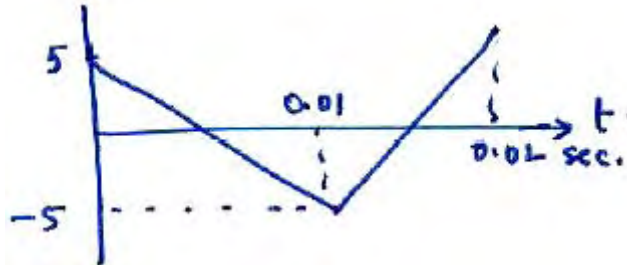- b) Find the form factor of the wave form shown below. [8+7]



- 4.a) Deduce the expression for regulation of a single phase transformer.
 b) A single phase transformer with a ratio of 240V/110V takes a no load current of 5A at 0.3 p. f. lagging. If secondary supplies a current of 95A at 0.88 p.f. lagging. Estimate the current taken by the primary. [8+7]
- 5.a) Explain the construction features of a dc machine with the help of neat diagrams.
 b) A 4 pole dc generator has 60 slots and 4 conductors per slot. The flux per pole is 0.03 Wb and speed is 900 rpm. Find the emf generated, if machine is
 i) Lap wound
 ii) Wave wound. [7+8]
- 6.a) A 240V DC series motor runs at 900 rpm taking a current of 30A. Calculate the speed if the load is reduced so that the motor is taking 20A. Total resistance of armature and field is $0.75\ \Omega$.
 b) Explain the various characteristics of DC shunt and series motors. [7+8]
- 7.a) Explain the construction and working principle of 3ϕ induction motor.
 b) A 3ϕ , 6-pole, 50Hz induction motor takes a power input of 30Kw at full load speed of 890 rmp. The total stator losses are 1500W and friction and wind age losses are 1 Kw. Calculate
 i) Slip
 ii) Shaft power
 iii) Efficiency. [8+7]
- 8.a) Explain the operation of the attraction type moving iron instruments?
 b) What are the merits of PMMC instruments? [7+8]

Code.No: A109211402

R09

SET-4


II B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
ELECTRICAL ENGINEERING
(MECHANICAL ENGINEERING)
(MECHATRONICS)

Time: 3hours


Max.Marks:75

Answer any FIVE questions
 All questions carry equal marks

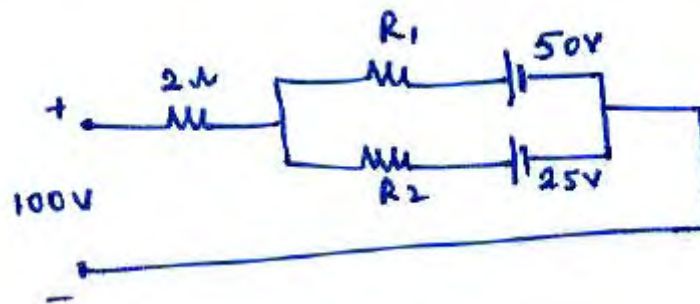
- 1.a) Define kirchhoff's laws and ohm's law.
 b) In the circuit shown below, what are the values of R_1 and R_2 , when current through R_1 is 2A and R_2 is 7A? What is the value of R_1 when the current flowing through R_2 is zero. [6+9]



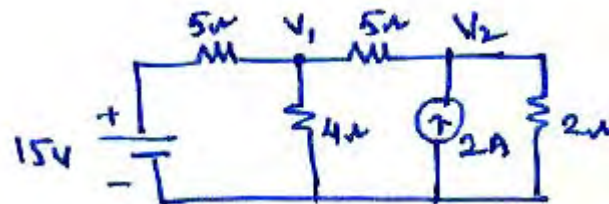
- 2.a) State and explain Thevenin's & Norton's theorems.
 b) Use nodal analysis to find V_1 and V_2 in the below circuit. [8+7]



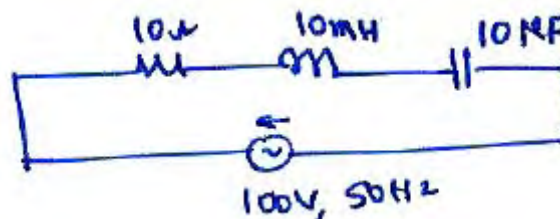- 3.a) In a series circuit shown in below Fig. Calculate the equivalent impedance, current in the circuit and the power factor.



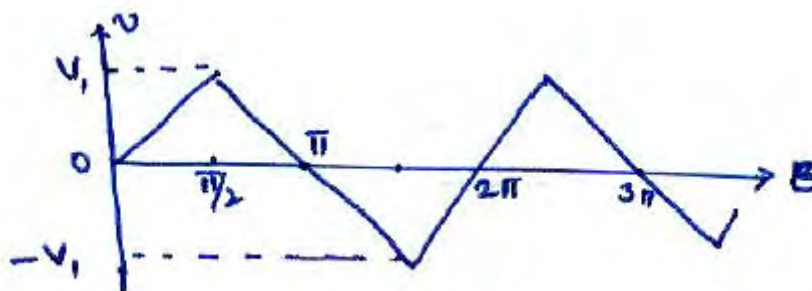- b) Calculate the RMS value of the voltage wave form shown below. [7+8]



- 4.a) Explain transformer as load with phasor diagram.
b) A 25KVA, 2500/250V, single phase transformer gave the following test results.
O.C. test: 250V, 1.2A, 100W
S.C test: 100V 8.7A, 340W.
Compute the equivalent circuit referred to HV and LV sides respectively. [8+7]
- 5.a) Derive the emf equation of a dc generator.
b) A short shunt Compound generator has armature, series field and shunt field resistances 0.03Ω , 0.05Ω and 250Ω respectively. If supply load current is 25A at a rated voltage of 220V. Find the emf generated and armature current. [8+7]
- 6.a) Deduce the condition for maximum efficiency of a DC motor.
b) A 250V DC shunt motor take a no-load current of 6A. Find its efficiency when it takes a line current of 20A when runs as a motor. The armature and field resistances are 0.5Ω and 200Ω respectively. [7+8]
- 7.a) Explain the principle of operation of a 3ϕ induction motor.
b) Derive the torque equation of a 3ϕ induction motor. [7+8]
- 8.a) Explain the various possible torques in a measuring instruments.
b) Explain the operation of the repulsion type moving iron instrument. [8+7]

FIRSTRANKER