

Code No: NR/RR 221003

NR/RR

Set No. 2

II B.Tech II Semester Examinations, December 2010

PULSE AND DIGITAL CIRCUITS

Common to Electronics And Control Engineering, Electronics And
Instrumentation Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Bring out the necessity and importance of Time base circuits. [6]
- (b) In the UJT sweep circuit, $V_{BB} = 20V$, $V_{yy} = 50V$, $R = 5k$, $C = 0.01$ micro F. UJT has $\eta = 0.5$. Calculate
 - i. amplitude of sweep signal
 - ii. Slope and displacement errors and
 - iii. estimated recovery time. [10]

Design a collector coupled monostable multi to meet the following specifications:

silicon n-p-n transistors are used in the design with $h_{fe}(\min) = 20$, V_{BE} cutoff voltage for the normally OFF transistor is $-1V$; I_{CBO} and voltage drops across saturated transistors are negligible. The base drive to the transistor in saturation is 60% in excess of minimum required. $V_{CC} = 9V$, $I_C = 3mA$, pulse width is 4msec. choose $R_{C1} = R_{C2}$ and $R_1 = R_2$. [16]

3. (a) A symmetrical square wave of peak to peak amplitude V and frequency ' f ' is applied to a high pass RC circuit. Find the percentage tilt. [12]
- (b) How can this tilt be reduced? [4]
4. (a) Calculate the output levels of the following circuit for inputs of 0 and -6 Volts and verify that the circuit is an inverter. What is the minimum value of h_{FE} required. Neglect junction saturation voltages and assume an ideal diode. (figure 2a) [8]

 


Figure 2a

- (b) Write about diode switching times. [8]

Code No: NR/RR 221003

NR/RR

Set No. 2

5. (a) Illustrate the terms 'synchronization' and 'frequency division' of a sweep generator. [8]
- (b) A free-running relaxation oscillator has sweep amplitude of 100 V and a period of 1 msec. Synchronizing pulses are applied to the device such that breakdown voltage is lowered by 50 V at each pulse. The synchronizing pulse frequency is 4 kHz. What is the amplitude and frequency of synchronized oscillator waveform? [8]
6. Explain the operation of an RC controlled free running blocking oscillator with neat sketch of circuit and voltage waveforms. Derive the expression for duty cycle. What are the advantages of the circuit? [16]
7. For the circuit shown in figure 8, make a plot of V_0 against V_i for the range of V_i from 0 to 50V. Indicate all slopes and voltage levels, and diode conducting region. Assume ideal diodes. [16]

 


Figure 8

8. (a) Distinguish between logic gate and sampling gate. [4]
- (b) Why is a sampling referred as a linear gate? [4]
- (c) Illustrate the principle of operation of a linear gate using series switch and shunts witch. What are the disadvantages? [8]

Code No: NR/RR 221003

NR/RR

Set No. 4

II B.Tech II Semester Examinations, December 2010

PULSE AND DIGITAL CIRCUITS

Common to Electronics And Control Engineering, Electronics And
Instrumentation Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

- Design a collector coupled monostable multi to meet the following specifications:
silicon n-p-n transistors are used in the design with $h_{fe}(\min)=20$, V_{BE} cutoff voltage for the normally OFF transistor is $-1V$; I_{CBO} and voltage drops across saturated transistors are negligible. The base drive to the transistor in saturation is 60% in excess of minimum required. $V_{cc}=9V$, $I_c=3mA$. pulse width is 4msec. choose $R_{C1}=R_{C2}$ and $R_1=R_2$. [16]
- Bring out the necessity and importance of Time base circuits. [6]
 - In the UJT sweep circuit, $V_{BB} = 20V$, $V_{yy} = 50V$, $R=5k$, $C=0.01$ micro F. UJT has $\eta=0.5$. Calculate
 - amplitude of sweep signal
 - Slope and displacement errors and
 - estimated recovery time. [10]
- For the circuit shown in figure 8, make a plot of V_o against V_i for the range of V_i from 0 to 50V. Indicate all slopes and voltage levels, and diode conducting region. Assume ideal diodes. [16]

 


Figure 8

- Distinguish between logic gate and sampling gate. [4]
 - Why is a sampling referred as a linear gate? [4]
 - Illustrate the principle of operation of a linear gate using series switch and shunts witch. What are the disadvantages? [8]
- Calculate the output levels of the following circuit for inputs of 0 and -6 Volts and verify that the circuit is an inverter. What is the minimum value of h_{FE} required. Neglect junction saturation voltages and assume an ideal diode. (figure 2a) [8]

Code No: NR/RR 221003

NR/RR

Set No. 4

 


Figure 2a

- (b) Write about diode switching times. [8]
6. (a) Illustrate the terms 'synchronization' and 'frequency division' of a sweep generator. [8]
- (b) A free-running relaxation oscillator has sweep amplitude of 100 V and a period of 1 msec. Synchronizing pulses are applied to the device such that breakdown voltage is lowered by 50 V at each pulse. The synchronizing pulse frequency is 4 kHz. What is the amplitude and frequency of synchronized oscillator waveform? [8]
7. (a) A symmetrical square wave of peak to peak amplitude V and frequency ' f ' is applied to a high pass RC circuit. Find the percentage tilt. [12]
- (b) How can this tilt be reduced? [4]
8. Explain the operation of an RC controlled free running blocking oscillator with neat sketch of circuit and voltage waveforms. Derive the expression for duty cycle. What are the advantages of the circuit? [16]

Code No: NR/RR 221003

NR/RR

Set No. 1

II B.Tech II Semester Examinations, December 2010

PULSE AND DIGITAL CIRCUITS

Common to Electronics And Control Engineering, Electronics And
Instrumentation Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Bring out the necessity and importance of Time base circuits. [6]
- (b) In the UJT sweep circuit, $V_{BB} = 20V$, $V_{yy} = 50V$, $R = 5k$, $C = 0.01$ micro F. UJT has $\eta = 0.5$. Calculate
 - i. amplitude of sweep signal
 - ii. Slope and displacement errors and
 - iii. estimated recovery time. [10]

Design a collector coupled monostable multi to meet the following specifications:

silicon n-p-n transistors are used in the design with $h_{fe}(\min) = 20$, V_{BE} cutoff voltage for the normally OFF transistor is $-1V$; I_{CBO} and voltage drops across saturated transistors are negligible. The base drive to the transistor in saturation is 60% in excess of minimum required. $V_{cc} = 9V$, $I_c = 3mA$, pulse width is 4msec. choose $R_{C1} = R_{C2}$ and $R_1 = R_2$. [16]

3. Explain the operation of an RC controlled free running blocking oscillator with neat sketch of circuit and voltage waveforms. Derive the expression for duty cycle. What are the advantages of the circuit? [16]
4. (a) Distinguish between logic gate and sampling gate. [4]
- (b) Why is a sampling referred as a linear gate? [4]
- (c) Illustrate the principle of operation of a linear gate using series switch and shunts witch. What are the disadvantages? [8]
5. For the circuit shown in figure 8 , make a plot of V_o against V_i for the range of V_i from 0 to 50V. Indicate all slopes and voltage levels, and diode conducting region. Assume ideal diodes. [16]

 


Figure 8

Code No: NR/RR 221003

NR/RR

Set No. 1

6. (a) Illustrate the terms 'synchronization' and 'frequency division' of a sweep generator. [8]
- (b) A free-running relaxation oscillator has sweep amplitude of 100 V and a period of 1 msec. Synchronizing pulses are applied to the device such that breakdown voltage is lowered by 50 V at each pulse. The synchronizing pulse frequency is 4 kHz. What is the amplitude and frequency of synchronized oscillator waveform? [8]
7. (a) A symmetrical square wave of peak to peak amplitude V and frequency ' f ' is applied to a high pass RC circuit. Find the percentage tilt. [12]
- (b) How can this tilt be reduced? [4]
8. (a) Calculate the output levels of the following circuit for inputs of 0 and -6 Volts and verify that the circuit is an inverter. What is the minimum value of h_{FE} required. Neglect junction saturation voltages and assume an ideal diode. (figure 2a) [8]

 


Figure 2a

- (b) Write about diode switching times. [8]

Code No: NR/RR 221003

NR/RR

Set No. 3

II B.Tech II Semester Examinations, December 2010

PULSE AND DIGITAL CIRCUITS

Common to Electronics And Control Engineering, Electronics And
Instrumentation Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Illustrate the terms 'synchronization' and 'frequency division' of a sweep generator. [8]
- (b) A free-running relaxation oscillator has sweep amplitude of 100 V and a period of 1 msec. Synchronizing pulses are applied to the device such that breakdown voltage is lowered by 50 V at each pulse. The synchronizing pulse frequency is 4 kHz. What is the amplitude and frequency of synchronized oscillator waveform? [8]
2. (a) Calculate the output levels of the following circuit for inputs of 0 and -6 Volts and verify that the circuit is an inverter. What is the minimum value of h_{FE} required. Neglect junction saturation voltages and assume an ideal diode. (figure 2a) [8]

 


Figure 2a

- (b) Write about diode switching times. [8]
3. Explain the operation of an RC controlled free running blocking oscillator with neat sketch of circuit and voltage waveforms. Derive the expression for duty cycle. What are the advantages of the circuit? [16]
4. Design a collector coupled monostable multi to meet the following specifications:
silicon n-p-n transistors are used in the design with $h_{fe}(\min)=20$, V_{BE} cutoff voltage for the normally OFF transistor is -1V; I_{CBO} and voltage drops across saturated transistors are negligible. The base drive to the transistor in saturation is 60% in excess of minimum required. $V_{CC}=9V$, $I_C=3mA$, pulse width is 4msec. choose $R_{C1}=R_{C2}$ and $R_1=R_2$. [16]
5. (a) A symmetrical square wave of peak to peak amplitude V and frequency 'f' is applied to a high pass RC circuit. Find the percentage tilt. [12]

Code No: NR/RR 221003

NR/RR

Set No. 3

- (b) How can this tilt be reduced? [4]
6. (a) Bring out the necessity and importance of Time base circuits. [6]
- (b) In the UJT sweep circuit, $V_{BB} = 20V$, $V_{yy} = 50V$, $R=5k$, $C=0.01$ micro F. UJT has $\eta=0.5$. Calculate
- amplitude of sweep signal
 - Slope and displacement errors and
 - estimated recovery time. [10]
7. (a) Distinguish between logic gate and sampling gate. [4]
- (b) Why is a sampling referred as a linear gate? [4]
- (c) Illustrate the principle of operation of a linear gate using series switch and shunts witch. What are the disadvantages? [8]
8. For the circuit shown in figure 8 , make a plot of V_o against V_i for the range of V_i from 0 to 50V. Indicate all slopes and voltage levels, and diode conducting region. Assume ideal diodes. [16]

 


Figure 8
