

Code No: NR220101

NR

Set No. 2

II B.Tech II Semester Examinations, December 2010
APPLIED ELECTRONICS
Civil Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. Discuss different types of strain gage configurations in detail. [16]
2. (a) Give the reason for employing negative voltage feedback in high gain amplifiers.
 (b) With a negative voltage feedback, an amplifier gives an output of 10V with an input of 0.5V. When feedback is removed, it requires 0.25V input for the same output. Calculate
 - i. gain without feedback
 - ii. Feedback factor B_V . [6+10]
3. Draw the block diagram of pH meter and explain its usefulness in measuring electrical quantities. [16]
4. (a) Write short notes on:
 - i. Frequency response of an amplifier, and
 - ii. Gain bandwidth product.
 (b) Draw the circuit of a common collector amplifier using NPN transistor and derive the expression for A_I , R_i , A_V & R_o . [6+10]
5. (a) Draw the structure of an n-channel JFET & explain its principle of operation.
 (b) Draw the static characteristic curves of an N-channel JFET & explain the different portions of the characteristics. Define the pinch-off voltage & indicate its location on drain characteristics. [8+8]
6. (a) Obtain 2 -input EX-OR gate using minimum number of NAND gates.
 (b) Obtain 2 - input EX-NOR gate using minimum number of NOR gates. [8+8]
7. (a) Explain the working of Zener diode under reverse bias and explain how it works as a voltage regulator.
 (b) Explain the concepts behind diffusion and transition capacitances of a PN junction diode with necessary details. [8+8]
8. (a) Explain the effects of probe compensation using waveforms.
 (b) Discuss the function of 10 to 1 probe. [8+8]

Code No: NR220101

NR

Set No. 4

II B.Tech II Semester Examinations, December 2010
APPLIED ELECTRONICS
Civil Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. (a) Explain the working of Zener diode under reverse bias and explain how it works as a voltage regulator.
- (b) Explain the concepts behind diffusion and transition capacitances of a PN junction diode with necessary details. [8+8]
2. (a) Obtain 2 -input EX-OR gate using minimum number of NAND gates.
- (b) Obtain 2 - input EX-NOR gate using minimum number of NOR gates. [8+8]
3. Draw the block diagram of pH meter and explain its usefulness in measuring electrical quantities. [16]
4. Discuss different types of strain gage configurations in detail. [16]
5. (a) Draw the structure of an n-channel JFET & explain it's principle of operation.
- (b) Draw the static characteristic curves of an N-channel JFET & explain the different portions of the characteristics. Define the pinch-off voltage & indicate it's location on drain characteristics. [8+8]
6. (a) Explain the effects of probe compensation using waveforms.
- (b) Discuss the function of 10 to 1 probe. [8+8]
7. (a) Give the reason for employing negative voltage feedback in high gain amplifiers.
- (b) With a negative voltage feedback, an amplifier gives an output of 10V with an input of 0.5V. When feedback is removed, it requires 0.25V input for the same output. Calculate
 - i. gain without feedback
 - ii. Feedback factor B_V . [6+10]
8. (a) Write short notes on:
 - i. Frequency response of an amplifier, and
 - ii. Gain bandwidth product.
- (b) Draw the circuit of a common collector amplifier using NPN transistor and derive the expression for A_I , R_i , A_V & R_o . [6+10]

Code No: NR220101

NR

Set No. 1

II B.Tech II Semester Examinations, December 2010
APPLIED ELECTRONICS
Civil Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Give the reason for employing negative voltage feedback in high gain amplifiers.
- (b) With a negative voltage feedback, an amplifier gives an output of 10V with an input of 0.5V. When feedback is removed, it requires 0.25V input for the same output. Calculate
 - i. gain without feedback
 - ii. Feedback factor B_V . [6+10]
2. (a) Write short notes on:
 - i. Frequency response of an amplifier, and
 - ii. Gain bandwidth product.
- (b) Draw the circuit of a common collector amplifier using NPN transistor and derive the expression for A_I , R_i , A_V & R_o . [6+10]
3. (a) Explain the working of Zener diode under reverse bias and explain how it works as a voltage regulator.
- (b) Explain the concepts behind diffusion and transition capacitances of a PN junction diode with necessary details. [8+8]
4. (a) Explain the effects of probe compensation using waveforms.
- (b) Discuss the function of 10 to 1 probe. [8+8]
5. (a) Draw the structure of an n-channel JFET & explain its principle of operation.
- (b) Draw the static characteristic curves of an N-channel JFET & explain the different portions of the characteristics. Define the pinch-off voltage & indicate its location on drain characteristics. [8+8]
6. Draw the block diagram of pH meter and explain its usefulness in measuring electrical quantities. [16]
7. (a) Obtain 2 -input EX-OR gate using minimum number of NAND gates.
- (b) Obtain 2 - input EX-NOR gate using minimum number of NOR gates. [8+8]
8. Discuss different types of strain gage configurations in detail. [16]

Code No: NR220101

NR

Set No. 3

II B.Tech II Semester Examinations, December 2010
APPLIED ELECTRONICS
Civil Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. (a) Explain the effects of probe compensation using waveforms.
 (b) Discuss the function of 10 to 1 probe. [8+8]
2. (a) Give the reason for employing negative voltage feedback in high gain amplifiers.
 (b) With a negative voltage feedback, an amplifier gives an output of 10V with an input of 0.5V. When feedback is removed, it requires 0.25V input for the same output. Calculate
 - i. gain without feedback
 - ii. Feedback factor B_V . [6+10]
3. (a) Write short notes on:
 - i. Frequency response of an amplifier, and
 - ii. Gain bandwidth product.
 (b) Draw the circuit of a common collector amplifier using NPN transistor and derive the expression for A_I , R_i , A_V & R_o . [6+10]
4. (a) Explain the working of Zener diode under reverse bias and explain how it works as a voltage regulator.
 (b) Explain the concepts behind diffusion and transition capacitances of a PN junction diode with necessary details. [8+8]
5. (a) Obtain 2 -input EX-OR gate using minimum number of NAND gates.
 (b) Obtain 2 - input EX-NOR gate using minimum number of NOR gates. [8+8]
6. Draw the block diagram of pH meter and explain its usefulness in measuring electrical quantities. [16]
7. (a) Draw the structure of an n-channel JFET & explain it's principle of operation.
 (b) Draw the static characteristic curves of an N-channel JFET & explain the different portions of the characteristics. Define the pinch-off voltage & indicate it's location on drain characteristics. [8+8]
8. Discuss different types of strain gage configurations in detail. [16]
