

Code.No: NR310404

NR

SET-1

III B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
LINEAR AND DIGITAL IC APPLICATIONS
(COMMON TO ECE, EIE, ECONE, MCT, ETM)

Time: 3hours**Max.Marks:80**

Answer any FIVE questions
All questions carry equal marks

- - -

1. a) Derive the voltage gain for non-inverting amplifier.
b) List different IC packages.
c) Draw the general block diagram of 741 and explain. [6+4+6]

2. a) Draw and explain logarithmic amplifier.
b) Define the following terms.
i) CMRR
ii) Slew rate
iii) Input offset voltage
iv) Input bias current. [8+8]

3. a) Draw and explain schematic diagram of IC565.
b) Write applications of PLL.
c) Write characteristics of three terminal regulators. [8+4+4]

4. a) Draw and explain balanced modulator IC1496
b) Write applications of 555 timer. [10+6]

5. a) Draw the BPF and explain.
b) Draw the ideal characteristics of LPF, HPF and BPF.
c) Explain need of all pass filters. [6+6+4]

6. a) Draw and explain DTL.
b) Draw the J-K Flip-Flop and explain operation with truth table. [8+8]

7. a) Explain interfacing of logic families.
b) Explain weighted Resistor R-2R ladder. [8+8]

8. a) Explain successive approximation with neat diagram.
b) What is sample and hold circuit and explain. [8+8]

--ooOoo--

Code.No: NR310404

NR

SET-2

III B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
LINEAR AND DIGITAL IC APPLICATIONS
(COMMON TO ECE, EIE, ECONE, MCT, ETM)

Time: 3hours**Max.Marks:80**

Answer any FIVE questions
All questions carry equal marks

- - -

1. a) Draw and explain schematic diagram of IC565.
 b) Write applications of PLL.
 c) Write characteristics of three terminal regulators. [8+4+4]

2. a) Draw and explain balanced modulator IC1496
 b) Write applications of 555 timer. [10+6]

3. a) Draw the BPF and explain.
 b) Draw the ideal characteristics of LPF, HPF and BPF.
 c) Explain need of all pass filters. [6+6+4]

4. a) Draw and explain DTL.
 b) Draw the J-K Flip-Flop and explain operation with truth table. [8+8]

5. a) Explain interfacing of logic families.
 b) Explain weighted Resistor R-2R ladder. [8+8]

6. a) Explain successive approximation with neat diagram.
 b) What is sample and hold circuit and explain. [8+8]

7. a) Derive the voltage gain for non-inverting amplifier.
 b) List different IC packages.
 c) Draw the general block diagram of 741 and explain. [6+4+6]

8. a) Draw and explain logarithmic amplifier.
 b) Define the following terms.
 i) CMRR
 ii) Slew rate
 iii) Input offset voltage
 iv) Input bias current. [8+8]

--ooOoo--

Code.No: NR310404

NR

SET-3

III B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
LINEAR AND DIGITAL IC APPLICATIONS
(COMMON TO ECE, EIE, ECONE, MCT, ETM)

Time: 3hours**Max.Marks:80**

Answer any FIVE questions
All questions carry equal marks

- - -

1. a) Draw the BPF and explain.
 b) Draw the ideal characteristics of LPF, HPF and BPF.
 c) Explain need of all pass filters. [6+6+4]

2. a) Draw and explain DTL.
 b) Draw the J-K Flip-Flop and explain operation with truth table. [8+8]

3. a) Explain interfacing of logic families.
 b) Explain weighted Resistor R-2R ladder. [8+8]

4. a) Explain successive approximation with neat diagram.
 b) What is sample and hold circuit and explain. [8+8]

5. a) Derive the voltage gain for non-inverting amplifier.
 b) List different IC packages.
 c) Draw the general block diagram of 741 and explain. [6+4+6]

6. a) Draw and explain logarithmic amplifier.
 b) Define the following terms.
 i) CMRR
 ii) Slew rate
 iii) Input offset voltage
 iv) Input bias current. [8+8]

7. a) Draw and explain schematic diagram of IC565.
 b) Write applications of PLL.
 c) Write characteristics of three terminal regulators. [8+4+4]

8. a) Draw and explain balanced modulator IC1496
 b) Write applications of 555 timer. [10+6]

--ooOoo--

Code.No: NR310404

NR

SET-4

III B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
LINEAR AND DIGITAL IC APPLICATIONS
(COMMON TO ECE, EIE, ECONE, MCT, ETM)

Time: 3hours**Max.Marks:80**

Answer any FIVE questions
All questions carry equal marks

- - -

1. a) Explain interfacing of logic families.
 b) Explain weighted Resister R-2R ladder. [8+8]
2. a) Explain successive approximation with neat diagram.
 b) What is sample and hold circuit and explain. [8+8]
3. a) Derive the voltage gain for non-inverting amplifier.
 b) List different IC packages.
 c) Draw the general block diagram of 741 and explain. [6+4+6]
4. a) Draw and explain logarithmic amplifier.
 b) Define the following terms.
 i) CMRR
 ii) Slew rate
 iii) Input offset voltage
 iv) Input bias current. [8+8]
5. a) Draw and explain schematic diagram of IC565.
 b) Write applications of PLL.
 c) Write characteristics of three terminal regulators. [8+4+4]
6. a) Draw and explain balanced modulator IC1496
 b) Write applications of 555 timer. [10+6]
7. a) Draw the BPF and explain.
 b) Draw the ideal characteristics of LPF, HPF and BPF.
 c) Explain need of all pass filters. [6+6+4]
8. a) Draw and explain DTL.
 b) Draw the J-K Flip-Flop and explain operation with truth table. [8+8]

--ooOoo--