

Code.No: R05010203

R05

SET-1


I B.TECH – EXAMINATIONS, DECEMBER - 2010
ELECTRICAL CIRCUITS
(COMMON TO EEE, E.CON.E, ICE)

Time: 3hours**Max.Marks:80**

Answer any FIVE questions
All questions carry equal marks

- - -

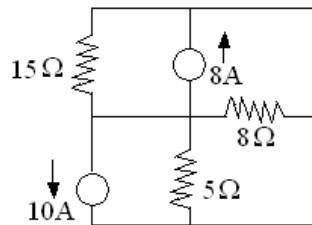- 1.a) Explain clearly the following:
 i) Active and Passive elements
 ii) Linear and Non linear elements
 iii) Unilateral and Bilateral elements.
- b) Determine the voltage drop across the 8 ohms resistor in the circuit shown using Kirchoff's law. [6+10]




- 2.a) Clearly explain the following:
 i) Self inductance (L)
 ii) Mutual inductance (M)
 iii) Dot convention.
- b) An Iron ring of mean length 50 cms has an air gap of 1 mm and a winding of 200 Turns. If the relative permeability of the Iron is 400, when a current of 1 Amp flows in the winding, determine the flux density Neglect leakage and fringing.
- c) State and explain Faraday's laws of electro magnetic induction. [6+6+4]
- 3.a) Define RMS value, Average value and form factor of an alternating quantity. Determine these values for a half wave rectified sine wave.
- b) A coil of 20 ohms resistance and inductance of 0.2H is connected in parallel with a capacitor of $100\mu F$. Determine the resonant frequency & input impedance at Resonance. [8+8]
- 4.a) Explain Two wattmeter method of measurement of power in a 3 phase system. Derive the expressions for the readings of two watt meters for measurement of power in a balanced 3 phase load.
- b) Each phase of a balanced star connected load consists of $R = 10$ ohms and $C = 10\mu F$. Calculate the line current and total real and reactive powers when a symmetrical 400V, 50 Hz, 3phase supply is applied to it. [8+8]

Code.No: R05010203

R05


SET-1

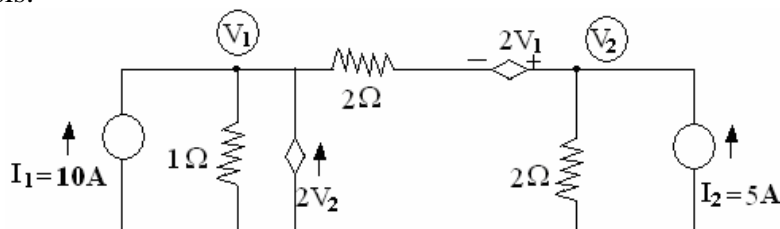- 5.a) Find the values of V_1 and V_2 in the network shown using Nodal method of Analysis.




- b) Define and explain the following with an example:
- Oriented Graph
 - Tree of a Graph
 - Tie set and a basic Tie set
 - Cut set and a basic Cut set.
- [10+6]

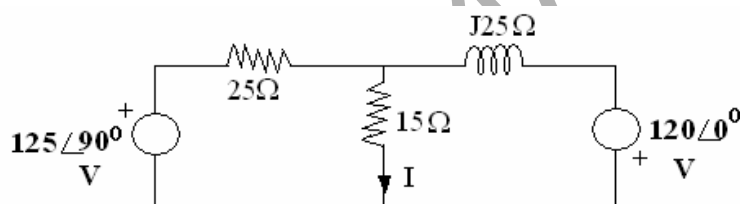- 6.a) State and explain Superposition Theorem.
- b) Determine the current I in the circuit shown using Superposition Theorem and Millman's Theorem.
- [4+12]



7. A series RLC circuit with $R = 3\Omega$, $L = 1H$ and $C = 0.5F$, is excited by a unit step voltage. Obtain the expression for $I(t)$ using Laplace Transform method. Assume that the circuit is initially relaxed. Sketch the variation of $I(t)$ and state whether the circuit is over damped, or under damped or critically damped.
- [16]

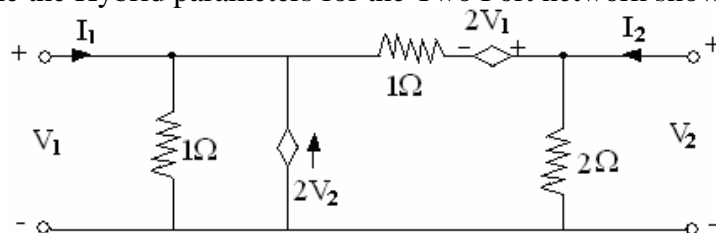- 8.a) Define Hybrid parameters of a Two Port network. Establish the relation between Hybrid Parameters and ABCD Parameters.
- b) Determine the Hybrid parameters for the Two Port network shown in figure.[8+8]



--oOo--

Code.No: R05010203

R05

SET-2


I B.TECH – EXAMINATIONS, DECEMBER - 2010
ELECTRICAL CIRCUITS
(COMMON TO EEE, E.CON.E, ICE)

Time: 3hours**Max.Marks:80**


Answer any FIVE questions
All questions carry equal marks

- - -

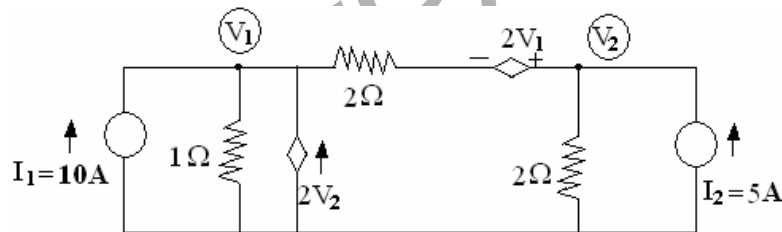- 1.a) Define RMS value, Average value and form factor of an alternating quantity. Determine these values for a half wave rectified sine wave.
- b) A coil of 20 ohms resistance and inductance of 0.2H is connected in parallel with a capacitor of $100\mu F$. Determine the resonant frequency & input impedance at Resonance. [8+8]
- 2.a) Explain Two wattmeter method of measurement of power in a 3 phase system. Derive the expressions for the readings of two watt meters for measurement of power in a balanced 3 phase load.
- b) Each phase of a balanced star connected load consists of $R = 10$ ohms and $C = 10\mu F$. Calculate the line current and total real and reactive powers when a symmetrical 400V, 50 Hz, 3phase supply is applied to it. [8+8]
- 3.a) Find the values of V_1 and V_2 in the network shown using Nodal method of Analysis.



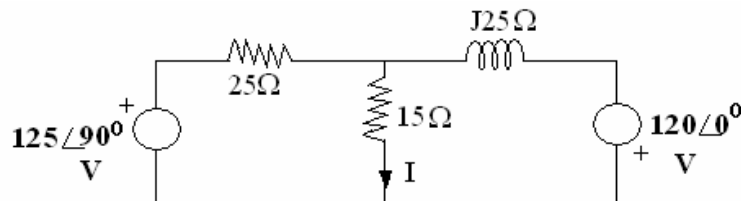- b) Define and explain the following with an example:
 - i) Oriented Graph
 - ii) Tree of a Graph
 - iii) Tie set and a basic Tie set
 - iv) Cut set and a basic Cut set.
 [10+6]
- 4.a) State and explain Superposition Theorem.
- b) Determine the current I in the circuit shown using Superposition Theorem and Millman's Theorem. [4+12]




Code.No: R05010203


R05

SET-2

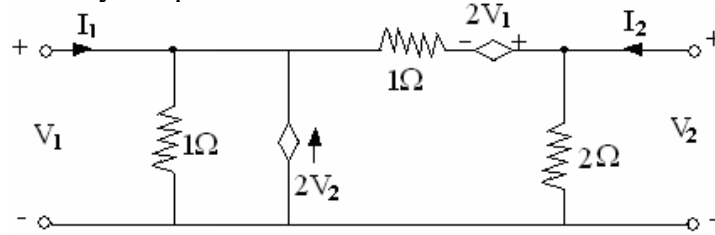5. A series RLC circuit with $R = 3\Omega$, $L = 1H$ and $C = 0.5F$, is excited by a unit step voltage. Obtain the expression for $I(t)$ using Laplace Transform method. Assume that the circuit is initially relaxed. Sketch the variation of $I(t)$ and state whether the circuit is over damped, or under damped or critically damped. [16]
- 6.a) Define Hybrid parameters of a Two Port network. Establish the relation between Hybrid Parameters and ABCD Parameters.
- b) Determine the Hybrid parameters for the Two Port network shown in figure.[8+8]



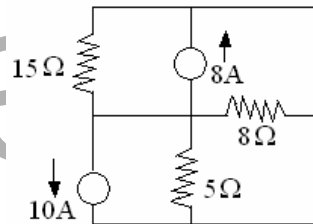- 7.a) Explain clearly the following:
- Active and Passive elements
 - Linear and Non linear elements
 - Unilateral and Bilateral elements.
- b) Determine the voltage drop across the 8 ohms resistor in the circuit shown using Kirchoff's law. [6+10]



- 8.a) Clearly explain the following:
- Self inductance (L)
 - Mutual inductance (M)
 - Dot convention.
- b) An Iron ring of mean length 50 cms has an air gap of 1 mm and a winding of 200 Turns. If the relative permeability of the Iron is 400, when a current of 1 Amp flows in the winding, determine the flux density Neglect leakage and fringing.
- c) State and explain Faraday's laws of electro magnetic induction. [6+6+4]

--oOo--

Code.No: R05010203

R05


SET-3

I B.TECH – EXAMINATIONS, DECEMBER - 2010
ELECTRICAL CIRCUITS
(COMMON TO EEE, E.CON.E, ICE)

Time: 3hours**Max.Marks:80**

Answer any FIVE questions
All questions carry equal marks

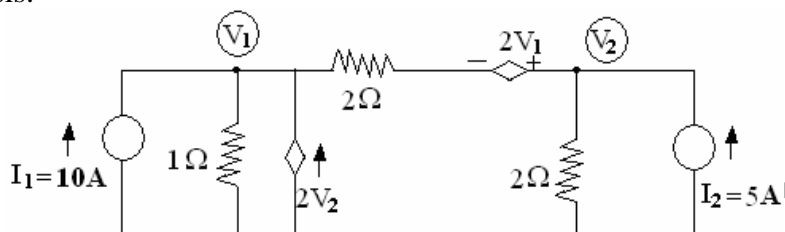- 1.a) Find the values of V_1 and V_2 in the network shown using Nodal method of Analysis.



- b) Define and explain the following with an example:


- Oriented Graph
- Tree of a Graph
- Tie set and a basic Tie set
- Cut set and a basic Cut set.

[10+6]

- 2.a) State and explain Superposition Theorem.

- b) Determine the current I in the circuit shown using Superposition Theorem and Millman's Theorem.

[4+12]

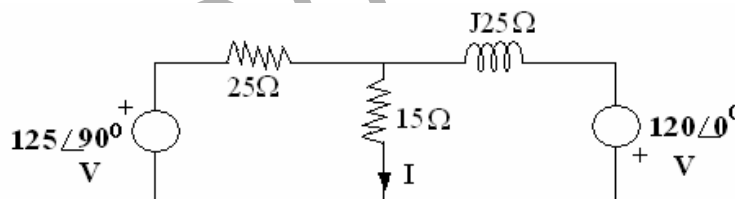


3. A series RLC circuit with $R = 3\Omega$, $L = 1H$ and $C = 0.5F$, is excited by a unit step voltage. Obtain the expression for $I(t)$ using Laplace Transform method. Assume that the circuit is initially relaxed. Sketch the variation of $I(t)$ and state whether the circuit is over damped, or under damped or critically damped.

[16]

- 4.a) Define Hybrid parameters of a Two Port network. Establish the relation between Hybrid Parameters and ABCD Parameters.

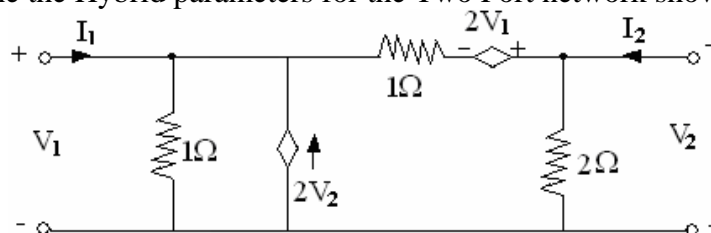- b) Determine the Hybrid parameters for the Two Port network shown in figure.[8+8]




Code.No: R05010203

R05

SET-3

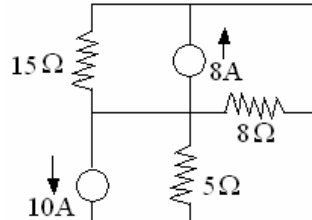- 5.a) Explain clearly the following:
- Active and Passive elements
 - Linear and Non linear elements
 - Unilateral and Bilateral elements.
- b) Determine the voltage drop across the 8 ohms resistor in the circuit shown using Kirchoff's law. [6+10]



- 6.a) Clearly explain the following:
- Self inductance (L)
 - Mutual inductance (M)
 - Dot convention.
- b) An Iron ring of mean length 50 cms has an air gap of 1 mm and a winding of 200 Turns. If the relative permeability of the Iron is 400, when a current of 1 Amp flows in the winding, determine the flux density Neglect leakage and fringing.
- c) State and explain Faraday's laws of electro magnetic induction. [6+6+4]
- 7.a) Define RMS value, Average value and form factor of an alternating quantity. Determine these values for a half wave rectified sine wave.
- b) A coil of 20 ohms resistance and inductance of 0.2H is connected in parallel with a capacitor of $100\mu F$. Determine the resonant frequency & input impedance at Resonance. [8+8]
- 8.a) Explain Two wattmeter method of measurement of power in a 3 phase system. Derive the expressions for the readings of two watt meters for measurement of power in a balanced 3 phase load.
- b) Each phase of a balanced star connected load consists of $R = 10$ ohms and $C = 10\mu F$. Calculate the line current and total real and reactive powers when a symmetrical 400V, 50 Hz, 3phase supply is applied to it. [8+8]

--oOo--

Code.No: R05010203

R05

SET-4


I B.TECH – EXAMINATIONS, DECEMBER - 2010
ELECTRICAL CIRCUITS
(COMMON TO EEE, E.CON.E, ICE)

Time: 3hours**Max.Marks:80**


Answer any FIVE questions
All questions carry equal marks

- - -

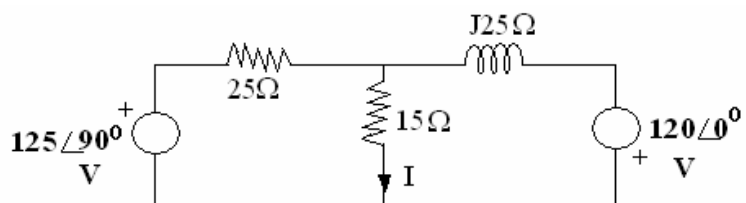
- 1.a) State and explain Superposition Theorem.
 b) Determine the current I in the circuit shown using Superposition Theorem and Millman's Theorem. [4+12]



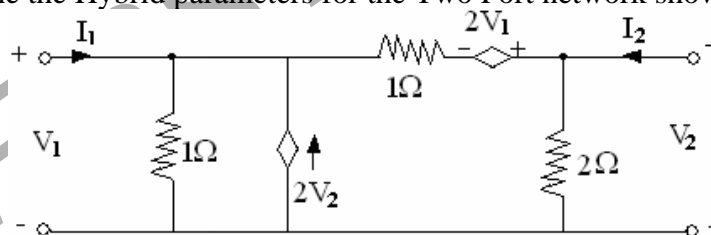2. A series RLC circuit with $R = 3\Omega$, $L = 1H$ and $C = 0.5F$, is excited by a unit step voltage. Obtain the expression for $I(t)$ using Laplace Transform method. Assume that the circuit is initially relaxed. Sketch the variation of $I(t)$ and state whether the circuit is over damped, or under damped or critically damped. [16]
- 3.a) Define Hybrid parameters of a Two Port network. Establish the relation between Hybrid Parameters and ABCD Parameters.
 b) Determine the Hybrid parameters for the Two Port network shown in figure.[8+8]



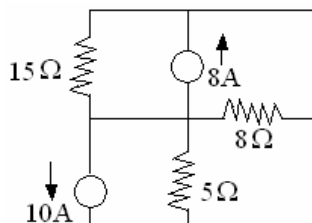- 4.a) Explain clearly the following:
 i) Active and Passive elements
 ii) Linear and Non linear elements
 iii) Unilateral and Bilateral elements.
 b) Determine the voltage drop across the 8 ohms resistor in the circuit shown using Kirchoff's law. [6+10]




Code.No: R05010203

R05

SET-4

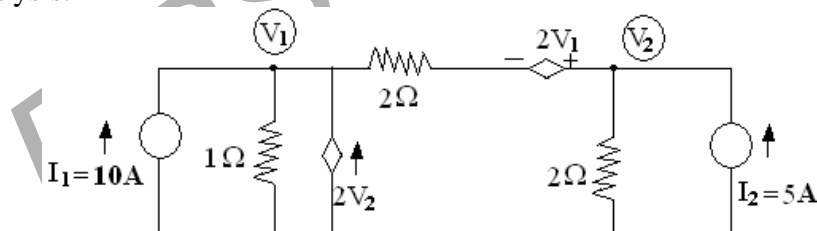- 5.a) Clearly explain the following:
- Self inductance (L)
 - Mutual inductance (M)
 - Dot convention.
- b) An Iron ring of mean length 50 cms has an air gap of 1 mm and a winding of 200 Turns. If the relative permeability of the Iron is 400, when a current of 1 Amp flows in the winding, determine the flux density Neglect leakage and fringing.
- c) State and explain Faraday's laws of electro magnetic induction. [6+6+4]
- 6.a) Define RMS value, Average value and form factor of an alternating quantity. Determine these values for a half wave rectified sine wave.
- b) A coil of 20 ohms resistance and inductance of 0.2H is connected in parallel with a capacitor of $100\mu F$. Determine the resonant frequency & input impedance at Resonance. [8+8]
- 7.a) Explain Two wattmeter method of measurement of power in a 3 phase system. Derive the expressions for the readings of two watt meters for measurement of power in a balanced 3 phase load.
- b) Each phase of a balanced star connected load consists of $R = 10$ ohms and $C = 10\mu F$. Calculate the line current and total real and reactive powers when a symmetrical 400V, 50 Hz, 3phase supply is applied to it. [8+8]
- 8.a) Find the values of V_1 and V_2 in the network shown using Nodal method of Analysis.



- b) Define and explain the following with an example:
- Oriented Graph
 - Tree of a Graph
 - Tie set and a basic Tie set
 - Cut set and a basic Cut set.
- [10+6]

--oOo--