

Code.No: R05010401

R05

SET-1


I B.TECH – EXAMINATIONS, DECEMBER - 2010
NETWORK ANALYSIS
(COMMON TO ECE, EIE, BME, ETM, ECC)

Time: 3hours**Max.Marks:80**


Answer any FIVE questions
All questions carry equal marks

- - -

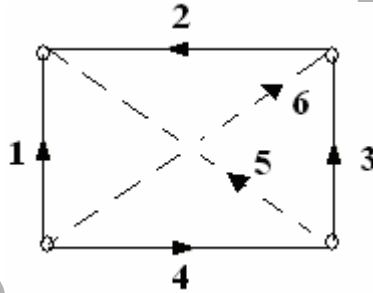- 1.a) Distinguish between:
 i) Ideal and practical sources and
 ii) Dependent and independent sources.
- b) The current in a 15 mH inductor can be expressed as $i(t) = [2 - e^{-1000t}] \times 10^{-3} \text{ Amps}$.
 Find:
 i) The voltage across the inductor $u(t)$ and
 ii) The instantaneous power $p(t)$.
- c) Write the basic Tie set matrix for the graph shown in figure, taking the Tree consisting of branches 2, 3, 4. [4+6+6]



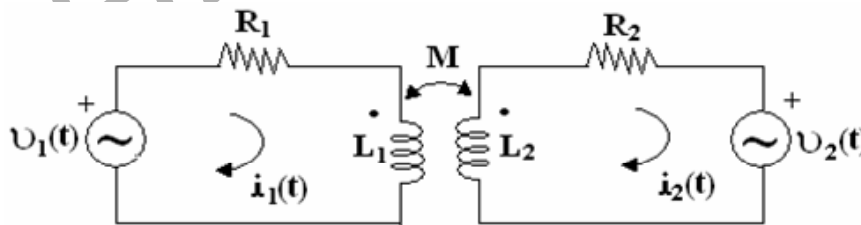- 2.a) Obtain the conductively coupled T-equivalent for the magnetically coupled circuit shown in figure.




- b) An Iron ring has a mean diameter of 25 cms, and a C.S. area of 4 cm^2 and is wound with 1000 Turns. An air gap of 1.5 mm width is cut in the ring. Determine the current required in the coil to produce a flux of 0.1 mwb in the air gap. The relative permeability of Iron is 800. Neglect leakage. [8+8]
- 3.a) Define Q-factor. Derive an equation showing the relation between Q-factor and Band width. What is selectivity and how it is related to Q-factor.
- b) Derive the expression for $i(t)$ when the switch S is suddenly closed at $t = 0$ in the circuit shown in figure. Sketch the variation of $i(t)$, $v_R(t)$ and $v_L(t)$ with respect to Time.

Code.No: R05010401


R05

SET-1

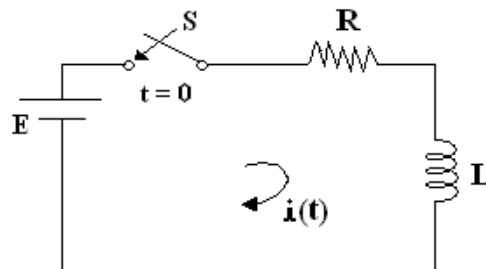


What is the time constant of the above circuit and explain its significance? [8+8]

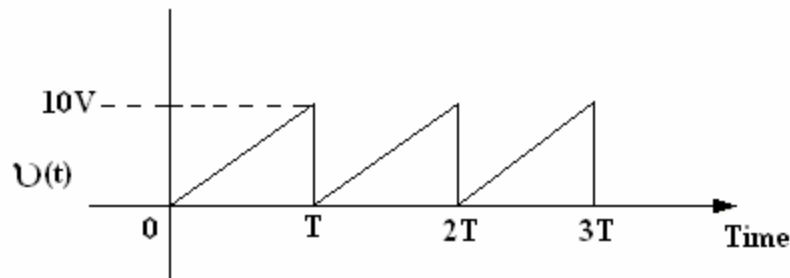
- 4.a) Define RMS value, Average value and form factor of an alternating quantity. Determine these values for the periodic function shown in figure.



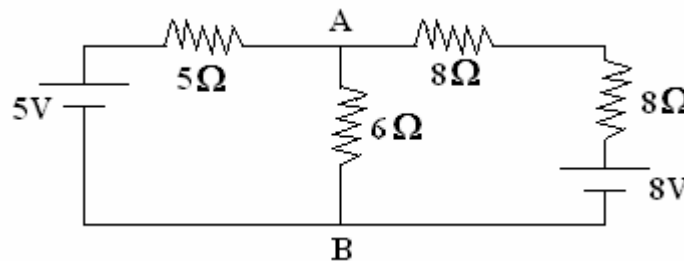
- b) A series R-L circuit with $R = 5 \text{ ohms}$ and $L = 0.2\text{H}$ has an applied voltage source of $v(t) = 10e^{-100t}$ applied at $t = 0$. Determine the current through the circuit $i(t)$. Use Laplace Transform method of solution. [8+8]
- 5.a) State and explain Norton's Theorem.
- b) Obtain Norton's Equivalent for the circuit shown with respect to terminals A and B.



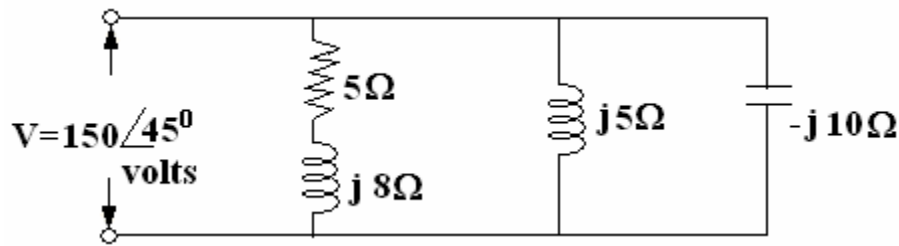
- c) Obtain the branch currents in the circuit shown and draw the phasor diagram. [4+6+6]



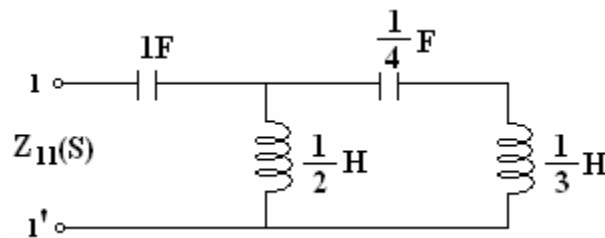- 6.a) Find the driving point impedance function $Z_{11}(S)$ of the LC network shown in figure.



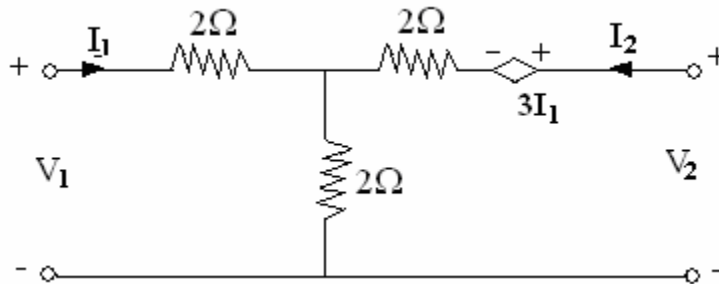- b) Determine the 'h' parameters of the network shown in figure. [8+8]



- 7.a) Explain clearly the following terms:
- Propagation constant
 - Attenuation.
- b) A symmetrical T-section has an inductance of 0.47H in each series arm and a 300 μF capacitor in the shunt arm.
- Find the characteristic impedance at frequencies of 50 Hz and 100 Hz.
 - If the T-section is terminated in the characteristic impedance, find the ratio of load current to input current at both the frequencies. [6+10]
- 8.a) What is an LC immittance function? State the properties of such functions.
- b) Design a constant 'K' T-section low pass filter having cutoff frequency of 2 kHz and nominal characteristic impedance of 600 ohms. [8+8]

--oOo--

Code.No: R05010401

R05

SET-2


I B.TECH – EXAMINATIONS, DECEMBER - 2010
NETWORK ANALYSIS
(COMMON TO ECE, EIE, BME, ETM, ECC)

Time: 3hours**Max.Marks:80**

Answer any FIVE questions
All questions carry equal marks


- - -

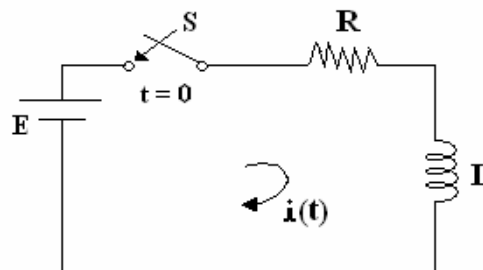- 1.a) Define Q-factor. Derive an equation showing the relation between Q-factor and Band width. What is selectivity and how it is related to Q-factor.
- b) Derive the expression for $i(t)$ when the switch S is suddenly closed at $t = 0$ in the circuit shown in figure. Sketch the variation of $i(t)$, $v_R(t)$ and $v_L(t)$ with respect to Time.




What is the time constant of the above circuit and explain its significance? [8+8]

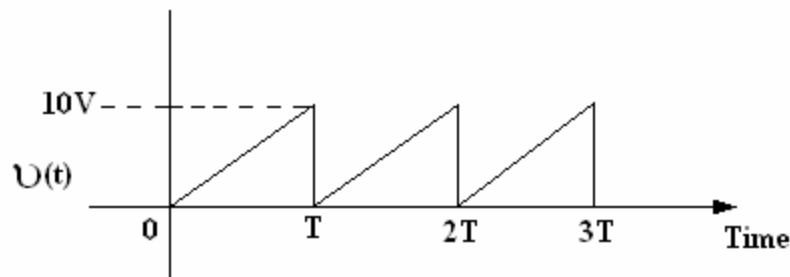- 2.a) Define RMS value, Average value and form factor of an alternating quantity. Determine these values for the periodic function shown in figure.



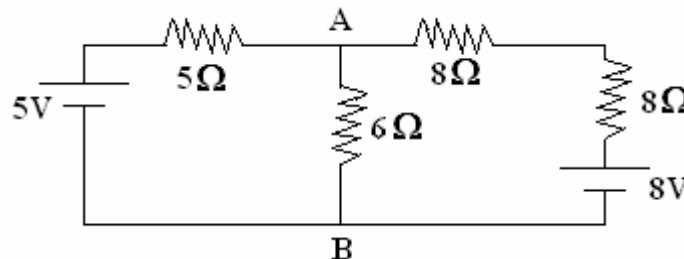- b) A series R-L circuit with $R = 5 \text{ ohms}$ and $L = 0.2\text{H}$ has an applied voltage source of $v(t) = 10e^{-100t}$ applied at $t = 0$. Determine the current through the circuit $i(t)$. Use Laplace Transform method of solution. [8+8]
- 3.a) State and explain Norton's Theorem.
- b) Obtain Norton's Equivalent for the circuit shown with respect to terminals A and B.




Code.No: R05010401


R05

SET-2

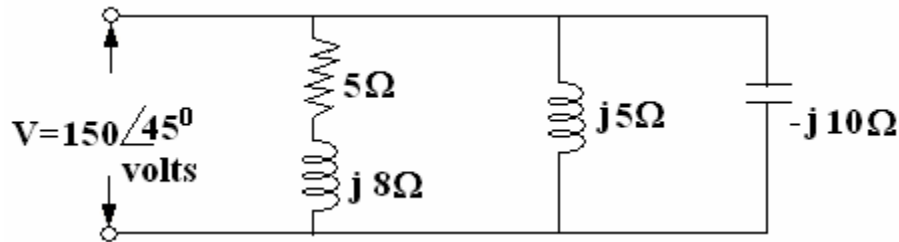
- c) Obtain the branch currents in the circuit shown and draw the phasor diagram. [4+6+6]



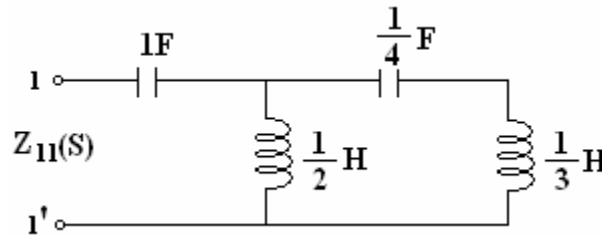- 4.a) Find the driving point impedance function $Z_{11}(S)$ of the LC network shown in figure.



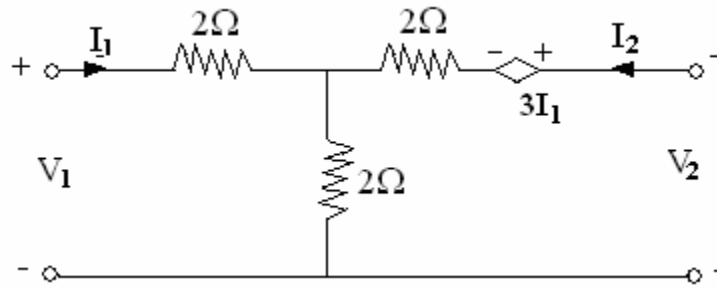- b) Determine the 'h' parameters of the network shown in figure. [8+8]




- 5.a) Explain clearly the following terms:
 i) Propagation constant and
 ii) Attenuation.
- b) A symmetrical T-section has an inductance of 0.47H in each series arm and a 300 μF capacitor in the shunt arm.
 i) Find the characteristic impedance at frequencies of 50 Hz and 100 Hz.
 ii) If the T-section is terminated in the characteristic impedance, find the ratio of load current to input current at both the frequencies. [6+10]
- 6.a) What is an LC immittance function? State the properties of such functions.
- b) Design a constant 'K' T-section low pass filter having cutoff frequency of 2 kHz and nominal characteristic impedance of 600 ohms. [8+8]

Code.No: R05010401


R05

SET-2

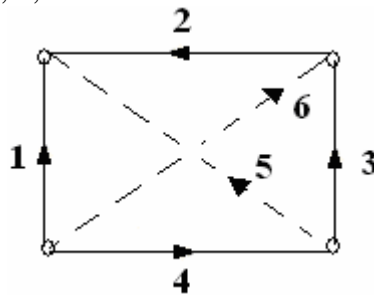- 7.a) Distinguish between:
- Ideal and practical sources and
 - Dependent and independent sources.
- b) The current in a 15 mH inductor can be expressed as $i(t) = [2 - e^{-1000t}] \times 10^{-3} \text{ Amps}$.
Find:
- The voltage across the inductor $u(t)$ and
 - The instantaneous power $p(t)$.
- c) Write the basic Tie set matrix for the graph shown in figure, taking the Tree consisting of branches 2, 3, 4. [4+6+6]



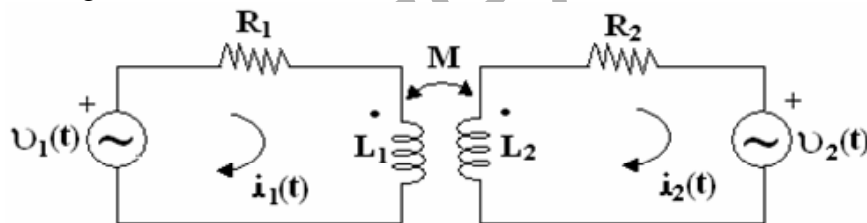- 8.a) Obtain the conductively coupled T-equivalent for the magnetically coupled circuit shown in figure.



- b) An Iron ring has a mean diameter of 25 cms, and a C.S. area of 4 cm^2 and is wound with 1000 Turns. An air gap of 1.5 mm width is cut in the ring. Determine the current required in the coil to produce a flux of 0.1 mwb in the air gap. The relative permeability of Iron is 800. Neglect leakage. [8+8]

--oOo--

Code.No: R05010401

R05


SET-3

I B.TECH – EXAMINATIONS, DECEMBER - 2010
NETWORK ANALYSIS
(COMMON TO ECE, EIE, BME, ETM, ECC)


Time: 3hours**Max.Marks:80**

Answer any FIVE questions
All questions carry equal marks

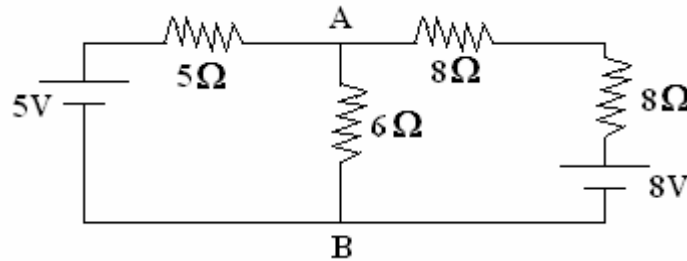
- 1.a) State and explain Norton's Theorem.
 b) Obtain Norton's Equivalent for the circuit shown with respect to terminals A and B.



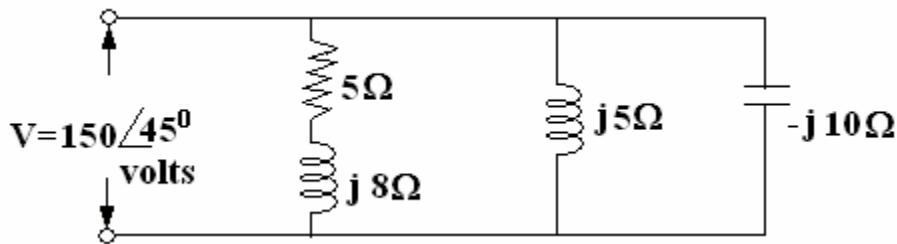- c) Obtain the branch currents in the circuit shown and draw the phasor diagram. [4+6+6]



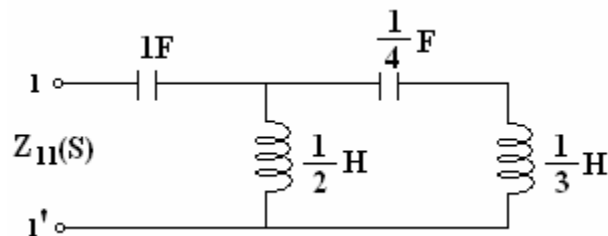- 2.a) Find the driving point impedance function $Z_{11}(S)$ of the LC network shown in figure.




- b) Determine the 'h' parameters of the network shown in figure.

[8+8]


Code.No: R05010401

R05

SET-3

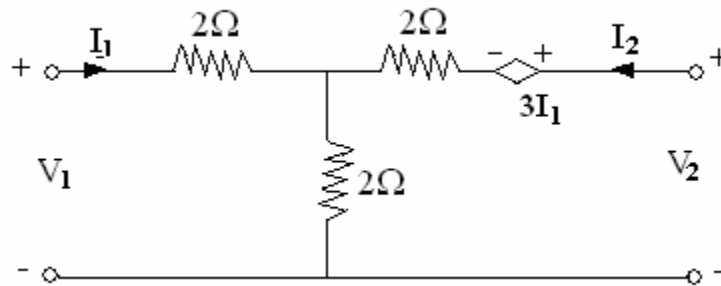

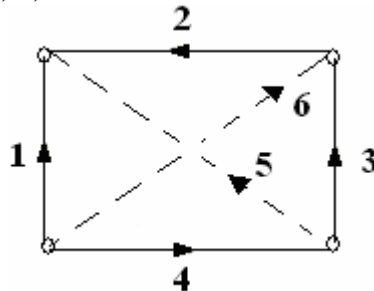- 3.a) Explain clearly the following terms:
- Propagation constant and
 - Attenuation.
- b) A symmetrical T-section has an inductance of 0.47H in each series arm and a $300\ \mu\text{F}$ capacitor in the shunt arm.
- Find the characteristic impedance at frequencies of 50 Hz and 100 Hz .
 - If the T-section is terminated in the characteristic impedance, find the ratio of load current to input current at both the frequencies. [6+10]
- 4.a) What is an LC immittance function? State the properties of such functions.
- b) Design a constant 'K' T-section low pass filter having cutoff frequency of 2 kHz and nominal characteristic impedance of 600 ohms . [8+8]
- 5.a) Distinguish between:
- Ideal and practical sources and
 - Dependent and independent sources.
- b) The current in a 15 mH inductor can be expressed as $i(t) = [2 - e^{-1000t}] \times 10^{-3}\text{ Amps}$. Find:
- The voltage across the inductor $u(t)$ and
 - The instantaneous power $p(t)$.
- c) Write the basic Tie set matrix for the graph shown in figure, taking the Tree consisting of branches 2, 3, 4. [4+6+6]




Code.No: R05010401


R05

SET-3

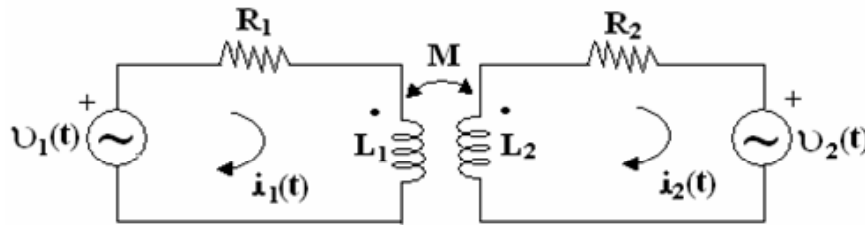- 6.a) Obtain the conductively coupled T-equivalent for the magnetically coupled circuit shown in figure.




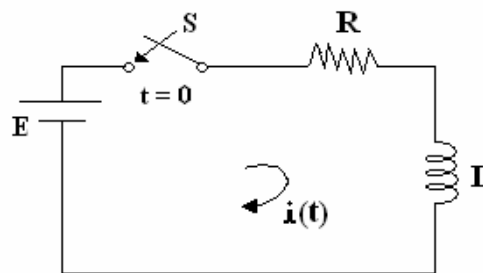- b) An Iron ring has a mean diameter of 25 cms, and a C.S. area of 4 cm^2 and is wound with 1000 Turns. An air gap of 1.5 mm width is cut in the ring. Determine the current required in the coil to produce a flux of 0.1 mwb in the air gap. The relative permeability of Iron is 800. Neglect leakage. [8+8]
- 7.a) Define Q-factor. Derive an equation showing the relation between Q-factor and Band width. What is selectivity and how it is related to Q-factor.
- b) Derive the expression for $i(t)$ when the switch S is suddenly closed at $t = 0$ in the circuit shown in figure. Sketch the variation of $i(t)$, $v_R(t)$ and $v_L(t)$ with respect to Time.



What is the time constant of the above circuit and explain its significance? [8+8]

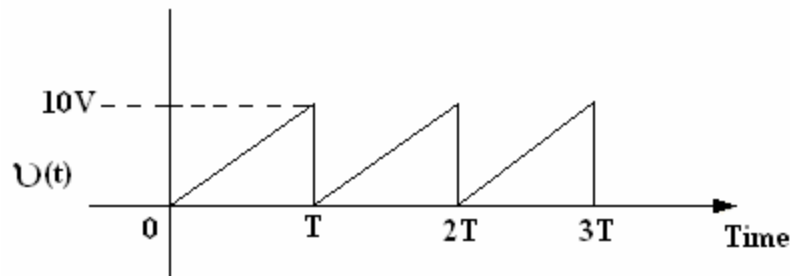- 8.a) Define RMS value, Average value and form factor of an alternating quantity. Determine these values for the periodic function shown in figure.



- b) A series R-L circuit with $R = 5 \text{ ohms}$ and $L = 0.2\text{H}$ has an applied voltage source of $v(t) = 10e^{-100t}$ applied at $t = 0$. Determine the current through the circuit $i(t)$. Use Laplace Transform method of solution. [8+8]

--oOo--

Code.No: R05010401

R05

SET-4


I B.TECH – EXAMINATIONS, DECEMBER - 2010
NETWORK ANALYSIS
(COMMON TO ECE, EIE, BME, ETM, ECC)

Time: 3hours**Max.Marks:80**


Answer any FIVE questions
All questions carry equal marks

- - -

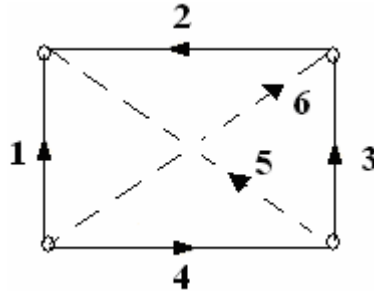- 1.a) Explain clearly the following terms:
 - i) Propagation constant and
 - ii) Attenuation.
- b) A symmetrical T-section has an inductance of 0.47H in each series arm and a 300 μF capacitor in the shunt arm.
 - i) Find the characteristic impedance at frequencies of 50 Hz and 100 Hz.
 - ii) If the T-section is terminated in the characteristic impedance, find the ratio of load current to input current at both the frequencies. [6+10]
- 2.a) What is an LC immittance function? State the properties of such functions.
- b) Design a constant 'K' T-section low pass filter having cutoff frequency of 2 kHz and nominal characteristic impedance of 600 ohms. [8+8]
- 3.a) Distinguish between:
 - i) Ideal and practical sources and
 - ii) Dependent and independent sources.
- b) The current in a 15 mH inductor can be expressed as $i(t) = [2 - e^{-1000t}] \times 10^{-3}$ Amps .
 Find:
 - i) The voltage across the inductor $u(t)$ and
 - ii) The instantaneous power $p(t)$.
- c) Write the basic Tie set matrix for the graph shown in figure, taking the Tree consisting of branches 2, 3, 4. [4+6+6]



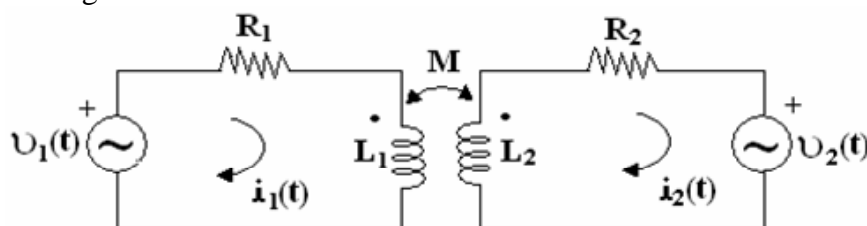- 4.a) Obtain the conductively coupled T-equivalent for the magnetically coupled circuit shown in figure.




Code.No: R05010401

R05


SET-4

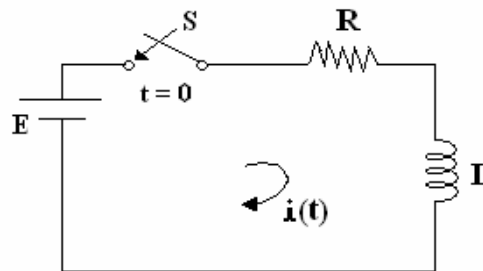- b) An Iron ring has a mean diameter of 25 cms, and a C.S. area of 4 cm^2 and is wound with 1000 Turns. An air gap of 1.5 mm width is cut in the ring. Determine the current required in the coil to produce a flux of 0.1 mwb in the air gap. The relative permeability of Iron is 800. Neglect leakage. [8+8]
- 5.a) Define Q-factor. Derive an equation showing the relation between Q-factor and Band width. What is selectivity and how it is related to Q-factor.
- b) Derive the expression for $i(t)$ when the switch S is suddenly closed at $t = 0$ in the circuit shown in figure. Sketch the variation of $i(t)$, $v_R(t)$ and $v_L(t)$ with respect to Time.



What is the time constant of the above circuit and explain its significance? [8+8]

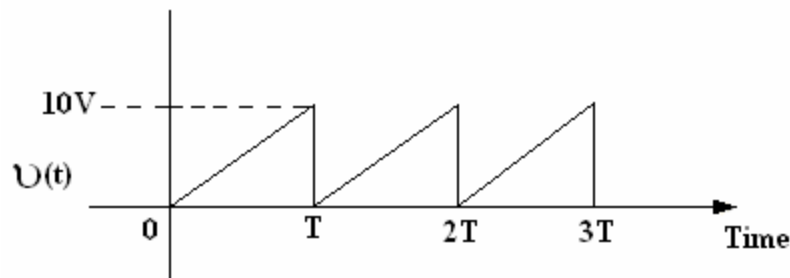- 6.a) Define RMS value, Average value and form factor of an alternating quantity. Determine these values for the periodic function shown in figure.




- b) A series R-L circuit with $R = 5 \text{ ohms}$ and $L = 0.2\text{H}$ has an applied voltage source of $v(t) = 10e^{-100t}$ applied at $t = 0$. Determine the current through the circuit $i(t)$. Use Laplace Transform method of solution. [8+8]

Code.No: R05010401


R05

SET-4

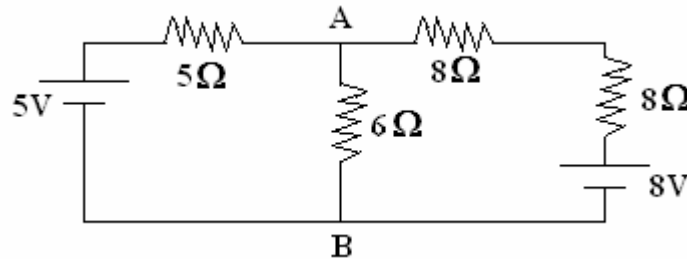
- 7.a) State and explain Norton's Theorem.
 b) Obtain Norton's Equivalent for the circuit shown with respect to terminals A and B.



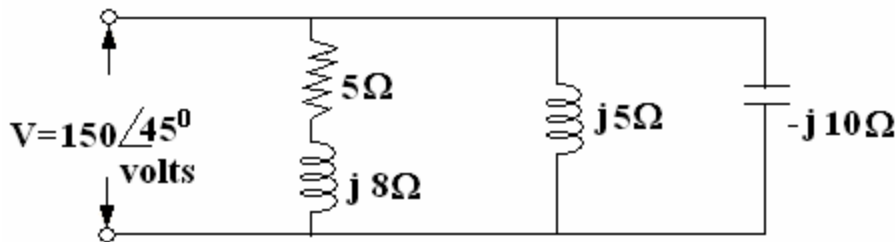- c) Obtain the branch currents in the circuit shown and draw the phasor diagram. [4+6+6]



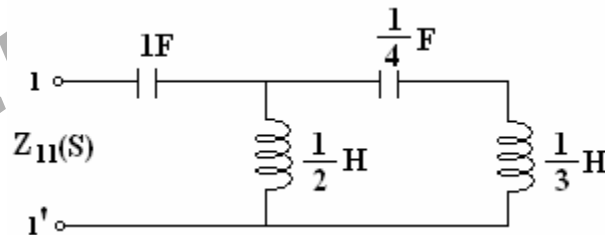- 8.a) Find the driving point impedance function $Z_{11}(s)$ of the LC network shown in figure.



- b) Determine the 'h' parameters of the network shown in figure. [8+8]

