

Code No: R05210204

R05**Set No. 2**

II B.Tech I Semester Examinations, November 2010

SWITCHING THEORY AND LOGIC DESIGN

Common to BME, ICE, E.COMP.E, E.CONT.E, EIE, EEE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

- Explain, How error occurred in a data transmission can be detected using parity bit. [6]
 - Perform the subtraction with the following unsigned binary numbers by taking the 2's complement of the subtrahend. [5 × 2 = 10]
 - 101011 - 111000
 - 1110 - 110010
 - 11010 - 1101
 - 110 - 101000
 - 11010 - 10000
- Minimise on the map the five variable function. [16]
 $F = \sum m(0, 1, 4, 5, 6, 13, 14, 15, 22, 24, 25, 28, 29, 30, 31)$
- A Clocked sequential circuit with two inputs x and y and a single output Z using J - K flip flops is as shown in figure 7:

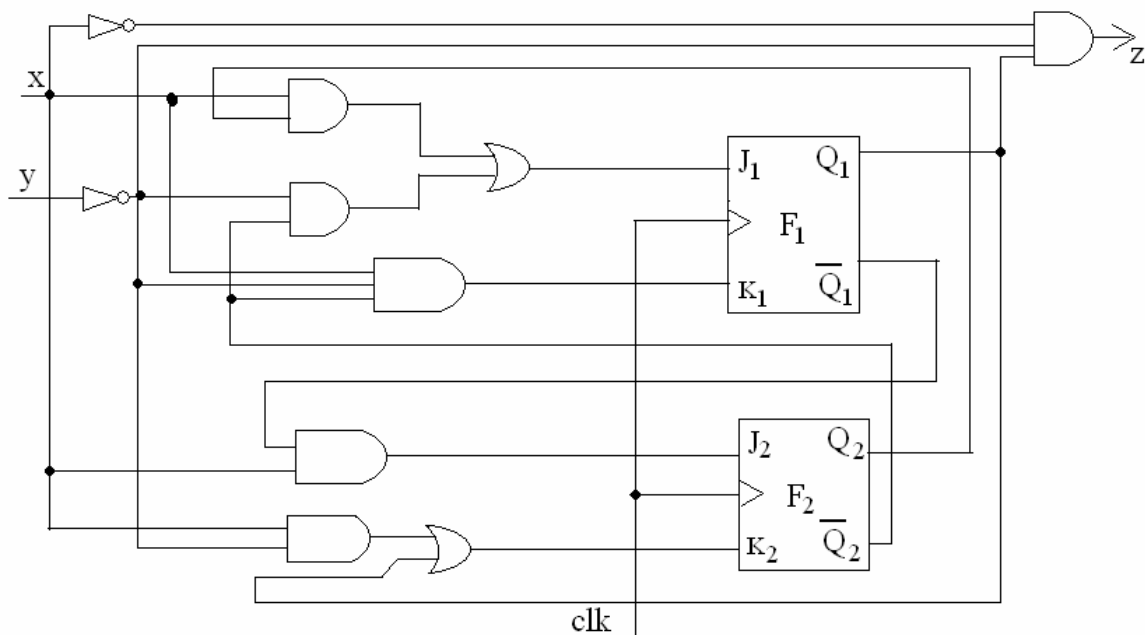


Figure 7

Code No: R05210204

R05

Set No. 2

- (a) Obtain input equations.
 - (b) List the state table
 - (c) Draw the corresponding state diagram.
 - (d) Derive state - equations. [4+4+4+4]
4. (a) List the PLA programming table for the BCD to excess-3 code converter.
- (b) A ROM chip of $4,096 \times 8$ bits has two chip select inputs and operates from a 5-volt power supply. How many pins are needed for the integrated circuit package? Draw the block diagram of this ROM. [8+8]
5. For the ASM chart given below figure 8:

FIRSTRANKER

Code No: R05210204

R05

Set No. 2

 


Figure 8

- (a) Draw the state diagram.
- (b) Design the control unit using D flip-flops and a decoder. [8+8]
6. (a) Using the method of flip flop conversion carry out the following conversions.
- i. S-R to T
 - ii. J-K to D [4x2=8]
- (b) Verify the circuit and explain its function. With the timing waveforms. Shown in figure 1 [8]

Code No: R05210204

R05

Set No. 2

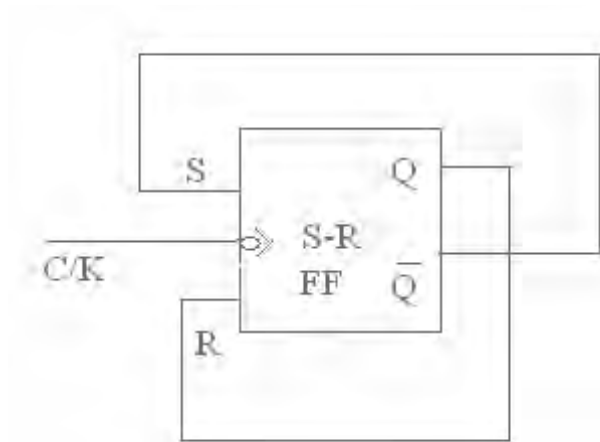


Figure 1

7. (a) Simplify the following expressions and implement them with NAND gate circuits. [8]
- $AB' + ABD + ABD' + A'C'D' + A'BC'$
 - $BD + BCD' + AB'C'D'$
- (b) Obtain the Dual of the following Boolean expressions.
- $AB + A(B+C) + B'(B+D)$
 - $A + B + A'B'C$ [4]
- (c) Obtain the complement of the following Boolean expressions.
- $A'B + A'BC' + A'BCD + A'BC'D'E$
 - $ABEF + ABE'F' + A'B'EF$ [4]
8. Design and implement a Binary to Gray converter. [16]

Code No: R05210204

R05

Set No. 4

II B.Tech I Semester Examinations, November 2010

SWITCHING THEORY AND LOGIC DESIGN

Common to BME, ICE, E.COMP.E, E.CONT.E, EIE, EEE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. A Clocked sequential circuit with two inputs x and y and a single output Z using J - K flip flops is as shown in figure 7:

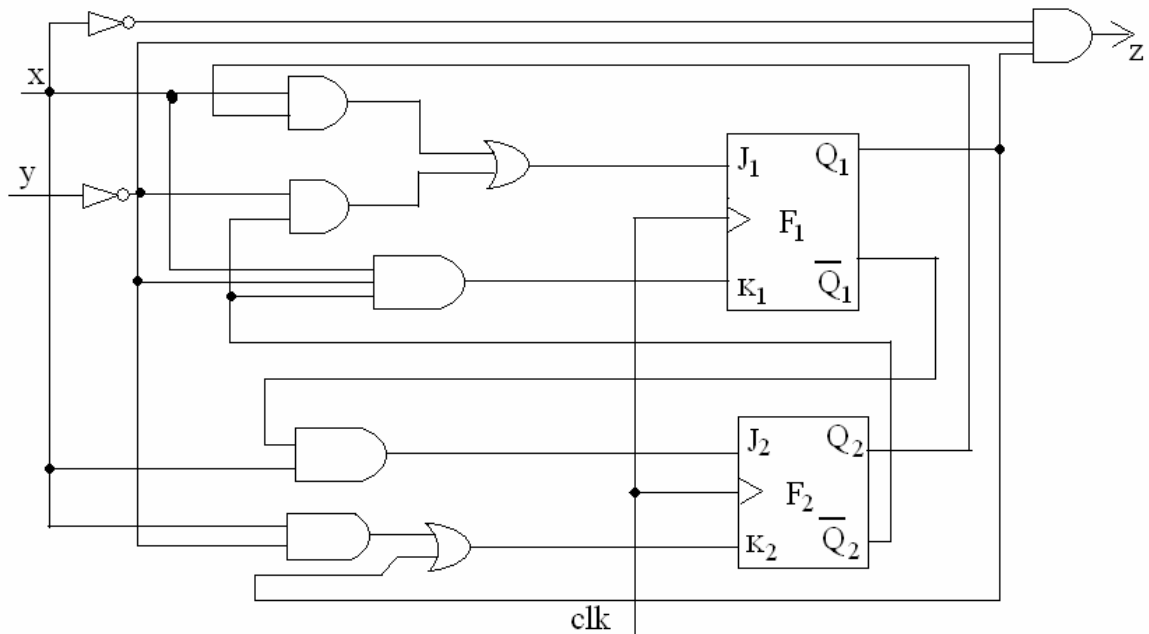


Figure 7

- Obtain input equations.
 - List the state table
 - Draw the corresponding state diagram.
 - Derive state - equations. [4+4+4+4]
2. Minimise on the map the five variable function.
 $F = \sum m(0, 1, 4, 5, 6, 13, 14, 15, 22, 24, 25, 28, 29, 30, 31)$. [16]
3. (a) Using the method of flip flop conversion carry out the following conversions.
- S-R to T

Code No: R05210204

R05

Set No. 4

ii. J-K to D

[4x2=8]

(b) Verify the circuit and explain its function. With the timing waveforms.

Shown in figure 1

[8]

 


Figure 1

4. Design and implement a Binary to Gray converter. [16]
5. (a) List the PLA programming table for the BCD to excess-3 code converter.
 (b) A ROM chip of $4,096 \times 8$ bits has two chip select inputs and operates from a 5-volt power supply. How many pins are needed for the integrated circuit package? Draw the block diagram of this ROM. [8+8]
6. (a) Simplify the following expressions and implement them with NAND gate circuits. [8]
 i. $AB' + ABD + ABD' + A'C'D' + A'BC'$
 ii. $BD + BCD' + AB'C'D'$
 (b) Obtain the Dual of the following Boolean expressions.
 i. $AB + A(B+C) + B'(B+D)$
 ii. $A + B + A'B'C$ [4]
 (c) Obtain the complement of the following Boolean expressions.
 i. $A'B + A'BC' + A'BCD + A'BC'D'E$
 ii. $ABEF + ABE'F' + A'B'EF$ [4]
7. (a) Explain, How error occurred in a data transmission can be detected using parity bit. [6]
 (b) Perform the subtraction with the following unsigned binary numbers by taking the 2's complement of the subtrahend. $[5 \times 2 = 10]$
 i. $101011 - 111000$
 ii. $1110 - 110010$
 iii. $11010 - 1101$

Code No: R05210204

R05

Set No. 4

- iv. 110 - 101000
- v. 11010 - 10000

8. For the ASM chart given below figure 8:

 


Figure 8

- (a) Draw the state diagram.
- (b) Design the control unit using D flip-flops and a decoder. [8+8]

Code No: R05210204

R05**Set No. 1**

II B.Tech I Semester Examinations, November 2010

SWITCHING THEORY AND LOGIC DESIGN

Common to BME, ICE, E.COMP.E, E.CONT.E, EIE, EEE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. A Clocked sequential circuit with two inputs x and y and a single output Z using J - K flip flops is as shown in figure 7:

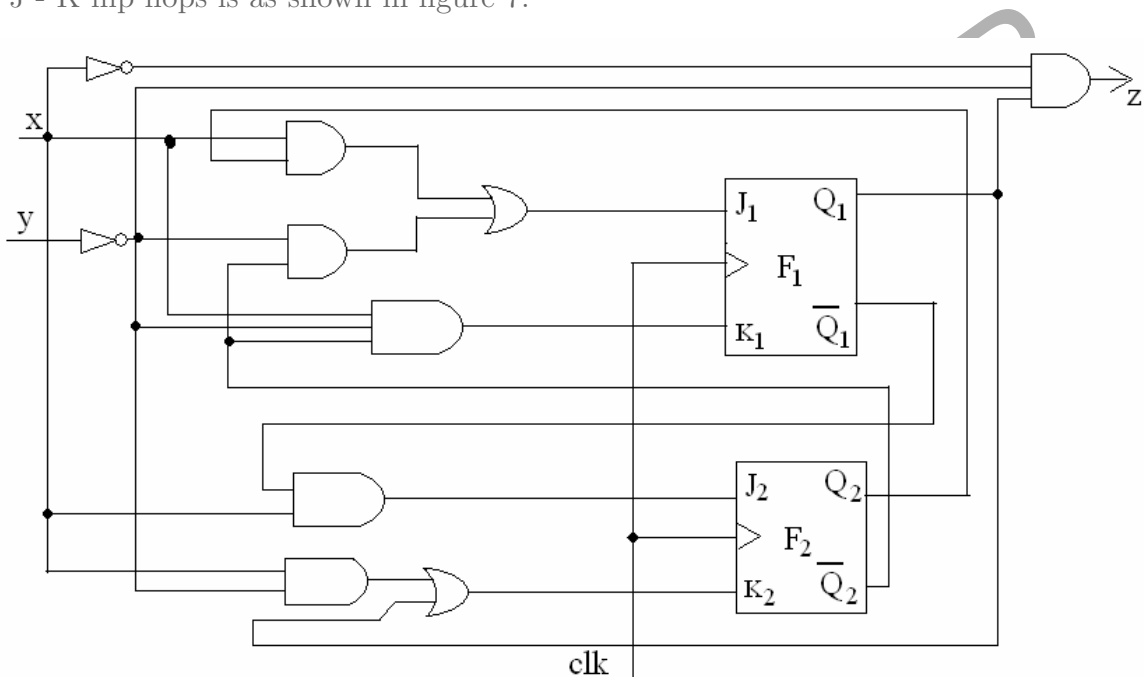


Figure 7

- (a) Obtain input equations.
 (b) List the state table
 (c) Draw the corresponding state diagram.
 (d) Derive state - equations. [4+4+4+4]
2. (a) Simplify the following expressions and implement them with NAND gate circuits. [8]
- $AB' + ABD + ABD' + A'C'D' + A'BC'$
 - $BD + BCD' + AB'C'D'$
- (b) Obtain the Dual of the following Boolean expressions.

Code No: R05210204

R05

Set No. 1

- i. $AB+A(B+C)+B'(B+D)$
 ii. $A+B+A'B'C$ [4]
- (c) Obtain the complement of the following Boolean expressions.
 i. $A'B+A'BC'+A'BCD+A'BC'D'E$
 ii. $ABEF+ABE'F'+A'B'EF$ [4]
3. (a) Explain, How error occurred in a data transmission can be detected using parity bit. [6]
 (b) Perform the subtraction with the following unsigned binary numbers by taking the 2's complement of the subtrahend. [5 × 2 = 10]
 i. $101011 - 111000$
 ii. $1110 - 110010$
 iii. $11010 - 1101$
 iv. $110 - 101000$
 v. $11010 - 10000$
4. Design and implement a Binary to Gray converter. [16]
5. (a) Using the method of flip flop conversion carry out the following conversions.
 i. S-R to T
 ii. J-K to D [4x2=8]
 (b) Verify the circuit and explain its function. With the timing waveforms. Shown in figure 1 [8]

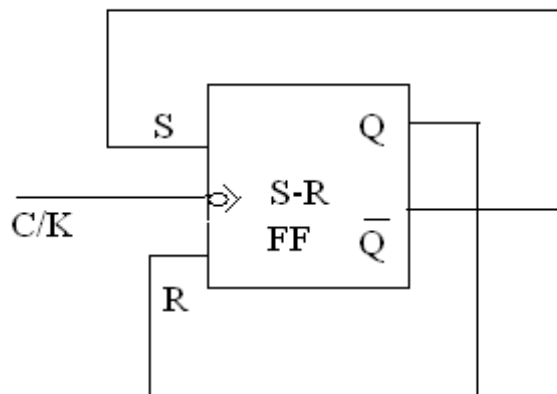


Figure 1

6. For the ASM chart given below figure 8:

Code No: R05210204

R05

Set No. 1

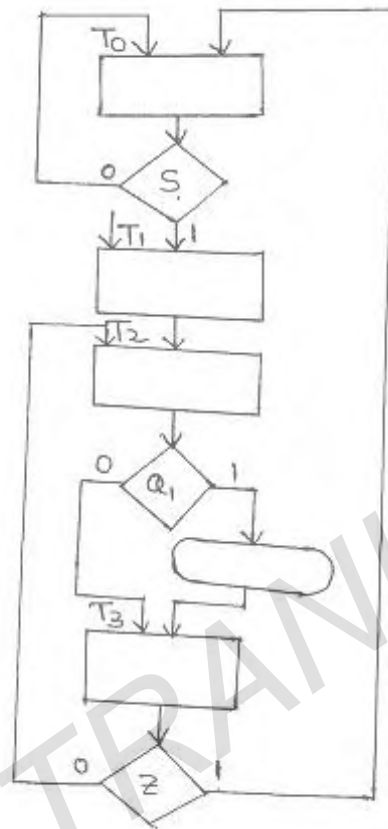


Figure 8

- (a) Draw the state diagram.
- (b) Design the control unit using D flip-flops and a decoder. [8+8]
7. (a) List the PLA programming table for the BCD to excess-3 code converter.
- (b) A ROM chip of $4,096 \times 8$ bits has two chip select inputs and operates from a 5-volt power supply. How many pins are needed for the integrated circuit package? Draw the block diagram of this ROM. [8+8]
8. Minimise on the map the five variable function.
 $F = \sum m(0, 1, 4, 5, 6, 13, 14, 15, 22, 24, 25, 28, 29, 30, 31)$. [16]

Code No: R05210204

R05**Set No. 3**

II B.Tech I Semester Examinations, November 2010

SWITCHING THEORY AND LOGIC DESIGN

Common to BME, ICE, E.COMP.E, E.CONT.E, EIE, EEE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Using the method of flip flop conversion carry out the following conversions.
 - i. S-R to T
 - ii. J-K to D
- (b) Verify the circuit and explain its function. With the timing waveforms. Shown in figure 1

 


Figure 1

2. (a) List the PLA programming table for the BCD to excess-3 code converter.
- (b) A ROM chip of $4,096 \times 8$ bits has two chip select inputs and operates from a 5-volt power supply. How many pins are needed for the integrated circuit package? Draw the block diagram of this ROM.
3. (a) Explain, How error occurred in a data transmission can be detected using parity bit.
- (b) Perform the subtraction with the following unsigned binary numbers by taking the 2's complement of the subtrahend.
 - i. 101011 - 111000
 - ii. 1110 - 110010
 - iii. 11010 - 1101
 - iv. 110 - 101000
 - v. 11010 - 10000
4. Minimise on the map the five variable function.

$$F = \sum m(0, 1, 4, 5, 6, 13, 14, 15, 22, 24, 25, 28, 29, 30, 31).$$

Code No: R05210204

R05

Set No. 3

5. Design and implement a Binary to Gray converter. [16]
6. (a) Simplify the following expressions and implement them with NAND gate circuits. [8]
- $AB' + ABD + ABD' + A'C'D' + A'BC'$
 - $BD + BCD' + AB'C'D'$
- (b) Obtain the Dual of the following Boolean expressions. [4]
- $AB + A(B+C) + B'(B+D)$
 - $A + B + A'B'C$
- (c) Obtain the complement of the following Boolean expressions. [4]
- $A'B + A'BC' + A'BCD + A'BC'D'E$
 - $ABEF + ABE'F' + A'B'EF$
7. A Clocked sequential circuit with two inputs x and y and a single output Z using J - K flip flops is as shown in figure 7:

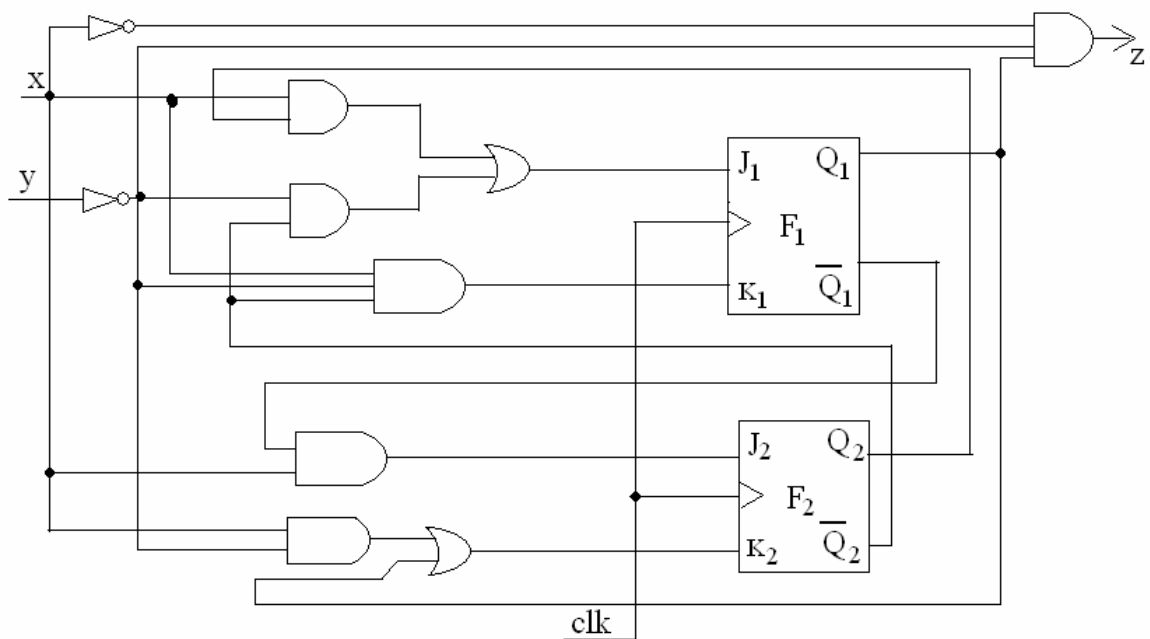


Figure 7

- Obtain input equations.
- List the state table
- Draw the corresponding state diagram.
- Derive state - equations. [4+4+4+4]

Code No: R05210204

R05

Set No. 3

8. For the ASM chart given below figure 8:

 


Figure 8

- (a) Draw the state diagram.
- (b) Design the control unit using D flip-flops and a decoder.

[8+8]
