

Code No: R05210504

R05**Set No. 2**

II B.Tech I Semester Examinations, November 2010

DIGITAL LOGIC DESIGNCommon to Information Technology, Computer Science And Engineering,
Computer Science And Systems Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Define the following terms related to flip-flops.
 - i. set-up time
 - ii. hold time
 - iii. propagation delay
 - iv. preset and
 - v. clear.
- (b) Distinguish between combinational logic and sequential logic. [10+6]
2. (a) Draw and explain 4-bit universal shift register.
- (b) Explain different types of shift registers. [8+8]
3. (a) Explain the block diagram of a memory unit. Explain the read and write operation a RAM can perform.
- (b)
 - i. How many 32K * 8 RAM chips are needed to provide a memory capacity of 256K bytes.
 - ii. How many lines of the address must be used to access 256K bytes? How many of these lines are connected to the address inputs of all chips?
 - iii. How many lines must be decoded for the chip select inputs? Specify the size of the decoder. [8+8]
4. (a) List the first 20 numbers in base 17. Use the letters A, B, C, D, E, F and G to represent the last seven digits. [4]
- (b) Convert the following numbers with the given radix to decimal.
 - i. 1234_5
 - ii. 1234_7
 - iii. 1234_{11}
 - iv. 333_4 [3+3+3+3]
5. (a) Describe the analysis procedure of asynchronous sequential logic using flow table
- (b) An asynchronous sequential circuit has two internal states and one output. The excitation and output functions describing the functions are: [6+10]

$$Y_1 = x_1x_2 + x_1y_2' + x_2'y_1$$

$$Y_2 = x_2 + x_1y_1'y_2 + x_1'y_1$$

$$z = x_2 + y_1$$

Code No: R05210504

R05**Set No. 2**

- i. Draw the logic diagram of the circuit.
 - ii. Derive the transition table and output map.
 - iii. Obtain a flow table for the circuit.
6. (a) Explain the concept of positive logic and negative logic. Also draw the truth tables for positive logic AND gate and negative logic OR gate.
- (b) Obtain the complement of the following Boolean expressions.
 - i. $B'C'D + (B + C + D)' + B'C'D'E$
 - ii. $AB + (AC)' + (AB + C)$.
- (c) Obtain the dual of the following Boolean expressions. [8+4+4]
 - i. $A'B'C' + A'BC' + AB'C' + ABC'$
 - ii. $AB + (AC)' + AB'C$.
7. (a) Show that wired circuit (Figure 2a) perform the following function:
 $Y = (A \oplus B) \bullet (C \oplus D)$

 


Figure 2a

- (b) A majority logic function is a Boolean function that is equal to 1 if the majority of the variables are 1. The function is 0 otherwise. Write the HDL user-defined primitive for 3 bit majority functions. Assume A, B, C are the input variable and Y is the output variable. [8+8]
8. (a) Using five lower - order demultiplexer, construct 6 to 64 line demultiplexer circuit. Use only block diagrams.
- (b) Design a Combinational logic circuit with three inputs A, B, C and three outputs x, y, z. If the binary input is 0, 1, 2, or 3, the binary output is one greater than the input. When the binary input is 4, 5, 6, or 7, the binary output is one less than the input. Draw the circuit using three-2 input AND gates, one 3 input OR gate, one 3 input X - OR gate and one inverter. [4+12]

Code No: R05210504

R05**Set No. 4**

II B.Tech I Semester Examinations, November 2010

DIGITAL LOGIC DESIGNCommon to Information Technology, Computer Science And Engineering,
Computer Science And Systems Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Show that wired circuit (Figure 2a) perform the following function:
 $Y = (A \oplus B) \bullet (C \oplus D)$

 


Figure 2a

- (b) A majority logic function is a Boolean function that is equal to 1 if the majority of the variables are 1. The function is 0 otherwise. Write the HDL user-defined primitive for 3 bit majority functions. Assume A, B, C are the input variable and Y is the output variable. [8+8]
2. (a) Explain the block diagram of a memory unit. Explain the read and write operation a RAM can perform.
- (b) i. How many 32K * 8 RAM chips are needed to provide a memory capacity of 256K bytes.
 ii. How many lines of the address must be used to access 256K bytes? How many of these lines are connected to the address inputs of all chips?
 iii. How many lines must be decoded for the chip select inputs? Specify the size of the decoder. [8+8]
3. (a) Explain the concept of positive logic and negative logic. Also draw the truth tables for positive logic AND gate and negative logic OR gate.
- (b) Obtain the complement of the following Boolean expressions.
 i. $B'C'D + (B + C + D)' + B'C'D'E$

Code No: R05210504

R05**Set No. 4**

- ii. $AB + (AC)' + (AB + C)$.
- (c) Obtain the dual of the following Boolean expressions. [8+4+4]
- i. $A'B'C' + A'BC' + AB'C' + ABC'$
- ii. $AB + (AC)' + AB'C$.
4. (a) Describe the analysis procedure of asynchronous sequential logic using flow table
- (b) An asynchronous sequential circuit has two internal states and one output. The excitation and output functions describing the functions are: [6+10]
- $$Y_1 = x_1x_2 + x_1y_2' + x_2'y_1$$
- $$Y_2 = x_2 + x_1y_1'y_2 + x_1'y_1$$
- $$z = x_2 + y_1$$
- i. Draw the logic diagram of the circuit.
- ii. Derive the transition table and output map.
- iii. Obtain a flow table for the circuit.
5. (a) Using five lower - order demultiplexer, construct 6 to 64 line demultiplexer circuit. Use only block diagrams.
- (b) Design a Combinational logic circuit with three inputs A, B, C and three outputs x, y, z. If the binary input is 0, 1, 2, or 3, the binary output is one greater than the input. When the binary input is 4, 5, 6, or 7, the binary output is one less than the input. Draw the circuit using three-2 input AND gates, one 3 input OR gate, one 3 input X - OR gate and one inverter. [4+12]
6. (a) Draw and explain 4-bit universal shift register.
- (b) Explain different types of shift registers. [8+8]
7. (a) Define the following terms related to flip-flops.
- i. set-up time
- ii. hold time
- iii. propagation delay
- iv. preset and
- v. clear.
- (b) Distinguish between combinational logic and sequential logic. [10+6]
8. (a) List the first 20 numbers in base 17. Use the letters A, B, C, D, E, F and G to represent the last seven digits. [4]
- (b) Convert the following numbers with the given radix to decimal.
- i. 1234_5
- ii. 1234_7
- iii. 1234_{11}
- iv. 333_4 [3+3+3+3]

Code No: R05210504

R05**Set No. 1**

II B.Tech I Semester Examinations, November 2010

DIGITAL LOGIC DESIGNCommon to Information Technology, Computer Science And Engineering,
Computer Science And Systems Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Draw and explain 4-bit universal shift register.
(b) Explain different types of shift registers. [8+8]
2. (a) Show that wired circuit (Figure 2a) perform the following function:
 $Y = (A \oplus B) \cdot (C \oplus D)$

 


Figure 2a

- (b) A majority logic function is a Boolean function that is equal to 1 if the majority of the variables are 1. The function is 0 otherwise. Write the HDL user-defined primitive for 3 bit majority functions. Assume A, B, C are the input variable and Y is the output variable. [8+8]
3. (a) Explain the concept of positive logic and negative logic. Also draw the truth tables for positive logic AND gate and negative logic OR gate.
(b) Obtain the complement of the following Boolean expressions.
 - i. $B'C'D + (B + C + D)' + B'C'D'E$
 - ii. $AB + (AC)' + (AB + C)$.
- (c) Obtain the dual of the following Boolean expressions. [8+4+4]
 - i. $A'B'C' + A'BC' + AB'C' + ABC'$
 - ii. $AB + (AC)' + AB'C$.

Code No: R05210504

R05**Set No. 1**

4. (a) Using five lower - order demultiplexer, construct 6 to 64 line demultiplexer circuit. Use only block diagrams.
- (b) Design a Combinational logic circuit with three inputs A, B, C and three outputs x, y, z. If the binary input is 0, 1, 2, or 3, the binary output is one greater than the input. When the binary input is 4, 5, 6, or 7, the binary output is one less than the input. Draw the circuit using three-2 input AND gates, one 3 input OR gate, one 3 input X - OR gate and one inverter. [4+12]
5. (a) Define the following terms related to flip-flops.
- set-up time
 - hold time
 - propagation delay
 - preset and
 - clear.
- (b) Distinguish between combinational logic and sequential logic. [10+6]
6. (a) Describe the analysis procedure of asynchronous sequential logic using flow table
- (b) An asynchronous sequential circuit has two internal states and one output. The excitation and output functions describing the functions are: [6+10]
- $$Y_1 = x_1x_2 + x_1y_2' + x_2'y_1$$
- $$Y_2 = x_2 + x_1y_1'y_2 + x_1'y_1$$
- $$z = x_2 + y_1$$
- Draw the logic diagram of the circuit.
 - Derive the transition table and output map.
 - Obtain a flow table for the circuit.
7. (a) Explain the block diagram of a memory unit. Explain the read and write operation a RAM can perform.
- (b)
 - How many 32K * 8 RAM chips are needed to provide a memory capacity of 256K bytes.
 - How many lines of the address must be used to access 256K bytes? How many of these lines are connected to the address inputs of all chips?
 - How many lines must be decoded for the chip select inputs? Specify the size of the decoder. [8+8]
8. (a) List the first 20 numbers in base17. Use the letters A, B, C, D, E, F and G to represent the last seven digits. [4]
- (b) Convert the following numbers with the given radix to decimal.
- 1234₅
 - 1234₇
 - 1234₁₁
 - 333₄
- [3+3+3+3]

Code No: R05210504

R05

Set No. 1

FIRSTRANKER

Code No: R05210504

R05**Set No. 3**

II B.Tech I Semester Examinations, November 2010

DIGITAL LOGIC DESIGNCommon to Information Technology, Computer Science And Engineering,
Computer Science And Systems Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Explain the block diagram of a memory unit. Explain the read and write operation a RAM can perform.
- (b)
 - i. How many 32K * 8 RAM chips are needed to provide a memory capacity of 256K bytes.
 - ii. How many lines of the address must be used to access 256K bytes? How many of these lines are connected to the address inputs of all chips?
 - iii. How many lines must be decoded for the chip select inputs? Specify the size of the decoder. [8+8]
2. (a) Show that wired circuit (Figure 2a) perform the following function:

$$Y = (A \oplus B) \cdot (C \oplus D)$$

 


Figure 2a

- (b) A majority logic function is a Boolean function that is equal to 1 if the majority of the variables are 1. The function is 0 otherwise. Write the HDL user-defined primitive for 3 bit majority functions. Assume A, B, C are the input variable and Y is the output variable. [8+8]
3. (a) Draw and explain 4-bit universal shift register.
- (b) Explain different types of shift registers. [8+8]
4. (a) Describe the analysis procedure of asynchronous sequential logic using flow table

Code No: R05210504

R05**Set No. 3**

- (b) An asynchronous sequential circuit has two internal states and one output. The excitation and output functions describing the functions are: [6+10]
- $$Y_1 = x_1x_2 + x_1y_2' + x_2'y_1$$
- $$Y_2 = x_2 + x_1y_1'y_2 + x_1'y_1$$
- $$z = x_2 + y_1$$
- Draw the logic diagram of the circuit.
 - Derive the transition table and output map.
 - Obtain a flow table for the circuit.
5. (a) Define the following terms related to flip-flops.
- set-up time
 - hold time
 - propagation delay
 - preset and
 - clear.
- (b) Distinguish between combinational logic and sequential logic. [10+6]
6. (a) Explain the concept of positive logic and negative logic. Also draw the truth tables for positive logic AND gate and negative logic OR gate.
- (b) Obtain the complement of the following Boolean expressions.
- $B'C'D + (B + C + D)' + B'C'D'E$
 - $AB + (AC)' + (AB + C)$.
- (c) Obtain the dual of the following Boolean expressions. [8+4+4]
- $A'B'C' + A'BC' + AB'C' + ABC'$
 - $AB + (AC)' + AB'C$.
7. (a) Using five lower - order demultiplexer, construct 6 to 64 line demultiplexer circuit. Use only block diagrams.
- (b) Design a Combinational logic circuit with three inputs A, B, C and three outputs x, y, z. If the binary input is 0, 1, 2, or 3, the binary output is one greater than the input. When the binary input is 4, 5, 6, or 7, the binary output is one less than the input. Draw the circuit using three-2 input AND gates, one 3 input OR gate, one 3 input X - OR gate and one inverter. [4+12]
8. (a) List the first 20 numbers in base 17. Use the letters A, B, C, D, E, F and G to represent the last seven digits. [4]
- (b) Convert the following numbers with the given radix to decimal.
- 1234_5
 - 1234_7
 - 1234_{11}
 - 333_4
- [3+3+3+3]
