

Code No: R05220403

**R05****Set No. 2**

II B.Tech II Semester Examinations, December 2010

**SWITCHING THEORY AND LOGIC DESIGN****Common to Electronics And Telematics, Electronics And Communication Engineering****Time: 3 hours****Max Marks: 80****Answer any FIVE Questions  
All Questions carry equal marks**

\*\*\*\*\*

1. (a) Specify the size of a ROM (number of words and numbers bits per word) that will accommodate the truth table of a BCD to seven segment decoder with an enable input.  
(b) Write a brief note on programmable logic devices. [8+8]
2. (a) Compare synchronous & Asynchronous circuits  
(b) Design a Mod-6 synchronous counter using J-K flip flops. [6+10]
3. Clocked sequential circuit with single input  $x$  and single output  $Z$  is described by the following J - K flip - flops. Input equations and output equations of Z  

$$J_1 = Q_2 \quad K_1 = Q_2 \bar{x}$$

$$J_2 = \bar{x} \quad K_2 = x \oplus Q_1 \quad Z = (\bar{Q}_1 + Q_2)x$$
  - (a) Draw the schematic circuit diagram.
  - (b) Obtain state - table.
  - (c) Obtain state diagram.
  - (d) Obtain state equations. [4+4+4+4]
4. (a) Generate Hamming code for the given 11 bit message 10010110101 and rewrite the entire message with Hamming code. [8]  
(b) The binary numbers listed have a sign bit in the left most position and, if negative numbers are in 2's complement form. Perform the arithmetic operations indicated and verify the answers. [4×2=8]
  - i. 101011 + 111001
  - ii. 001111 + 110010
  - iii. 111001 - 011010
  - iv. 101111 - 100110
5. (a) Simplify the following Boolean expressions. [8]
  - i.  $A'C' + ABC + AC'$  to three literals
  - ii.  $(x'y' + z)' + z + xy + wz$  to three literals
  - iii.  $A'B(D' + C'D) + B(A + A'CD)$  to one literal
  - iv.  $(A' + C)(A' + C')(A + B + C'D)$  to four literals
- (b) Obtain the complement of the following Boolean expressions. [8]

Code No: R05220403

**R05****Set No. 2**

- i.  $B'C'D + (B+C+D)' + B'C'D'E$
  - ii.  $AB + (AC)' + (AB+C)$
  - iii.  $A'B'C' + A'BC' + AB'C' + ABC'$
  - iv.  $AB + (AC)' + AB'C$
6. (a) What is a cell of a K-map? What is meant by pair, a quad, and an octet of a map and how many variables are eliminated? [8]
- (b) Reduce the following function using K- map and implement it using NAND logic.  $F = \sum m(0, 2, 3, 4, 5, 6, )$  [8]
7. For the ASM chart given 2:

 


Figure 2

- (a) Draw the state diagram.
  - (b) Design the control unit using D flip-flops and a decoder. [8+8]
8. (a) Implement the following multiple output combinational logic using a 4 line to 16 line Decoder.
- $$Y_1 = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BC\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D}$$
- $$Y_2 = \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}D + \bar{A}BCD + A\bar{B}\bar{C}D$$
- $$Y_3 = \bar{A}BCD + ABC\bar{D} + ABCD.$$

Code No: R05220403

**R05**

**Set No. 2**

(b) Explain the terms Multiplexing and Demultiplexing.

[10+6]

\*\*\*\*\*

FIRSTRANKER

Code No: R05220403

**R05****Set No. 4**

II B.Tech II Semester Examinations, December 2010

**SWITCHING THEORY AND LOGIC DESIGN**Common to Electronics And Telematics, Electronics And Communication  
Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. (a) Simplify the following Boolean expressions. [8]
  - i.  $A'C' + ABC + AC'$  to three literals
  - ii.  $(x'y' + z)' + z + xy + wz$  to three literals
  - iii.  $A'B(D' + C'D) + B(A + A'CD)$  to one literal
  - iv.  $(A' + C)(A' + C')(A + B + C'D)$  to four literals
- (b) Obtain the complement of the following Boolean expressions. [8]
  - i.  $B'C'D + (B + C + D)' + B'C'D'E$
  - ii.  $AB + (AC)' + (AB + C)$
  - iii.  $A'B'C' + A'BC' + AB'C' + ABC'$
  - iv.  $AB + (AC)' + AB'C$
2. For the ASM chart given 2:

Code No: R05220403

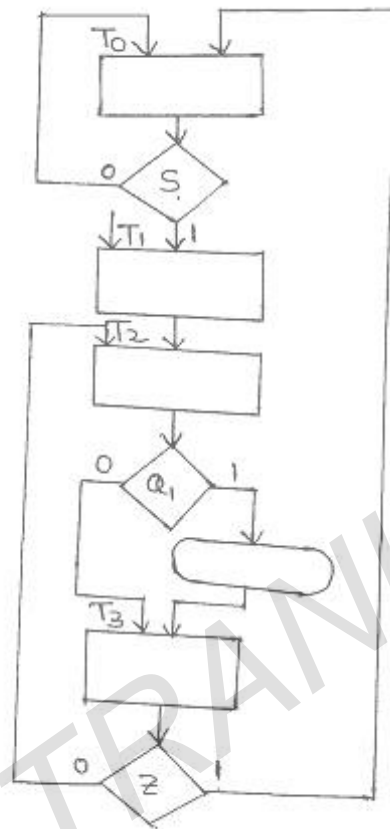
**R05****Set No. 4**

Figure 2

- (a) Draw the state diagram.
  - (b) Design the control unit using D flip-flops and a decoder. [8+8]
3. (a) Compare synchronous & Asynchronous circuits
- (b) Design a Mod-6 synchronous counter using J-K flip flops. [6+10]
4. Clocked sequential circuit with single input  $x$  and single output  $Z$  is described by the following J - K flip - flops. Input equations and output equations of  $Z$
- $$J_1 = Q_2 \quad K_1 = Q_2 \bar{x}$$
- $$J_2 = \bar{x} \quad K_2 = x \oplus Q_1 \quad Z = (\bar{Q}_1 + Q_2)x$$
- (a) Draw the schematic circuit diagram.
  - (b) Obtain state - table.
  - (c) Obtain state diagram.
  - (d) Obtain state equations. [4+4+4+4]
5. (a) Generate Hamming code for the given 11 bit message 10010110101 and rewrite the entire message with Hamming code. [8]
- (b) The binary numbers listed have a sign bit in the left most position and, if negative numbers are in 2's complement form. Perform the arithmetic operations indicated and verify the answers. [4×2=8]

Code No: R05220403

**R05****Set No. 4**

- i.  $101011 + 111001$
  - ii.  $001111 + 110010$
  - iii.  $111001 - 011010$
  - iv.  $101111 - 100110$
6. (a) What is a cell of a K-map? What is meant by pair, a quad, and an octet of a map and how many variables are eliminated? [8]
- (b) Reduce the following function using K- map and implement it using NAND logic.  $F = \sum m(0, 2, 3, 4, 5, 6, )$  [8]
7. (a) Specify the size of a ROM (number of words and numbers bits per word) that will accommodate the truth table of a BCD to seven segment decoder with an enable input.
- (b) Write a brief note on programmable logic devices. [8+8]
8. (a) Implement the following multiple output combinational logic using a 4 line to 16 line Decoder.  

$$Y_1 = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}CD + \bar{A}\bar{B}C\bar{D} + \bar{A}BC\bar{D} + A\bar{B}C\bar{D} + A\bar{B}CD$$

$$Y_2 = \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}BC\bar{D} + A\bar{B}C\bar{D}$$

$$Y_3 = \bar{A}BCD + A\bar{B}C\bar{D} + ABCD.$$
- (b) Explain the terms Multiplexing and Demultiplexing. [10+6]

\*\*\*\*\*

Code No: R05220403

**R05****Set No. 1**

II B.Tech II Semester Examinations, December 2010

**SWITCHING THEORY AND LOGIC DESIGN**

Common to Electronics And Telematics, Electronics And Communication Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. For the ASM chart given 2:

 


Figure 2

- (a) Draw the state diagram.
- (b) Design the control unit using D flip-flops and a decoder. [8+8]
2. (a) Implement the following multiple output combinational logic using a 4 line to 16 line Decoder.
- $$Y_1 = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + A\bar{B}C\bar{D} + A\bar{B}C\bar{D}$$
- $$Y_2 = \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + A\bar{B}\bar{C}D$$
- $$Y_3 = \bar{A}BCD + A\bar{B}C\bar{D} + ABCD.$$
- (b) Explain the terms Multiplexing and Demultiplexing. [10+6]

Code No: R05220403

**R05****Set No. 1**

3. (a) Simplify the following Boolean expressions. [8]
- $A'C' + ABC + AC'$  to three literals
  - $(x'y' + z)' + z + xy + wz$  to three literals
  - $A'B(D' + C'D) + B(A + A'CD)$  to one literal
  - $(A' + C)(A' + C')(A + B + C'D)$  to four literals
- (b) Obtain the complement of the following Boolean expressions. [8]
- $B'C'D + (B + C + D)' + B'C'D'E$
  - $AB + (AC)' + (AB + C)$
  - $A'B'C' + A'BC' + AB'C' + ABC'$
  - $AB + (AC)' + AB'C$
4. (a) Specify the size of a ROM (number of words and numbers bits per word) that will accommodate the truth table of a BCD to seven segment decoder with an enable input.
- (b) Write a brief note on programmable logic devices. [8+8]
5. (a) What is a cell of a K-map? What is meant by pair, a quad, and an octet of a map and how many variables are eliminated? [8]
- (b) Reduce the following function using K-map and implement it using NAND logic.  $F = \sum m(0, 2, 3, 4, 5, 6, )$  [8]
6. (a) Generate Hamming code for the given 11 bit message 10010110101 and rewrite the entire message with Hamming code. [8]
- (b) The binary numbers listed have a sign bit in the left most position and, if negative numbers are in 2's complement form. Perform the arithmetic operations indicated and verify the answers. [4×2=8]
- $101011 + 111001$
  - $001111 + 110010$
  - $111001 - 011010$
  - $101111 - 100110$
7. Clocked sequential circuit with single input x and single output Z is described by the following J - K flip - flops. Input equations and output equations of Z
- $$J_1 = Q_2 \quad K_1 = Q_2\bar{x}$$
- $$J_2 = \bar{x} \quad K_2 = x \oplus Q_1 \quad Z = (\bar{Q}_1 + Q_2)x$$
- Draw the schematic circuit diagram.
  - Obtain state - table.
  - Obtain state diagram.
  - Obtain state equations. [4+4+4+4]
8. (a) Compare synchronous & Asynchronous circuits
- (b) Design a Mod-6 synchronous counter using J-K flip flops. [6+10]

\*\*\*\*\*



Code No: R05220403

**R05****Set No. 3**

II B.Tech II Semester Examinations, December 2010

**SWITCHING THEORY AND LOGIC DESIGN**

Common to Electronics And Telematics, Electronics And Communication Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. (a) Compare synchronous & Asynchronous circuits  
(b) Design a Mod-6 synchronous counter using J-K flip flops. [6+10]
2. For the ASM chart given 2:

 


Figure 2

- (a) Draw the state diagram.
- (b) Design the control unit using D flip-flops and a decoder. [8+8]
3. (a) Specify the size of a ROM (number of words and numbers bits per word) that will accommodate the truth table of a BCD to seven segment decoder with an enable input.  
(b) Write a brief note on programmable logic devices. [8+8]

Code No: R05220403

**R05****Set No. 3**

4. (a) Simplify the following Boolean expressions. [8]
- $A'C' + ABC + AC'$  to three literals
  - $(x'y' + z)' + z + xy + wz$  to three literals
  - $A'B(D' + C'D) + B(A + A'CD)$  to one literal
  - $(A' + C)(A' + C')(A + B + C'D)$  to four literals
- (b) Obtain the complement of the following Boolean expressions. [8]
- $B'C'D + (B + C + D)' + B'C'D'E$
  - $AB + (AC)' + (AB + C)$
  - $A'B'C' + A'BC' + AB'C' + ABC'$
  - $AB + (AC)' + AB'C$
5. (a) Implement the following multiple output combinational logic using a 4 line to 16 line Decoder.
- $$Y_1 = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BC\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D}$$
- $$Y_2 = \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}D + A\bar{B}\bar{C}D$$
- $$Y_3 = \bar{A}BCD + A\bar{B}C\bar{D} + ABCD$$
- (b) Explain the terms Multiplexing and Demultiplexing. [10+6]
6. Clocked sequential circuit with single input x and single output Z is described by the following J - K flip - flops. Input equations and output equations of Z
- $$J_1 = Q_2 \quad K_1 = Q_2\bar{x}$$
- $$J_2 = \bar{x} \quad K_2 = x \oplus Q_1 \quad Z = (\bar{Q}_1 + Q_2)x$$
- Draw the schematic circuit diagram.
  - Obtain state - table.
  - Obtain state diagram.
  - Obtain state equations. [4+4+4+4]
7. (a) What is a cell of a K-map? What is meant by pair, a quad, and an octet of a map and how many variables are eliminated? [8]
- (b) Reduce the following function using K- map and implement it using NAND logic.  $F = \sum m(0, 2, 3, 4, 5, 6, )$  [8]
8. (a) Generate Hamming code for the given 11 bit message 10010110101 and rewrite the entire message with Hamming code. [8]
- (b) The binary numbers listed have a sign bit in the left most position and, if negative numbers are in 2's complement form. Perform the arithmetic operations indicated and verify the answers. [4×2=8]
- $101011 + 111001$
  - $001111 + 110010$
  - $111001 - 011010$
  - $101111 - 100110$

\*\*\*\*\*