

Code No: R05320402

R05**Set No. 2**

III B.Tech II Semester Examinations, December 2010

VLSI DESIGNCommon to Bio-Medical Engineering, Electronics And Telematics,
Electronics And Communication Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

- How to represent a tristate in VHDL and explain it with suitable program.
 - What is rat's-nest wiring diagram? Explain its significance in system design. [8+8]
- Draw and explain the FPGA chip architecture.
 - Draw and explain the AND/NOR representation of PLA. [8+8]
- Why stuck-at faults occur in CMOS circuits? Explain with suitable logical diagram and layout.
 - Draw a schematic for a CMOS edge-sensitive scan-register and also draw some circuit level diagrams of its implementation. [8+8]
- Briefly discuss the limits of scaling. Why scaling is necessary for VLSI circuits? [16]
- Calculate the ON resistance of the circuit shown in the figure 7 from V_{DD} to GND. If n-channel sheet resistance $R_{sn} = 10^4 \Omega$ per square and P-channel sheet resistance $R_{sp} = 2.5 \times 10^4 \Omega$ per square. [16]

 


Figure 7

- Explain CMOS P - well fabrication process steps with neat sketches.
 - Draw and explain the cross sectional view of N- well CMOS inverter. [8+8]
- Calculate body factor of threshold for the given parameters
 $N_A = 3 \times 10^{16} \text{ cm}^{-3}$, $t_{ox} = 200 \text{ \AA}$, $\epsilon_{ox} = 3.9 \times 8.85 \times 10^{-14} \text{ F/cm}$,
 $\epsilon_{si} = 11.7 \times 8.85 \times 10^{-14} \text{ F/cm}$, Electron charge $= 1.6 \times 10^{-19} \text{ coulombs}$.

Code No: R05320402

R05

Set No. 2

- (b) Mention the parameters on which the threshold voltage depends. [8+8]
8. (a) Draw and explain the layout for a combinational adder appropriate for a data path.
- (b) Draw the Serial/parallel multiplier structure and explain how multiplication is performed. [8+8]

FIRSTRANKER

Code No: R05320402

R05**Set No. 4**

III B.Tech II Semester Examinations, December 2010

VLSI DESIGN

Common to Bio-Medical Engineering, Electronics And Telematics,
Electronics And Communication Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. Briefly discuss the limits of scaling. Why scaling is necessary for VLSI circuits? [16]
2. Calculate the ON resistance of the circuit shown in the figure 7 from V_{DD} to GND. If n- channel sheet resistance $R_{sn} = 10^4 \Omega$ per square and P-channel sheet resistance $R_{sp} = 2.5 \times 10^4 \Omega$ per square. [16]

 


Figure 7

3. (a) Draw and explain the FPGA chip architecture.
(b) Draw and explain the AND/NOR representation of PLA. [8+8]
4. (a) How to represent a tristate in VHDL and explain it with suitable program.
(b) What is rat's-nest wiring diagram? Explain its significance in system design. [8+8]
5. (a) Calculate body factor of threshold for the given parameters
 $N_A = 3 \times 10^{16} \text{ cm}^{-3}$, $t_{ox} = 200 \text{ \AA}$, $\epsilon_{ox} = 3.9 \times 8.85 \times 10^{-14} \text{ F/cm}$,
 $\epsilon_{si} = 11.7 \times 8.85 \times 10^{-14} \text{ F/cm}$, Electron charge $= 1.6 \times 10^{-19} \text{ coulombs}$.
(b) Mention the parameters on which the threshold voltage depends. [8+8]
6. (a) Explain CMOS P - well fabrication process steps with neat sketches.
(b) Draw and explain the cross sectional view of N- well CMOS inverter. [8+8]
7. (a) Draw and explain the layout for a combinational adder appropriate for a data path.
(b) Draw the Serial/parallel multiplier structure and explain how multiplication is performed. [8+8]

Code No: R05320402

R05

Set No. 4

8. (a) Why stuck-at faults occur in CMOS circuits? Explain with suitable logical diagram and layout.
- (b) Draw a schematic for a CMOS edge-sensitive scan-register and also draw some circuit level diagrams of its implementation. [8+8]

FIRSTRANKER

Code No: R05320402

R05**Set No. 1**

III B.Tech II Semester Examinations, December 2010

VLSI DESIGNCommon to Bio-Medical Engineering, Electronics And Telematics,
Electronics And Communication Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

- Draw and explain the FPGA chip architecture.
 - Draw and explain the AND/NOR representation of PLA. [8+8]
- Calculate the ON resistance of the circuit shown in the figure 7 from V_{DD} to GND. If n-channel sheet resistance $R_{sn} = 10^4 \Omega$ per square and P-channel sheet resistance $R_{sp} = 2.5 \times 10^4 \Omega$ per square. [16]

 


Figure 7

- Briefly discuss the limits of scaling. Why scaling is necessary for VLSI circuits? [16]
- How to represent a tristate in VHDL and explain it with suitable program.
 - What is rat's-nest wiring diagram? Explain its significance in system design. [8+8]
- Explain CMOS P - well fabrication process steps with neat sketches.
 - Draw and explain the cross sectional view of N- well CMOS inverter. [8+8]
- Why stuck-at faults occur in CMOS circuits? Explain with suitable logical diagram and layout.
 - Draw a schematic for a CMOS edge-sensitive scan-register and also draw some circuit level diagrams of its implementation. [8+8]
- Calculate body factor of threshold for the given parameters
 $N_A = 3 \times 10^{16} \text{ cm}^{-3}$, $t_{ox} = 200 \text{ \AA}$, $\epsilon_{ox} = 3.9 \times 8.85 \times 10^{-14} \text{ F/cm}$,
 $\epsilon_{si} = 11.7 \times 8.85 \times 10^{-14} \text{ F/cm}$, Electron charge $= 1.6 \times 10^{-19} \text{ coulombs}$.

Code No: R05320402

R05

Set No. 1

- (b) Mention the parameters on which the threshold voltage depends. [8+8]
8. (a) Draw and explain the layout for a combinational adder appropriate for a data path.
- (b) Draw the Serial/parallel multiplier structure and explain how multiplication is performed. [8+8]

FIRSTRANKER

Code No: R05320402

R05**Set No. 3**

III B.Tech II Semester Examinations, December 2010

VLSI DESIGNCommon to Bio-Medical Engineering, Electronics And Telematics,
Electronics And Communication Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

- How to represent a tristate in VHDL and explain it with suitable program.
 - What is rat's-nest wiring diagram? Explain its significance in system design. [8+8]
- Draw and explain the FPGA chip architecture.
 - Draw and explain the AND/NOR representation of PLA. [8+8]
- Briefly discuss the limits of scaling. Why scaling is necessary for VLSI circuits? [16]
- Why stuck-at faults occur in CMOS circuits? Explain with suitable logical diagram and layout.
 - Draw a schematic for a CMOS edge-sensitive scan-register and also draw some circuit level diagrams of its implementation. [8+8]
- Explain CMOS P - well fabrication process steps with neat sketches.
 - Draw and explain the cross sectional view of N- well CMOS inverter. [8+8]
- Draw and explain the layout for a combinational adder appropriate for a data path.
 - Draw the Serial/parallel multiplier structure and explain how multiplication is performed. [8+8]
- Calculate the ON resistance of the circuit shown in the figure 7 from V_{DD} to GND. If n- channel sheet resistance $R_{sn} = 10^4 \Omega$ per square and P-channel sheet resistance $R_{sp} = 2.5 \times 10^4 \Omega$ per square. [16]

 


Figure 7

Code No: R05320402

R05

Set No. 3

8. (a) Calculate body factor of threshold for the given parameters
 $N_A = 3 \times 10^{16} \text{ cm}^{-3}$, $t_{ox} = 200 \text{ \AA}$, $\epsilon_{ox} = 3.9 \times 8.85 \times 10^{-14} \text{ F/cm}$,
 $\epsilon_{si} = 11.7 \times 8.85 \times 10^{-14} \text{ F/cm}$, Electron charge $= 1.6 \times 10^{-19} \text{ coulombs}$.
- (b) Mention the parameters on which the threshold voltage depends. [8+8]

FIRSTRANKER