

Code No: R07A10401

R07**Set No. 2**

I B.Tech Examinations, December 2010
BASIC ELECTRONIC DEVICES AND CIRCUITS
Electrical And Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Draw and explain a fixed bias circuit. Explain why the circuit is unsatisfactory if the transistor is replaced by another of the same type.
(b) Find the value of thermal resistance required for the Ge transistor for self bias circuit with the collector current of 1.5mA at 25 °C and it increases by 0.131mA over a temperature range of 25 to 75 °C in order for the circuit to be thermally stable. Assume $V_{cc}=30V$ and $R_c=2.0K$ and $R_e=4.7K$. [8+8]
2. (a) Explain the input and output characteristics of BJT in CB configuration.
(b) Compare important characteristics of BJT and FET. [10+6]
3. (a) Draw and explain the approximate model of a CC amplifier.
(b) Find the voltage gain and current gain of a CE amplifier whose $h_{ie} = 1 K\Omega$, $h_{fe} = 50$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 25 \mu A/V$. Consider the source and load resistance of $1 K\Omega$ both. [8+8]
4. (a) Explain the construction, operation and applications of the varactor diode.
(b) In a p-type semiconductor, the Fermi level lies 0.4 eV above the valance band. Determine the new position of the Fermi level if the concentration of acceptor atoms is multiplied by a factor of:
 - i. 0.5 and

Code No: R07A10401

R07**Set No. 2**

ii. 4.0.

$$KT = 0.025\text{eV.} \quad [10+6]$$

5. (a) Draw the schematic diagram of a CRT and explain about the various sections and the materials used.
- (b) In a CRT, the electrons emitted are accelerated by a potential of 500V. The length of the deflecting plates is 1.3 cm. Distance between the deflecting plates is 0.5 cm. The distance between the centre of the deflecting plates and the screen is 20 cm. Determine the value of electrostatic deflection sensitivity. [8+8]
6. (a) Prove that the amplitude of the oscillations is limited by the onset of nonlinearity.
- (b) Design a phase-shift oscillator to operate at a frequency of 5kHz. Use a MOS-FET with $\mu=55$ and $r_d=5.5\text{K}$. The phase shift network is not to load down the amplifier. Find the minimum value of the drain circuit resistance R_d for which the circuit will oscillate. [8+8]
7. (a) Derive the expression for ripple factor in a full wave rectifier using an inductor filter.
- (b) In a full wave rectifier using an LC-filter $L=10\text{ H}$, $C=100\mu\text{ F}$ and $R_L=500\Omega$. Calculate I_{dc} , V_{dc} for an input $V=30\sin(100\pi t)$. [8+8]
8. (a) State the three fundamental assumptions which are made in order that the expression $A_f=A/(1+A\beta)$ be satisfied exactly.
- (b) The output impedance may be calculated as the ratio of the open circuit voltage to the short circuit current. Using this method evaluate output resistance with feedback R_{of} for a voltage-series feedback amplifier. [6+10]

Code No: R07A10401

R07**Set No. 4**

I B.Tech Examinations, December 2010
BASIC ELECTRONIC DEVICES AND CIRCUITS
Electrical And Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. (a) Derive the expression for ripple factor in a full wave rectifier using an inductor filter.
- (b) In a full wave rectifier using an LC-filter $L=10$ H, $C=100\mu$ F and $R_L=500\Omega$. Calculate I_{dc} , V_{dc} for an input $V=30\sin(100\pi t)$. [8+8]
2. (a) Explain the input and output characteristics of BJT in CB configuration.
- (b) Compare important characteristics of BJT and FET. [10+6]
3. (a) Explain the construction, operation and applications of the varactor diode.
- (b) In a p-type semiconductor, the Fermi level lies 0.4 eV above the valance band. Determine the new position of the Fermi level if the concentration of acceptor atoms is multiplied by a factor of:
 - i. 0.5 and
 - ii. 4.0. $KT = 0.025eV$. [10+6]
4. (a) Draw and explain the approximate model of a CC amplifier.
- (b) Find the voltage gain and current gain of a CE amplifier whose $h_{ie} = 1$ K Ω , $h_{fe} = 50$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 25 \mu A/V$. Consider the source and load resistance of 1 K Ω both. [8+8]

Code No: R07A10401

R07

Set No. 4

5. (a) Prove that the amplitude of the oscillations is limited by the onset of nonlinearity.
- (b) Design a phase-shift oscillator to operate at a frequency of 5kHz. Use a MOS-FET with $\mu=55$ and $r_d=5.5K$. The phase shift network is not to load down the amplifier. Find the minimum value of the drain circuit resistance R_d for which the circuit will oscillate. [8+8]
6. (a) Draw and explain a fixed bias circuit. Explain why the circuit is unsatisfactory if the transistor is replaced by another of the same type.
- (b) Find the value of thermal resistance required for the Ge transistor for self bias circuit with the collector current of 1.5mA at 25 °C and it increases by 0.131mA over a temperature range of 25 to 75 °C in order for the circuit to be thermally stable. Assume $V_{cc}=30V$ and $R_c=2.0K$ and $R_e=4.7K$. [8+8]
7. (a) State the three fundamental assumptions which are made in order that the expression $A_f=A/(1+A \beta)$ be satisfied exactly.
- (b) The output impedance may be calculated as the ratio of the open circuit voltage to the short circuit current. Using this method evaluate output resistance with feedback R_{of} for a voltage-series feedback amplifier. [6+10]
8. (a) Draw the schematic diagram of a CRT and explain about the various sections and the materials used.
- (b) In a CRT, the electrons emitted are accelerated by a potential of 500V. The length of the deflecting plates is 1.3 cm. Distance between the deflecting plates is 0.5 cm. The distance between the centre of the deflecting plates and the screen is 20 cm. Determine the value of electrostatic deflection sensitivity. [8+8]

Code No: R07A10401

R07**Set No. 1**

I B.Tech Examinations, December 2010
BASIC ELECTRONIC DEVICES AND CIRCUITS
Electrical And Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) State the three fundamental assumptions which are made in order that the expression $A_f = A/(1+A\beta)$ be satisfied exactly.
- (b) The output impedance may be calculated as the ratio of the open circuit voltage to the short circuit current. Using this method evaluate output resistance with feedback R_{of} for a voltage-series feedback amplifier. [6+10]
2. (a) Derive the expression for ripple factor in a full wave rectifier using an inductor filter.
- (b) In a full wave rectifier using an LC-filter $L=10$ H, $C=100\mu$ F and $R_L=500\Omega$. Calculate I_{dc} , V_{dc} for an input $V=30\sin(100\pi t)$. [8+8]
3. (a) Draw and explain the approximate model of a CC amplifier.
- (b) Find the voltage gain and current gain of a CE amplifier whose $h_{ie} = 1$ K Ω , $h_{fe} = 50$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 25$ μ A/V. Consider the source and load resistance of 1 K Ω both. [8+8]
4. (a) Explain the construction, operation and applications of the varactor diode.
- (b) In a p-type semiconductor, the Fermi level lies 0.4 eV above the valance band. Determine the new position of the Fermi level if the concentration of acceptor atoms is multiplied by a factor of:

Code No: R07A10401

R07

Set No. 1

i. 0.5 and

ii. 4.0.

$$KT = 0.025\text{eV.} \quad [10+6]$$

5. (a) Explain the input and output characteristics of BJT in CB configuration.
(b) Compare important characteristics of BJT and FET. [10+6]
6. (a) Prove that the amplitude of the oscillations is limited by the onset of nonlinearity.
(b) Design a phase-shift oscillator to operate at a frequency of 5kHz. Use a MOS-FET with $\mu=55$ and $r_d=5.5\text{K}$. The phase shift network is not to load down the amplifier. Find the minimum value of the drain circuit resistance R_d for which the circuit will oscillate. [8+8]
7. (a) Draw the schematic diagram of a CRT and explain about the various sections and the materials used.
(b) In a CRT, the electrons emitted are accelerated by a potential of 500V. The length of the deflecting plates is 1.3 cm. Distance between the deflecting plates is 0.5 cm. The distance between the centre of the deflecting plates and the screen is 20 cm. Determine the value of electrostatic deflection sensitivity. [8+8]
8. (a) Draw and explain a fixed bias circuit. Explain why the circuit is unsatisfactory if the transistor is replaced by another of the same type.
(b) Find the value of thermal resistance required for the Ge transistor for self bias circuit with the collector current of 1.5mA at 25 °C and it increases by 0.131mA over a temperature range of 25 to 75 °C in order for the circuit to be thermally stable. Assume $V_{cc}=30\text{V}$ and $R_c=2.0\text{K}$ and $R_e=4.7\text{K}$. [8+8]

Code No: R07A10401

R07**Set No. 3**

I B.Tech Examinations, December 2010
BASIC ELECTRONIC DEVICES AND CIRCUITS
Electrical And Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. (a) State the three fundamental assumptions which are made in order that the expression $A_f = A/(1+A\beta)$ be satisfied exactly.
 (b) The output impedance may be calculated as the ratio of the open circuit voltage to the short circuit current. Using this method evaluate output resistance with feedback R_{of} for a voltage-series feedback amplifier. [6+10]
2. (a) Draw and explain the approximate model of a CC amplifier.
 (b) Find the voltage gain and current gain of a CE amplifier whose $h_{ie} = 1 \text{ K}\Omega$, $h_{fe} = 50$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 25 \mu\text{A/V}$. Consider the source and load resistance of $1 \text{ K}\Omega$ both. [8+8]
3. (a) Derive the expression for ripple factor in a full wave rectifier using an inductor filter.
 (b) In a full wave rectifier using an LC-filter $L=10 \text{ H}$, $C=100\mu \text{ F}$ and $R_L=500\Omega$. Calculate I_{dc} , V_{dc} for an input $V=30\sin(100\pi t)$. [8+8]
4. (a) Prove that the amplitude of the oscillations is limited by the onset of nonlinearity.
 (b) Design a phase-shift oscillator to operate at a frequency of 5kHz. Use a MOS-FET with $\mu=55$ and $r_d=5.5\text{K}$. The phase shift network is not to load down

Code No: R07A10401

R07**Set No. 3**

the amplifier. Find the minimum value of the drain circuit resistance R_d for which the circuit will oscillate. [8+8]

5. (a) Draw and explain a fixed bias circuit. Explain why the circuit is unsatisfactory if the transistor is replaced by another of the same type.
- (b) Find the value of thermal resistance required for the Ge transistor for self bias circuit with the collector current of 1.5mA at 25 °C and it increases by 0.131mA over a temperature range of 25 to 75 °C in order for the circuit to be thermally stable. Assume $V_{cc}=30V$ and $R_c=2.0K$ and $R_e=4.7K$. [8+8]
6. (a) Explain the input and output characteristics of BJT in CB configuration.
- (b) Compare important characteristics of BJT and FET. [10+6]
7. (a) Draw the schematic diagram of a CRT and explain about the various sections and the materials used.
- (b) In a CRT, the electrons emitted are accelerated by a potential of 500V. The length of the deflecting plates is 1.3 cm. Distance between the deflecting plates is 0.5 cm. The distance between the centre of the deflecting plates and the screen is 20 cm. Determine the value of electrostatic deflection sensitivity. [8+8]
8. (a) Explain the construction, operation and applications of the varactor diode.
- (b) In a p-type semiconductor, the Fermi level lies 0.4 eV above the valance band. Determine the new position of the Fermi level if the concentration of acceptor atoms is multiplied by a factor of:
- 0.5 and
 - 4.0.
- $KT = 0.025eV$. [10+6]
