

Code No: R07A1EC02

**R07****Set No. 2**

**I B.Tech Examinations, December 2010  
ELECTRICAL CIRCUIT ANALYSIS**

Common to Instrumentation And Control Engineering, Electrical And  
Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. Find the Z and Y parameters of the circuit shown in figure 2. [16]

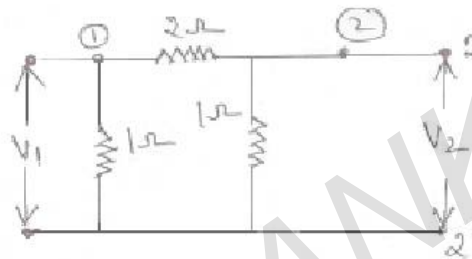


Figure 2

2. Draw the graph of the lattice network shown in the figure 7. Deduce the tie-set and cut-set matrices, and from those, find the relationship between independent and dependent variables. [16]

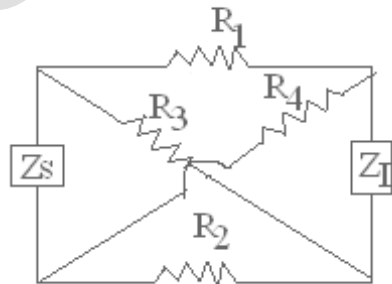


Figure 7

3. Two impedances  $(15-j10) \Omega$  and  $(10+j15) \Omega$  are connected in parallel. The supply voltage is 200V, 50Hz. Calculate
- The admittance
  - Conductance
  - Susceptance of the combined circuit
  - Total current and
  - Total power factor
  - Total power consumed in each branch and total power. [16]

Code No: R07A1EC02

**R07****Set No. 2**

4. Derive an expression for current response of RLC series circuit with sinusoidal excitation. Assume the circuit is working in critical damping conditions. [16]
5. (a) Calculate load current  $I_L$  using Millman's theorem as shown in figure 4a.

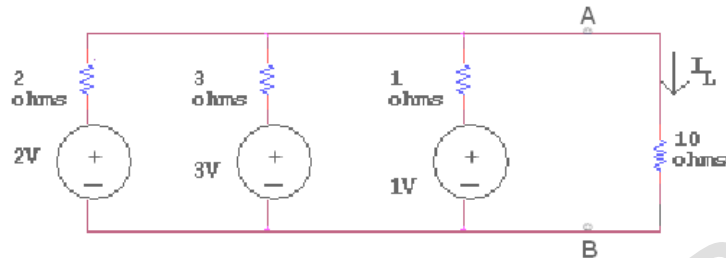


Figure 4a

- (b) State and explain the theorems in voltage and current source representations. [6+10]
6. (a) Derive an expression for the energy stored in an inductor and a capacitor.  
(b) Obtain an expression for Co-efficient of coupling. [10+6]
7. A three phase, 4 wire, 400V, 50Hz system supplies a load of 50KW at a power factor of 0.75 lagging between the red phase and neutral; 60KW at a power factor of 0.85 leading between the yellow phase and neutral and 70KW at unity power factor between the blue phase and neutral. Find the current in the neutral conductor. [16]
8. (a) State and explain the Kirchhoff's Law which can be applied to loop current method.  
(b) For the network shown in figure 1b, determine the equivalent resistance between the terminals A and B, if each resistance value is equal to 1 ohms. [6+10]

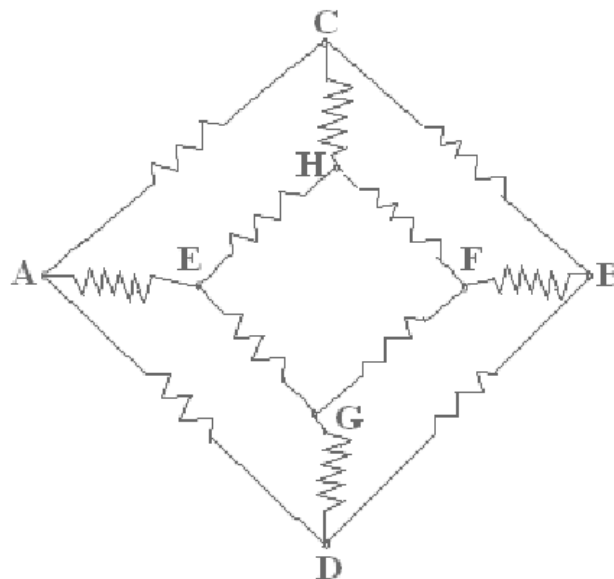


Figure 1b

Code No: R07A1EC02

R07

Set No. 2

\*\*\*\*\*

FIRSTRANKER

Code No: R07A1EC02

**R07****Set No. 4**

**I B.Tech Examinations, December 2010  
ELECTRICAL CIRCUIT ANALYSIS**

Common to Instrumentation And Control Engineering, Electrical And  
Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

- Derive an expression for the energy stored in an inductor and a capacitor.
  - Obtain an expression for Co-efficient of coupling. [10+6]
- State and explain the Kirchhoff's Law which can be applied to loop current method.
  - For the network shown in figure 1b, determine the equivalent resistance between the terminals A and B, if each resistance value is equal to 1 ohms. [6+10]

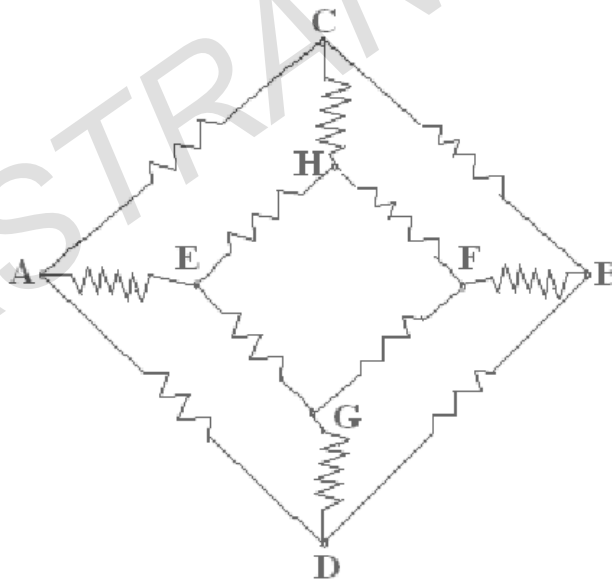


Figure 1b

- Calculate load current  $I_L$  using Millman's theorem as shown in figure 4a.

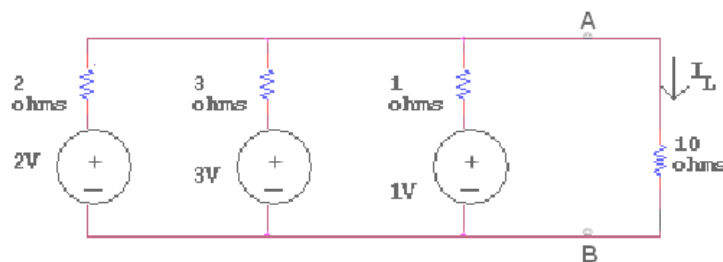


Figure 4a

- State and explain the theorems in voltage and current source representations. [6+10]

Code No: R07A1EC02

**R07****Set No. 4**

4. Find the Z and Y parameters of the circuit shown in figure 2. [16]

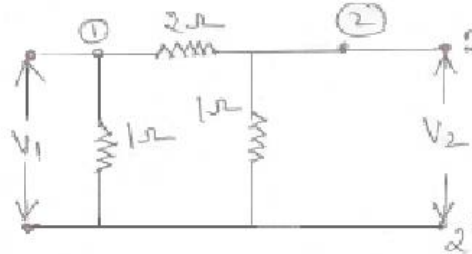


Figure 2

5. Draw the graph of the lattice network shown in the figure 7. Deduce the tie-set and cut-set matrices, and from those, find the relationship between independent and dependent variables. [16]

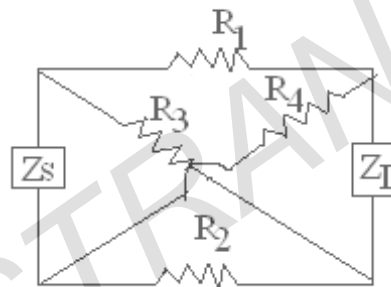


Figure 7

6. Derive an expression for current response of RLC series circuit with sinusoidal excitation. Assume the circuit is working in critical damping conditions. [16]
7. A three phase, 4 wire, 400V, 50Hz system supplies a load of 50KW at a power factor of 0.75 lagging between the red phase and neutral; 60KW at a power factor of 0.85 leading between the yellow phase and neutral and 70KW at unity power factor between the blue phase and neutral. Find the current in the neutral conductor. [16]
8. Two impedances  $(15-j10) \Omega$  and  $(10+j15) \Omega$  are connected in parallel. The supply voltage is 200V, 50Hz. Calculate
- The admittance
  - Conductance
  - Susceptance of the combined circuit
  - Total current and
  - Total power factor
  - Total power consumed in each branch and total power. [16]

\*\*\*\*\*

Code No: R07A1EC02

**R07****Set No. 1**

**I B.Tech Examinations, December 2010  
ELECTRICAL CIRCUIT ANALYSIS**

**Common to Instrumentation And Control Engineering, Electrical And  
Electronics Engineering**

Time: 3 hours

Max Marks: 80

**Answer any FIVE Questions  
All Questions carry equal marks**

\*\*\*\*\*

1. Draw the graph of the lattice network shown in the figure 7. Deduce the tie-set and cut-set matrices, and from those, find the relationship between independent and dependent variables. [16]

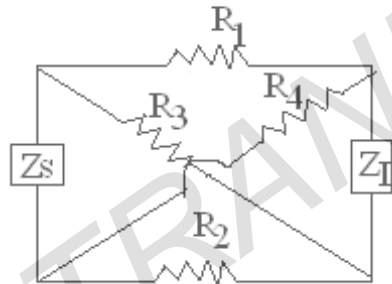


Figure 7

2. (a) Derive an expression for the energy stored in an inductor and a capacitor.  
(b) Obtain an expression for Co-efficient of coupling. [10+6]
3. A three phase, 4 wire, 400V, 50Hz system supplies a load of 50KW at a power factor of 0.75 lagging between the red phase and neutral; 60KW at a power factor of 0.85 leading between the yellow phase and neutral and 70KW at unity power factor between the blue phase and neutral. Find the current in the neutral conductor. [16]
4. Find the Z and Y parameters of the circuit shown in figure 2. [16]

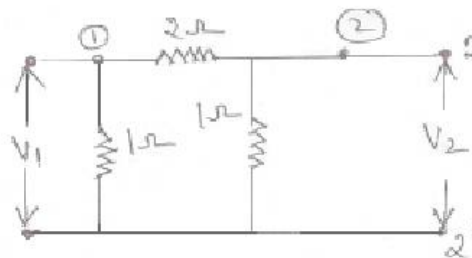


Figure 2

5. (a) State and explain the Kirchhoff's Law which can be applied to loop current method.

Code No: R07A1EC02

R07

Set No. 1

- (b) For the network shown in figure 1b, determine the equivalent resistance between the terminals A and B, if each resistance value is equal to 1 ohms.

[6+10]

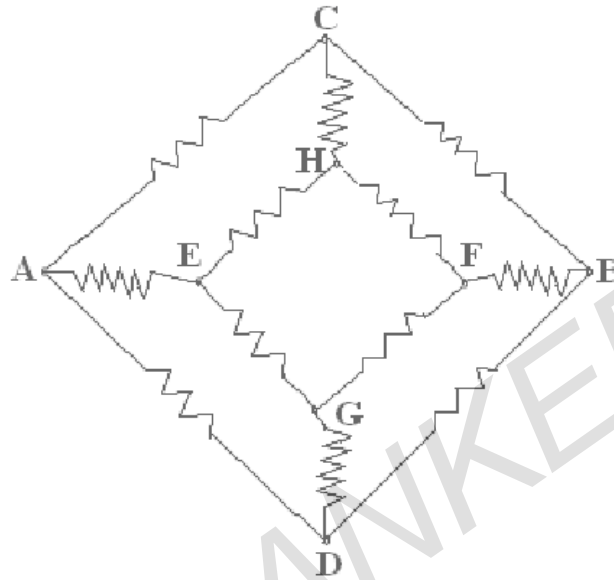


Figure 1b

6. Two impedances  $(15-j10) \Omega$  and  $(10+j15) \Omega$  are connected in parallel. The supply voltage is 200V, 50Hz. Calculate
- The admittance
  - Conductance
  - Susceptance of the combined circuit
  - Total current and
  - Total power factor
  - Total power consumed in each branch and total power. [16]
7. Derive an expression for current response of RLC series circuit with sinusoidal excitation. Assume the circuit is working in critical damping conditions. [16]
8. (a) Calculate load current  $I_L$  using Millman's theorem as shown in figure 4a.

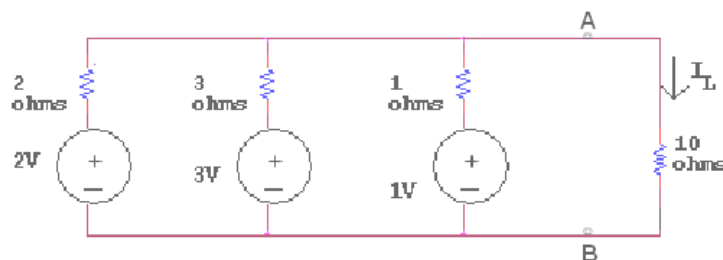


Figure 4a

- (b) State and explain the theorems in voltage and current source representations.

[6+10]

Code No: R07A1EC02

R07

Set No. 1

\*\*\*\*\*

FIRSTRANKER



Code No: R07A1EC02

**R07****Set No. 3**

I B.Tech Examinations, December 2010  
ELECTRICAL CIRCUIT ANALYSIS

Common to Instrumentation And Control Engineering, Electrical And  
Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

- State and explain the Kirchhoff's Law which can be applied to loop current method.
  - For the network shown in figure 1b, determine the equivalent resistance between the terminals A and B, if each resistance value is equal to 1 ohms.

[6+10]

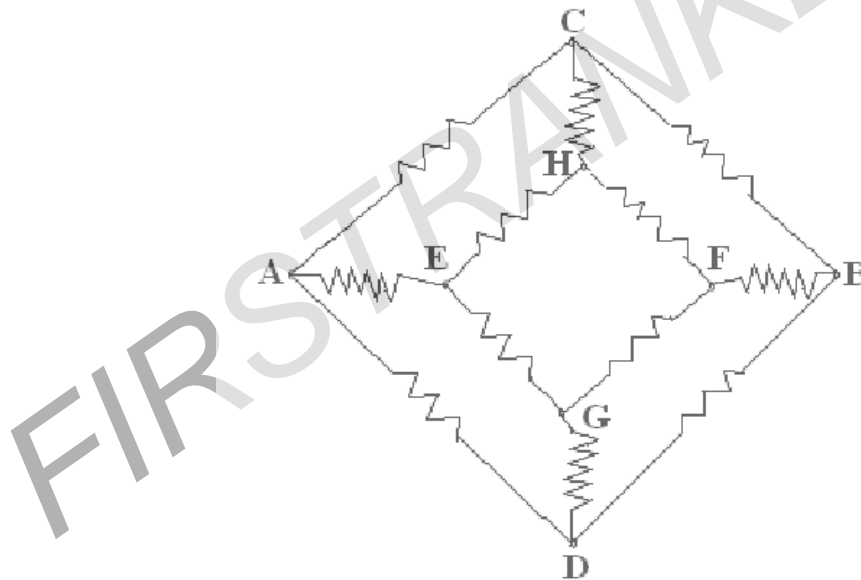


Figure 1b

- Find the Z and Y parameters of the circuit shown in figure 2.

[16]

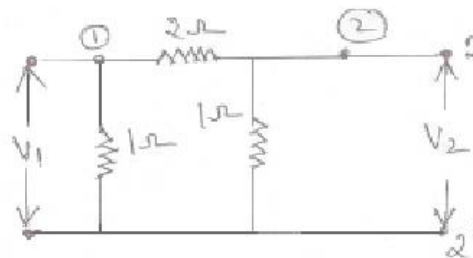


Figure 2

- Derive an expression for the energy stored in an inductor and a capacitor.
  - Obtain an expression for Co-efficient of coupling.

[10+6]

Code No: R07A1EC02

**R07****Set No. 3**

4. (a) Calculate load current  $I_L$  using Millman's theorem as shown in figure 4a.

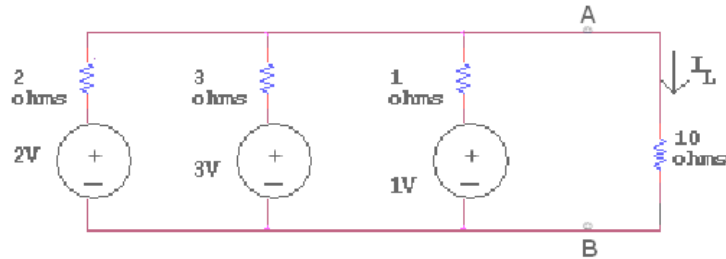


Figure 4a

- (b) State and explain the theorems in voltage and current source representations. [6+10]

5. A three phase, 4 wire, 400V, 50Hz system supplies a load of 50KW at a power factor of 0.75 lagging between the red phase and neutral; 60KW at a power factor of 0.85 leading between the yellow phase and neutral and 70KW at unity power factor between the blue phase and neutral. Find the current in the neutral conductor. [16]
6. Derive an expression for current response of RLC series circuit with sinusoidal excitation. Assume the circuit is working in critical damping conditions. [16]
7. Draw the graph of the lattice network shown in the figure 7. Deduce the tie-set and cut-set matrices, and from those, find the relationship between independent and dependent variables. [16]

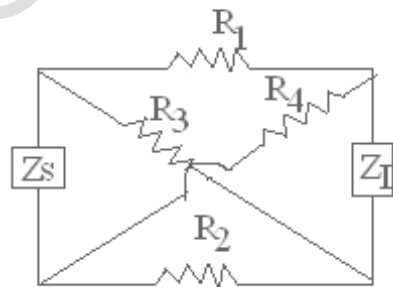


Figure 7

8. Two impedances  $(15-j10) \Omega$  and  $(10+j15) \Omega$  are connected in parallel. The supply voltage is 200V, 50Hz. Calculate
- The admittance
  - Conductance
  - Susceptance of the combined circuit
  - Total current and
  - Total power factor
  - Total power consumed in each branch and total power. [16]

\*\*\*\*\*