

Code No: RR10204

RR

Set No. 2

I B.Tech Examinations, December 2010

NETWORK THEORY

Common to BME, IT, ICE, E.COMP.E, ETM, E.CONT.E, EIE, CSE, ECE, CSSE, EEE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Find ABCD parameters for the following network shown in figure 4a.

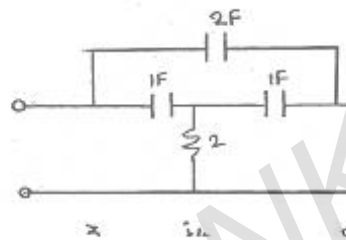


Figure 4a

- (b) Show that the total energy stored in the series RLC circuit is a constant when a constant voltage at resonance frequency is applied: Define Q-factor in terms of this energy. [8+8]
2. (a) Explain the terms Graph, Tree, and a Cutset of a network with suitable example.
- (b) For the network shown in figure 6b, determine the value of the node voltages V_1 & V_2 . Determine the power dissipated in each of the resistors.

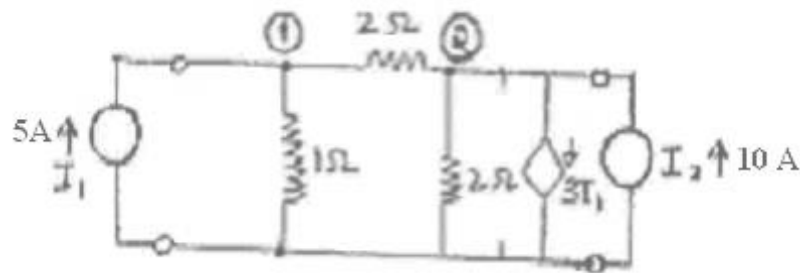


Figure 6b

- (c) Obtain the expression for the propagation constant of symmetrical T-network. [4+8+4]
3. (a) Explain why the voltage across capacitor cannot change instantaneously?
- (b) What is the significance of time constant for R-L circuit? What are the different ways of defining time constant?
- (c) Switch t is close at $t = 0$. Find initial conditions for voltage across capacitor, i_1 , i_2 , $\frac{di_1}{dt}$ and $\frac{di_2}{dt}$. In the following network shown in figure 2c. [2+4+10]

Code No: RR10204

RR

Set No. 2

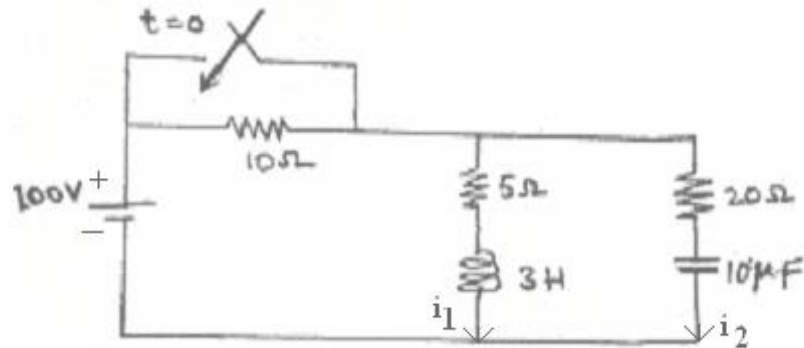


Figure 2c

4. (a) State and explain the superposition theorem.
 (b) Using super position theorem find the current in 2 ohms resistor from the following network shown in figure3b. [6+10]

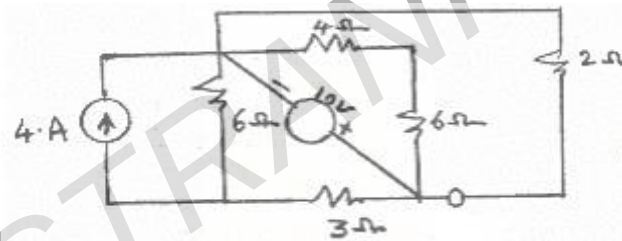


Figure 3b

5. (a) Get the expression for complex power and the sign of the active power.
 (b) Find I_1 , I_2 , I_3 and I Find also the power consumed for the network shown in figure 7b. Draw the phasor diagram. [4+12]

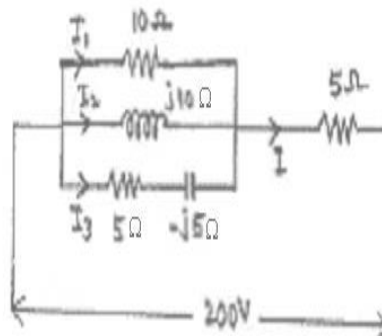


Figure 7b

6. (a) A 3phase 4000V system has a delta connected load with $Z_{ab}=(8+j6)\Omega$, $Z_{bc}=(12+j16)\Omega$ and $Z_{ca}=(6-j8)\Omega$. Find the phase currents and line currents. Determine the power consumed by each load impedance. Draw the phasor diagram.
 (b) Three impedances are connected in figure 5b shown across a 400V, 50HZ, 3 phase supply. Find the readings of the watt meters. [10+6]

Code No: RR10204

RR

Set No. 2

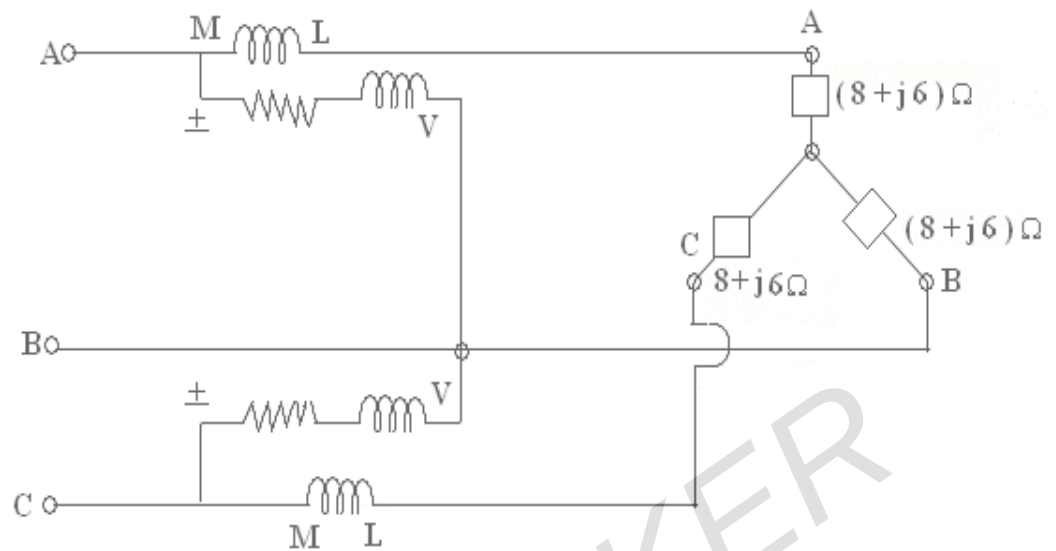


Figure 5b

7. (a) Write down the integro differential equations for the magnetically coupled circuit shown in figure 1a. The mutual inductances between L_1 and L_2 , L_2 and L_3 , and L_3 and L_1 are respectively M_{12} , M_{23} and M_{13} .

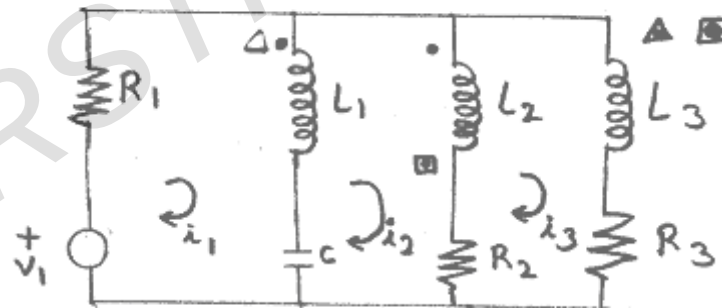


Figure 1a

- (b) Derive the relation between the flux density B and magnetising force H . Also derive the expression for reluctance. [8+8]
8. (a) State and explain KCL and KVL
- (b) Distinguish between
- independent and dependent sources
 - Ideal and practical sources.
- (c) Find V_s if $r_1 = 2 \Omega$, $r_2 = 1 \Omega$, $r_3 = 5 \Omega$ the following figure 8c. [4+4+8]

Code No: RR10204

RR

Set No. 2

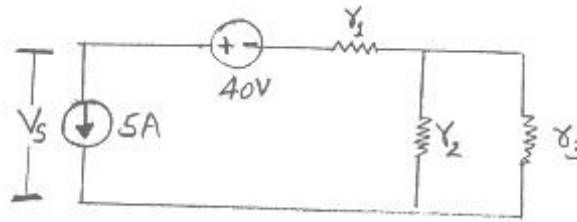


Figure 8c

FIRSTRANKER

Code No: RR10204

RR

Set No. 4

I B.Tech Examinations, December 2010

NETWORK THEORY

Common to BME, IT, ICE, E.COMP.E, ETM, E.CONT.E, EIE, CSE, ECE, CSSE, EEE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) State and explain the superposition theorem.
- (b) Using super position theorem find the current in 2 ohms resistor from the following network shown in figure3b. [6+10]

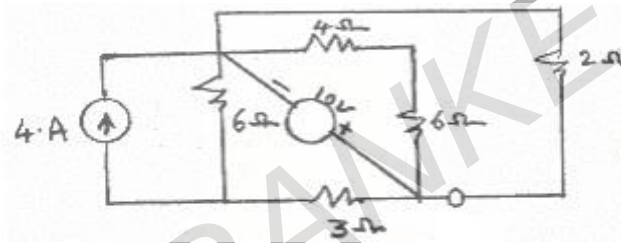


Figure 3b

2. (a) Write down the integro differential equations for the magnetically coupled circuit shown in figure1a. The mutual inductances between L_1 and L_2 , L_2 and L_3 , and L_3 and L_1 are respectively M_{12} , M_{23} and M_{13} .

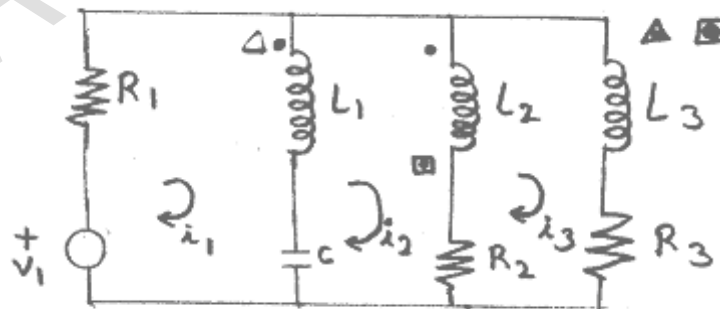


Figure 1a

- (b) Derive the relation between the flux density B and magnetising force H . Also derive the expression for reluctance. [8+8]
3. (a) A 3phase 4000V system has a delta connected load with $Z_{ab}=(8+j6)\Omega$, $Z_{bc}=(12+j16)\Omega$ and $Z_{ca}=(6-j8)\Omega$. Find the phase currents and line currents. Determine the power consumed by each load impedance. Draw the phasor diagram.
- (b) Three impedances are connected in figure 5b shown across a 400V, 50HZ, 3 phase supply. Find the readings of the watt meters. [10+6]

Code No: RR10204

RR

Set No. 4

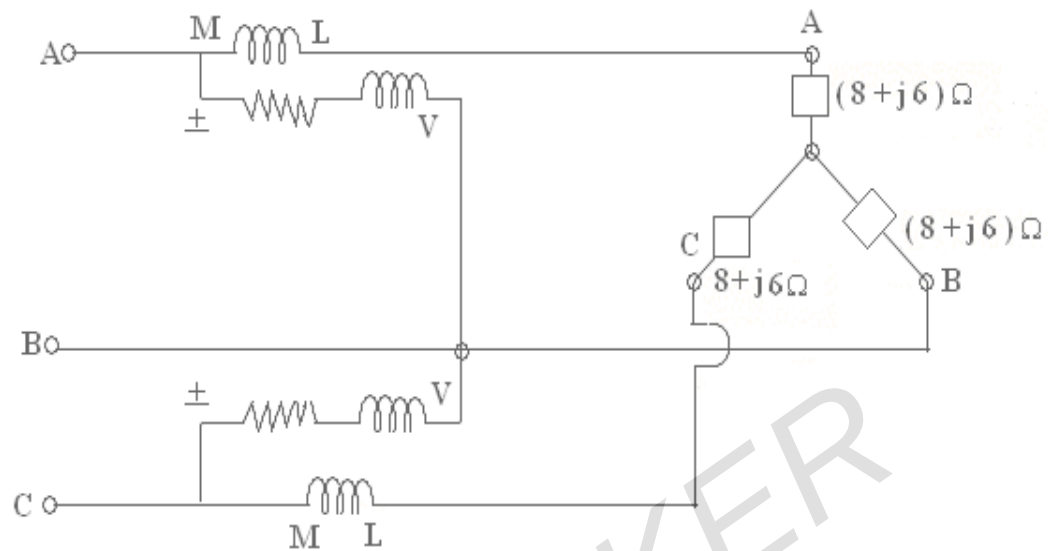


Figure 5b

4. (a) Explain the terms Graph, Tree, and a Cutset of a network with suitable example.
- (b) For the network shown in figure 6b, determine the value of the node voltages V_1 & V_2 . Determine the power dissipated in each of the resistors.

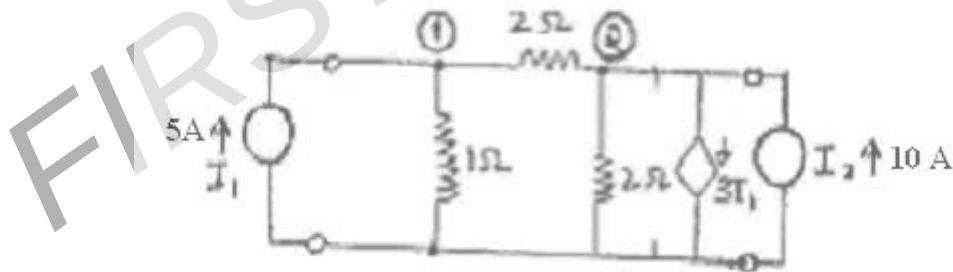


Figure 6b

- (c) Obtain the expression for the propagation constant of symmetrical T-network. [4+8+4]
5. (a) State and explain KCL and KVL
- (b) Distinguish between
- independent and dependent sources
 - Ideal and practical sources.
- (c) Find V_s if $r_1 = 2\Omega$, $r_2 = 1\Omega$, $r_3 = 5\Omega$ in the following figure 8c. [4+4+8]

Code No: RR10204

RR

Set No. 4

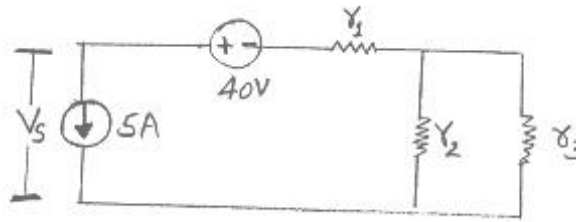


Figure 8c

6. (a) Find ABCD parameters for the following network shown in figure 4a.

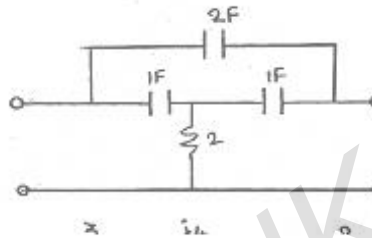


Figure 4a

- (b) Show that the total energy stored in the series RLC circuit is a constant when a constant voltage at resonance frequency is applied: Define Q-factor in terms of this energy. [8+8]
7. (a) Get the expression for complex power and the sign of the active power.
- (b) Find I_1 , I_2 , I_3 and I Find also the power consumed for the network shown in figure 7b. Draw the phasor diagram. [4+12]

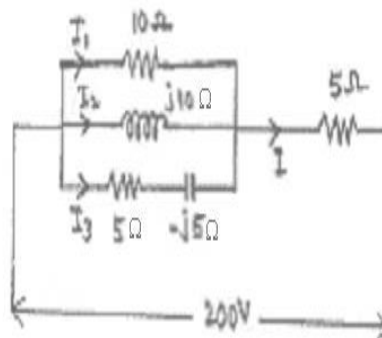


Figure 7b

8. (a) Explain why the voltage across capacitor cannot change instantaneously?
- (b) What is the significance of time constant for R-L circuit? What are the different ways of defining time constant?
- (c) Switch t is close at $t = 0$. Find initial conditions for voltage across capacitor, i_1 , i_2 , $\frac{di_1}{dt}$ and $\frac{di_2}{dt}$. In the following network shown in figure 2c. [2+4+10]

Code No: RR10204

RR

Set No. 4

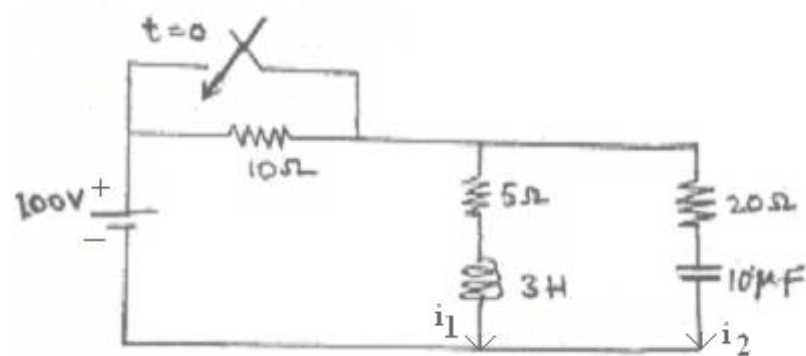


Figure 2c

Code No: RR10204

RR

Set No. 1

I B.Tech Examinations, December 2010

NETWORK THEORY

Common to BME, IT, ICE, E.COMP.E, ETM, E.CONT.E, EIE, CSE, ECE, CSSE, EEE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Explain why the voltage across capacitor cannot change instantaneously?
- (b) What is the significance of time constant for R-L circuit? What are the different ways of defining time constant?
- (c) Switch t is close at $t = 0$. Find initial conditions for voltage across capacitor, i_1 , i_2 , $\frac{di_1}{dt}$ and $\frac{di_2}{dt}$. In the following network shown in figure 2c. [2+4+10]

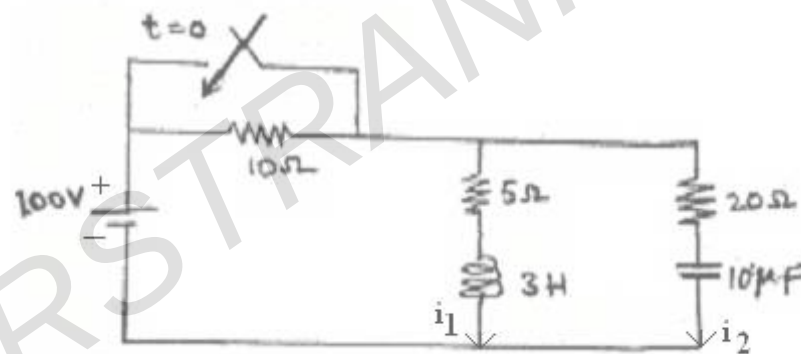


Figure 2c

2. (a) Get the expression for complex power and the sign of the active power.
- (b) Find I_1 , I_2 , I_3 and I Find also the power consumed for the network shown in figure 7b. Draw the phasor diagram. [4+12]

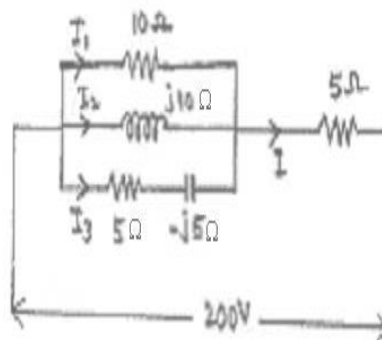


Figure 7b

3. (a) State and explain the superposition theorem.

Code No: RR10204

RR

Set No. 1

- (b) Using super position theorem find the current in 2 ohms resistor from the following network shown in figure3b. [6+10]

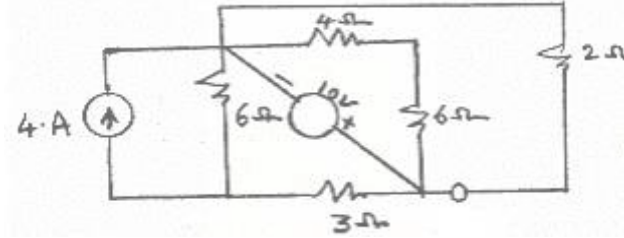


Figure 3b

4. (a) Find ABCD parameters for the following network shown in figure4a.

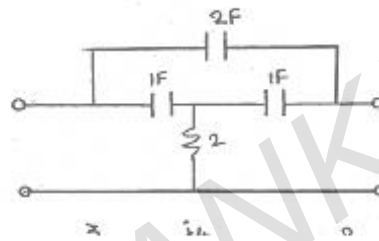


Figure 4a

- (b) Show that the total energy stored in the series RLC circuit is a constant when a constant voltage at resonance frequency is applied: Define Q-factor in terms of this energy. [8+8]
5. (a) A 3phase 4000V system has a delta connected load with $Z_{ab}=(8+j6)\Omega$, $Z_{bc}=(12+j16)\Omega$ and $Z_{ca}=(6-j8)\Omega$. Find the phase currents and line currents. Determine the power consumed by each load impedance. Draw the phasor diagram.
- (b) Three impedances are connected in figure 5b shown across a 400V, 50HZ, 3 phase supply. Find the readings of the watt meters. [10+6]

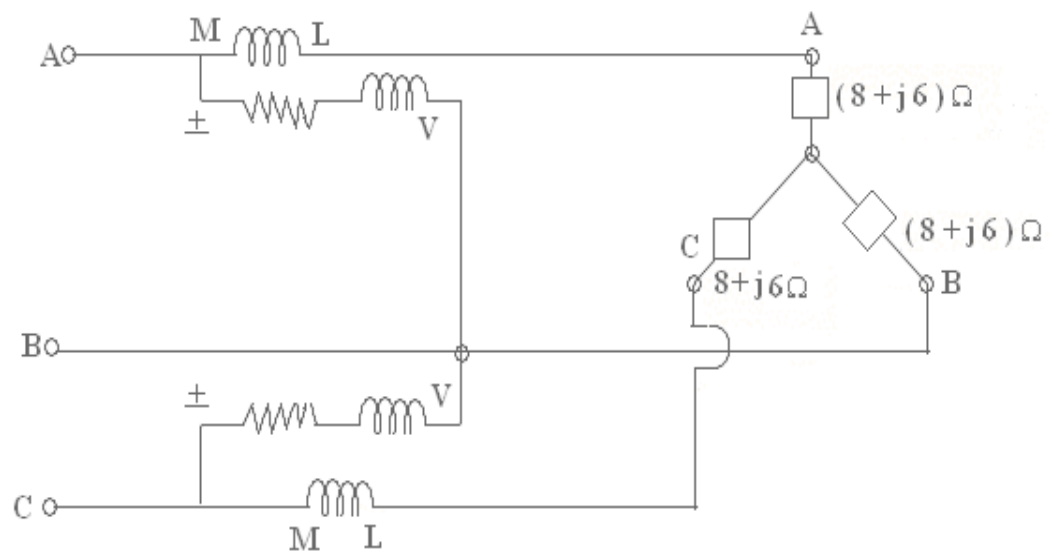


Figure 5b

Code No: RR10204

RR

Set No. 1

6. (a) Write down the integro differential equations for the magnetically coupled circuit shown in figure 1a. The mutual inductances between L_1 and L_2 , L_2 and L_3 , and L_3 and L_1 are respectively M_{12} , M_{23} and M_{13} .

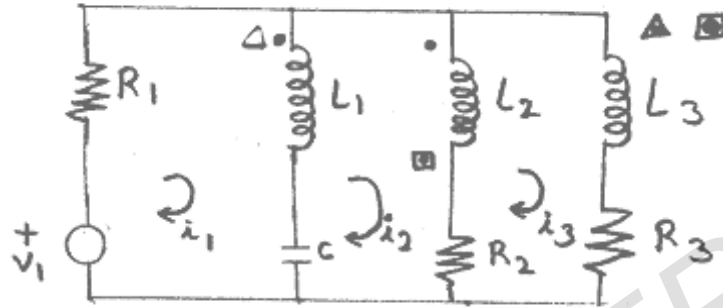


Figure 1a

- (b) Derive the relation between the flux density B and magnetising force H . Also derive the expression for reluctance. [8+8]
7. (a) Explain the terms Graph, Tree, and a Cutset of a network with suitable example.
- (b) For the network shown the figure 6b, determine the value of the node voltages V_1 & V_2 . Determine the power dissipated in each of the resistors.

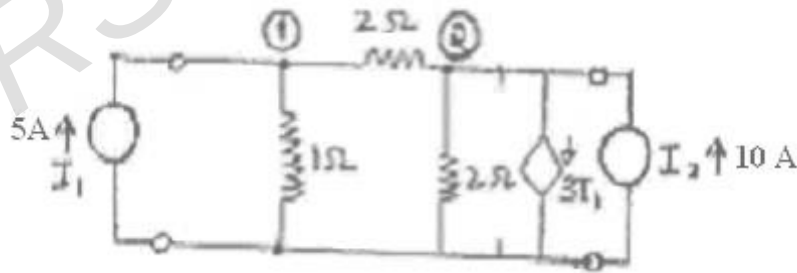


Figure 6b

- (c) Obtain the expression for the propagation constant of symmetrical T-network. [4+8+4]
8. (a) State and explain KCL and KVL
- (b) Distinguish between
- independent and dependent sources
 - Ideal and practical sources.
- (c) Find V_s if $r_1 = 2 \Omega$, $r_2 = 1 \Omega$, $r_3 = 5 \Omega$ the following figure 8c. [4+4+8]

Code No: RR10204

RR

Set No. 1

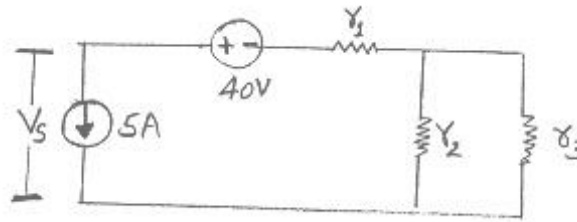


Figure 8c

FIRSTRANKER

Code No: RR10204

RR

Set No. 3

I B.Tech Examinations, December 2010

NETWORK THEORY

Common to BME, IT, ICE, E.COMP.E, ETM, E.CONT.E, EIE, CSE, ECE, CSSE, EEE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Write down the integro differential equations for the magnetically coupled circuit shown in figure 1a. The mutual inductances between L_1 and L_2 , L_2 and L_3 , and L_3 and L_1 are respectively M_{12} , M_{23} and M_{13} .

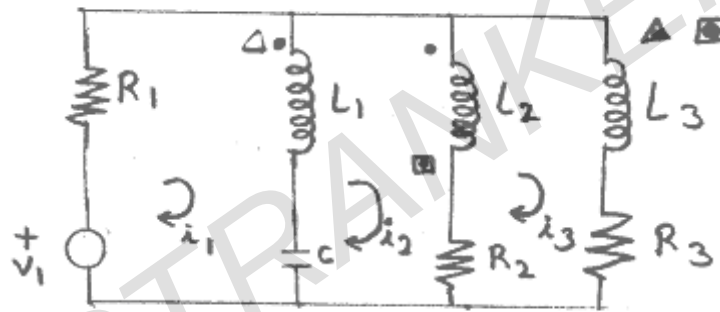


Figure 1a

- (b) Derive the relation between the flux density B and magnetising force H . Also derive the expression for reluctance. [8+8]
2. (a) Explain why the voltage across capacitor cannot change instantaneously?
- (b) What is the significance of time constant for R-L circuit? What are the different ways of defining time constant?
- (c) Switch t is close at $t = 0$. Find initial conditions for voltage across capacitor, i_1 , i_2 , $\frac{di_1}{dt}$ and $\frac{di_2}{dt}$. In the following network shown in figure 2c. [2+4+10]

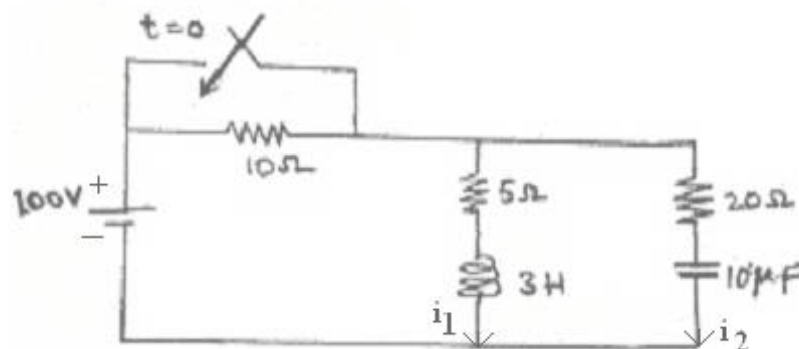


Figure 2c

Code No: RR10204

RR

Set No. 3

3. (a) State and explain the superposition theorem.
 (b) Using super position theorem find the current in 2 ohms resistor from the following network shown in figure3b. [6+10]

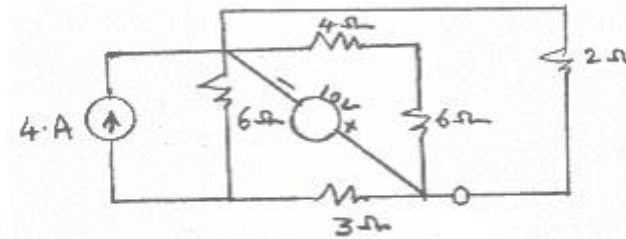


Figure 3b

4. (a) Find ABCD parameters for the following network shown in figure4a.

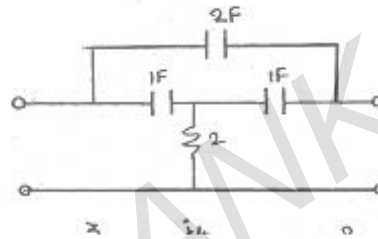


Figure 4a

- (b) Show that the total energy stored in the series RLC circuit is a constant when a constant voltage at resonance frequency is applied: Define Q-factor in terms of this energy. [8+8]
5. (a) A 3phase 4000V system has a delta connected load with $Z_{ab}=(8+j6)\Omega$, $Z_{bc}=(12+j16)\Omega$ and $Z_{ca}=(6-j8)\Omega$. Find the phase currents and line currents. Determine the power consumed by each load impedance. Draw the phasor diagram.
- (b) Three impedances are connected in figure 5b shown across a 400V, 50HZ, 3 phase supply. Find the readings of the watt meters. [10+6]

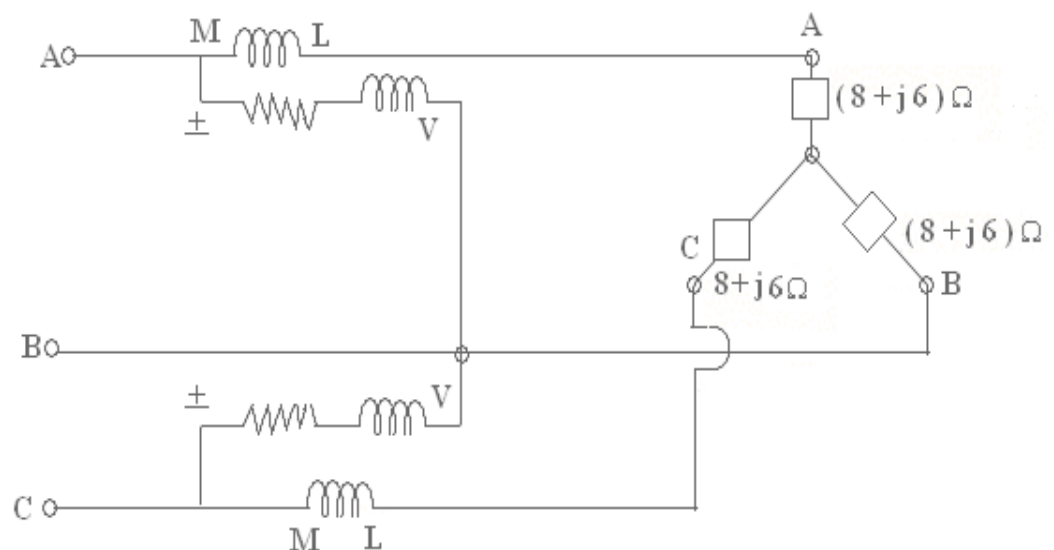


Figure 5b

Code No: RR10204

RR

Set No. 3

6. (a) Explain the terms Graph, Tree, and a Cutset of a network with suitable example.
- (b) For the network shown in figure 6b, determine the value of the node voltages V_1 & V_2 . Determine the power dissipated in each of the resistors.

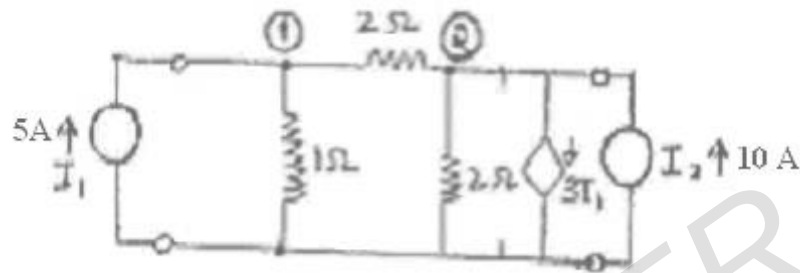


Figure 6b

- (c) Obtain the expression for the propagation constant of symmetrical T-network. [4+8+4]
7. (a) Get the expression for complex power and the sign of the active power.
- (b) Find I_1 , I_2 , I_3 and I . Find also the power consumed for the network shown in figure 7b. Draw the phasor diagram. [4+12]

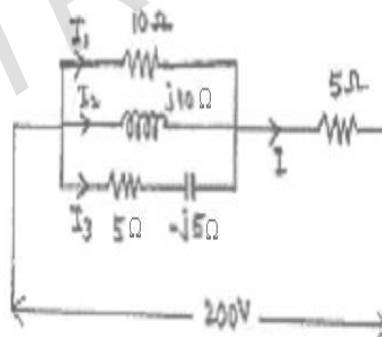


Figure 7b

8. (a) State and explain KCL and KVL
- (b) Distinguish between
- independent and dependent sources
 - Ideal and practical sources.
- (c) Find V_s if $r_1 = 2\Omega$, $r_2 = 1\Omega$, $r_3 = 5\Omega$ in the following figure 8c. [4+4+8]

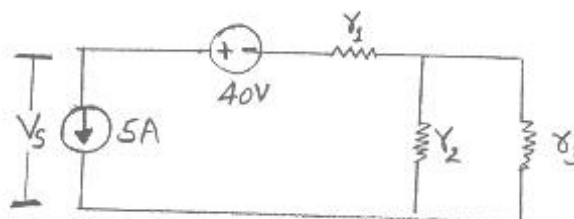


Figure 8c

Code No: RR10204

RR

Set No. 3

FIRSTRANKER