

Code.No: RR12302

RR

SET-1

I B.TECH – EXAMINATIONS, DECEMBER - 2010
ELECTRICAL AND ELECTRONICS ENGINEERING
(BIO – TECHNOLOGY)


Time: 3hours

Max.Marks:80


Answer any FIVE questions
All questions carry equal marks

- - -

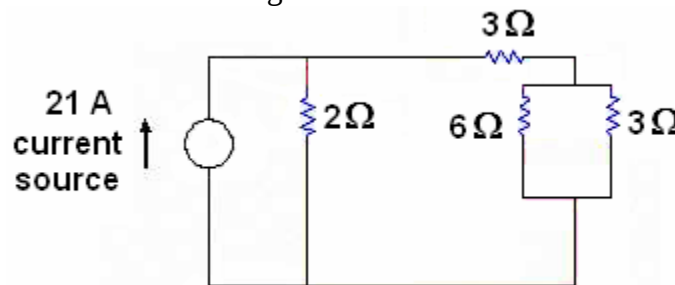
- 1.a) Name the different types of elements that constitute an electric circuit.
 b) A 20V source with an internal resistance of 2Ω is connected to a load resistance of 8Ω . Find the load current. Verify your result by transforming the voltage source into current source as shown in the figure.



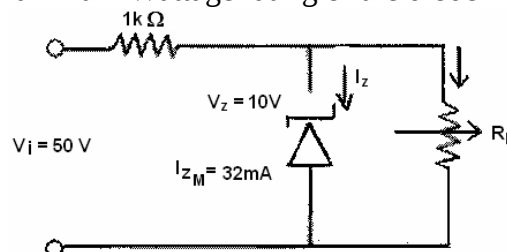- c) In the above circuit, calculate the current through 6Ω resistor. [4+4+8]
- 2.a) Does the induction motor have any similarities with the transformer. Compare the similarities and differences between them.
 b) A 20h.p, 400V, 50HZ, 3-phase induction motor has an efficiency of 80% and working at 0.7 p.f. The motor is connected to 400 volts, 3-phase supply calculate the current drawn by the motor from the mains. [8+8]
- 3.a)i) Find the resistivity of intrinsic silicon at 300°K . It is given the n_i at 300°K in silicon is $1.5 \times 10^{10}/\text{cm}^3$, $\mu_p = 500 \text{ cm}^2/\text{V-S}$, $\mu_n = 1300 \text{ cm}^2/\text{V-S}$.
 ii) If an acceptor impurity is added to the extent of 1 impurity atom in 2×10^8 silicon atoms, find it's resistivity.
 iii) If a donor impurity is added to the extent of 1 impurity atom in 5×10^7 silicon atoms, find it's resistivity.
 b) Prove that the concentration of free electron in an intrinsic semiconductor is given by $n = N_c e^{-(E_c - E_f)/KT}$ [12+4]
4. For the network shown in the figure determine the range of R_L and I_L that will result in V_{RL} being maintained at 10 V:
 a) Determine the maximum Wattage rating of the diode



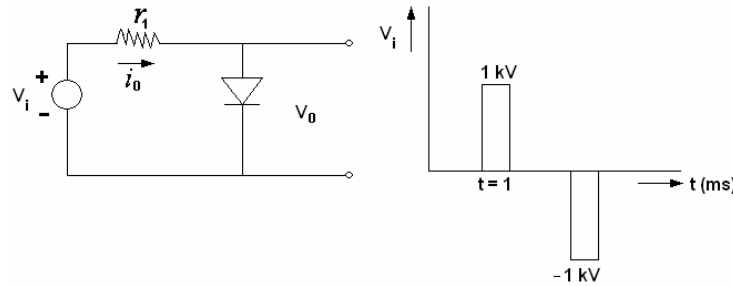- b) The reverse saturation current of the diode is $1 \mu\text{A}$. Its peak inverse Voltage is 500V . Find r_i , V_0 that PIV is not exceeded as shown in figure. [16]



- 5.a) Derive the expression for:
- Average current
 - DC output voltage
 - RMS current,
 - RMS voltage across the load,
 - Rectifier efficiency
 - Regulation for full wave rectifier whose input a sine wave.
- b) Prove that the regulation of both half wave and full wave rectifier is given by %

$$\text{regulation} = \frac{R_f}{R_L} \times 100.$$
 [10+6]
- 6.a) With the help of block diagrams, explain the four different feed back topologies.
 b) Draw the circuit of a voltage series feedback amplifier with BJT. What is the effect of this feedback as R_i and R_0 ? [6+10]
- 7.a) Draw the circuit diagram of wien bridge oscillator using BJT. Show that the gain of the amplifier must be at least 3 for the oscillations to occur.
 b) For the fixed-bias Ge transistor, n-p-n type, the junction voltages at saturation and cutoff one in active region, may be assumed to zero. This circuit operates properly over the temperature range -50°C to 75°C and to just start malfunctioning at these extremes. The various circuit specifications are: $V_{CC} = 4.5\text{V}$, $V_{BB} = 3\text{V}$, $h_{FE} = 40$ at -50°C , and $h_{fe} = 60$ at 75°C , $I_{CBO} = 4 \mu\text{A}$ at 25°C and doubles every 10°C . Collector current is $10 \mu\text{A}$. Design the values of R_{c1} , R_1 and R_2 . [8+8]
- 8.a) Explain how a shift register is used as a Ring counter. Draw the O/P waveform from each flip-flop of a 3-stage unit.
 b) Prove that if $w'x + yz = 0$, then $wx + y'(w' + z') = wx + xz + x'z' + w'y'z$
 c) Represent the given negative numbers in sign-magnitude, 1'S and 2'S complement representation in 12-bit format:
 i) -64
 ii) -512. [6+6+4]

Code.No: RR12302

RR

SET-2

I B.TECH – EXAMINATIONS, DECEMBER - 2010
ELECTRICAL AND ELECTRONICS ENGINEERING
(BIO – TECHNOLOGY)

Time: 3hours


Max.Marks:80

Answer any FIVE questions
All questions carry equal marks


- 1.a)i) Find the resistivity of intrinsic silicon at 300⁰K. It is given the n_i at 300⁰K in silicon is $1.5 \times 10^{10}/\text{Cm}^3$, $\mu_p = 500 \text{ cm}^2 / \text{V} - \text{S}$, $\mu_n = 1300 \text{ cm}^2 / \text{V} - \text{S}$.
- ii) If an acceptor impurity is added to the extent of 1 impurity atom in 2×10^8 silicon atoms, find it's resistivity.
- iii) If a donor impurity is added to the extent of 1 impurity atom in 5×10^7 silicon atoms, find it's resistivity.
- b) Prove that the concentration of free electron in an intrinsic semiconductor is given by $n = N_c e^{-(E_c - E_f)/KT}$ [12+4]

2. For the network shown in the figure determine the range of R_L and I_L that will result in V_{RL} being maintained at 10 V:

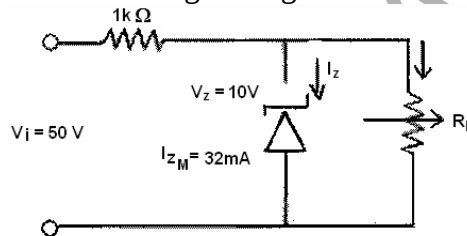- a) Determine the maximum Wattage rating of the diode



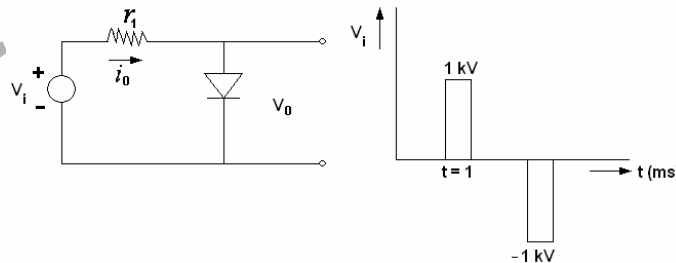- b) The reverse saturation current of the diode is 1 μ A. Its peak inverse Voltage is 500V. Find r_i , V_0 that PIV is not exceeded as shown in figure. [16]



- 3.a) Derive the expression for:
- Average current
 - DC output voltage
 - RMS current,
 - RMS voltage across the load,
 - Rectifier efficiency
 - Regulation for full wave rectifier whose input a sine wave.
- b) Prove that the regulation of both half wave and full wave rectifier is given by %


$$\text{regulation} = \frac{R_f}{R_L} \times 100. \quad [10+6]$$

Code.No: RR12302

RR

SET-2

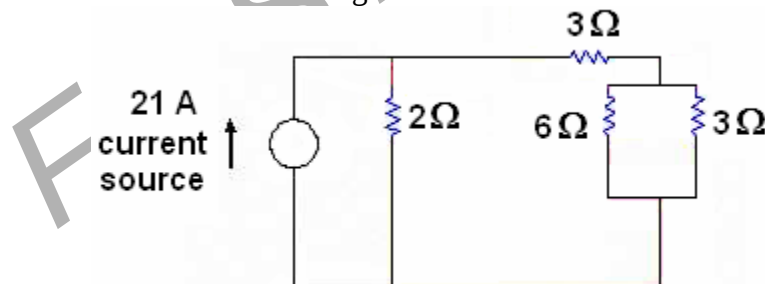- 4.a) With the help of block diagrams, explain the four different feed back topologies.
 b) Draw the circuit of a voltage series feedback amplifier with BJT. What is the effect of this feedback as R_i and R_o ? [6+10]
- 5.a) Draw the circuit diagram of wien bridge oscillator using BJT. Show that the gain of the amplifier must be at least 3 for the oscillations to occur.
 b) For the fixed-bias Ge transistor, n-p-n type, the junction voltages at saturation and cutoff one in active region, may be assumed to zero. This circuit operates properly over the temperature range -50°C to 75°C and to just start malfunctioning at these extremes. The various circuit specifications are: $V_{CC} = 4.5\text{V}$, $V_{BB} = 3\text{V}$, $h_{FE} = 40$ at -50°C , and $h_{fe} = 60$ at 75°C , $I_{CBO} = 4\mu\text{A}$ at 25°C and doubles every 10°C . Collector current is $10\mu\text{A}$. Design the values of R_{c1} , R_1 and R_2 . [8+8]
- 6.a) Explain how a shift register is used as a Ring counter. Draw the O/P waveform from each flip-flop of a 3-stage unit.
 b) Prove that if $w'x + yz = 0$, then $wx + y'(w' + z') = wx + xz + x'z' + w'y'z$
 c) Represent the given negative numbers in sign-magnitude, 1'S and 2'S complement representation in 12-bit format:
 i) -64
 ii) -512. [6+6+4]
- 7.a) Name the different types of elements that constitute an electric circuit.
 b) A 20V source with an internal resistance of 2Ω is connected to a load resistance of 8Ω . Find the load current. Verify your result by transforming the voltage source into current source as shown in the figure.



- c) In the above circuit, calculate the current through 6Ω resistor. [4+4+8]
- 8.a) Does the induction motor have any similarities with the transformer. Compare the similarities and differences between them.
 b) A 20h.p, 400V, 50HZ, 3-phase induction motor has an efficiency of 80% and working at 0.7 p.f. The motor is connected to 400 volts, 3-phase supply calculate the current drawn by the motor from the mains. [8+8]

--oOo--

Code.No: RR12302

RR

SET-3

I B.TECH – EXAMINATIONS, DECEMBER - 2010
ELECTRICAL AND ELECTRONICS ENGINEERING
(BIO – TECHNOLOGY)

Time: 3 hours


Max.Marks:80

Answer any FIVE questions
All questions carry equal marks

- - -

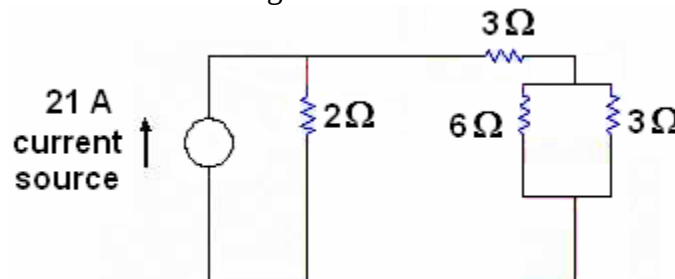- 1.a) Derive the expression for:
 - i) Average current
 - ii) DC output voltage
 - iii) RMS current,
 - iv) RMS voltage across the load,
 - v) Rectifier efficiency
 - vi) Regulation for full wave rectifier whose input a sine wave.
- b) Prove that the regulation of both half wave and full wave rectifier is given by %

$$\text{regulation} = \frac{R_f}{R_L} \times 100.$$
 [10+6]
- 2.a) With the help of block diagrams, explain the four different feed back topologies.
- b) Draw the circuit of a voltage series feedback amplifier with BJT. What is the effect of this feedback as R_i and R_o ? [6+10]
- 3.a) Draw the circuit diagram of wien bridge oscillator using BJT. Show that the gain of the amplifier must be at least 3 for the oscillations to occur.
- b) For the fixed-bias Ge transistor, n-p-n type, the junction voltages at saturation and cutoff one in active region, may be assumed to zero. This circuit operates properly over the temperature range -50°C to 75°C and to just start malfunctioning at these extremes. The various circuit specifications are: $V_{CC} = 4.5\text{V}$, $V_{BB} = 3\text{V}$, $h_{FE} = 40$ at -50°C , and $h_{fe} = 60$ at 75°C , $I_{CBO} = 4\mu\text{A}$ at 25°C and doubles every 10°C . Collector current is $10\mu\text{A}$. Design the values of R_{C1} , R_1 and R_2 . [8+8]
- 4.a) Explain how a shift register is used as a Ring counter. Draw the O/P waveform from each flip-flop of a 3-stage unit.
- b) Prove that if $w'x + yz = 0$, then $wx + y'(w' + z') = wx + xz + x'z' + w'y'z$
- c) Represent the given negative numbers in sign-magnitude, 1'S and 2'S complement representation in 12-bit format:
 - i) -64
 - ii) -512. [6+6+4]
- 5.a) Name the different types of elements that constitute an electric circuit.
- b) A 20V source with an internal resistance of 2Ω is connected to a load resistance of 8Ω . Find the load current. Verify your result by transforming the voltage source into current source as shown in the figure.




- c) In the above circuit, calculate the current through 6Ω resistor. [4+4+8]

Code.No: RR12302


RR

SET-3

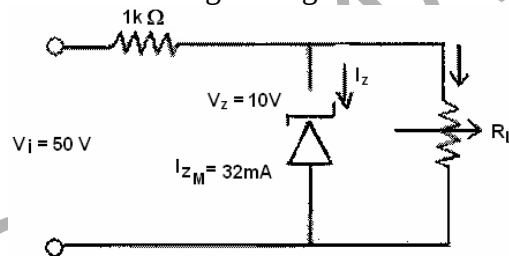- 6.a) Does the induction motor have any similarities with the transformer. Compare the similarities and differences between them.
- b) A 20h.p, 400V, 50HZ, 3-phase induction motor has an efficiency of 80% and working at 0.7 p.f. The motor is connected to 400 volts, 3-phase supply calculate the current drawn by the motor from the mains. [8+8]
- 7.a)i) Find the resistivity of intrinsic silicon at 300 °K. It is given the n_i at 300 °K in silicon is $1.5 \times 10^{10}/\text{Cm}^3$, $\mu_p = 500 \text{ cm}^2 / \text{V} - \text{S}$, $\mu_n = 1300 \text{ cm}^2 / \text{V} - \text{S}$.
- ii) If an acceptor impurity is added to the extent of 1 impurity atom in 2×10^8 silicon atoms, find it's resistivity.
- iii) If a donor impurity is added to the extent of 1 impurity atom in 5×10^7 silicon atoms, find it's resistivity.
- b) Prove that the concentration of free electron in an intrinsic semiconductor is given by $n = N_c e^{-(E_c - E_f)/KT}$ [12+4]
8. For the network shown in the figure determine the range of R_L and I_L that will result in V_{RL} being maintained at 10 V:
- a) Determine the maximum Wattage rating of the diode



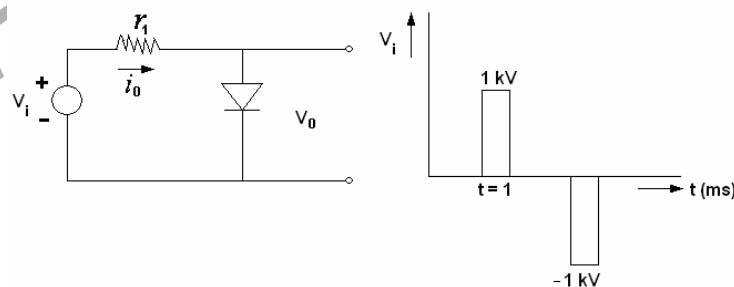- b) The reverse saturation current of the diode is $1 \mu\text{A}$. Its peak inverse Voltage is 500V. Find r_i , V_0 that PIV is not exceeded as shown in figure. [16]



--oOo--

Code.No: RR12302

RR

SET-4


I B.TECH – EXAMINATIONS, DECEMBER - 2010
ELECTRICAL AND ELECTRONICS ENGINEERING
(BIO – TECHNOLOGY)

Time: 3hours

Max.Marks:80

Answer any FIVE questions
All questions carry equal marks

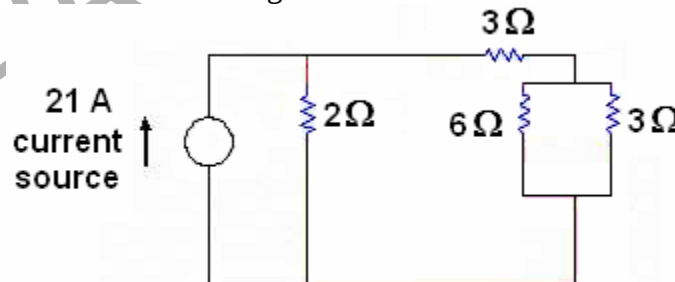- 1.a) Draw the circuit diagram of wien bridge oscillator using BJT. Show that the gain of the amplifier must be at least 3 for the oscillations to occur.
- b) For the fixed-bias Ge transistor, n-p-n type, the junction voltages at saturation and cutoff one in active region, may be assumed to zero. This circuit operates properly over the temperature range -50°C to 75°C and to just start malfunctioning at these extremes. The various circuit specifications are: $V_{CC} = 4.5\text{V}$, $V_{BB} = 3\text{V}$, $h_{FE} = 40$ at -50°C , and $h_{fe} = 60$ at 75°C , $I_{CBO} = 4\mu\text{A}$ at 25°C and doubles every 10°C . Collector current is $10\mu\text{A}$. Design the values of R_{C1} , R_1 and R_2 . [8+8]
- 2.a) Explain how a shift register is used as a Ring counter. Draw the O/P waveform from each flip-flop of a 3-stage unit.
- b) Prove that if $w'x + yz = 0$, then $wx + y'(w' + z') = wx + xz + x'z' + w'y'z$
- c) Represent the given negative numbers in sign-magnitude, 1'S and 2'S complement representation in 12-bit format:
 - i) -64
 - ii) -512. [6+6+4]
- 3.a) Name the different types of elements that constitute an electric circuit.
- b) A 20V source with an internal resistance of 2Ω is connected to a load resistance of 8Ω . Find the load current. Verify your result by transforming the voltage source into current source as shown in the figure.




- c) In the above circuit, calculate the current through 6Ω resistor. [4+4+8]
- 4.a) Does the induction motor have any similarities with the transformer. Compare the similarities and differences between them.
- b) A 20hp, 400V, 50HZ, 3-phase induction motor has an efficiency of 80% and working at 0.7 p.f. The motor is connected to 400 volts, 3-phase supply calculate the current drawn by the motor from the mains. [8+8]
- 5.a)i) Find the resistivity of intrinsic silicon at 300°K . It is given the n_i at 300°K in silicon is $1.5 \times 10^{10}/\text{cm}^3$, $\mu_p = 500\text{cm}^2/\text{V-S}$, $\mu_n = 1300\text{cm}^2/\text{V-S}$.
- ii) If an acceptor impurity is added to the extent of 1 impurity atom in 2×10^8 silicon atoms, find it's resistivity.

Code.No: RR12302


RR

SET-4

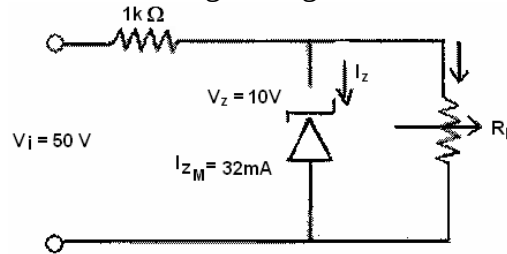- iii) If a donor impurity is added to the extent of 1 impurity atom in 5×10^7 silicon atoms, find its resistivity.
- b) Prove that the concentration of free electron in an intrinsic semiconductor is given by $n = N_c e^{-(E_c - E_f)/KT}$ [12+4]
6. For the network shown in the figure determine the range of R_L and I_L that will result in V_{RL} being maintained at 10 V:
- a) Determine the maximum Wattage rating of the diode



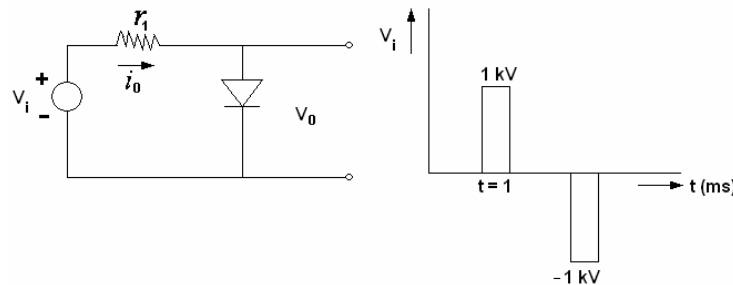- b) The reverse saturation current of the diode is $1 \mu A$. Its peak inverse Voltage is 500V. Find r_i , V_0 that PIV is not exceeded as shown in figure. [16]



- 7.a) Derive the expression for:
- Average current
 - DC output voltage
 - RMS current,
 - RMS voltage across the load,
 - Rectifier efficiency
 - Regulation for full wave rectifier whose input a sine wave.
- b) Prove that the regulation of both half wave and full wave rectifier is given by %

$$\text{regulation} = \frac{R_f}{R_L} \times 100.$$
 [10+6]
- 8.a) With the help of block diagrams, explain the four different feed back topologies.
- b) Draw the circuit of a voltage series feedback amplifier with BJT. What is the effect of this feedback as R_i and R_0 ? [6+10]

--oOo--