

Code No: RR220203

RR

Set No. 2

II B.Tech II Semester Examinations, December 2010

LINEAR AND DIGITAL IC APPLICATIONS

Common to Instrumentation And Control Engineering, Electronics And
Computer Engineering, Electrical And Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Explain the terms Lock range, Capture range and Pull-in time of a PLL. How are Lock Range and Capture range determined? [8]
(b) Design a PLL circuit using IC 565 to get:
 - i. Free-running frequency = 4.5 KHz
 - ii. Lock range of 2 KHz and
 - iii. Capture range = 100 Hz .
 Assume a supply voltage of + or - 10V. Show the circuit diagram with all component values. [3+3+2]
2. (a) Define the terms: SVRR, CMRR, input bias current, input offset voltage, Gain Bandwidth product.
(b) What are the differences between the inverting and non inverting terminals? What do you mean by the term "virtual ground"? [10+6]
3. (a) The 741C Op-Amp is configured as a non-inverting amplifier having the following parameters: $A=400000$, $R_1=470\Omega$, $R_F=4.7\text{K}\Omega$, $R_i=33\text{M}\Omega$, $R_o=60\Omega$, $f_o=5\text{Hz}$, Unity gain bandwidth= 0.6MHz , supply voltages= $\pm 15\text{V}$, maximum output voltage swing = $\pm 13\text{V}$. Computer the values of:
 - i. A_F closed loop voltage gain,
 - ii. R_{iF} input resistance with feedback,
 - iii. R_{oF} output resistance with feedback, and
 - iv. f_F bandwidth with feedback. [4×3]
 (b) Explain the operation of zero crossing detector using Op-Amps. [4]
4. (a) List out different types of A/D converters and compare their merits and demerits.
(b) Give the schematic circuit of an A/D converter widely used in digital voltmeters and explain its operation. Derive expression for output voltage. [8+8]
5. (a) An integrator with $R=400\Omega$ and $C=1\text{ }\mu\text{F}$ is used to generate a triangular waveform from a 500 Hz square wave that alternates between $\pm 12\text{V}$. What should be the minimum slew rate of the Op-amp? What is the maximum output voltage? [2×4]
(b) Draw and explain the operation of an analog multiplexer. [2+6]

Code No: RR220203

RR

Set No. 2

6. (a) Compare different logic families and mention their advantages and disadvantages?
(b) Which is the fastest non-saturated logic gate? Draw the circuit and explain its functions. [8+8]
7. (a) What are the advantages of active filters over passive ones?
(b) Design a second order low pass Butterworth filter for a cut off frequency of $2kHz$. Assume necessary data.
(c) What is an all pass filter? Draw the circuit of all pass filters. [5+6+5]
8. Explain the operation of Monostable multivibrator using 555 timer. Derive the expression of time delay of a Monostable multivibrator using 555 timer. [8+8]

Code No: RR220203

RR

Set No. 4

II B.Tech II Semester Examinations, December 2010

LINEAR AND DIGITAL IC APPLICATIONS

Common to Instrumentation And Control Engineering, Electronics And
Computer Engineering, Electrical And Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) List out different types of A/D converters and compare their merits and demerits.
(b) Give the schematic circuit of an A/D converter widely used in digital voltmeters and explain its operation. Derive expression for output voltage. [8+8]
2. (a) What are the advantages of active filters over passive ones?
(b) Design a second order low pass Butterworth filter for a cut off frequency of 2kHz . Assume necessary data.
(c) What is an all pass filter? Draw the circuit of all pass filters. [5+6+5]
3. (a) Compare different logic families and mention their advantages and disadvantages?
(b) Which is the fastest non-saturated logic gate? Draw the circuit and explain its functions. [8+8]
4. (a) Define the terms: SVRR, CMRR, input bias current, input offset voltage, Gain Bandwidth product.
(b) What are the differences between the inverting and non inverting terminals? What do you mean by the term "virtual ground"? [10+8]
5. (a) Explain the terms Lock range, Capture range and Pull-in time of a PLL. How are Lock Range and Capture range determined? [8]
(b) Design a PLL circuit using IC 565 to get:
 - i. Free-running frequency = 4.5 KHz
 - ii. Lock range of 2 KHz and
 - iii. Capture range = 100 Hz .
 Assume a supply voltage of + or - 10V. Show the circuit diagram with all component values. [3+3+2]
6. (a) An integrator with $R=400\Omega$ and $C=1\mu\text{F}$ is used to generate a triangular waveform from a 500 Hz square wave that alternates between $\pm 12\text{V}$. What should be the minimum slew rate of the Op-amp? What is the maximum output voltage? [2+4]
(b) Draw and explain the operation of an analog multiplexer. [2+6]

Code No: RR220203

RR

Set No. 4

7. Explain the operation of Monostable multivibrator using 555 timer. Derive the expression of time delay of a Monostable multivibrator using 555 timer. [8+8]
8. (a) The 741C Op-Amp is configured as a non-inverting amplifier having the following parameters: $A=400000$, $R_1=470\Omega$, $R_F=4.7K\Omega$, $R_i=33M\Omega$, $R_o=60\Omega$, $f_o=5Hz$, Unity gain bandwidth= $0.6MHz$, supply voltages= $\pm 15V$, maximum output voltage swing = $\pm 13V$. Computer the values of:
- i. A_F closed loop voltage gain,
 - ii. R_{iF} input resistance with feedback,
 - iii. R_{oF} output resistance with feedback, and
 - iv. f_F bandwidth with feedback. [4×3]
- (b) Explain the operation of zero crossing detector using Op-Amps. [4]

Code No: RR220203

RR

Set No. 1

II B.Tech II Semester Examinations, December 2010

LINEAR AND DIGITAL IC APPLICATIONS

Common to Instrumentation And Control Engineering, Electronics And
Computer Engineering, Electrical And Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) An integrator with $R=400\Omega$ and $C=1\mu F$ is used to generate a triangular waveform from a 500 Hz square wave that alternates between $\pm 12V$. What should be the minimum slew rate of the Op-amp? What is the maximum output voltage? [2+4]
- (b) Draw and explain the operation of an analog multiplexer. [2+6]
2. (a) What are the advantages of active filters over passive ones?
- (b) Design a second order low pass Butterworth filter for a cut off frequency of $2kHz$. Assume necessary data.
- (c) What is an all pass filter? Draw the circuit of all pass filters. [5+6+5]
3. (a) The 741C Op-Amp is configured as a non-inverting amplifier having the following parameters: $A=400000$, $R_1=470\Omega$, $R_F=4.7K\Omega$, $R_i=33M\Omega$, $R_o=60\Omega$, $f_o=5Hz$, Unity gain bandwidth=0.6MHz, supply voltages= $\pm 15V$, maximum output voltage swing = $\pm 13V$. Compute the values of:
 - i. A_F closed loop voltage gain,
 - ii. R_{iF} input resistance with feedback,
 - iii. R_{oF} output resistance with feedback, and
 - iv. f_F bandwidth with feedback. [4+3]
- (b) Explain the operation of zero crossing detector using Op-Amps. [4]
4. (a) Define the terms: SVRR, CMRR, input bias current, input offset voltage, Gain Bandwidth product.
- (b) What are the differences between the inverting and non inverting terminals? What do you mean by the term "virtual ground"? [10+6]
5. (a) Compare different logic families and mention their advantages and disadvantages?
- (b) Which is the fastest non-saturated logic gate? Draw the circuit and explain its functions. [8+8]
6. (a) List out different types of A/D converters and compare their merits and demerits.
- (b) Give the schematic circuit of an A/D converter widely used in digital voltmeters and explain its operation. Derive expression for output voltage. [8+8]

Code No: RR220203

RR

Set No. 1

7. Explain the operation of Monostable multivibrator using 555 timer. Derive the expression of time delay of a Monostable multivibrator using 555 timer. [8+8]
8. (a) Explain the terms Lock range, Capture range and Pull-in time of a PLL. How are Lock Range and Capture range determined? [8]
- (b) Design a PLL circuit using IC 565 to get:
- i. Free-running frequency = 4.5 KHz
 - ii. Lock range of 2 KHz and
 - iii. Capture range = 100 Hz .

Assume a supply voltage of + or - 10V. Show the circuit diagram with all component values. [3+3+2]

Code No: RR220203

RR

Set No. 3

II B.Tech II Semester Examinations, December 2010

LINEAR AND DIGITAL IC APPLICATIONS

Common to Instrumentation And Control Engineering, Electronics And
Computer Engineering, Electrical And Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Explain the terms Lock range, Capture range and Pull-in time of a PLL. How are Lock Range and Capture range determined? [8]
(b) Design a PLL circuit using IC 565 to get:
 - i. Free-running frequency = 4.5 KHz
 - ii. Lock range of 2 KHz and
 - iii. Capture range = 100 Hz .
 Assume a supply voltage of + or - 10V. Show the circuit diagram with all component values. [3+3+2]
2. Explain the operation of Monostable multivibrator using 555 timer. Derive the expression of time delay of a Monostable multivibrator using 555 timer. [8+8]
3. (a) List out different types of A/D converters and compare their merits and demerits.
(b) Give the schematic circuit of an A/D converter widely used in digital voltmeters and explain its operation. Derive expression for output voltage. [8+8]
4. (a) The 741C Op-Amp is configured as a non-inverting amplifier having the following parameters: $A=400000$, $R_1=470\Omega$, $R_F=4.7\text{K}\Omega$, $R_i=33\text{M}\Omega$, $R_o=60\Omega$, $f_o=5\text{Hz}$, Unity gain bandwidth= 0.6MHz , supply voltages= $\pm 15\text{V}$, maximum output voltage swing = $\pm 13\text{V}$. Compute the values of:
 - i. A_F closed loop voltage gain,
 - ii. R_{iF} input resistance with feedback,
 - iii. R_{oF} output resistance with feedback, and
 - iv. f_F bandwidth with feedback. [4×3]
 (b) Explain the operation of zero crossing detector using Op-Amps. [4]
5. (a) Define the terms: SVRR, CMRR, input bias current, input offset voltage, Gain Bandwidth product.
(b) What are the differences between the inverting and non inverting terminals? What do you mean by the term "virtual ground"? [10+6]
6. (a) Compare different logic families and mention their advantages and disadvantages?

Code No: RR220203

RR

Set No. 3

- (b) Which is the fastest non-saturated logic gate? Draw the circuit and explain its functions. [8+8]
7. (a) What are the advantages of active filters over passive ones?
- (b) Design a second order low pass Butterworth filter for a cut off frequency of $2kHz$. Assume necessary data.
- (c) What is an all pass filter? Draw the circuit of all pass filters. [5+6+5]
8. (a) An integrator with $R=400\Omega$ and $C=1\mu F$ is used to generate a triangular waveform from a 500 Hz square wave that alternates between $\pm 12V$. What should be the minimum slew rate of the Op-amp? What is the maximum output voltage? [2+4]
- (b) Draw and explain the operation of an analog multiplexer. [2+6]
