

Code No: RR311001

RR

Set No. 2

III B.Tech I Semester Examinations, November 2010

LINEAR AND DIGITAL IC APPLICATIONS

Common to BME, MECT, ETM, E.CONT.E, EIE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions

All Questions carry equal marks

1. (a) Explain in detail the following terms with reference to PLL
 - i. Lock range
 - ii. Capture range
 - iii. Capture transient
 - iv. Pull-in-time. [8]
- (b) i. Draw the internal functional diagram of NE 566 VCO and derive expression for free running frequency.
- ii. From the given component values find the free running frequency Control voltage $V_C = 10.9V$, $V_{CC} = 12V$, $R_1 = 4.7k$ and $C_1 = 1.1nF$. [8]
2. (a) Define the terms [4]
 - i. Positive logic
 - ii. Negative logic
- (b) Show that positive logic EX-OR operation is equivalent to negative logic EX-NOR operation. [4]
- (c) Draw the circuit 3 input D.T.L. NAND gate and explain its operation with the help of truth-table. How can you improve the Fan-out of the circuit. Explain with the help of modified circuit. [8]
3. (a) Explain the operation of a delay equalizer circuit with neat sketches. Derive an expression relating input and output voltages of the equalizer. [8+2]
- (b) For the all pass filter, determine the phase shift between input and output at $f = 2 \text{ kHz}$. To obtain a positive phase shift. What modifications are necessary in the circuit? [6]
4. (a) What feedback is preferred for oscillators and why? What is the effect of negative feedback? [8]
- (b) Design an OP-AMP based relaxation oscillator and derive the frequency of oscillation. [8]
5. (a) Explain the operation of Monostable multivibrator using 555 timer. Derive the expression of time delay of a Monostable multivibrator using 555 timer. [10]
- (b) Design a Monostable multivibrator using 555 timer to produce a pulse width of 100 m sec. [6]

Code No: RR311001

RR

Set No. 2

6. (a) List and explain the two special cases of inverting amplifiers. [6]
(b) What is a voltage follower? What are its features and applications? [4]
(c) Derive the expression for the output voltage of a non inverting amplifier [6]
7. (a) Compare different A/D converters for their merits and demerits. [8]
(b) Give the schematic circuit diagram of a successive approximation type A/D converter and explain the operations of this system. [8]
8. (a) What is an OP-AMP? Why it is called so? [4]
(b) Explain the parameters that should be considered for ac and dc applications of an OP-AMP [5]
(c) Draw and explain the three open loop OP-AMP configurations with neat circuit diagram [7]

Code No: RR311001

RR

Set No. 4

III B.Tech I Semester Examinations, November 2010

LINEAR AND DIGITAL IC APPLICATIONS

Common to BME, MECT, ETM, E.CONT.E, EIE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Explain in detail the following terms with reference to PLL
 - i. Lock range
 - ii. Capture range
 - iii. Capture transient
 - iv. Pull-in-time. [8]
- (b) i. Draw the internal functional diagram of NE 566 VCO and derive expression for free running frequency.
 ii. From the given component values find the free running frequency Control voltage $V_C = 10.9V$, $V_{CC} = 12V$, $R_1 = 4.7k$ and $C_1 = 1.1nF$. [8]
2. (a) List and explain the two special cases of inverting amplifiers. [6]
 (b) What is a voltage follower? What are its features and applications? [4]
 (c) Derive the expression for the output voltage of a non inverting amplifier [6]
3. (a) What feedback is preferred for oscillators and why? What is the effect of negative feedback? [8]
 (b) Design an OP-AMP based relaxation oscillator and derive the frequency of oscillation. [8]
4. (a) Define the terms [4]
 - i. Positive logic
 - ii. Negative logic
- (b) Show that positive logic EX-OR operation is equivalent to negative logic EX-NOR operation. [4]
 (c) Draw the circuit 3 input D.T.L. NAND gate and explain its operation with the help of truth-table. How can you improve the Fan-out of the circuit. Explain with the help of modified circuit. [8]
5. (a) What is an OP-AMP? Why it is called so? [4]
 (b) Explain the parameters that should be considered for ac and dc applications of an OP-AMP [5]
 (c) Draw and explain the three open loop OP-AMP configurations with neat circuit diagram [7]

Code No: RR311001

RR

Set No. 4

6. (a) Explain the operation of a delay equalizer circuit with neat sketches. Derive an expression relating input and output voltages of the equalizer. [8+2]
- (b) For the all pass filter, determine the phase shift between input and output at $f=2$ kHz. To obtain a positive phase shift. What modifications are necessary in the circuit? [6]
7. (a) Explain the operation of Monostable multivibrator using 555 timer. Derive the expression of time delay of a Monostable multivibrator using 555 timer. [10]
- (b) Design a Monostable multivibrator using 555 timer to produce a pulse width of 100 m sec. [6]
8. (a) Compare different A/D converters for their merits and demerits. [8]
- (b) Give the schematic circuit diagram of a successive approximation type A/D converter and explain the operations of this system. [8]

Code No: RR311001

RR

Set No. 1

III B.Tech I Semester Examinations, November 2010

LINEAR AND DIGITAL IC APPLICATIONS

Common to BME, MECT, ETM, E.CONT.E, EIE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) What feedback is preferred for oscillators and why? What is the effect of negative feedback? [8]
(b) Design an OP-AMP based relaxation oscillator and derive the frequency of oscillation. [8]
2. (a) What is an OP-AMP? Why it is called so? [4]
(b) Explain the parameters that should be considered for ac and dc applications of an OP-AMP [5]
(c) Draw and explain the three open loop OP-AMP configurations with neat circuit diagram [7]
3. (a) Define the terms [4]
 i. Positive logic
 ii. Negative logic
(b) Show that positive logic EX-OR operation is equivalent to negative logic EX-NOR operation. [4]
(c) Draw the circuit 3 input D.T.L. NAND gate and explain its operation with the help of truth-table. How can you improve the Fan-out of the circuit. Explain with the help of modified circuit. [8]
4. (a) Explain the operation of Monostable multivibrator using 555 timer. Derive the expression of time delay of a Monostable multivibrator using 555 timer. [10]
(b) Design a Monostable multivibrator using 555 timer to produce a pulse width of 100 μ sec. [6]
5. (a) Explain the operation of a delay equalizer circuit with neat sketches. Derive an expression relating input and output voltages of the equalizer. [8+2]
(b) For the all pass filter, determine the phase shift between input and output at $f=2$ kHz. To obtain a positive phase shift. What modifications are necessary in the circuit? [6]
6. (a) List and explain the two special cases of inverting amplifiers. [6]
(b) What is a voltage follower? What are its features and applications? [4]
(c) Derive the expression for the output voltage of a non inverting amplifier [6]

Code No: RR311001

RR

Set No. 1

7. (a) Compare different A/D converters for their merits and demerits. [8]
(b) Give the schematic circuit diagram of a successive approximation type A/D converter and explain the operations of this system. [8]
8. (a) Explain in detail the following terms with reference to PLL
i. Lock range
ii. Capture range
iii. Capture transient
iv. Pull-in-time. [8]
- (b) i. Draw the internal functional diagram of NE 566 VCO and derive expression for free running frequency.
ii. From the given component values find the free running frequency Control voltage $V_C = 10.9V$, $V_{CC} = 12V$, $R_1 = 4.7k$ and $C_1 = 1.1nF$. [8]

Code No: RR311001

RR**Set No. 3****III B.Tech I Semester Examinations, November 2010****LINEAR AND DIGITAL IC APPLICATIONS****Common to BME, MECT, ETM, E.CONT.E, EIE****Time: 3 hours****Max Marks: 80****Answer any FIVE Questions****All Questions carry equal marks**

1. (a) What is an OP-AMP? Why it is called so? [4]
 (b) Explain the parameters that should be considered for ac and dc applications of an OP-AMP [5]
 (c) Draw and explain the three open loop OP-AMP configurations with neat circuit diagram [7]
2. (a) List and explain the two special cases of inverting amplifiers. [6]
 (b) What is a voltage follower? What are its features and applications? [4]
 (c) Derive the expression for the output voltage of a non inverting amplifier [6]
3. (a) Compare different A/D converters for their merits and demerits. [8]
 (b) Give the schematic circuit diagram of a successive approximation type A/D converter and explain the operations of this system. [8]
4. (a) Explain the operation of a delay equalizer circuit with neat sketches. Derive an expression relating input and output voltages of the equalizer. [8+2]
 (b) For the all pass filter, determine the phase shift between input and output at $f=2$ kHz. To obtain a positive phase shift. What modifications are necessary in the circuit? [6]
5. (a) Define the terms [4]
 i. Positive logic
 ii. Negative logic
 (b) Show that positive logic EX-OR operation is equivalent to negative logic EX-NOR operation . [4]
 (c) Draw the circuit 3 input D.T.L. NAND gate and explain its operation with the help of truth-table. How can you improve the Fan-out of the corcuit. Explain with the help of modified circuit. [8]
6. (a) What feedback is preferred for oscillators and why? What is the effect of negative feedback? [8]
 (b) Design an OP-AMP based relaxation oscillator and derive the frequency of oscillation. [8]
7. (a) Explain the operation of Monostable multivibrator using 555 timer. Derive the expression of time delay of a Monostable multivibrator using 555 timer. [10]

Code No: RR311001

RR

Set No. 3

- (b) Design a Monostable multivibrator using 555 timer to produce a pulse width of 100 m sec. [6]
8. (a) Explain in detail the following terms with reference to PLL
- i. Lock range
 - ii. Capture range
 - iii. Capture transient
 - iv. Pull-in-time. [8]
- (b) i. Draw the internal functional diagram of NE 566 VCO and derive expression for free running frequency.
- ii. From the given component values find the free running frequency Control voltage $V_C = 10.9V$, $V_{CC} = 12V$, $R_1 = 4.7k$ and $C_1 = 1.1nF$. [8]
