RR

Set No. 2

IV B.Tech I Semester Examinations, November 2010 TV ENGINEERING

Electronics And Communication Engineering

Time: 3 hours Max Marks: 80

Answer any FIVE Questions All Questions carry equal marks

- 1. (a) Explain the principle of operation of burst phase ident amplifier and color killer generation circuit.
 - (b) Explain how R,G & B video signals can be directly obtained from Y and demodulated U & V signals. [8+8]
- 2. (a) Explain why ion traps are used in picture tubes. With neat diagrams, discuss about bent gun and diagonal cut tilted lens ion traps.
 - (b) Explain how the electron beam is focused using electrostatic focusing in a pictures tube. [10+6]
- 3. (a) Draw the circuit of NTSC coder and explain how the chrominance signal is interleaved with the Y signal after quadrature modulation.
 - (b) Write short notes on color sub carrier frequency in NTSC system. [10+6]
- 4. (a) Explain the block diagram of video amplifier in B&W receiver.
 - (b) Describe briefly the factors that influence the choice of PIF = 38.9 MHz and SIF = 33.4 MHz in 625 line (CCIR-B) TV system. [8+8]
- 5. (a) With the help of circuit diagram, explain the principle of operation of forward AGC.
 - (b) Explain the requirements of AGC circuit and what is the purpose of delayed AGC. [8+8]
- 6. (a) With a neat diagram, explain the importance of interlaced scanning.
 - (b) With a suitable diagram, describe the principle of operation of color camera.

 Also explain why dichroic mirrors are used in the camera. [8+8]
- 7. (a) Explain the operation of single ended AFC circuit.
 - (b) Draw the block diagram of sync separator, AFC network and deflection circuits of a television receiver. [10+6]
- 8. (a) Draw camera outputs for V_R , V_G , V_B for primary and complementary colors. Why and how are the outputs normalized.
 - (b) Explain the significance of color difference signals. Write expressions for R-Y, B-Y and G-Y in terms of R,G,B. [8+8]

RR

Set No. 4

IV B.Tech I Semester Examinations, November 2010 TV ENGINEERING

Electronics And Communication Engineering

Time: 3 hours Max Marks: 80

Answer any FIVE Questions All Questions carry equal marks

- 1. (a) Explain the block diagram of video amplifier in B&W receiver.
 - (b) Describe briefly the factors that influence the choice of PIF = 38.9 MHz and SIF = 33.4 MHz in 625 line (CCIR-B) TV system. [8+8]
- 2. (a) Draw camera outputs for V_R , V_G , V_B for primary and complementary colors. Why and how are the outputs normalized.
 - (b) Explain the significance of color difference signals. Write expressions for R-Y, B-Y and G-Y in terms of R,G,B. [8+8]
- 3. (a) With the help of circuit diagram, explain the principle of operation of forward AGC.
 - (b) Explain the requirements of AGC circuit and what is the purpose of delayed AGC. [8+8]
- 4. (a) Explain the operation of single ended AFC circuit.
 - (b) Draw the block diagram of sync separator, AFC network and deflection circuits of a television receiver. [10+6]
- 5. (a) With a neat diagram, explain the importance of interlaced scanning.
 - (b) With a suitable diagram, describe the principle of operation of color camera.

 Also explain why dichroic mirrors are used in the camera. [8+8]
- 6. (a) Draw the circuit of NTSC coder and explain how the chrominance signal is interleaved with the Y signal after quadrature modulation.
 - (b) Write short notes on color sub carrier frequency in NTSC system. [10+6]
- 7. (a) Explain why ion traps are used in picture tubes. With neat diagrams, discuss about bent gun and diagonal cut tilted lens ion traps.
 - (b) Explain how the electron beam is focused using electrostatic focusing in a pictures tube. [10+6]
- 8. (a) Explain the principle of operation of burst phase ident amplifier and color killer generation circuit.
 - (b) Explain how R,G & B video signals can be directly obtained from Y and demodulated U & V signals. [8+8]

RR

Set No. 1

IV B.Tech I Semester Examinations, November 2010 TV ENGINEERING

Electronics And Communication Engineering

Time: 3 hours Max Marks: 80

Answer any FIVE Questions All Questions carry equal marks

- 1. (a) Explain the operation of single ended AFC circuit.
 - (b) Draw the block diagram of sync separator, AFC network and deflection circuits of a television receiver. [10+6]
- 2. (a) Draw camera outputs for V_R , V_G , V_B for primary and complementary colors. Why and how are the outputs normalized.
 - (b) Explain the significance of color difference signals. Write expressions for R-Y, B-Y and G-Y in terms of R,G,B. [8+8]
- 3. (a) Explain the block diagram of video amplifier in B&W receiver.
 - (b) Describe briefly the factors that influence the choice of PIF = 38.9 MHz and SIF = 33.4 MHz in 625 line (CCIR-B) TV system. [8+8]
- 4. (a) Explain the principle of operation of burst phase ident amplifier and color killer generation circuit.
 - (b) Explain how R,G & B video signals can be directly obtained from Y and demodulated U & V signals. [8+8]
- 5. (a) Explain why ion traps are used in picture tubes. With neat diagrams, discuss about bent gun and diagonal cut tilted lens ion traps.
 - (b) Explain how the electron beam is focused using electrostatic focusing in a pictures tube. [10+6]
- 6. (a) With a neat diagram, explain the importance of interlaced scanning.
 - (b) With a suitable diagram, describe the principle of operation of color camera.

 Also explain why dichroic mirrors are used in the camera. [8+8]
- 7. (a) With the help of circuit diagram, explain the principle of operation of forward AGC.
 - (b) Explain the requirements of AGC circuit and what is the purpose of delayed AGC. [8+8]
- 8. (a) Draw the circuit of NTSC coder and explain how the chrominance signal is interleaved with the Y signal after quadrature modulation.
 - (b) Write short notes on color sub carrier frequency in NTSC system. [10+6]

RR

Set No. 3

IV B.Tech I Semester Examinations, November 2010 TV ENGINEERING

Electronics And Communication Engineering

Time: 3 hours Max Marks: 80

Answer any FIVE Questions All Questions carry equal marks

- 1. (a) Explain why ion traps are used in picture tubes. With neat diagrams, discuss about bent gun and diagonal cut tilted lens ion traps.
 - (b) Explain how the electron beam is focused using electrostatic focusing in a pictures tube. [10+6]
- 2. (a) With the help of circuit diagram, explain the principle of operation of forward AGC.
 - (b) Explain the requirements of AGC circuit and what is the purpose of delayed AGC. [8+8]
- 3. (a) Explain the block diagram of video amplifier in B&W receiver.
 - (b) Describe briefly the factors that influence the choice of PIF = 38.9 MHz and SIF = 33.4 MHz in 625 line (CCIR-B) TV system. [8+8]
- 4. (a) Explain the principle of operation of burst phase ident amplifier and color killer generation circuit.
 - (b) Explain how R,G & B video signals can be directly obtained from Y and demodulated U & V signals. [8+8]
- 5. (a) Draw the circuit of NTSC coder and explain how the chrominance signal is interleaved with the Y signal after quadrature modulation.
 - (b) Write short notes on color sub carrier frequency in NTSC system. [10+6]
- 6. (a) With a neat diagram, explain the importance of interlaced scanning.
 - (b) With a suitable diagram, describe the principle of operation of color camera.

 Also explain why dichroic mirrors are used in the camera. [8+8]
- 7. (a) Explain the operation of single ended AFC circuit.
 - (b) Draw the block diagram of sync separator, AFC network and deflection circuits of a television receiver. [10+6]
- 8. (a) Draw camera outputs for V_R , V_G , V_B for primary and complementary colors. Why and how are the outputs normalized.
 - (b) Explain the significance of color difference signals. Write expressions for R-Y, B-Y and G-Y in terms of R,G,B. [8+8]