

Code.No: RR410506

RR

SET-1


IV B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
FAULT TOLERANT SYSTEMS
(COMMON TO CSE, ECC)

Time: 3hours

Max.Marks:80

Answer any FIVE questions
All questions carry equal marks

 1. a) What is meant by Reliability? Derive an expression for Reliability of a system in times of constant fault rate λ .
 b) A system has about 1, 00,000 components each with a failure rate of 0.75% per 1000 hours. What is the period of 0.98 reliability of this system. [8+8]
2. Design a 4 bit Line as feedback shift register to generate a signature to test the given circuit for the stuck at faults indicated below. [16]



3. a) Show that simplex system has better reliability factor than a TMR in the presence of one faulty module.
 b) Design a sift out modular redundant system of 4 channels. [8+8]
4. a) Explain how a Hybrid (3,S) system is better than a static and dynamic systems. Derive an expression for $R(t)$ of hybrid system. Extend the same for (N, S) system.
 b) Write a brief role on software redundancy techniques. [8+8]
5. a) Design a totally self checking checker circuit proposed by Mawf and Friedman for a m out of n code.
 b) Explain the principle of operation of strongly fault secure circuit with an example. [8+8]
6. Design a totally self checking checker circuit using PLA for the given multi input and multi output circuit.

$$f_1(A,B,C,D) = \sum (1,2,4,7,8,11,13)$$

$$f_2(A,B,C,D) = \sum (0,4,5,6,9,10,14)$$

$$f_3(A,B,C,D) = \sum (2,3,7,9,11,14,15)$$

$$f_4(A,B,C,D) = \sum (1,5,7,9,11,13)$$

[16]

7. a) List out the properties of a Design for testable circuit.
b) Obtain the list pattern for the given Boolean expression using control logic where five tests are sufficient to detect all faults in this circuit.
$$f(A,B,C,D) = \overline{A}\overline{B} + \overline{A}\overline{B}\overline{C} + BD.$$
 [8+8]
8. a) What are the advantages of LSSD technique?
b) Draw the logic diagram of Hazard free polarity hold latch and explain its flow table and excitation table.
c) Write a brief note on Build in self test. [5+5+6]

FIRSTRANKER

Code.No: RR410506

RR

SET-2


IV B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
FAULT TOLERANT SYSTEMS
(COMMON TO CSE, ECC)

Time: 3hours**Max.Marks:80**

Answer any FIVE questions
All questions carry equal marks

- - -

 1. a) Show that simplex system has better reliability factor than a TMR in the presence of one faulty module.
 b) Design a sift out modular redundant system of 4 channels. [8+8]
2. a) Explain how a Hybrid (3,S) system is better than a static and dynamic systems. Derive an expression for $R(t)$ of hybrid system. Extend the same for (N, S) system.
 b) Write a brief role on software redundancy techniques. [8+8]
3. a) Design a totally self checking checker circuit proposed by Mawf and Friedman for a m out of n code.
 b) Explain the principle of operation of strongly fault secure circuit with an example. [8+8]
4. Design a totally self checking checker circuit using PLA for the given multi input and multi out put circuit.
 $f_1(A,B,C,D) = \sum (1,2,4,7,8,11,13)$
 $f_2(A,B,C,D) = \sum (0,4,5,6,9,10,14)$
 $f_3(A,B,C,D) = \sum (2,3,7,9,11,14,15)$
 $f_4(A,B,C,D) = \sum (1,5,7,9,11,13)$ [16]
5. a) List out the properties of a Design for testable circuit.
 b) Obtain the list pattern for the given Boolean expression using control logic where five tests are sufficient to detect all faults in this circuit.
 $f(A,B,C,D) = \overline{A}\overline{B} + \overline{A}\overline{B}\overline{C} + BD.$ [8+8]
6. a) What are the advantages of LSSD technique?
 b) Draw the logic diagram of Hazard free polarity hold latch and explain its flow table and excitation table.
 c) Write a brief note on Build in self test. [5+5+6]
7. a) What is meant by Reliability? Derive an expression for Reliability of a system in times of constant fault rate λ .
 b) A system has about 1, 00,000 components each with a failure rate of 0.75% per 1000 hours. What is the period of 0.98 reliability of this system? [8+8]



Code.No: RR410506

RR

SET-3

IV B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
FAULT TOLERANT SYSTEMS
(COMMON TO CSE, ECC)

Time: 3hours**Max.Marks:80**

Answer any FIVE questions
All questions carry equal marks

- - -

1. a) Design a totally self checking checker circuit proposed by Mawf and Friedman for a m out of n code.
 b) Explain the principle of operation of strongly fault secure circuit with an example. [8+8]


2. Design a totally self checking checker circuit using PLA for the given multi input and multi out put circuit.
 $f_1(A,B,C,D) = \sum (1,2,4,7,8,11,13)$
 $f_2(A,B,C,D) = \sum (0,4,5,6,9,10,14)$
 $f_3(A,B,C,D) = \sum (2,3,7,9,11,14,15)$
 $f_4(A,B,C,D) = \sum (1,5,7,9,11,13)$ [16]

3. a) List out the properties of a Design for testable circuit.
 b) Obtain the list pattern for the given Boolean expression using control logic where five tests are sufficient to detect all faults in this circuit.
 $f(A,B,C,D) = \overline{A}\overline{B} + \overline{A}\overline{B}\overline{C} + BD.$ [8+8]

4. a) What are the advantages of LSSD technique?
 b) Draw the logic diagram of Hazard free polarity hold latch and explain its flow table and excitation table.
 c) Write a brief note on Build in self test. [5+5+6]

5. a) What is meant by Reliability? Derive an expression for Reliability of a system in times of constant fault rate λ .
 b) A system has about 1, 00,000 components each with a facture rate of 0.75% per 1000 hours. What is the period of 0.98 reliability of this system? [8+8]

 6. Design a 4 bit Line as feedback shift register to generate a signature to test the given circuit for the stuck at faults indicated below. [16]



7. a) Show that simplex system has better reliability factor than a TMR in the presence of one faulty module.
 b) Design a sift out modular redundant system of 4 channels. [8+8]
8. a) Explain how a Hybrid (3,S) system is better than a static and dynamic systems. Derive an expression for $R(t)$ of hybrid system. Extend the same for (N, S) system.
 b) Write a brief role on software redundancy techniques. [8+8]

Code.No: RR410506

RR

SET-4

IV B.TECH – I SEM EXAMINATIONS, NOVEMBER - 2010
FAULT TOLERANT SYSTEMS
(COMMON TO CSE, ECC)


Time: 3hours

Max.Marks:80

Answer any FIVE questions
All questions carry equal marks

 1. a) List out the properties of a Design for testable circuit.
 b) Obtain the list pattern for the given Boolean expression using control logic where five tests are sufficient to detect all faults in this circuit.

$$f(A,B,C,D) = \overline{A}B + \overline{A}\overline{B}C + BD.$$
 [8+8]
2. a) What are the advantages of LSSD technique?
 b) Draw the logic diagram of Hazard free polarity hold latch and explain its flow table and excitation table.
 c) Write a brief note on Build in self test. [5+5+6]
3. a) What is meant by Reliability? Derive an expression for Reliability of a system in times of constant fault rate λ .
 b) A system has about 1, 00,000 components each with a failure rate of 0.75% per 1000 hours. What is the period of 0.98 reliability of this system? [8+8]
4. Design a 4 bit Line as feedback shift register to generate a signature to test the given circuit for the stuck at faults indicated below. [16]



5. a) Show that simplex system has better reliability factor than a TMR in the presence of one faulty module.
 b) Design a sift out modular redundant system of 4 channels. [8+8]
6. a) Explain how a Hybrid (3,S) system is better than a static and dynamic systems. Derive an expression for $R(t)$ of hybrid system. Extend the same for (N, S) system.
 b) Write a brief role on software redundancy techniques. [8+8]

7. a) Design a totally self checking checker circuit proposed by Mawf and Friedman for a m out of n code.
b) Explain the principle of operation of strongly fault secure circuit with an example. [8+8]
8. Design a totally self checking checker circuit using PLA for the given multi input and multi out put circuit.
 $f_1(A,B,C,D) = \sum (1,2,4,7,8,11,13)$
 $f_2(A,B,C,D) = \sum (0,4,5,6,9,10,14)$
 $f_3(A,B,C,D) = \sum (2,3,7,9,11,14,15)$
 $f_4(A,B,C,D) = \sum (1,5,7,9,11,13)$ [16]

FIRSTRANKER