

R10 Code No: R31042

Set No. 1

III B.Tech I Semester Supplementary Examinations, October/November -2017 **DIGITAL IC APPLICATIONS**

(Common to Electronics and Communication Engineering, Electronics and Instrumentation Engineering, Bio Medical Engineering, Electronics and Computer **Engineering**)

Time: 3 hours Max. Marks: 75

Answer any FIVE Questions

		All Questions carry equal marks *****	
1	a) b)	List out different logic families of CMOS logic and explain each one in detail. Draw the circuit diagram of NAND gate by using CMOS logic and explain its operation along with truth table.	[7M] [8M]
2	a)	Draw and Explain the concept of CMOS/TTL interfacing along with one example.	[8M]
	b)	List out the difference between TTL, DTL ECL and CMOS logic family with one example.	[7M]
3	a)	Design a BCD to Binary Code Converters and explain its operations.	[8M]
	b)	Define multiplexer and implement the 32X1 MUX using 4X1 MUXs relevant digital IC.	[7M]
4	a)	Draw the circuit diagram of Floating-Point Encoder with relevant digital IC and explain its operation.	[8M]
	b)	What is ALU and explain its operation along with circuit diagram in detail?	[7M]
5	a)	Design a Mod-10 Counter using Digital IC and explain its operation along with output wave forms.	[8M]
	b)	What is Race around condition and how to avoid it? Convert JK flip flop to T flip flop with circuit diagram?	[7M]
6	a)	Draw the circuit diagram of Johnson Counter and explain its operation in detail.	[8M]
	b)	Explain the operation of SIPO shift register with the help of timing diagram.	[7M]
7	a)	Design a PAL circuit diagram of a Boolean function $F(a,b,c,d)=\sum 0,1,2,4,6,8,10,12,14,15$	[8M]
	b)	List out the comparisons of PLA and PAL with examples.	[7M]
8	a)	Draw the Internal structure of Dynamic RAM and explain its operation in detail.	[10M]
	b)	Explain the concept of SRAM along with circuit diagram.	[5M]
		de de de de	
