

Code No: **RT42042**

R13

Set No. 1

IV B.Tech II Semester Supplementary Examinations, July/August - 2017 ELECTRONIC MEASUREMENTS AND INSTRUMENTATION

(Electronics and Communication Engineering)

Time: 3 hours Max. Ma			ks: 70	
		Question paper consists of Part-A and Part-B		
		Answer ALL sub questions from Part-A		
		Answer any THREE questions from Part-B		

1		PART-A (22 Marks)	F 4 3	
1.	a)	What are the indications of precision? Explain	[3]	
	b)	What is Digital Fourier analyzer? Explain	[3]	
	c)	Draw the vertical amplifier of CRO and what are its functions	[4]	
	d)	What are the applications and limitations of Wheatstone bridge	[4]	
	e)	How do you select a transducer? Explain	[4]	
	f)	What are the objectives of a DAS	[4]	
		DADE D (2.14 10.15 1.)		
•		$\underline{\mathbf{PART-B}}(3x16 = 48 Marks)$	F07	
2.	a)	Discuss in detail about the range extension of differential voltmeters	[8]	
	b)	A 200 Ω basic movement is to be used as an ohmmeter requiring full scale		
		deflection of 1 mA and internal battery voltage of 5 V. A half scale deflection		
		marking of 2 k is desired. Calculate		
		i. The values of R_1 and R_2	507	
		ii. Maximum value of R to compensate for a 3% drop in battery	[8]	
		voltage		
2			F07	
3.	a)	Draw the block diagram of a spectrum analyzer and explain its working.	[8]	
	b)	Draw and explain the working principle of harmonic distortion analyzer.	[8]	
		William and the state of the st		
4.	a)	What are active probes used with CRO? Draw the circuit of a FET probe and	F07	
	1 \	explain	[8]	
	b)	Draw the circuit diagram of a simple compensated attenuator and explain its	F07	
		working	[8]	
_				
5.	a)	Illustrate the method of measurement of unknown inductance by Maxwell's	F07	
	1 \	bridge 12	[8]	
	b)	A sheet of 4.5 mm thick Bakelite is tested at 50 Hz between 12 cm in diameter.		
		The Schering bridge uses a standard air capacitor C ₂ of 105 pF capacitor, a non-		
		reactive, R_4 of $1000/\Pi$ in parallel with a variable capacitor and is obtained with		
		$C_4 = 0.5 \mu F$ and $R_3 = 260 \Omega$. Calculate the capacitance, PF and relative	F07	
		permittivity of the sheet	[8]	
_	`		FO1	
6.	a)	Draw the construction diagram and explain the working of LVDT	[8]	
	b)	What is a thermistor? Explain. Write about its advantages and disadvantages	[8]	
7.		Write short notes on the following		
1.		Write short notes on the following		
		a) Measurement of force b) Multi channel DAS	[14]	
		b) Multi channel DAS	[16]	