

Code No: R31026 m R10

Set No. 1

Max. Marks: 75

## III B.Tech I Semester Supplementary Examinations, May - 2017 LINEAR & DIGITAL IC APPLICATION

(Electrical and Electronics Engineering)

Time: 3 hours

Answer any FIVE Questions All Questions carry equal marks \*\*\*\*\*

a) Explain about DC analysis of single input balanced output configuration. [8M]

1	u)	Explain about De unarysis of single input buttineed output configuration.	[01/1]
	b)	Explain about Level transistor and also its importance.	[7M]
2	a)	Explain the terms (i) input and output offset voltages and currents ii) slew rate	[8M]
3	b) a)	Draw the block diagram of Op-amp and explain function of each block. Explain the application of Op-amp (i) V to I and I to V converters (ii) Square wave generations.	[7M] [8M]
	b)	Draw the instrumentation amplifier and explain its operation.	[7M]
4	a)	Draw the functional block diagram of 555 timer and explain its operation.	[8M]
	b)	Draw the 565 PLL block diagram and explain its operation.	[7M]
5	a)	Draw the weighted resister DAC and explain its operation.	[8M]
	b)	Design a band pass filter and draw its output responses.	[7M]
6	a)	Draw and explain about the Binary Adder- Subtractor in detail.	[8M]
	b)	Draw the two bit comparator circuit and explain its operation.	[7M]
7	a)	Draw the excitation and conversions of T flip flop to D flip flop and explain its operation.	[8M]
	b)	Draw the Ring counter and explain its operation.	[7M]
8	a)	Draw and explain about static RAM Internal structure	[7M]
	b)	Briefly list out the comparisons of PROM, PLA and PAL.	[8M]

\*\*\*\*