

Code No: RT31026

R13

SET - 1

III B. Tech I Semester Supplementary Examinations, May - 2017

LINEAR & DIGITAL IC APPLICATIONS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70


- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
2. Answering the question in **Part-A** is compulsory
3. Answer any **THREE** Questions from **Part-B**

PART -A

- 1
 - a) Discuss the role of a level translator in op amp. [4M]
 - b) Discuss the features of voltage regulator. [3M]
 - c) Design a adder circuit using an op amp to get output expression $V_0 = -(0.1 V_1 + V_2 + 10V_3)$ [4M]
 - d) Explain the principle of VCO. [4M]
 - e) What are the advantages and disadvantages of active filter over passive? [4M]
 - f) Define the terms: Linearity, settling time with respect to DAC. [3M]

PART -B

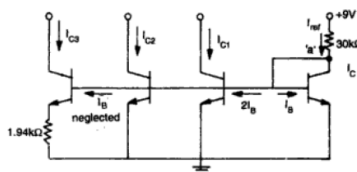- 2
 - a) Explain the cascade differential amplifier stages. [4M]
 - b) For the circuit shown below fig .Find the I_{C1} , I_{C2} and I_{C3} . Assume $\beta=125$. [8M]



- c) Compare the different configurations of differential amplifier. [4M]
- 3
 - a) Discuss the causes and equation for slew rate. [4M]
 - b) Design an offset compensating network for a given op amp to meet the specified requirements. [8M]
 - c) Discuss about the 78xx series regulator. [4M]
- 4
 - a) Draw an AC voltage follower and explain. [4M]
 - b) What is a comparator? Discuss the non inverting comparator and obtain its input and output waveforms. [8M]
 - c) Discuss the application of op amp as a current to voltage converter. [4M]
- 5
 - a) Discuss the 555 timer in monostable operation. Also discuss the applications for it. [10M]
 - b) Explain how the PLL can be used as a FSK demodulator? [6M]

Code No: RT31026

R13

SET - 1

- 6 a) Draw a second order filter and obtain the frequency response and output voltage for it. [8M]
b) Design a WBPF having $f_l=400\text{Hz}$, $f_h=2\text{KHz}$ with a pass band gain of 4. Find Q of the filter. [8M]
- 7 a) Draw the functional diagram of a dual slope integrating type ADC and also obtain expression for the output voltage. [8M]
b) What are the important observations can be made for dual slope integrating type ADC and draw backs of it. [5M]
c) What would be the output voltage produced by a D/A converter whose output range is 0 to 10V with a binary number s 10111100(for a 8 bit DAC) [3M]

2 of 2