

Code No: **R32025**

R10

Set No. 1

III B.Tech II Semester Supplementary Examinations, April - 2017

POWER SEMICONDUCTOR DRIVES

(Electrical and Electronics Engineering)

Time: 3 hours**Max. Marks: 75**

Answer any FIVE Questions

All Questions carry equal marks

- | | | | |
|---|----|--|-------|
| 1 | a) | Discuss the speed control of DC motor above its rated speed. | [7M] |
| | b) | Explain in detail about the various speed control techniques of an induction motor. | [8M] |
| 2 | a) | A 200V , 875 rpm, 150A separately excited DC motor has an armature resistance of 0.06 ohm. It is fed from single phase fully controlled rectifier with an AC voltage of 220V , 50Hz. Assuming continuous conduction, calculate
1) Firing angle for rated motor torque and 750 rpm
2) Motor speed for firing angle of 160 degrees and rated torque. | [8M] |
| | b) | Draw and explain speed torque characteristics of full converter fed separately excited DC motor. | [7M] |
| 3 | a) | Explain the speed torque characteristics of three phase semi controlled converter connected to DC series motor. | [8M] |
| | b) | Derive the speed torque equations for three phase semi controlled converter connected to dc series motor. | [7M] |
| 4 | | What is four quadrant operation? Explain the closed loop operation of dc motor using block diagram. | [15M] |
| 5 | a) | Explain the operation of four quadrant fed separately excited DC motor and dc series motor with necessary waveforms. | [8M] |
| | b) | Explain the working of step up and step down choppers. | [7M] |
| 6 | a) | Explain the control of single phase induction motor using AC voltage controller. | [7M] |
| | b) | Explain the variable frequency control of an induction motor and explain the speed torque characteristics. | [8M] |
| 7 | a) | Explain the speed control and performance characteristics of static Kramer's drive. | [8M] |
| | b) | Describe the static rotor resistance control for speed control of an induction motor. | [7M] |
| 8 | a) | What is self controlled mode of synchronous motor? | [5M] |
| | b) | Explain the modes of variable frequency control of induction motor in detail. | [10M] |
