

Code No: **R41023****R10****Set No. 1****IV B.Tech I Semester Supplementary Examinations, October/November - 2017****SWITCH GEAR & PROTECTION****(Electrical and Electronics Engineering)****Time: 3 hours****Max. Marks: 75****Answer any FIVE Questions
All Questions carry equal marks**

- 1 a) Derive an expression for the restriking voltage, and also derive RRRV expression. [8]
b) Explain the importance of ratings and specifications of circuit breaker. [7]
- 2 a) Explain current chopping in vacuum circuit breaker. Write the disadvantages of vacuum circuit breakers. [8]
b) Discuss about the properties of SF₆ gas and relate the properties to the circuit breaker operation. [7]
- 3 a) With the help of neat sketch explain the principle of operation of percentage Differential relays. [8]
b) Explain the function of an IDMT relay? Discuss in detail about its advantages and disadvantages. [7]
- 4 a) What are the abnormal conditions in a synchronous generator? Explain which protection is necessary for each abnormal condition. [8]
b) A 3 phase, 10 MVA, 6.6 kV generator is delivering a load of 8 MW at 0.8 p.f. Find the value of neutral resistance R, If 10% of the winding is unprotected. The relay setting is 20%. The per phase reactance is 10%. [7]
- 5 a) Discuss the working principle of the alarm based relay to protect a transformer. [10]
b) Explain the differential protection of a Y – Δ transformer and draw its circuit diagram with CT connections. [5]
- 6 a) Explain the bus bar protection using differential principle. [8]
b) Explain over-current protection schemes of the feeder protection. [7]
- 7 a) What are the main components constituting static relays? Explain with neat block diagram. [8]
b) Explain the working of static over current relay with neat schematic diagram. [7]
- 8 a) Write short notes on Protection against arcing grounds. [8]
b) A 33kV, 50 Hz network has a capacitance to neutral of 1.0μF per phase. Calculate the reactance of an arc suppression coil suitable for the system to avoid adverse effect of arcing ground. [7]