

Code No: R1621042

R16

SET - 1

II B. Tech I Semester Regular Examinations, October/November - 2017

SWITCHING THEORY AND LOGIC DESIGN

(Com to ECE, EIE and ECC)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)

2. Answer **ALL** the question in **Part-A**

3. Answer any **FOUR** Questions from **Part-B**

~~~~~

**PART -A**

1. a) Convert the binary number 11011101 to gray code. (2M)
- b) Find the dual of the function:  $A'B(C+D)+B'C'D+AB'C$ . (2M)
- c) What is a de-multiplexer? Write its applications. (3M)
- d) Write the merits and demerits of PROM. (2M)
- e) What are the differences between Johnson and ripple counter. (2M)
- f) What is a state diagram? Describe with an example. (3M)

**PART -B**

2. a) Express the following numbers in decimal: (7M)
  - (i)  $(26.24)_8$
  - (ii)  $(16.5)_{16}$
- b) Generate the Hamming code word for the message 1110010111. (7M)
3. a) Implement the following Boolean function with only two input NOR gates: (7M)
 
$$F=(AB'+CD')E+BC(A+B)$$
- b) Simplify the following Boolean function with the don't conditions  $d$  using K-map method: (7M)
 
$$F(A, B, C, D)=\Sigma(4, 5, 7, 12, 13, 14); d(A, B, C, D)=\Sigma(1, 9, 11, 15)$$
4. a) Design a 4-bit binary comparator with basic gates. (7M)
- b) Implement the following Boolean functions with a decoder. (7M)
  - (i)  $F1=\Sigma(3, 6, 7, 10, 13, 15)$
  - (ii)  $F2=\Sigma(1, 9, 12, 15)$
  - (iii)  $F3=\Sigma(2, 6, 8, 10, 14, 15)$
5. a) Implement the following Boolean functions using PLA. (7M)
  - (i)  $F1= \Sigma(0, 1, 2, 4)$
  - (ii)  $F2= \Sigma(0, 5, 6, 7)$
- b) Design a full adder circuit with a PAL. (7M)
6. a) Draw the circuit of a JK master slave flip-flop with active high clear and active low preset and explain its operation. (7M)
- b) Design a Mod-10 counter using RS flip-flops (7M)

Code No: R1621042

**R16**

**SET - 1**

7. a) What are the capabilities and limitations of finite state machines? Explain. (7M)
- b) Reduce the number of states in the following state table and tabulate the reduced state table. (7M)

| PS | NS, O/P |      |
|----|---------|------|
|    | X=0     | X=1  |
| a  | f, 0    | b, 0 |
| b  | d, 0    | c, 0 |
| c  | f, 0    | e, 0 |
| d  | g, 1    | a, 0 |
| e  | d, 0    | c, 0 |
| f  | f, 1    | b, 1 |
| g  | g, 0    | h, 1 |
| h  | g, 1    | a, 0 |

Code No: R1621042

**R16**
**SET - 2**
**II B. Tech I Semester Regular Examinations, October/November - 2017**
**SWITCHING THEORY AND LOGIC DESIGN**

(Com to ECE, EIE and ECC)

Time: 3 hours

Max. Marks: 70

 Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)

 2. Answer **ALL** the question in **Part-A**

 3. Answer any **FOUR** Questions from **Part-B**
**PART -A**

1. a) Find the 10's complement of 2476. (2M)
- b) Define the essential prime implicants in a K-map method. (3M)
- c) What is a multiplexer? Write its applications. (2M)
- d) Compare PROM, PLA and PAL. (3M)
- e) Write the differences between the synchronous and asynchronous sequential circuits. (2M)
- f) Write the features of Moore machine. (2M)

**PART -B**

2. a) Convert the following number to Hexadecimal: (7M)
  - (i)  $(735.5)_8$
  - (ii)  $(1011011)_2$
- b) Perform the following subtraction in binary using 1's and 2's complement method:  $(677)_{10} - (899)_{10}$  (7M)
3. a) Find the complement and dual of the given function: (7M)
 
$$xy + x(wz + wz')$$
- b) Simplify the following Boolean function using tabular method: (7M)
 
$$F(A, B, C, D) = \Sigma(2, 4, 6, 10, 12); d(A, B, C, D) = \Sigma(0, 8, 9, 13)$$
4. a) Realize 4:16 decoder using 2:4 decoders. (7M)
- b) Implement the following Boolean function with 4X1 multiplexer and external gates. Connect inputs B and C to the selection lines. (7M)
 
$$F(A, B, C, D) = \Sigma(1, 2, 4, 7, 8, 9, 10, 11, 13, 15)$$
5. a) Draw the internal structure of 8X1 PROM and explain its operation. (7M)
- b) Give the realization of the following Boolean functions using PLA with 5 inputs, 4 outputs and 8 and gates. (7M)
 
$$F1 = \Sigma(0, 1, 2, 3, 11, 11, 13, 14, 15, 16, 17, 18, 19, 27, 28, 29, 30, 31)$$

$$F2 = \Sigma(4, 5, 6, 7, 8, 9, 10, 11, 20, 21, 22, 23, 30)$$
6. a) Convert the JK flip into T flip-flop. (5M)
- b) Design a Mod-12 counter using D flip-flops. (9M)

1 of 2

[WWW.MANARESULTS.CO.IN](http://WWW.MANARESULTS.CO.IN)


Code No: R1621042

**R16**

SET - 2

7. a) Design a synchronous sequential circuit which goes through the following states: 1, 3, 5, 3, 6, 1, 3, 5. (7M)
- b) Convert the following Mealy machine into a corresponding Moore machine. (7M)

| PS | NS, Z |      |
|----|-------|------|
|    | X=0   | X=1  |
| A  | C, 0  | B, 0 |
| B  | A, 1  | D, 0 |
| C  | B, 1  | A, 1 |
| D  | D, 1  | C, 0 |

Code No: R1621042

**R16**

**SET - 3**

**II B. Tech I Semester Regular Examinations, October/November - 2017**

**SWITCHING THEORY AND LOGIC DESIGN**

(Com to ECE, EIE and ECC)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)

2. Answer **ALL** the question in **Part-A**

3. Answer any **FOUR** Questions from **Part-B**

~~~~~

PART -A

1. a) What are the universal gates? Why they are called as universal gates? (3M)
- b) Find the complement of the function: $A'B(C+D)+B'C'D+AB'C$. (3M)
- c) Write the truth table of a full subtractor. (2M)
- d) Write the merits and demerits of PLA. (2M)
- e) Write the differences between the Combinational and sequential circuits. (2M)
- f) What is a state table? Describe with an example. (2M)

PART -B

2. a) Convert the following numbers to Binary: (7M)
 - (i) $(27.315)_{10}$
 - (ii) $(68BE)_{16}$
- b) Reduce the following Boolean function to four literals and draw the logic diagram: $(A'+C)(A'+C')(A+B+C'D)$ (7M)
3. a) Implement the following Boolean function with only two input NAND gates: (7M)

$$F=(AB'+D')E+C(A'+B')$$
- b) Simplify the following Boolean function with the don't conditions d using K-map method: (7M)

$$F(A, B, C, D)=\Sigma(1,3,8,10,15); d(A, B, C, D)=\Sigma(0, 2, 9)$$
4. a) Design an excess-3 adder circuit and explain its operation. (7M)
- b) Implement the following Boolean function with 8X1 multiplexer and external gates: (7M)

$$F(A, B, C, D)=\Sigma(1, 3, 4, 11, 12, 13, 14, 15)$$
5. a) Design a 3-bit binary to Excess-3 code converter using a PROM. (7M)
- b) Implement the following Boolean functions using PLA. (7M)
 - (i) $F1=\Sigma(0, 1, 2, 4)$
 - (ii) $F2=\Sigma(0, 5, 6, 7)$
6. a) What is the drawback of JK flip-flop? How is it eliminated in Master Slave flip-flop? Explain. (7M)
- b) Design a decade counter using T flip-flops. (7M)

WWW.MANARESULTS.CO.IN

of 2



Code No: R1621042

R16

SET - 3

7. a) Obtain the state table and state diagram for a sequence detector to recognize the occurrence of sequence bits 110 & 001. (7M)
- b) Find the equivalence partition and reduced table for the given state machine. (7M)

PS	NS, O/P	
	X= 0	X=1
A	B, 0	E, 0
B	E, 0	D, 0
C	D, 1	A, 0
D	B, 1	E, 0
E	C, 0	D, 0

Code No: R1621042

R16

SET - 4

II B. Tech I Semester Regular Examinations, October/November - 2017

SWITCHING THEORY AND LOGIC DESIGN

(Com to ECE, EIE and ECC)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)

2. Answer **ALL** the question in **Part-A**

3. Answer any **FOUR** Questions from **Part-B**

PART -A

1. a) Find the 2's complement of the decimal number 97. (2M)
- b) What are the prime implicants in a K-map method? (2M)
- c) What is a decoder? Write its applications. (2M)
- d) Write the merits and demerits of PAL. (2M)
- e) What are registers? Write their applications. (3M)
- f) Write the features of Mealy machine. (3M)

PART -B

2. a) Convert the following numbers to Octal: (7M)
 - (i) $(1010.1010)_2$
 - (ii) $(FAFA)_{16}$
- b) Reduce the following Boolean function to three literals and draw the logic diagram: $(x'y'+z)' + z + xy + wz$ (7M)
3. a) Find the dual and complement of the following function: (7M)

$$A'BD' + B'(C' + D') + A'C'$$
- b) Simplify the following Boolean function using tabular method: (7M)

$$F(A, B, C, D) = \Sigma(0, 6, 8, 13, 14); d(A, B, C, D) = \Sigma(2, 4, 10)$$
4. a) Design a BCD adder circuit and explain its operation. (7M)
- b) Implement the following Boolean function with 4X1 multiplexer and external gates: (7M)

$$F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$$
5. a) Realize the following Boolean functions using a PROM (7M)
 - (i) $F1 = \Sigma(0, 4, 7)$
 - (ii) $F2 = \Sigma(1, 3, 6)$
 - (iii) $F3 = \Sigma(1, 3, 4, 6)$
- b) Design a BCD to Excess-3 code converter using a PAL. (7M)
6. a) Convert JK flip-flop into D flip-flop. (7M)
- b) Design a modulo-10 ripple counter using RS flip-flops. (7M)

Code No: R1621042

R16

SET - 4

7. a) Design a sequence detector that detects the overlapping sequence of 011010 (5M)
using T flip-flops.
- b) Draw the diagram of Mealy type state machine for serial adder and explain its (9M)
operation.

www.FirstRanker.com