

Code No: RT41041

**R13****Set No. 1**

IV B.Tech I Semester Supplementary Examinations, March - 2017

**VLSI DESIGN**

(Common to Electronics &amp; Communication Engineering, and Electronics &amp; Instrumentation Engineering)

Time: 3 hours

Max. Marks: 70

*Question paper consists of Part-A and Part-B**Answer ALL sub questions from Part-A**Answer any THREE questions from Part-B*

\*\*\*\*\*

**PART-A (22 Marks)**

1. a) Write down the equations for  $I_{ds}$  of an n-channel enhancement MOSFET operating in Non-saturated region and saturated region? [4]
- b) Define stick diagram and layout diagram? [4]
- c) Explain about the constraints in choice of layers. [4]
- d) Draw the basic structure of a dynamic CMOS gate? [4]
- e) List out the back-end steps in ASIC design flow? [3]
- f) List out the front-end steps in FPGA design flow? [3]

**PART-B (3x16 = 48 Marks)**

2. a) Explain the nMOS enhancement mode fabrication process for different conditions of  $V_{ds}$ ? [8]
- b) Derive an equation for transconductance of an n-channel enhancement MOSFET operating in active region. [8]
3. a) Design a stick diagram and layout for two input CMOS NAND gate indicating all the regions and layers. [8]
- b) Explain 2 $\mu$ m Double Metal, Double Poly. CMOS / BiCMOS Rules. [8]
4. a) What are the issues involved in driving large capacitor loads in VLSI circuit regions? Explain. [8]
- b) Calculate the gate capacitance value of 5mm technology minimum size transistor with gate to channel value is  $4 \times 10^{-4}$  pF/mm<sup>2</sup>. [8]
5. a) How switch logic can be implemented using Pass Transistors? Explain. [8]
- b) Draw the transistor circuit diagram of shift register capable of holding and shifting 4-bit word. Explain the circuit operation. [8]
6. a) What are FPGAs? Explain the principle and operation. [8]
- b) Explain how the pass transistors are used to connect wire segments for the purpose of FPGA programming. [8]
7. a) Clearly explain each step of high level design flow of an ASIC. [8]
- b) Write a short note on mixed signal design? [8]