

Code No: RT31041

R13**SET - 1****III B. Tech I Semester Supplementary Examinations, May - 2016****PULSE AND DIGITAL CIRCUITS**

(Common to ECE and EIE)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)2. Answering the question in **Part-A** is compulsory3. Answer any **THREE** Questions from **Part-B**

PART -A

- 1
 - a) Describe about ringing circuit. [3M]
 - b) State clamping circuit theorem. [4M]
 - c) Explain piecewise linear characteristics of a diode. [4M]
 - d) What are the types of triggering? Distinguish between them. [4M]
 - e) What are the applications of Time-base generator? [3M]
 - f) What do you mean by sampling gate? Give the applications of sampling gate? [4M]

PART -B

- 2
 - a) Discuss about attenuators. [4M]
 - b) Analyze the low pass circuit for the exponential inputs, with help of waveforms. [8M]
 - c) Discuss the application of an attenuator in a CRO. [4M]
- 3
 - a) Draw the basic circuit diagram of positive peak clamper circuit and explain its operation. [8M]
 - b) Explain transfer characteristics of emitter coupled clipper and derive necessary equations. [8M]
- 4
 - a) Draw the circuits of 3-input OR-gate using diodes for: [8M]
(i) Positive logic, (ii) Negative logic and explain the operation of circuit.
 - b) Give the comparison of different logic families. [8M]
- 5
 - a) What are different types of multivibrators? Explain the stable state of a multivibrator. [8M]
 - b) Sketch the circuit diagram of Schmitt trigger and explain its operation. [8M]
- 6
 - a) With the help of neat circuit diagram and waveforms explain transistor miller time base generator. [8M]
 - b) Discuss about the recovery time of a sweep circuit. How do you achieve short recovery time? [8M]
- 7
 - a) Explain the process of synchronization of a sweep circuit. [8M]
 - b) Write notes on: [8M]
i) Astable relaxation circuits ii) Monostable relaxation circuits
