

**Total No. of Pages : 02**

**B.Tech.(CSE/IT) (2011 Onwards) (Sem.-3)**

**Subject Code : BTCS-303**

**Max. Marks : 60**

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

**1. Write briefly :**

- Solve  $(10101)_2 + (10011)_2$ .
- What is 1's complement? Explain with example.
- Explain De-Morgan's theorem.
- Which device can be used to change from serial data to parallel data?
- What do you understand by volatile memory?
- What is the difference between PROM and EPROM?
- Write the name of various types of Analog to Digital Converters.
- What is the use of Dynamic RAM?
- What can be done to avoid racing problem in JK-Flip flop?
- Write one advantage of ECL logic family.

**SECTION-B**

2. Explain the principle of Duality.
3. Draw and explain the operation of TTL 2- input AND Gate.
4. Explain the working of 'T' and 'D' Flip-flops.
5. Explain the working of weighted type Digital to Analog Converter.
6. Explain the working of 6-Transistor static RAM cell.

**SECTION-C**

7. Find the minimum sum of products expression for the function  
 $f(a, b, c, d) = \Sigma m(1, 3, 4, 6, 7, 9, 11, 12, 13, 15)$  using K-Map method.
8. Design a 32 to 1 Multiplexer using 4 to 1 Multiplexer and explain its working.
9. a) Design a 4 bit synchronous ring counter. Explain its working with the help of timing diagram.  
b) Explain the working of 4 bit successive approximation type ADC.