

Roll No.

Total No. of Pages : 2

Total No. of Questions : 09

B.Tech. (EE/EEE) (Sem.-3)

ELECTRONIC DEVICES AND CIRCUITS

Subject Code : EE-207

Paper ID : [A0405]

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTION TO CANDIDATES :

- SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
- SECTION-B contains FIVE questions carrying FIVE marks each and students has to attempt any FOUR questions.
- SECTION-C contains THREE questions carrying TEN marks each and students has to attempt any TWO questions.

SECTION-A**1. Write briefly :**

- Give the band structure of conductor.
- Why p-type impurities are called as acceptor impurities?
- What is mass action law?
- Discuss the effect of temperature on conductivity of semiconductors.
- Why is the collector region wider than the emitter region in a transistor?
- A silicon diode has a saturation current of $7.5\mu\text{A}$ at room temperature. Calculate the saturation current at 400K.
- Discuss the application of thermistor.
- Calculate the voltage gain of negative feedback amplifier with an internal gain of 125 and feedback factor is 0.1.
- Why is positive feedback necessary to produce oscillations?
- Why is negative feedback used in OP-AMP?

SECTION-B

- Discuss the conduction of current in metals. Define temperature coefficient of resistance.
- Discuss the effect of temperature on conductivity of semiconductors. Explain why semiconductors behave as insulator at low temperature.
- Define ripple factor and derive its value for full wave rectifier.
- Explain how the negative feedback in an amplifier reduces distortion and noise?
- Give the characteristics of ideal operational amplifier. Draw the transfer characteristics of OP-AMP in open loop.

SECTION-C

- Explain the continuity equation.
- (a) Discuss the working of an NPN transistor in common emitter configuration.
(b) Plot the drain characteristics of n-channel MOSFET. What is the difference between ohmic and triode region?
- (a) What are the factors which determine the stability of a feedback amplifier?
(b) Using accurate analysis explain how is operational amplifier configured as a voltage divider biasing circuit.

