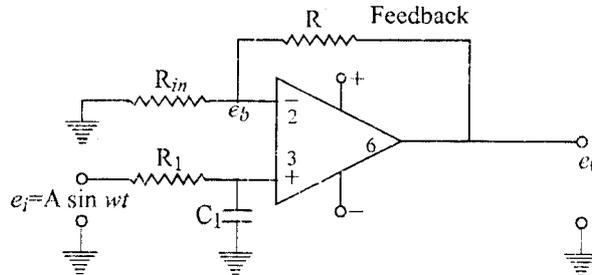



- 3) a) What is the main advantage of constant current bias over emitter bias?
- b) Explain the differences between constant current bias and current mirror.
- c) Why level translator is used with cascaded differential amplifier?
- 4) Obtain the expression for the output voltage e_o for the circuit shown :



- 5) Draw the high frequency equivalent circuit of an op amp. Explain in detail the major sources responsible for capacitive effect. Also evaluate the expression for output voltage gain as a function of frequency.
- 6) What is a VCO? Explain its operation in detail using its block diagram. Also draw the connection diagram using IC 566 and its output waveforms.

SECTION-C

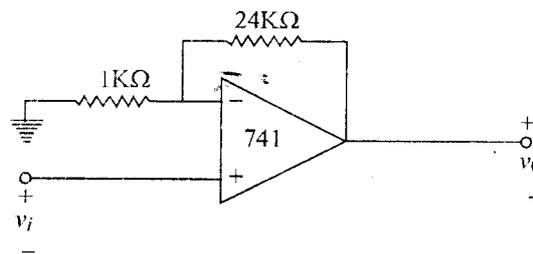- 7) Draw the schematic diagram and analyze the operation of a Wein bridge oscillator and design the circuit for producing a specified output frequency. Also discuss how additional negative feedback can be applied to a Wein bridge oscillator to stabilize the loop.
- 8) Consider the Non inverting amplifier circuit shown using 741 op amp. The circuit is to be used to amplify some complex analog signals. Investigate the frequency limits of operation when the input signal has a peak value of (a) 20mV and (b) 500mV. Assume that $B = 1\text{MHz}$ and $S = 0.5\text{V}/\mu\text{s}$.



- 9) Draw the standard block diagram representation of a feedback amplifier and show how the inverting amplifier fits the model. Calculate the actual values of the low frequency closed loop gain, the input resistance, and the output resistance for a inverting op amp circuit.