

Roll No.

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech. (EE/EEE) (Sem.-3)

MAGNETIC CIRCUITS & TRANSFORMERS

Subject Code : EE 203

Paper ID : [A0403]

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTION TO CANDIDATES :

- SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
- SECTION-B contains FIVE questions carrying FIVE marks each and students has to attempt any FOUR questions.
- SECTION-C contains THREE questions carrying TEN marks each and students has to attempt any TWO questions.

SECTION-A**I. Write briefly :**

- Define mutual induction.
- How eddy current losses can be reduced?
- State Faraday's law of electromagnetic induction.
- Define MMF & reluctance. Give their units.
- What is meant by leakage reactance of transformer?
- Define voltage regulation of transformer.
- Why open circuit test is performed on low voltage side of transformer?
- What are the advantages of autotransformer?
- What are the disadvantages of open delta connection in 3-phase transformer?
- Draw the connection diagram for Y-delta connection.

CT Inst. o

SECTION-B

- Find the relation for energy stored in magnetic field.
- What is hysteresis? How hysteresis losses can be reduced?
- Explain the principle & operation of autotransformer.
- Define efficiency & all day efficiency of transformer. Calculate for max. efficiency of transformer.
- What is the effect of saturation on exciting current of transformer?

SECTION-C

- The maximum efficiency of a 500kVA, 3300/1100V transformer is 97% and occurs at 3/4th full load. Calculate the regulation of full loaded, 0.8 pf.
- Explain the working principle of transformer and draw the equivalent circuit for induction loading of 1-phase transformer.
- Draw and explain open delta connection. Compare the advantages of open delta-delta connection.

