



### SECTION-B

2. Discuss the working of Zener as voltage regulator. Derive the expression for source and load effect.
3. Discuss the phase shift network attenuation and amplifier gain requirement in a Wein Bridge oscillator. Write its frequency equation.
4. In a Class C amplifier with 1MHz signal frequency, determine the suitable tank circuit component values. Calculate the max AC power delivered to the load if  $V_{CEmax} = 0.5V$ ,  $V_{cc} = 30V$ ,  $R_L = 1.2k\Omega$ .
5. Using well labeled I-V characteristics briefly explain the UJT operation.
6. Sketch the T-equivalent circuit of CB configuration. Identify and discuss the origin of each component.

### SECTION-C

7. What is a small signal amplifier? Explain why the voltage divider with emitter resistor is considered to be the best biasing arrangement for stabilization of Q-point? What is the effect of not connecting an emitter by pass capacitor?
8. a) Derive the Input and Output impedance, Current and Voltage gain of CE amplifier using h-parameter equivalent circuit.  
b) Calculate these circuit parameters for the circuit shown in figure1. Transistor h-parameters are:  $h_{fe} = 75$ ,  $h_{ie} = 2.1k\Omega$ ,  $h_{oe} = 1\mu S$ .

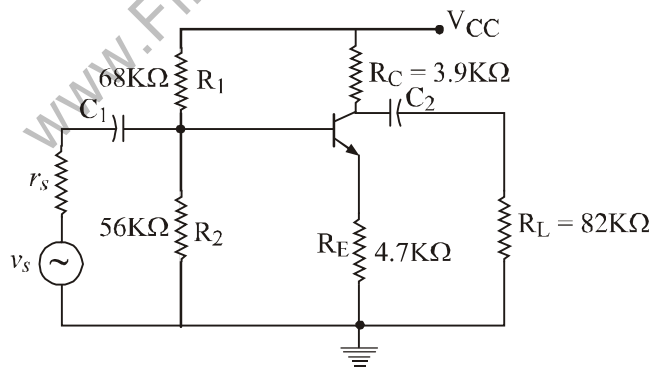


Figure.1

9. Discuss the working and applications of Class B push-pull amplifier. Derive the expression for max power delivered to the load. How the cross-over distortion can be eliminated?