

Roll No.

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech.(ECE/EE/EEE/EIE) (Sem.-3rd)

NETWORK ANALYSIS AND SYNTHESIS

Subject Code : EE-201

Paper ID : [A0305]

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTION TO CANDIDATES :

- SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
- SECTION-B contains FIVE questions carrying FIVE marks each and students has to attempt any FOUR questions.
- SECTION-C contains THREE questions carrying TEN marks each and students has to attempt any TWO questions.

SECTION-A**1. Answer briefly :**

- State and prove superposition property of Laplace transform.
- How does the concept of poles and zeros arise in describing a network function?
- Differentiate between a natural response and a forced response.
- Using the basic definition of Laplace transform, obtain the Laplace transform of cosine function.
- Establish the conditions for equivalence of Thevenin's theorem and Norton's theorem.
- What is m derived filter?
- What is ladder network?
- What is attenuation?
- Compare band pass and band stop filters.
- State the properties of a Hurwitz Polynomial.

SECTION-B

- Carry out the complete analysis of series R-L circuit with a rectangular pulse of width a and magnitude E . Draw neat diagram and graphs. Also, derive all the relevant expressions.
- What are circuit elements? Discuss in detail, the characteristics of each element giving example of each type.
- Design the T and Π sections of m derived filter with $R_0 = 600$ ohms, a cut-off frequency of 3kHz and a ripple attenuation $f_\infty = 2700$ Hz.
- An electric network consists of a parallel combination of a capacitor with a series connected resistance R and inductor L . The poles and zeros of the driving point impedance of the network are Zero at $z = -2$, poles at $s = -1 + j4$ and $-1 - j4$. If $Z(0) = 1$, find the values of R , L and C .
- Show that the image impedances of the series and shunt half sections of a filter are respectively equal to the iterative impedances of the corresponding full section.

SECTION-C

- Find the first and second Foster forms and the partial fraction forms of the function $Z(s) = \frac{s(s^2 + 4)}{(s^2 + 1)(s^2 + 9)}$.
- State and Prove Thevenin's theorem as applied to a network. Discuss the various methods to calculate the Thevenin's voltage and the applicability of each method.
- Show that the image impedances of the series and shunt derived half sections of a filter are respectively equal to the mid shunt and mid series iterative impedances of the corresponding full section.
 - State and prove 'Initial value Theorem' as applied to a network function.

