

GUJARAT TECHNOLOGICAL UNIVERSITY

BE (SPFU)- SEMESTER- 1st/ 2nd • EXAMINATION – 2018

Subject Code: ENG005

Date: 28-05-2018

Subject Name: Linear Electrical Networks

Time: 02.30 PM to 05.00 PM

Total Marks: 70

Instructions:

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain Star delta transformation with example. **07**
(b) Explain Norton's theorem. **07**
or
(b) Explain Thevenin's theorem.
- Q.2** (a) Explain Kirchhoff's current and voltage law. **07**
(b) Explain series and parallel connection. Also compare them. **07**
- Q.3** (a) What is resistor? How to calculate the resistor value by color code? **07**
(b) Explain loop, node, path, network and circuit **07**
or
Explain series RLC circuit in detail.
- Q.4** (a) What is mesh analysis? Explain in detail with suitable example **07**
(b) Explain the time domain behavior of two port passive network. **07**
- Q.5 Write a short note (any two) 14**
(a) Hybrid parameter
(b) Superposition theorem
(c) Maximum power transfer theorem
-