

A logic family is a collection of different IC chips that have similar input, output and internal circuit characteristics, but that perform different logic functions.

Chips from the same family can be interconnected to perform any desired logic function. On the other hand, chips from differing families may not be compatible; they may use different power supply voltages or may use different input & output conditions to represent logic values.

The most successful bipolar logic family is transistor-transistor logic (TTL). First introduced in the 1960s, TTL now is actually a family of logic families that are compatible with each other but differ in speed, power consumption, and cost.

Metal-Oxide Semiconductor ~~field~~ field-effect transistor (MOSFET), or simply MOS transistor, were difficult to fabricate in the early days, and it wasn't until the 1960s that a wave of developments made MOS based logic & memory circuits practical. Even then, MOS circuits lagged bipolar circuits considerably in speed and were attractive ~~and~~ only in selected applications because of their lower power consumption and higher levels of integration.



design of MOS circuits, in particular Complementary MOS (CMOS) circuits, vastly increased their performance & popularity. By far the majority of new large-scale integrated circuits, such as microprocessors & memories, use CMOS. CMOS circuits now account for the vast majority of the world wide IC market.

CMOS logic is both the most capable & the easiest to understand Commercial digital logic technology.

As a consequence of the industry's transition from TTL to CMOS over long periods of time, many CMOS families were designed to be somewhat compatible with TTL.

### CMOS LOGIC

The basic building blocks in CMOS logic circuits are MOS transistors. In any logic circuit, there is a range of voltages that is interpreted as a logic 0, and another, nonoverlapping range that is interpreted as a logic 1.

A typical CMOS logic circuit operates from a 5-volt power supply. Such a circuit may interpret any voltage in the range 0-1.5V as a logic 0, and in the range 3.5 - 5.0V as a logic 1. Thus, the definitions of Low & High for 5-volt CMOS logic are as shown in figure 1.

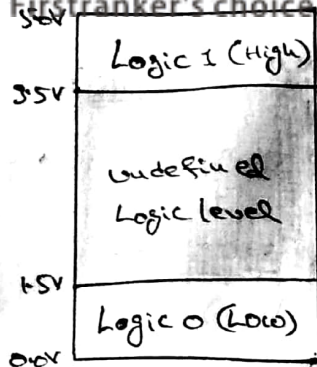


Fig 1: Logic levels for typical CMOS logic circuits

Voltages in the intermediate range (1.5 - 3.5V) are not expected to occur except during signal transitions, and yield undefined logic values (i.e., a circuit may interpret them as either 0 or 1).

### MOS Transistors:

A MOS transistor can be modeled as a 3-terminal device that acts like a voltage controlled resistance. As suggested by figure 2, an i/p voltage applied to one terminal controls the resistance between the remaining two terminals. In digital logic applications, a MOS transistor is operated so its resistance is always either very high (and the transistor is OFF) or very low (and the transistor is ON).

There are two types of MOS transistors, n-channel or p-channel; the names refer to the type of semiconductor material used for the resistance-controlled terminals.


 


Fig 2: The MOS transistor as a voltage controlled resistance.

 The circuit symbol for an n-channel MOS (NMOS) transistor is shown in figure 3.



Voltage-controlled resistance  
increase  $V_{GS} \Rightarrow$  decrease  $R_{DS}$   
i.e.  $V_{GS} \propto \frac{1}{R_{DS}}$   
Note: normally  $V_{GS} \geq 0$

Fig 3: Circuit symbol for an n-channel MOS (NMOS) transistor



The terminals are called gate, source, & drain. As you might guess from the orientation of the circuit symbol, the drain is normally at a higher voltage than the source.

The voltage from gate to source ( $V_{GS}$ ) in an NMOS transistor is normally zero or positive. If  $V_{GS} = 0$ , then the resistance from drain to source ( $R_{DS}$ ) is very high, at least a Megohm ( $10^6 \Omega$ ) or more. As we increase  $V_{GS}$  (i.e., increase the voltage on the gate),  $R_{DS}$  decreases to a very low value, 10 $\Omega$  or less in some devices.

The circuit symbol for a p-channel MOS (PMOS) transistor is shown in figure 4.9.

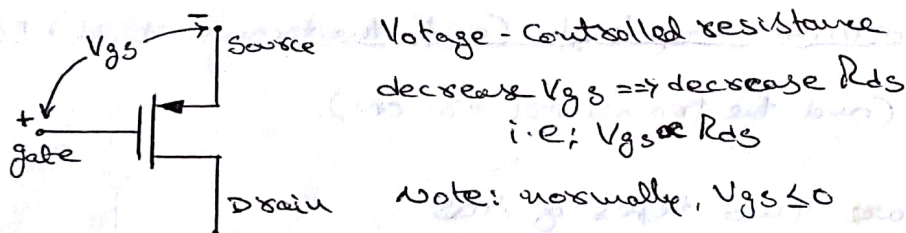



Fig 4.9 Circuit symbol for a p-channel MOS (PMOS) transistor

Operation is analogous to that of an NMOS transistor, except that the source is normally at a higher voltage than the drain, and  $V_{GS}$  is normally zero or negative. If  $V_{GS}$  is zero, then the resistance from source to drain ( $R_{DS}$ ) is very high. As we algebraically decrease  $V_{GS}$  (i.e., decrease the voltage on the gate),  $R_{DS}$  decreases to a very low value.



CMOS and PMOS transistors are used together in a complementary way to form CMOS logic.

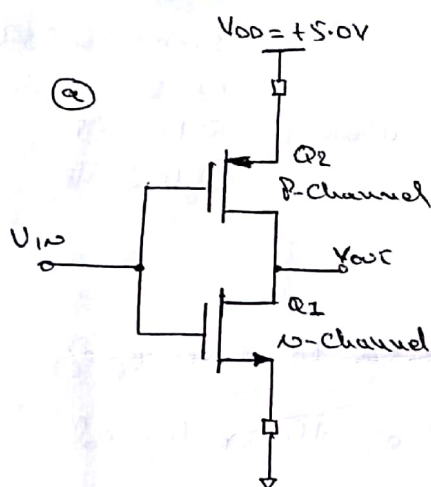The simplest CMOS circuit, a logic inverter, requires only one of each type of transistor, connected as shown in figure 5(a). The power-supply voltage,  $V_{DD}$ , typically may be in the range 2-6V and is most often set at 5.0V for compatibility with TTL circuits.



(b)

$V_{IN}$	$Q_1$	$Q_2$	$V_{OUT}$
0.0(L)	OFF	ON	5.0(H)
5.0(H)	ON	OFF	0.0(L)

(c)

 


Fig: 5 CMOS inverter (a) circuit diagram

(b) functional behaviour

(c) Logic Symbol

case-I

$V_{IN}$  is 0.0V.

In this case, the bottom, n-channel transistor  $Q_1$  is OFF, since its  $V_{GS}$  is 0, but the top, p-channel transistor  $Q_2$  is ON, since its  $V_{GS}$  is a large -ve (-5.0V). Therefore,  $Q_2$  presents only a small resistance between the power-supply terminal ( $V_{DD}$ , +5.0V) and the o/p terminal ( $V_{OUT}$ ), and the o/p voltage is 5.0V.

Case - II

$V_{IN}$  is 5.0V.

Here,  $Q_1$  is ON, since its  $V_{GS}$  is a large +ve value (+5.0V) but  $Q_2$  is OFF, since its  $V_{GS}$  is 0. Thus,  $Q_1$  presents a small resistance between the o/p terminal and ground. The output voltage is 0V.

Another way to visualize CMOS operation uses Switches. As shown in figure 5, the n-channel (bottom) transistor is modeled by a normally open switch, and the p-channel (top) transistor by a normally-closed switch. Applying a HIGH voltage changes each switch to the opposite of its normal state, as shown in (b).


 
 


Fig 5  
Switch model for  
CMOS inverter  
(a) Low  $V_{in}$   
(b) High  $V_{in}$

The switch model gives rise to a way of drawing CMOS circuits that makes their logical behaviour more readily apparent. As shown in Fig 7, different symbols are used for the p- & n-channel transistors to reflect their logical behaviour. The n-channel transistor (Q1) is switched 'on', & current flows between source & drain, when a HIGH voltage is applied to its gate; this seems natural enough.

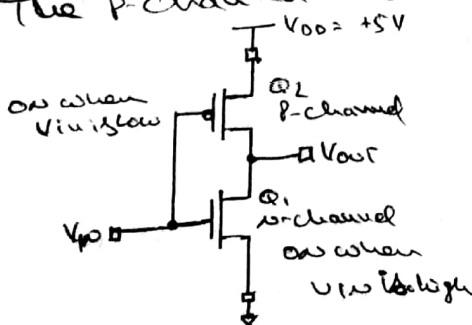The p-channel transistor (Q2) has the opposite behaviour.



It is 'on' when a Low voltage is applied; the inversion bubble on its gate indicates this inverting behaviour.

Fig 7: CMOS inverter logical operation



NAND gate can be constructed using CMOS.

A  $k$ -input gate uses  $k$  p-channel or  $k$  n-channel transistors. Figure 8.3 shows a 2-input CMOS NAND gate.


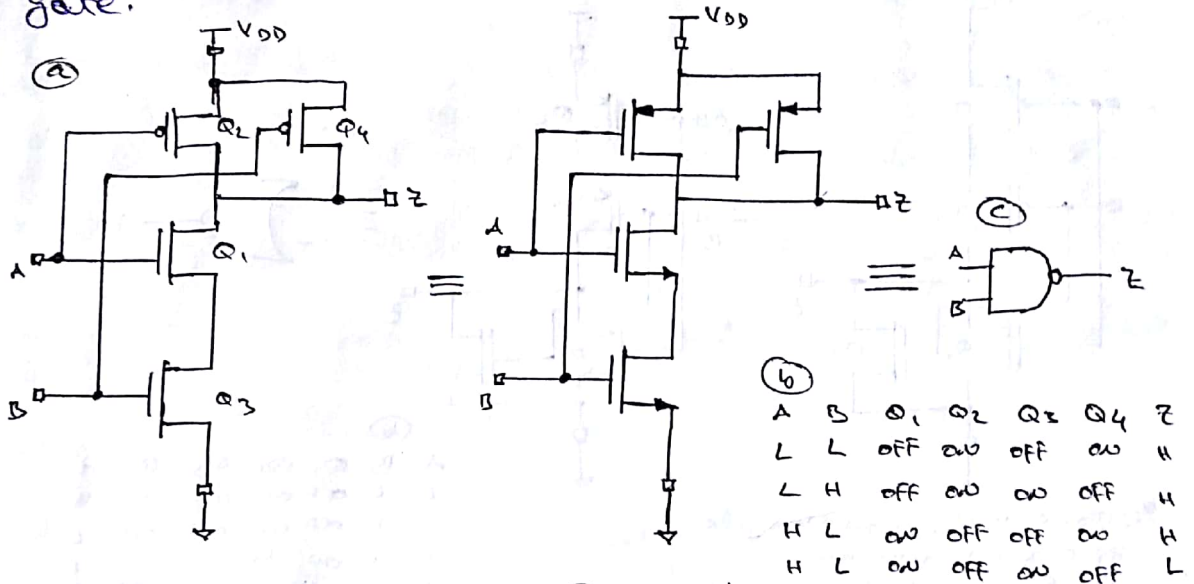


Fig 8.3: CMOS 2-input NAND gate (a) circuit (b) function table (c) logic symbol

 If either input is LOW, the output  $Z$  has a low-impedance connection to  $V_{DD}$  through the corresponding p-channel transistor, and the path to ground is blocked by the corresponding "OFF" n-channel transistor. If both inputs are HIGH, the path to  $V_{DD}$  is blocked, and  $Z$  has a low-impedance connection to ground. Fig 9.14 shows the switch model for the NAND gate's operation.



NOR gate can be constructed using CMOS.

A K-input gate uses K n-channel & K p-channel transistors. Figure ~~8.15~~ shows a CMOS NOR gate.

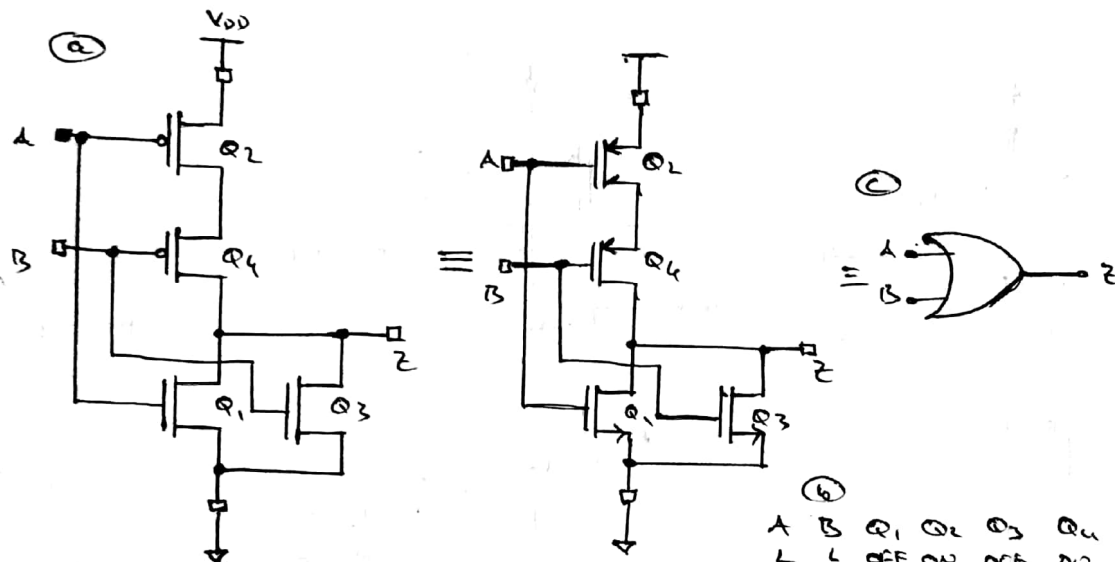


Fig 8.15: CMOS 2-input NOR gate


- (a) circuit diagram
- (b) function table
- (c) logic symbol

If both i/p's are Low, then the o/p Z has a Low impedance connection to V<sub>DD</sub> through the 'ON' p-channel transistors, and the path to ground is blocked by the 'OFF' n-channel transistors. If either input is High, the path to V<sub>DD</sub> is blocked, and Z has a Low-impedance connection to ground. Figure shows the switch model for the NOR gate's operation.




For CMOS, and in most other logic families the Simplest gates are inverters, and the next Simplest are NAND gates & NOR gates.

 CMOS non inverting buffers and AND and OR gates are obtained by connecting an inverter to the o/p of the corresponding inverting gate. Thus, Fig 3.13 Shows a non inverting buffer and figure 3.14 Shows an AND gate. Combining NOR with an inverter yields an OR gate as shown in Fig 3.15



(b)

A	B	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Q <sub>4</sub>	Q <sub>5</sub>	Q <sub>6</sub>	Z
L	L	OFF	ON	OFF	ON	ON	OFF	L
L	H	OFF	ON	ON	OFF	ON	OFF	L
H	L	ON	OFF	OFF	ON	ON	OFF	L
H	H	ON	OFF	ON	OFF	OFF	ON	H

 

(c)

Fig : CMOS 2-input AND gate (a) circuit diagram (b) Function table (c) logic symbol

## Electrical Behaviour of CMOS Circuits

### CMOS Steady State Electrical Behaviour

The steady-state behaviour is the behaviour of the circuit when input signals are not changing.

### Logic level and noise margin

The CMOS device manufacturer specifies the four voltage parameters in the datasheet. These are:

$V_{IH(min)}$  - High level input voltage.

It is a minimum voltage level required for a logical 1 at an i/p. Any voltage below this level will not be accepted as a high by the logic circuit.

$V_{IL(max)}$  - Low level input voltage.


It is a maximum voltage level required for a logic 0 at an i/p. Any voltage above this level will not be accepted as a low by the logic circuit.

$V_{OH(min)}$  - High-level output voltage

It is a minimum voltage level of a logic circuit output in the logic 1 state under defined load conditions.

$V_{OL(max)}$  - Low-level output voltage

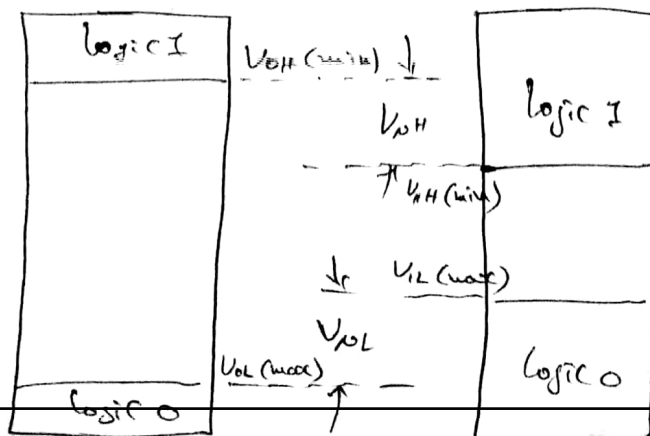It is a maximum voltage level at a logic circuit output in the logic 0 state under defined load conditions.





$$V_{OL} = V_{IL}(\text{max}) - V_{OL}(\text{max})$$

voltage levels & noise margin

The power supply voltage  $V_{CC}$  & ground are often called the power supply rails.

Cmos levels are typically a fraction of the power supply rails.

$$V_{OH}(\text{min}) : V_{CC} - 0.1V$$

$$V_{IH}(\text{min}) : 70\% \text{ of } V_{CC}$$

$$V_{IL}(\text{max}) : 30\% \text{ of } V_{CC}$$

$$V_{OL}(\text{max}) : \text{Ground} + 0.1V$$


Like voltage levels, device manufacturers also specify current parameters. These are,


$I_{IH}$  - High level input current : It is a current that flows into an i/p when a specified high-level voltage is applied to that i/p.

$I_{IL}$  - low level input current : It is a current that flows into an i/p when specified low-level voltage is applied to that i/p


$I_{OH}$  - High level o/p current : It is a current that flows from an o/p in the logical 1 state under specified load condition.

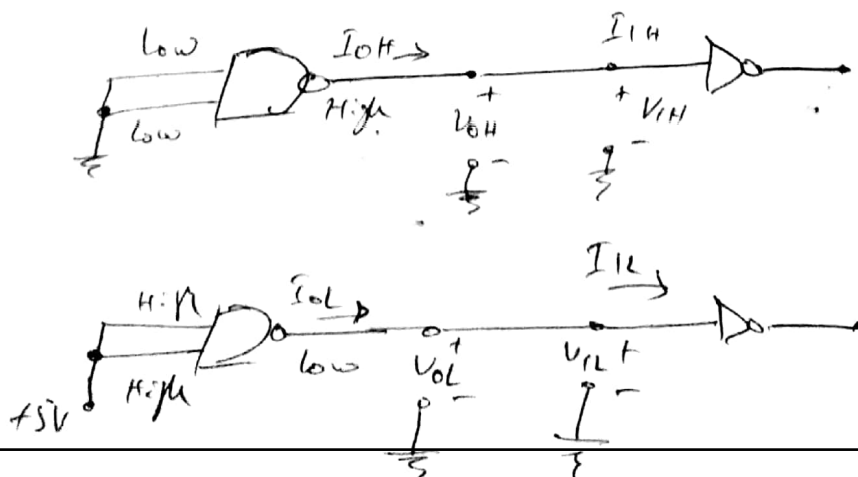$I_{OL}$  - Low level o/p current : It is the current that flows from an o/p in the logical 0 state under specified load condition.



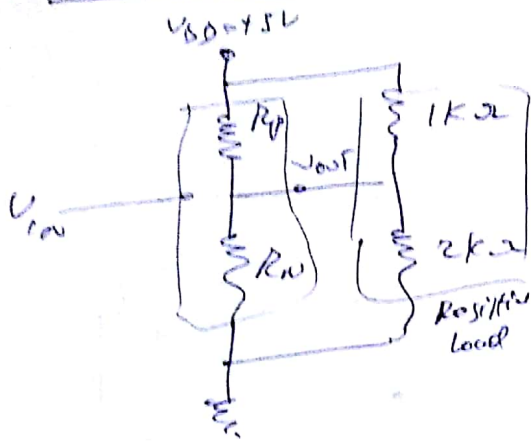

Resistive load of CMOS given by

 


Resistive load modeled by a Thevenin equivalent circuit

$$V_{TH} = \frac{2k}{2k+1k} \times 5V = 3.33V$$

$$R_{TH} = 1k \parallel 2k = 667\Omega$$


Condition 1: Input High

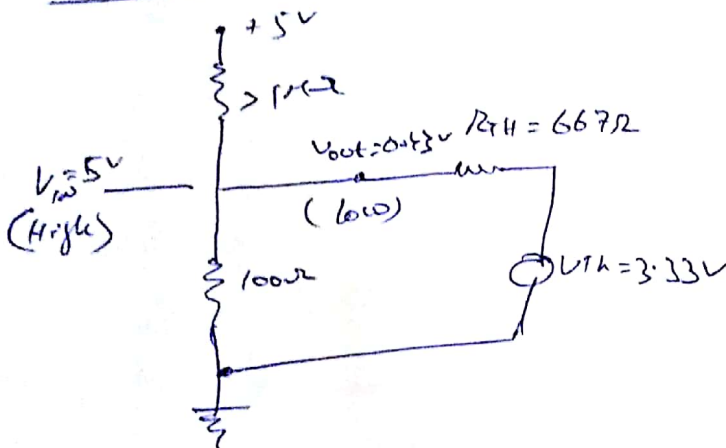

$$V_{out} = \frac{V_{TH} \times 100}{(100 + 667)} = \frac{3.33V \times 100}{100 + 667}$$

$$= \underline{\underline{0.43V}}$$

Condition 2: Input Low

 


$$V_{out} = \frac{(V_{DD} - V_{TH}) R_{TH}}{R_{TH} + 200} + V_{TH}$$


$$= \frac{(5 - 3.33) \times 667}{667 + 200} + 3.33$$

$$= \underline{\underline{4.61V}}$$




 

 
$$\begin{aligned} \text{Sinking curr} &= \frac{V_{OL} (max)}{R_L} \\ &= \frac{0.43V}{100} \\ &= \underline{\underline{4.3mA}} \end{aligned}$$


 
$$\begin{aligned} \text{Sourcing curr} &= \frac{V_{DD} - V_{OH} (min)}{R_p} \\ &= \frac{5 - 4.61}{200} \\ &= \underline{\underline{1.95mA}} \end{aligned}$$



Ⓐ output low

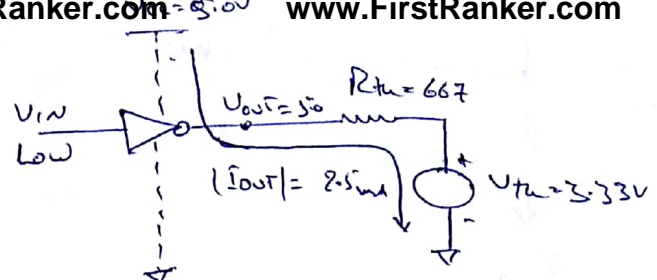

Ⓑ output HIGH

Assume on resistance of transistors equal to zero, i.e. no voltage drop across it, all very good worst case estimates of op. circuit.

low low out put

$$I_{out} = \frac{V_{th}}{R_{th}} = \frac{3.33}{667} = \underline{5 \text{ mA}}$$


for high output

$$I_{out} = \frac{5 - 3.33}{667} = \underline{2.5 \text{ mA}}$$

Circuit Behaviour with non ideal i/p.


If the i/p voltage is not close to the power supply rail, then the on transistor may not be fully 'on' & its resistance may increase. Like wise, the 'off' transistor may not be fully 'off' & its resistance may be quite a bit less than one MΩ. These two effects combine to move the output voltage away from the power supply rail.

EXR

 
 
$$V_{out} = \frac{(2.5 \text{ k}) 5}{2.5 \text{ k} + 400} = \underline{4.31 \text{ V}}$$







What's worse is that the old structure is now consume nontrivial amount of power. The current flow with the 1.5V  $\gamma/\alpha$  is

$$I_{wired} = \frac{5}{400\Omega + 2.5k} = 1.72 \text{ mA}$$

& power consumption is

$$P_{wired} = 5.00 \times I_{wired} = 5 \times 1.72 \text{ mA} = \underline{8.62 \text{ mW}}$$

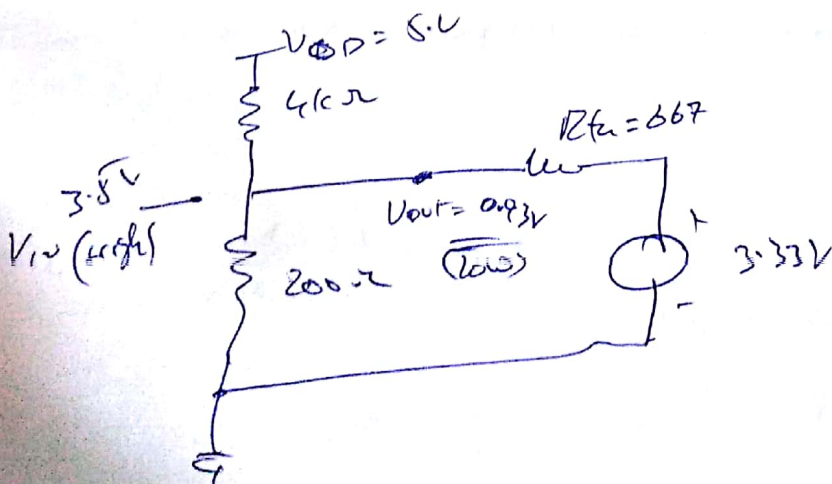 The o/p voltage of CMOS inverter deteriorates further with a negative level.



following eqs.

$$R_p(ON) = \frac{V_{DD} - V_{OH(max)}}{|I_{OH(max)}|}$$

$$R_N(ON) = \frac{V_{OL(max)}}{I_{OL(max)}}$$

Let us consider the parameters of CMOS HC-series listed in the table

Parameter	CMOS load	Parameter	TTL load
$I_{OL(max)C}$	0.02 mA	$I_{OL(max)T}$	4.0 mA
$V_{OL(max)C}$	0.1 V	$V_{OL(max)T}$	0.33 V
$I_{OH(max)C}$	-0.02 mA	$I_{OH(max)T}$	-4.0 mA
$V_{OH(min)C}$	4.4 V	$V_{OH(min)T}$	3.84 V

From the table

$$R_p(ON) = \frac{5 - 3.84}{|-4.0 \times 10^{-3}|} = \frac{2902}{1752} \quad \left. \vphantom{\frac{2902}{1752}} \right\} \text{For TTL load}$$

$$R_N(ON) = \frac{0.33}{4 \times 10^{-3}} = 82.5 \Omega$$



$$R_p(ON) = \frac{5 - 4.4}{0.02 \times 10^{-3}} = 0.03$$

$$R_N(ON) = \frac{0.1}{0.02 \times 10^{-3}} = 0.005$$



The maximum current that the o/p can sink in the low state while still maintaining an o/p voltage smaller than  $V_{OL(max)}$

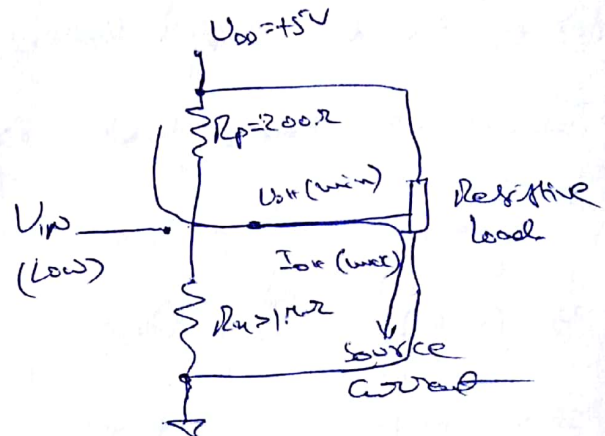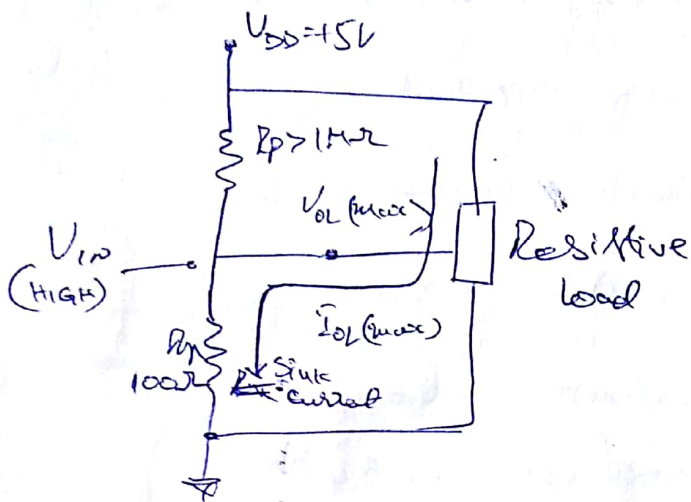$I_{OH(max)}$ : The maximum current that the o/p can source/supply in the HIGH state while still maintaining an o/p voltage greater than  $V_{OH(min)}$




Sink current: A device o/p is said to sink current when current flows from the power supply, through the load, and through the device o/p to ground.

$$\begin{aligned} \text{Sink current} = I_{\text{sink}} = I_{OL(max)} &= \frac{V_{OL(max)}}{R_L} \quad (\text{or}) \quad \frac{V_{out}}{R_L} \\ &= \frac{0.43V}{100} = \underline{\underline{4.3 \text{ mA}}} \end{aligned}$$




Source current: The o/p is said to source current when current flows from the power supply, out of the device o/p, and through the load to ground.
 
$$\begin{aligned} \text{Source current} = I_{\text{source}} = I_{OH(max)} &= \frac{V_{DD} - V_{out}}{R_P} = \frac{V_{OH(min)}}{R_P} \\ &= \frac{V_{DD} - V_{out}}{R_P} \\ &= \frac{5 - 4.61}{200} = \frac{0.39}{200} = \underline{\underline{1.95 \text{ mA}}} \end{aligned}$$



www.FirstRanker.com


(19)

   

0-2 -0  
2-3 1  
3-5 1


Diode logic

AND

 

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1


Transistor logic

 


$$I_E = I_B + I_C$$

$$I_C = I_E - I_B$$



OR

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

 


$$I_C = I_B + I_E$$

  

D2  
R1  
DTL



 

$\Rightarrow V_{IN}$  is low  $\Rightarrow V_{BE0}$  is low  $\Rightarrow Q_1$  is in cutoff  $\Rightarrow V_{OUT} = V_{CC}$  (proper choice)

$\Rightarrow R_B \rightarrow Q_1$  saturation for  $V_{IN} = V_{LO}$

$V_{BE0}$  i.e. Voltage across collector to base + emitter of  $Q_0$

is  $V_{BE0} = V_{IN} + V_{CE1}(\text{sat})$

$$= V_{LO} + 0.2V$$


$$= 0 + 0.2 = 0.2V$$

this is insufficient to drive transistor  $Q_0$  hence  $Q_0$  is in cutoff

$$\therefore V_{OH} = V_{OUT} = V_{CC}$$

$\Rightarrow$  If  $V_{IN} \rightarrow V_{BE0}$  will reach  $0.7V$  (ON)  $\rightarrow Q_0$  will forward bias

### Standard TTL NAND gate (7400)

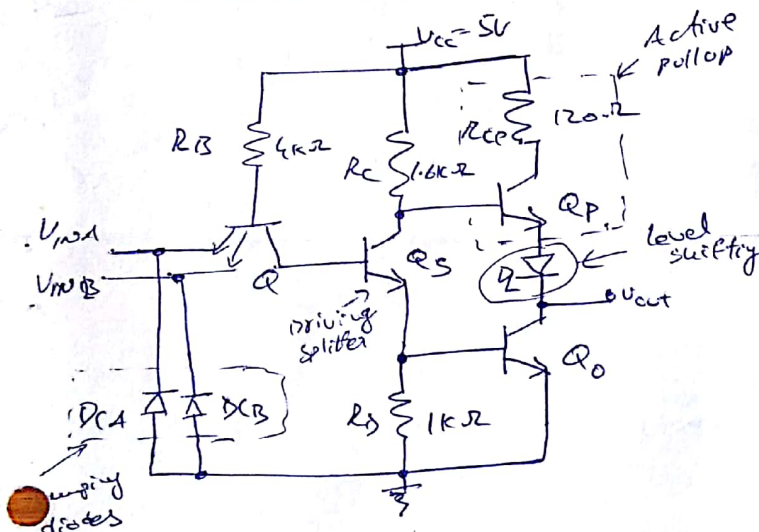

$\rightarrow$  clamping diodes:  $D_1, D_2$ : To protect I/O from negative spikes

$\rightarrow$  Discharge resistor  $R_5$ : Provides a discharge path for the base of  $Q_0$  when switching from sat. to cutoff (at both) faster speed.

$\rightarrow$  Active pull-up ( $Q_{P1}$   $R_{CP}$ ): Provides larger current to load gates w/o for faster charging of load gates and increased fan-out.

$\rightarrow$  level shifting Diode ( $D_3$ ): Provides voltage isolation ( $0.7V$ )  $V_{IN}$   $Q_0$  &  $Q_P$  to ensure no simultaneous conduction of both.

### LEVEL SHIFTING DIODE

For OL, to ensure  $Q_P$  &  $Q_0$  will not conduct simultaneously.

$Q_S = \text{sat}, Q_P = \text{cutoff}??$  El  $Q_0 = \text{sat}$ .  $V_{OUT} = OL$

$$V_{BEP} = V_{BP} - V_{EP} \rightarrow ①$$


$$V_{BP} = V_{BE0}(\text{sat}) + V_{CES}(\text{sat}) \rightarrow ②$$

$$V_{EP} = V_{CE0}(\text{sat}) + V_{DL}(\text{on}) \rightarrow ③$$

$$\therefore V_{BEP} = V_{BE0}(\text{sat}) + V_{CES}(\text{sat}) - V_{CE0}(\text{sat}) + V_{DL}(\text{on})$$

$$= V_{BE0}(\text{sat}) + V_{DL}(\text{on}) < V_{BE}(\text{FA})$$

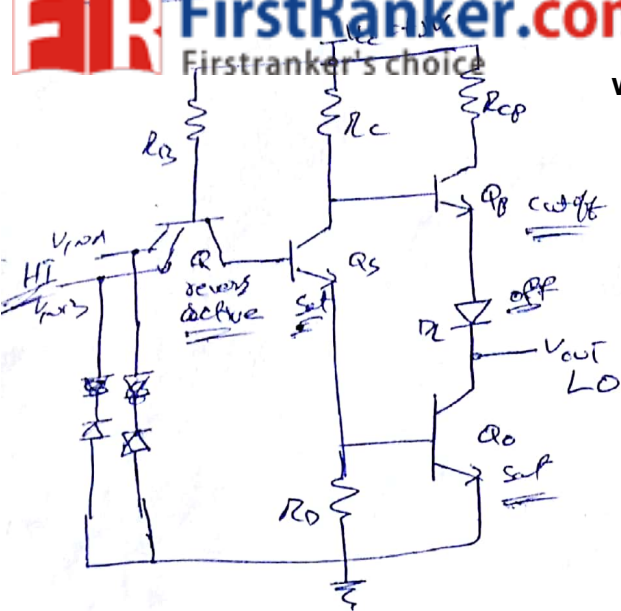$\Rightarrow Q_P$  cannot be conducting  $\rightarrow$  cutoff because of level shifting  $D_3$ .



(i.e. 0) then  $Q_1$  is on & the base voltage is at its lowest value  $V - I_1 R_1$ . Here again  $R_1$  is used generally each element having its fixed values in practice. The collector of  $Q_1$  at the base of  $Q_3$  are low so that  $Q_3$  is off. In this situation the base of  $Q_2$  is high turning this transistor on while the base of  $Q_1$  is 0 & this transistor is off. In this situation the o/p is connected to the high voltage line 'V' & it gives high.

If  $V_{IN A}$  &  $V_{IN B}$  both are at high level  $Q_1$  is off, turning  $Q_2$  on. This reduces the voltage on the base of  $Q_3$  below its emitter voltage so that  $Q_3$  becomes non-conducting. The base of  $Q_1$  on the other hand is driven up by an amount  $I_2 R_2$  & becomes conducting. The base of  $Q_2$  on the other hand is driven to ground and the o/p is connected to ground through  $Q_1$  & the o/p is low.

$V_{IN A}$	$V_{IN B}$	$Q_1$	$Q_2$	$Q_3$	$Q_4$	O/P
0	0	ON	OFF	ON	OFF	1
0	1	ON	OFF	ON	OFF	1
1	0	ON	OFF	ON	OFF	1
1	1	OFF	ON	OFF	ON	0



## Entity Declaration:-

1. An entity declaration describes the external interface of the entity, that is it gives the black-box view.
2. It specifies the name of the entity, the names of interface ports, their mode (i.e. direction) and the type of ports.

The syntax is

entity entity-name is

generic (list-of-generics-and-their-types)

Port (list-of-interface-port-names-and-their

entity-item-declarations] types);

[begin

entity-statements]

end entity-name;

## Architecture Body:-

1. It describes the internal view of an entity.
2. It describes the functionality or the structure of the entity

3. The syntax is

architecture architecture-name of entity-name

[architecture-item-declarations]

begin

Concurrent-statements;



Cocurrent - Procedure - Call

Concurrent - assertion - statement

Concurrent - signal - assignment - statement

Component - instantiation - statement

Generate - statement

end architecture-name;

### 3) Process Statement:-

1. A Process statement contains sequential statements that describe the functionality of a portion of an entity in sequential terms.

Syntax is

[Process-label:] Process [sensitivity-list]

[process-item-declarations]

begin

Sequential-statements;

Variable-assignment-statement

Signal-assignment-statement

wait-statement

if-statement

case-statement

loop-statement

null-statement

exit-statement

next-statement

assertion-statement

Procedure-call-statement

return-statement

end process [process-label];

1. Variable can be declared and used inside a process statement.
2. A variable is assigned a value using the variable assignment statement that typically has the form
- $$\text{Variable} - \text{object} = \text{expression}$$

Consider the following process statement

Process (A)

Variable events-on-A: Integer := 0;

begin

events-on-A := events-on-A + 1;

end process;

### 3.3. Signal Assignment statement

1. Signals are assigned values using a signal assignment statement the simplest form of signal assignment statement is

$$\text{Signal-object} \leftarrow \text{expression} [\text{after delay-value}]$$

### 3.4 Wait Statement

1. A process may be suspended by means of a sensitivity list.
2. That is, when a process has a sensitivity list.
3. It always suspends after executing the last sequential statement in the process.
4. The wait statement provides an alternative way to suspend the execution of a process.



wait on Sensitivity - list;

wait until boolean-expression;

wait for time-expression;

5. They may also be combined in a single wait statement.

### 3.5 If statement

1. An 'if' statement selects a sequence of statements for execution based on the value of a condition.
2. The condition can be any expression that evaluates to a boolean value.

The general form of an if statement is

```

if boolean-expression
    sequential-statements
elsif boolean-expression then
    sequential-statements
else
    sequential-statements
end if;
```

### 3.6 Case statement

The format of a case statement is

Case expression is

when choice  $\Rightarrow$  seq-statements

when choice  $\Rightarrow$  seq-statements

-- Can have any no. of statements

when other  $\Rightarrow$  Seq-statements

end case;



1. The statement null is a sequential statement that does not cause any action to take place and execution continues with the next statement.

### 3.8 Loop statement

1. A loop statement is used to iterate through a set of sequential statements.
2. The syntax of a loop statement is  
[loop-label:] iteration-scheme that has the form for identifier in range.

### 3.9 Exit statement

1. The exit statement is a sequential statement that can be used only inside a loop.
2. It causes execution to jump out of the innermost loop or the loop whose label is specified.

The syntax for an exit statement is

exit [loop-label] [when condition]:

### 3.10 Next statement

1. The next statement is also a sequential statement that can be used only inside a loop.
2. The syntax is the same as that for the exit statement except that the keyword next replaces the keyword exit.

The syntax for Next statement  
next [loop-label] [when condition];

### 3.11 Assertion Statement

1. ~~Ass~~ Assertion statements are useful in modeling constraints of an entity.

The syntax is

assert boolean-expression  
[report string-expression]  
[severity expression];


### 3.12 More on Signal Assignment Statement

1. Signal assignment statement used inside a process that illustrated the delta delay model.
2. Aside from the delta delay model, there are two other types of delay models that can be used with signal assignments, inertial and transport.

#### 3.12.1 Inertial Delay Model:-


1. In this delay model the delays often found in switching circuits.
2. It represents the time for which an input value must be stable before the value is allowed to propagate to the output.

$Z \leftarrow A$  after 10ns.

 



 1. Transport delay models the delays in hardware that do not exhibit any inertial delay
2. This delay represents pure propagation delay, that is any changes on an input is transported to the output, no matter how small, after the specified delay.



### 3.12.3 Creating Signal waveforms

1. In all examples of signal assignment statements that we have seen so far, we have always assigned a single value to a signal; this need not be so.

$\text{Phase1} \leftarrow '0', '1' \text{ after } 8\text{ns}, '0' \text{ after } 13\text{ns}, '1' \text{ after } 18\text{ns};$

### 3.12.4 Signal drivers

50ns;

1. The driver of a signal holds its current value and all its future values as a sequence of one or more transactions, where each transaction identifies the value to appear on the signal along with the time at which the value is to appear.

Program  
begin

$\text{Rout} \leftarrow 3 \text{ after } 5\text{ns}, 21 \text{ after } 10\text{ns}, 14 \text{ after } 17\text{ns};$

end program;




3.13 Other Sequential Statements :-  
1. There are two other forms of sequential statements.

- (i) Procedure Call Statement
- (ii) Return statement.

### 3.14 Multiple processes:-

 1. A process statement is a concurrent statement, it is possible to have more than one process within an architecture body.
2. This makes it possible to capture the behaviour of interfacing processes.



A Combinational logic circuit is one whose o/p's depend only on its current i/p's.

A Combinational circuit may contain an arbitrary no. of logic gates and inverters but no feedback loops.

In combinational circuit, ANALYSIS we start with a logic diagram & proceed to a formal description of the function performed by that circuit. Such as a truth table or a logic expression.

In SYNTHESIS we do the reverse, starting with a formal description & proceeding to a logic diagram.


### • DECODER

A decoder is a multiple-i/p, multiple-o/p logic circuit that converts coded i/p into coded o/p's, where the i/p & o/p codes are different.

The i/p code generally has fewer bits than the o/p code, & there is a one-to-one mapping from i/p code words into o/p code words.

In a one-to-one mapping, each i/p code word produces a different o/p code word.


## General structure of decoder

 

The most commonly used i/p code is an  $n$ -bit binary code, where an  $n$ -bit word represents one of  $2^n$  different coded values, normally the integers from 0 to  $2^n - 1$ .

The most commonly used o/p code is a set of  $n$  code which contains  $n$  bits, where one bit is asserted at any time.

### 2 to 4 Decoder

 


Logic - Symbol.

A	B	$Y_0$	$Y_1$	$Y_2$	$Y_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1


Truth table

### Internal Structure

 




2 to 4 decoder with enable i/p

 


Truth table

EN	A	B	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	0	0	0	1

logic symbol

 


3 to 8 decoder with enable i/p

 


EN	A	B	C	Y <sub>7</sub>	Y <sub>6</sub>	Y <sub>5</sub>	Y <sub>4</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0

 1 1 0 1 0 0 1 0 0 0 0 0  
1 1 1 0 0 1 0 0 0 0 0 0  
1 1 1 1 1 0 0 0 0 0 0 0






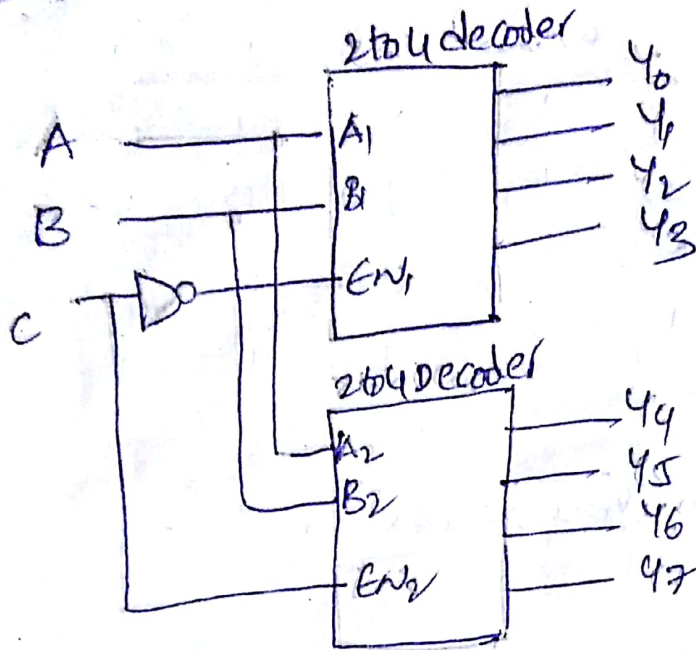
Design 3 to 8 decoder using 2 to 4 decoder



C	B	A	Y <sub>7</sub>	Y <sub>6</sub>	Y <sub>5</sub>	Y <sub>4</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

MSI DECODER


74x139 Dual 2 to 4 Decoder

  




G-L	A	B	Y <sub>0</sub> -L	Y <sub>1</sub> -L	Y <sub>2</sub> -L	Y <sub>3</sub> -L
1	x	x	0	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1

### Internal structure of 74x139

 

Two identical & independent 2 to 4 decoders are contained in a single MSI part, the 74x139.

 The internal structure shows that the o/p & the enable i/p of the 139 are active low. Most MSI encoders were originally designed with active-low o/p's. Since TTL inverting gates are generally faster than non-inverting ones.



$G_1$	$G_{2A-L}$	$G_{2B-L}$	A	B	C	$Y_{7-L}$	$Y_{6-L}$	$Y_{5-L}$	$Y_{4-L}$	$Y_{3-L}$	$Y_{2-L}$	$Y_{1-L}$	$Y_{0-L}$
0	x	x	x	x	x	1							
x	1	x	x	x	x		1						
x	x	1	x	x	x			1					
1	0	0	0	0	0				1				
1	0	0	0	0	1					1			
1	0	0	0	1	0						1		
1	0	0	0	1	1							1	
1	0	0	1	0	0								1
1	0	0	1	0	1								
1	0	0	1	1	0								
1	0	0	1	1	1								

Like the 74x139, the 74x138 has active-low o/p & it has three enable i/p's ( $G_1$ ,  $G_{2A-L}$ ,  $G_{2B-L}$ ), all of which must be asserted for the selected o/p to be asserted.

The logic function of '138' is straight forward - an o/p is asserted if & only if

Thus, we can easily write logic equation for an internal o/p signal such as  $Y_5$  in terms of the internal i/p signal.

$$Y_5 = \underbrace{G_1 \cdot G_{2A} \cdot G_{2B}}_{\text{enable}} \cdot \underbrace{C \cdot \bar{B} \cdot A}_{\text{select}}$$

$$G_{2A} = G_{2A-L}$$


$$G_{2B} = G_{2B-L}$$

$$Y_5 = Y_{5-L}$$

$$\begin{aligned} \overline{Y_{5-L}} = \overline{Y_5} &= \overline{(G_1 \cdot G_{2A-L} \cdot G_{2B-L} \cdot C \cdot \bar{B} \cdot A)} \\ &= \overline{G_1} + \overline{G_{2A-L}} + \overline{G_{2B-L}} + \overline{C} + \overline{\bar{B}} + \overline{A} \end{aligned}$$

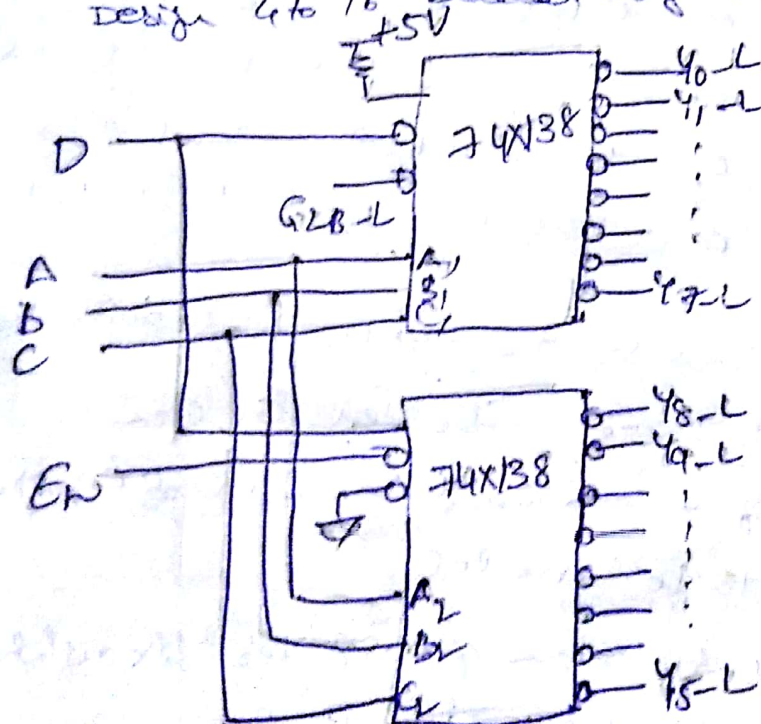
### CASCADING BINARY DECODERS

Design 4 to 16 Decoder using 74x138 decoder





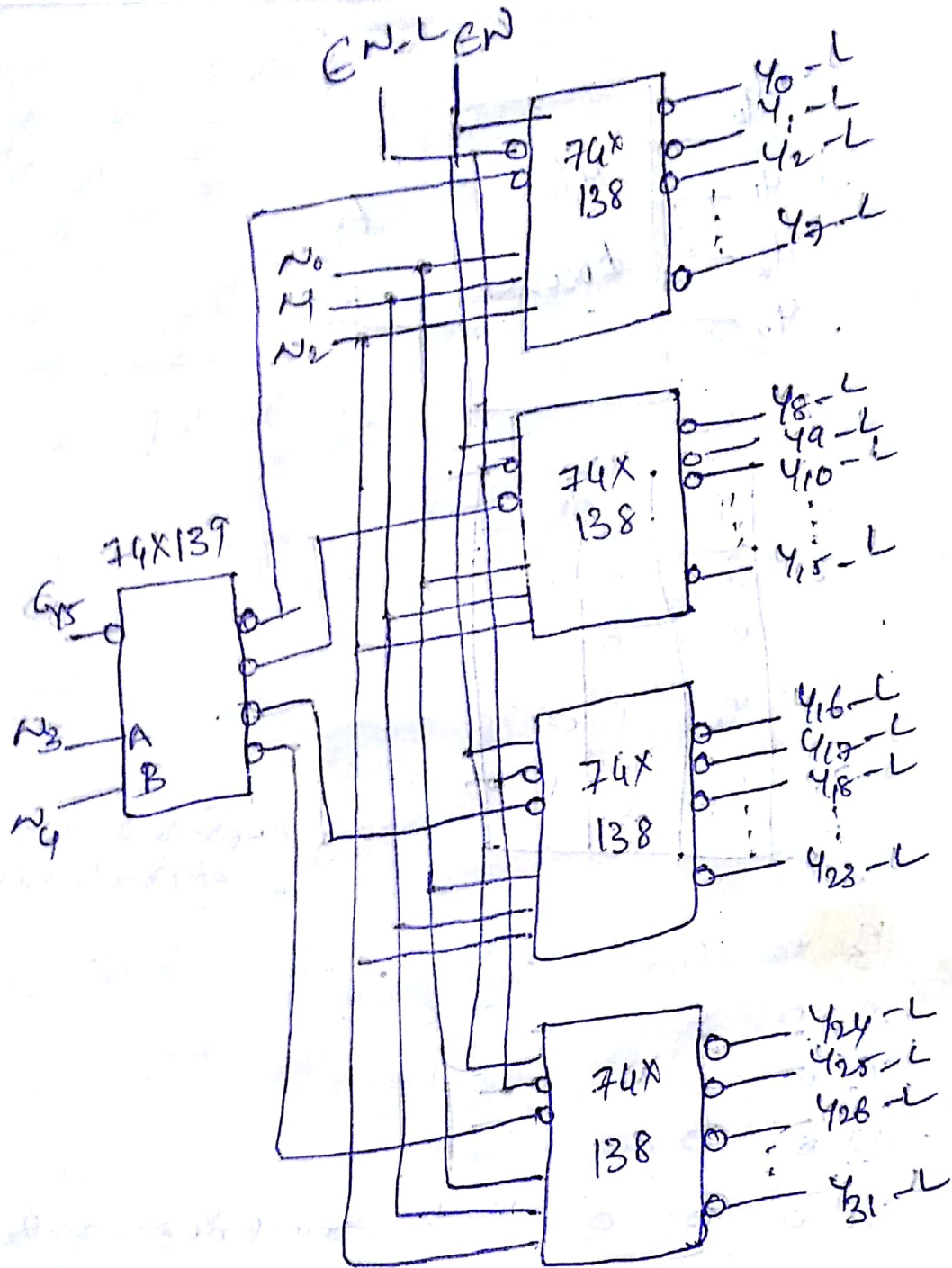Design 5 to 32 decoder using 74x138 & 74x139




### ENCODERS

It is a combinational logic circuit.

It has  $2^n$  inputs and  $n$  outputs. It performs

Exact opposite function of decoder. It performs some coding operations.

Design 4 to 2 decoder

 


logic symbol

IPS	O/Ps	
	A	B
y <sub>0</sub>	0	0
y <sub>1</sub>	0	1
y <sub>2</sub>	1	0
y <sub>3</sub>	1	1


wrong Representation of Truth table

y <sub>3</sub>	y <sub>2</sub>	y <sub>1</sub>	y <sub>0</sub>	A	B
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Exact Representation of Truth table.

 


10

 

Truth Table

$Y_7$	$Y_6$	$Y_5$	$Y_4$	$Y_3$	$Y_2$	$Y_1$	$Y_0$	A	B	C
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

 

Internal Structure



4-bit Priority Encoder

$\gamma_3$	$\gamma_2$	$\gamma_1$	$\gamma_0$	A	B	V
x	x	x	1	0	0	1
x	x	1	0	0	1	1
x	1	0	0	1	0	1
1	0	0	0	1	1	1
0	0	0	0	x	x	0

$\gamma_0 \rightarrow$  highest priority

V is valid i/p

For A

$\gamma_3 \gamma_2$	$\gamma_1 \gamma_0$	00	01	11	10
00					
01					
11					
10					

$$A = \overline{\gamma_1} \overline{\gamma_0} \gamma_3 + \overline{\gamma_1} \gamma_0 \overline{\gamma_2}$$

For B


$\gamma_3 \gamma_2$	$\gamma_1 \gamma_0$	00	01	11	10
00					
01					
11					
10					

$$B = \gamma_1 \gamma_0 + \overline{\gamma_0} \gamma_3 \overline{\gamma_2}$$

For V


$\gamma_3 \gamma_2$	$\gamma_1 \gamma_0$	00	01	11	10
00					
01					
11					
10					
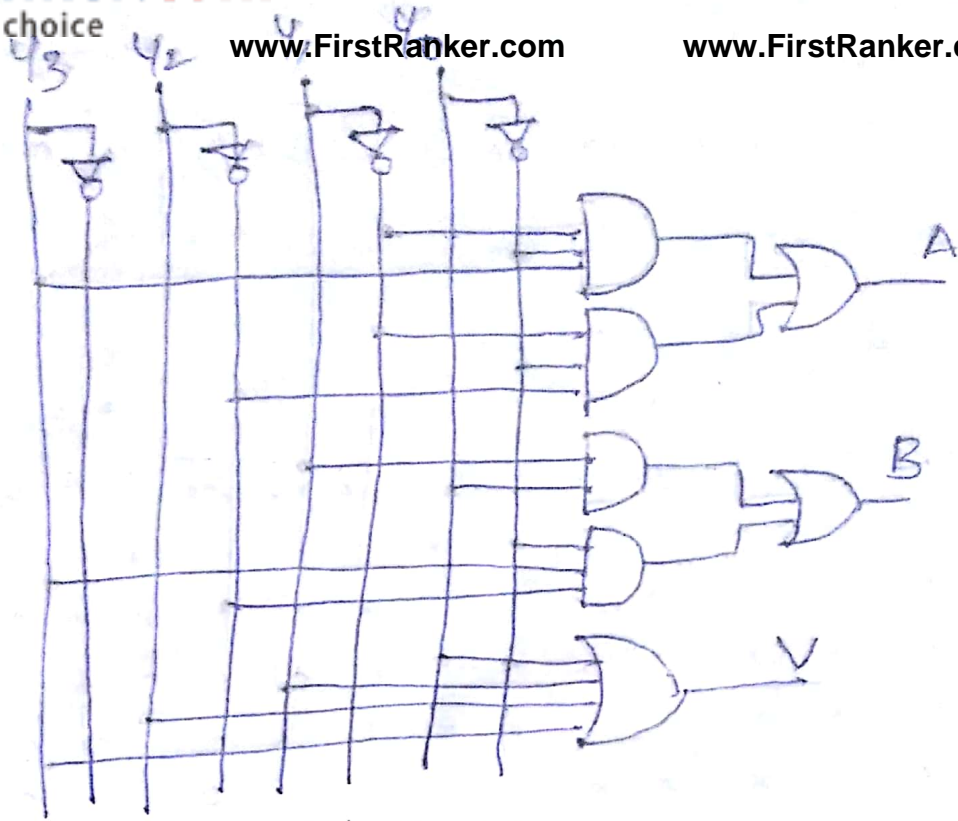
$$V = \gamma_0 + \gamma_1 + \gamma_2 + \gamma_3$$



4-bit Priority Encoder

74x148 is a 8bit priority Encoder

 

The 148 has a GS-L o/p that is asserted when the device is enabled & one or more of the request i/p's are asserted. The EO-L signal is an enable o/p designed to be connected to the EI-L i/p of another 148 that handles lower priority requests.

but no request ip is asserted, thus a lower priority 148 may be enabled.

### Truth Table


I/PS										O/PS			
En	I <sub>0</sub>	I <sub>1</sub>	I <sub>2</sub>	I <sub>3</sub>	I <sub>4</sub>	I <sub>5</sub>	I <sub>6</sub>	I <sub>7</sub>	I <sub>8</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	E <sub>0</sub>
1	x	x	x	x	x	x	x	x	x	1	1	1	1
0	x	x	x	x	x	x	x	0	0	0	0	0	1
0	x	x	x	x	x	x	0	1	0	0	0	0	1
0	x	x	x	x	x	0	1	1	0	0	0	0	1
0	x	x	x	x	0	1	1	1	0	0	0	0	1
0	x	x	x	0	1	1	1	1	0	0	0	0	1
0	x	x	0	1	1	1	1	1	0	0	0	0	1
0	x	0	1	1	1	1	1	1	0	0	0	0	1
0	0	1	1	1	1	1	1	1	1	0	0	0	1
0	0	1	1	1	1	1	1	1	1	1	0	0	1
0	1	1	1	1	1	1	1	1	1	1	1	0	1
0	1	1	1	1	1	1	1	1	1	1	1	1	0

### MULTIPLEXERS & DEMULTIPLEXERS

Mux: It is a Combinational logic circuit which has selection ip & data ip & only one output.

n selection ips & 2<sup>n</sup> data inputs & only one op.

 Mux is also called as data selector or digital switch.



Four way Switch



Design 2:1 Mux

2 → data i/p's


1 → selection i/p

1 → o/p.



Truth Table

S <sub>0</sub>	Y
0	D <sub>0</sub>
1	D <sub>1</sub>

 


Design 4:1 Mux

4 → data i/p's


2 → Selection i/p's

1 → o/p.

 


Truth Table

S <sub>1</sub>	S <sub>0</sub>	Y
0	0	D <sub>0</sub>
0	1	D <sub>1</sub>
1	0	D <sub>2</sub>
1	1	D <sub>3</sub>

 


A	B	Car	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S(A, B, C_{in}) = \sum m(1, 2, 4, 7)$$

 

## 74x151 Multiplexer


74x151 8:1 1 bit Mux

 


Truth table

I/P				O/Ps	
EN	C	B	A	Y	Y'
1	x	x	x	0	1
0	0	0	0	$\overline{D_0}$	$D_0$
0	0	0	1	$\overline{D_1}$	$D_1$
0	0	1	0	$\overline{D_2}$	$D_2$
0	0	1	1	$\overline{D_3}$	$D_3$
0	1	0	0	$\overline{D_4}$	$D_4$
0	1	0	1	$\overline{D_5}$	$D_5$
0	1	1	0	$\overline{D_6}$	$D_6$
0	1	1	1	$\overline{D_7}$	$D_7$

Internal structure

 



 


Truth Table


P/P		O/Ps			
$G-L$	$S-L$	$Y_1$	$Y_2$	$Y_3$	$Y_4$
1	X	0	0	0	0
0	0	$1A$	$2A$	$3A$	$4A$
0	1	$1B$	$2B$	$3B$	$4B$

$S-L \rightarrow$  Active low select input line

$G-L \rightarrow$  Active low gate pulse

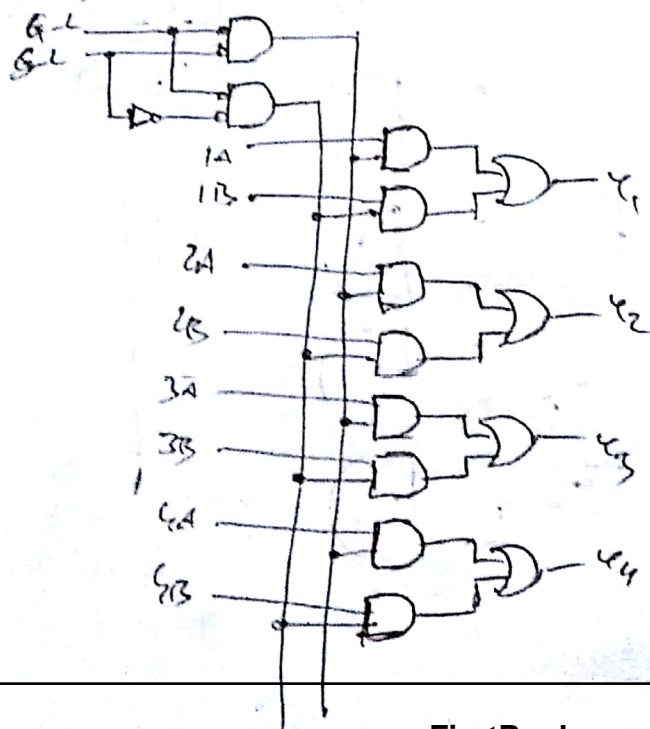

 Comparator is a Combinational logic circuit which compares two binary inputs of any length & gives the appropriate result i.e. greater than, less than & Equal to its o/p terminals.



If A & B are represent by only one bit length then

A	B	$A > B$	$A < B$	$A = B$
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	0	0	1

The above truth table has four rows.

$$2^n = 2^{2 \times 1} = 4 \text{ rows.}$$

where 'n' is no. of bits per i/p.

Both i/ps must be equal length.


From the Truth table

$$(A > B) = A \bar{B}$$

$$(A < B) = \bar{A} B$$

$$(A = B) = \bar{A} \bar{B} + AB$$

$$= \overline{A \oplus B} = A \odot B$$

 

## Four Bit Comparator

For Four Bit Comparator  $2^{4 \times 4} = 2^{16} = 65536$  rows

This is very complicated to Designer by using the above procedure (Truth table/Model)

Hence to simplify the design compare two equal weighted bits from MSB to LSB. Determine the conditions greater, less & equals.

A = A<sub>3</sub> A<sub>2</sub> A<sub>1</sub> A<sub>0</sub>

B = B<sub>3</sub> B<sub>2</sub> B<sub>1</sub> B<sub>0</sub>

If A<sub>3</sub> is 1 & B<sub>3</sub> is 0 then A<sub>3</sub> > B<sub>3</sub>, if

A<sub>3</sub> = B<sub>3</sub> only then we can compare A<sub>2</sub> & B<sub>2</sub>.  
if also we should not compare A<sub>2</sub> & B<sub>2</sub>.

In the same way only if A<sub>3</sub> = B<sub>3</sub>, A<sub>2</sub> > B<sub>2</sub>  
A<sub>2</sub> = B<sub>2</sub> then only we have to compare A<sub>1</sub> & B<sub>1</sub>

The result is if

$$A > B \Rightarrow A_3 > B_3 + x_3 (A_2 > B_2) + x_3 x_2 (A_1 > B_1) + x_3 x_2 x_1 (A_0 > B_0)$$

$$\Rightarrow A_3 \bar{B}_3 + x_3 A_2 \bar{B}_2 + x_3 x_2 A_1 \bar{B}_1 + x_3 x_2 x_1 A_0 \bar{B}_0$$



$$(A < B) \Rightarrow \bar{A}_3 B_3 + \bar{A}_3 A_1 B_1 + \bar{A}_3 A_1 B_0 + \bar{A}_3 A_1 B_0$$

$$(A = B) \Rightarrow X_3 X_2 X_1 X_0$$


$$X_3 = A_3 \odot B_3$$

$$X_2 = A_2 \odot B_2$$


$$X_1 = A_1 \odot B_1$$

$$X_0 = A_0 \odot B_0$$


### MSI Comparator

 


### To Compare Single Bit

 

### To Compare 1 bits

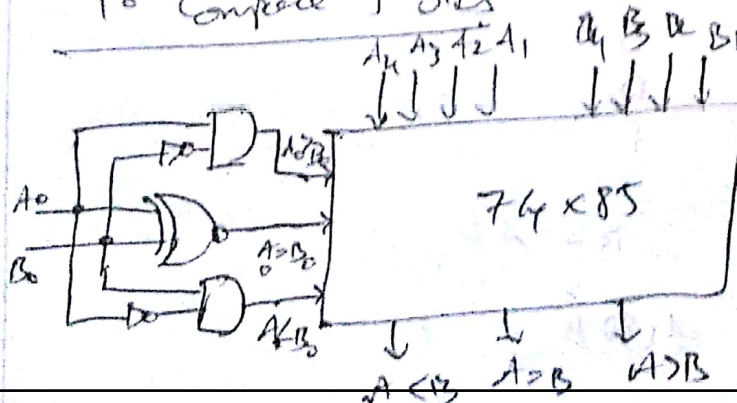

Design 8-bit Computer using 74x85

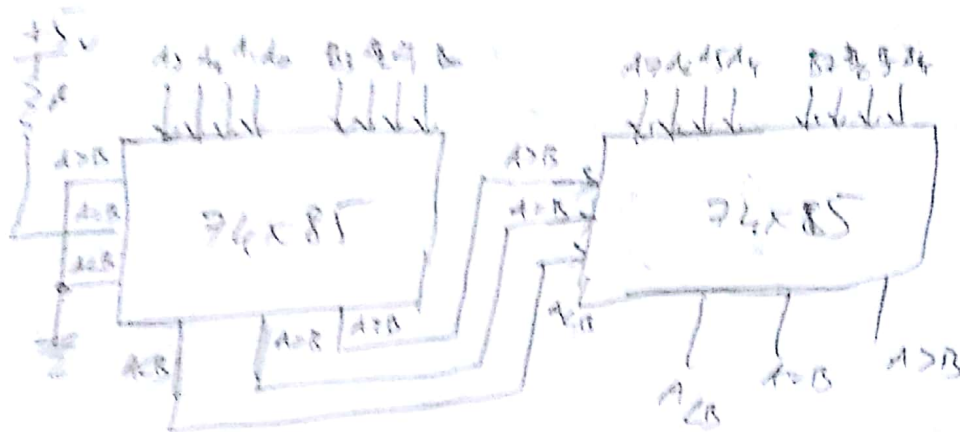

## ADDERS

HALF Adders

FULL Adders.

Half adder is used to add two single bits and it generates Sum and Carry outs.

Full adder is a combinational circuit which is used to add two single bits and it generates Sum and Carry outs.

### Half adder

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{Sum} = \overline{A}B + A\overline{B}$$

$$= A \oplus B$$

$$\text{Carry} = A \cdot B$$



### Full Adder


A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned}
 \text{Sum} &= A\bar{B}\bar{C}_{in} + A\bar{B}C_{in} + A\bar{B}C_{in} + A\bar{B}C_{in} \\
 &= A(\bar{B}\bar{C}_{in} + \bar{B}C_{in}) + \bar{A}(\bar{B}C_{in} + BC_{in}) \\
 &= A(\overline{B \oplus C_{in}}) + \bar{A}(B \oplus C_{in}) \\
 \text{Sum} &= A \oplus B \oplus C
 \end{aligned}$$

### Carry

A	B	Cin	Carry
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1
 
$$\text{Carry} = BC_{in} + AB + AC_{in}$$






$$\text{Sum} = A \oplus B \oplus C_{in}$$

$$\begin{aligned} \text{Carry} &= \bar{A} B C_{in} + A \bar{B} C_{in} + A B \bar{C}_{in} + A B C_{in} \\ &= C_{in} (\bar{A} B + A \bar{B}) + A B (\bar{C}_{in} + C_{in}) \end{aligned}$$
 
$$\text{Carry} = C_{in} (A \oplus B) + A B$$




### 4-bit parallel adder (Ripple carry adder)

$$A \Rightarrow \begin{matrix} C_3 & C_2 & C_1 & \\ A_3 & A_2 & A_1 & A_0 \end{matrix}$$

$$B \Rightarrow \begin{matrix} B_3 & B_2 & B_1 & B_0 \end{matrix}$$
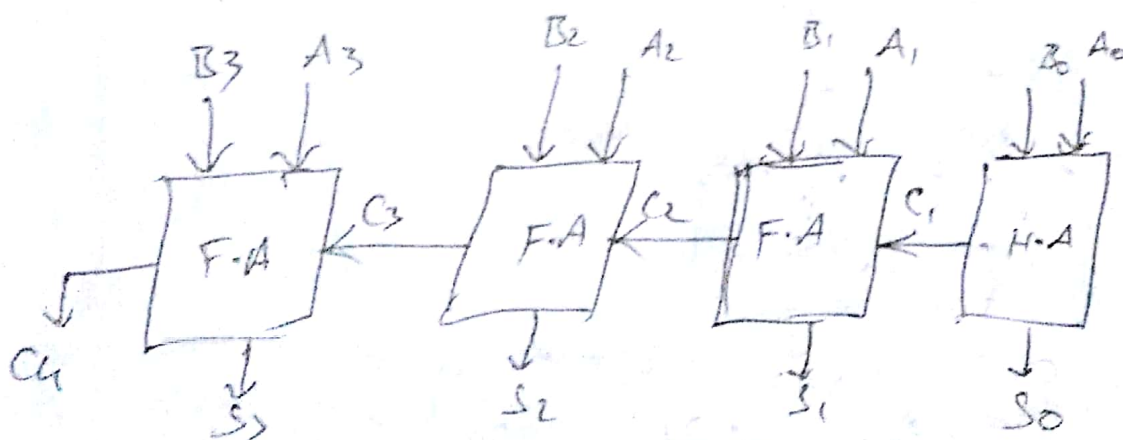
$$\begin{matrix} C_4 & S_3 & S_2 & S_1 & S_0 \end{matrix}$$



## BASIC BISTABLE ELEMENTS

The simplest sequential circuit consists of a pair of inverters forming a feedback loop, as shown in Fig 1. It has no inputs and two outputs,  $Q$  and  $Q_L$ .

Analysis. The circuit of Fig 1 is often called a bistable, since a strictly digital analysis shows that it ~~was~~ has two stable states. If  $Q$  is HIGH, then the bottom inverter has a HIGH i/p and a LOW o/p, which forces the top inverter's o/p HIGH as we assumed in the first place. But if  $Q$  is LOW, then the bottom inverter has a LOW i/p and a HIGH o/p, which forces  $Q$  LOW, another stable situation. We could use a single state variable, the state of signal  $Q$ , to describe the state of the circuit; there are two possible states,  $Q=0$  and  $Q=1$ .

 


Fig 1: A pair of inverters forming a bistable element.

The bistable element is so simple that it has no inputs and therefore no way of controlling or changing its state. When power is first applied to the circuit, it randomly comes up in one state or the other and stays there forever. Still, it serves our illustrative purpose very well, well, and we will actually show a couple of appli.

## LATCHES & FLIP FLOPS


Latches and Flip Flops are the basic building blocks of most sequential circuits. Typical digital systems use latches and Flip Flops that are prepackaged, functionally specified devices in a standard IC. In ASIC design environments, latches and Flip Flops are typically predefined or specified by the ASIC vendor.



All digital designers use the name flip-flop for a sequential device that normally samples its i/p's & changes its o/p only at times determined by a clocking signal.

On the other hand, most digital designers use the name latch for a sequential device that catches all of its i/p's continuously and changes its o/p's at any time, independent of a clocking signal.

### The NOR gate S-R latch

 


S	R	$Q_n$	$Q_{n+1}$	State
0	0	0	0	no change
0	0	1	1	
0	1	0	0	Reset (0)
0	1	1	0	
1	0	0	1	Set (1)
1	0	1	1	
1	1	0	x	Invalid
1	1	1	x	

Truth table

The analysis of the operation of the active HIGH NOR latch can be summarized as follows.

 1. SET=0, RESET=0: This is the normal resting state of the NOR latch and it has no effect on the o/p state. Q and  $\bar{Q}$  will remain in whatever state they were prior to the occurrence of this input condition.
2. SET=1, RESET=0: This will always set  $Q=1$ , where it will remain even after SET returns to 0.
3. SET=0, RESET=1: This will always reset  $Q=0$ , where it will remain even after RESET returns to 0.
4. SET=1, RESET=1: This condition tries to SET & RESET the latch at the same, & it produces  $Q=\bar{Q}=0$ ; if the i/p are returned to zero simultaneously, the resulting o/p state is erratic & unpredictable. This o/p condition should not be used if it is forbidden (invalid).






Logic Diagram

J	K	S	R	Q <sub>n</sub>	Q <sub>n+1</sub>	State
0	0	0	0	0	0	no change
0	0	0	0	1	1	
0	1	0	0	0	0	Reset (0)
0	1	0	1	1	0	
1	0	1	0	0	1	Set (1)
1	0	0	0	1	1	
1	1	1	0	0	1	Complement (Q <sub>n</sub> )
1	1	0	1	1	0	

Truth Table

### D latch

 


logic diagram

D	Q <sub>n</sub>	Q <sub>n+1</sub>
0	0	0
0	1	0
1	0	1
1	1	1

Truth table

### T-latch

 

logic diagram

T	Q <sub>n</sub>	Q <sub>n+1</sub>
0	0	0
0	1	1
1	0	1
1	1	0

Truth table

### SR Flip Flop

$Q_n$	$Q_{n+1}$	$S$	$R$
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

### JK Flip Flop

$Q_n$	$Q_{n+1}$	$J$	$K$
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

### D Flip Flop

$Q_n$	$Q_{n+1}$	$D$
0	0	0
0	1	1
1	0	0
1	1	1

### T Flip Flop

$Q_n$	$Q_{n+1}$	$T$
0	0	0
0	1	1
1	0	1
1	1	0

For the design of sequential circuits we should know the excitation tables of Flip Flops. The excitation table of a Flip Flop can be obtained from its truth table. It indicates the inputs required to be applied to the flip-flop to take it from the present state to the next state. The truth tables & excitation tables of various flip-flops are given above.

To convert one type of flip-flop into another type, a Combinational circuit is designed such that if the inputs of the required flip-flop (along with the o/p of the actual flip-flop if required) are fed as i/p's to the combinational circuit and the output of the combinational circuit is connected to the inputs of the actual flip-flop, then ~~the~~ the o/p of the actual flip-flop is the o/p of the required flip-flop. In other words, it means that, to convert one type of flip-flop into another type, we have to obtain the expressions for the i/p's of the existing flip-flop in terms of the i/p's of the required flip-flop & the present state variable of the existing flip-flop & implement them. The arrangement is shown in Fig 1.

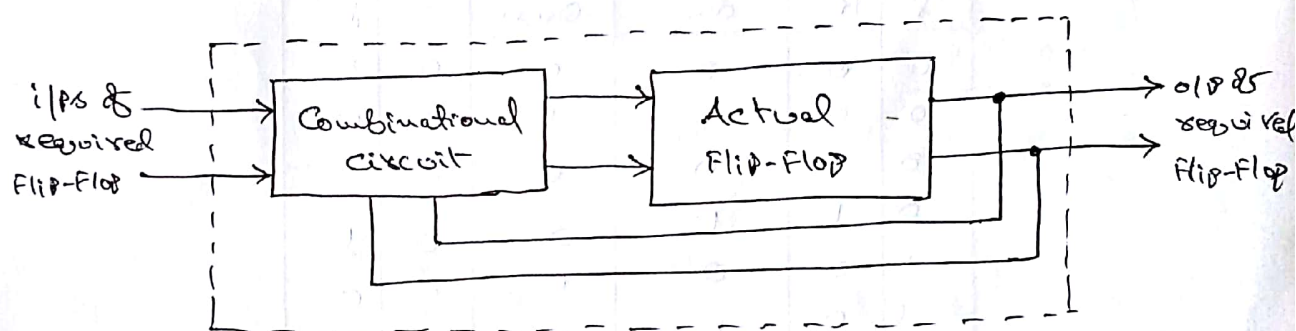


Fig 1- Block diagram for conversion of flip-flop.

### S-R Flip-Flop to J-K Flip-Flop:-

Here the External i/p's to the already available S-R Flip-Flop will be J and K. S and R are the o/p's of the Combinational circuit, which are also the actual i/p's to the S-R flip-flop. We write a truth table with J, K,  $Q_n$ ,  $Q_{n+1}$ , S, and R, where  $Q_n$  is the present state of the flip-flop &  $Q_{n+1}$  is the next state obtained when the particular J & K i/p's are applied, i.e.,  $Q_n$  denotes the state of the flip-flop before the application of the i/p's &  $Q_{n+1}$  refers to the state obtained by the flip-flop after the application of i/p's.



$Q_{n+1}$ , i.e. determine to which next state ( $Q_{n+1}$ ) the JK Flip Flop will go from the present state  $Q_n$  if the present inputs J & K are applied. Now Complete the table by writing the values of S & R required to get each  $Q_{n+1}$  from the corresponding  $Q_n$ , i.e. write what values of S & R are required to change the state of the Flip-Flop from  $Q_n$  to  $Q_{n+1}$ .

The Conversion table, the K-maps for S & R in terms of J, K &  $Q_n$  and the logic diagram showing the Conversion from S-R to J-K are shown in Fig-2

External inputs		Present State	Next State	Flip-Flop inputs.	
J	K	$Q_n$	$Q_{n+1}$	S	R
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	X	0
1	1	0	1	1	0
1	1	1	0	0	1

Conversion table

J \ K $Q_n$	00	01	11	10
0		X		
1	1	X		1

$$S = J\bar{Q}_n$$

J \ K $Q_n$	00	01	11	10
0	X		1	X
1			1	

$$R = KQ_n$$

K-maps for S & R

 


Fig-2



logic diagram

Here S-R flip flop is available & we want the operation of the D flip flop from it. So D is the external input & the outputs of the Combinational circuit are the inputs to the available S-R flip-flop. Express the inputs of the existing flip-flop S & R in terms of the external input D & the present state  $Q_n$ .


The conversion table, the K-maps for S & R in terms of D &  $Q_n$ , and the logic diagram showing the conversion from S-R to D are shown below figs.

External inputs	Present state	Next state	FlipFlop inputs.	
D	$Q_n$	$Q_{n+1}$	S	R
0	0	0	0	X
0	1	0	0	1
1	0	1	1	0
1	1	1	X	0

Conversion table

  

$$S = D$$

 

$$R = \bar{D}$$

K-maps for S & R

Fig-3

### J-K flip flop to T flip-flop:-


Here J-K flip flop is available & we want T flip-flop operation from it. So T is the external input & J & K are the actual inputs to the existing Flip-Flop. T &  $Q_n$  make four combinations. Express J & K in terms of T and  $Q_n$ .

The conversion table, the K-maps for J & K in terms of T &  $Q_n$ , & the logic diagram showing the conversion from J-K to T are shown in fig 4.




External Input	Present State	Next State	Flip-Flop inputs	
T	$Q_n$	$Q_{n+1}$	J	K
0	0	0	0	X
0	1	1	X	0
1	0	1	1	X
1	1	0	X	1

Conversion Table

 


$$J = T$$

 

$$K = T$$

K-maps for J &amp; K

 

Logic diagram

Fig 4: Conversion of JK flip flop to T Flip Flop

### SSI Latches & FlipFlops:

Several types of discrete latches & FlipFlops are available as SSI parts. SSI latches and FlipFlops have been eliminated to a large extent in modern designs as their functions are embedded in PLDs & FPGAs.

Fig-5 Shows the pinouts for several SSI sequential devices. The only latch in the figure is the 74x375, which contains four D latches, similar in function to the "generic" D latches. Because of pin limitation, the latches are arranged in pairs with a common  $\bar{C}$  control line for each pair.



Among the devices in Fig 5, the most important is the 74x74, which contains two independent positive-edge triggered D-flip flops with preset & clear inputs.

The 74x109 is a positive-edge-triggered J-K flip flop with an active low input (named  $\bar{K}$  or K-L). Another J-K flip flop is the 74x112, which has an active low clock input.

 


Fig 5: pinouts for SSI latches & flip flops

Ring Counter: This is the simplest Shift Register Counter. The basic ring counter using D FFs is shown in Fig 6. The realization of this counter using J-K FFs is shown in Fig 7. Its state diagram & the sequence table shown in Fig 8. Its timing diagram is shown in Fig 9. The flipflops are arranged as in a normal shift register, i.e., the Q out of each stage is connected to the D input of the next stage, but the Q out of the last FF is connected back to the D input of the first FlipFlop such that the array of FlipFlops is arranged in a ring & therefore, the name "Ring Counter".

 


Fig:6 Logic diagram of a 4-bit Ring Counter using D-FlipFlops


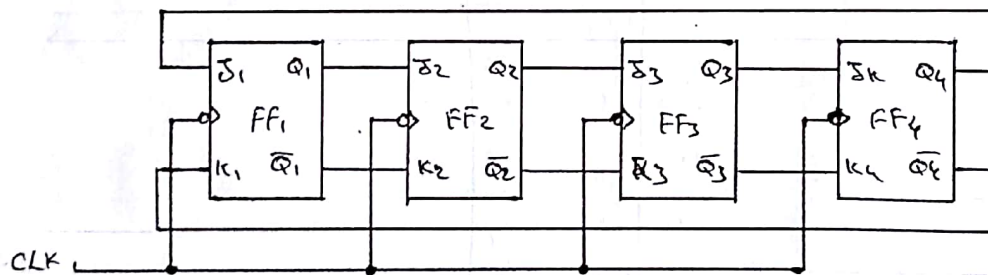


Fig:7 Logic diagram of a 4-bit Ring Counter using J-K FlipFlops

 

State diagram

Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Q <sub>4</sub>	After Clock
1	0	0	0	0
0	1	0	0	1
0	0	1	0	2
0	0	0	1	3
1	0	0	0	4
0	1	0	0	5
0	0	1	0	6
0	0	0	1	7

Sequence Table

Fig:8 State diagram & sequence table



 


Fig 8: Timing diagram of a 4-bit ring counter.

In most instances, only a single 1 is in the register and is made to circulate around the register as long as clock pulses are applied. Initially, the first FF is preset to a 1. So, the initial state is 1000, i.e.,  $Q_1=1$ ,  $Q_2=0$ ,  $Q_3=0$ , &  $Q_4=0$ . After each clock pulse, the contents of the register are shifted to the right by one bit and  $Q_4$  is shifted back to  $Q_1$ . The sequence repeats after four clock pulses. The most distinct states in the ring counter, i.e., the modulus of the ring counter is equal to the number of FFs used in the counter. An  $n$ -bit ring counter can count only  $n$  bits, whereas an  $n$ -bit ripple counter can count  $2^n$  bits. So, the ring counter ~~can count only  $n$  bits~~ is uneconomical compared to a ripple counter, but has the advantage of requiring no decoder, since we can read the count by simply noting which FF is set. Since it is entirely a synchronous operation & requires no gates external to FFs, it has the ~~number~~ further advantage of being very fast.

### Johnson Counter: (Twisted ring counter)

This counter is obtained from a serial-in, serial-out shift register by providing feedback from the inverted output of the last FF to the input of the first FF. The Q output of each stage is connected to the D input of the next stage, but the Q output of the last stage is connected to the D input of the first stage, therefore, the



The logic diagram of a 4-bit Johnson Counter using DFFs is shown in Fig 10. The realization of the same using JK FFs is shown in Fig 11. The state diagram and the sequence table are shown in Fig 12. The timing diagram of a Johnson Counter is shown in Fig 13.

 


Fig 10: logic diagram of a 4-bit twisted ring counter using D FFs


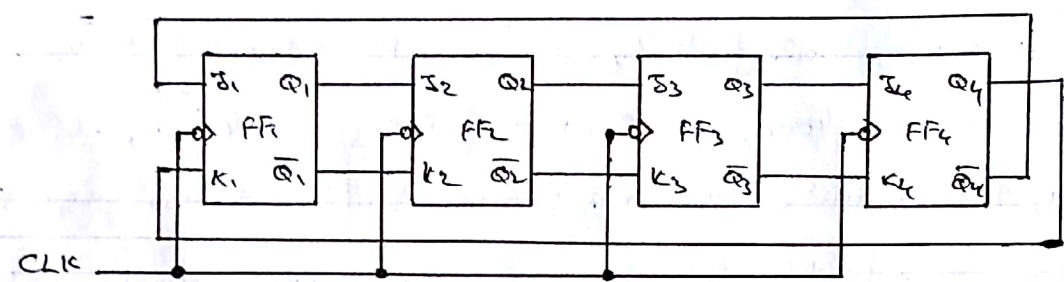


Fig 11: logic diagram of a 4-bit twisted ring counter using JK FFs

 

State diagram

Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Q <sub>4</sub>	After Clock
0	0	0	0	0
1	0	0	0	1
1	1	0	0	2
1	1	1	0	3
1	1	1	1	4
0	1	1	1	5
0	0	1	1	6
0	0	0	1	7
0	0	0	0	8
1	0	0	0	9

Sequence table

Fig 12: State diagram and sequence table of a Johnson Counter

Let initially all the FFs be reset, i.e., the state of the counter be 0000. After each clock pulse, the level of Q<sub>1</sub> is shifted to Q<sub>2</sub>, the level of Q<sub>2</sub> to Q<sub>3</sub>, Q<sub>3</sub> to Q<sub>4</sub> and the level of  $\bar{Q}_4$  to Q<sub>1</sub> and the sequence given in Fig 12 is obtained. This sequence is repeated after every eight clock pulses.

 


Fig 13: Timing diagram of a 4-bit twisted ring counter

An  $n$  FF Johnson Counter can have  $2n$  unique states & can count up to  $2n$  pulses. So it is a mod- $2n$  counter. It is more economical than the normal ring counter, but less economical than the ripple counter. It requires two 1/2 gates for decoding regardless of the size of the counter. Thus, it requires more decoding circuitry than that by the normal ring counter, but less than that by the ripple counter. It represents a middle ground between the ring counter & the ripple counter.

### Basic Sequential Logic Design Steps

The procedure for designing synchronous sequential circuits can be summarized by a list of recommended steps.

1. From the word description & specifications of the desired operation, derive a state diagram for the circuit.
2. Reduce the number of states if necessary.
3. Assign binary values to the states.
4. Obtain the binary-coded state table.
5. Choose the type of flip-flops to be table.
6. Derive the simplified flip-flop input equations & o/p equations.
7. Draw the logic diagram.



## DESIGN OF COUNTERS USING DIGITAL ICs

→ IC 7490 (Decade Binary Counter)

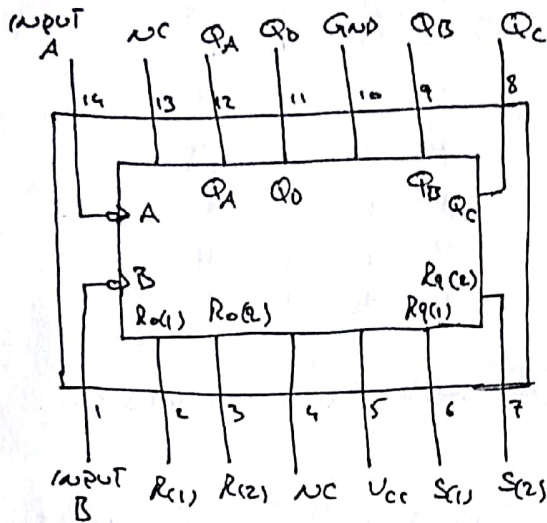


Fig: Connection diagram for 7490

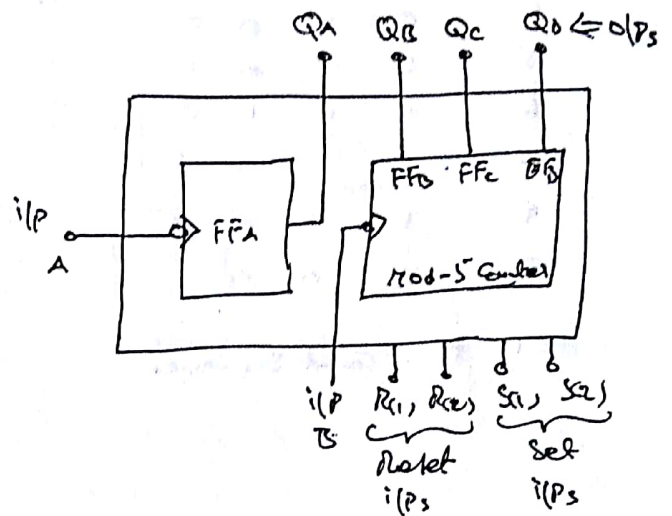


Fig: Basic internal structure of 7490

IC 7490 is a decade binary counter. It consists of four master-slave flip-flops & additional gating to provide a divide by two counter & a three stage binary counter for which the count length is divide-by-five.

Since the o/p from the divide by two section is not internally connected to the succeeding stages, the devices may be operated in various counting modes.

1. BCD Decade (8421) Counter: The B i/p must be externally connected to the QA o/p & A i/p receives the incoming count.
2. Symmetrical Bi-quinary Divide-by-Ten Counter: The QB o/p must be externally connected to the A i/p. The i/p count is then applied to the B i/p & a ~~1/10~~  $\div 10$  square wave is obtained at o/p QA.
3.  $\div 2$  &  $\div 5$  Counter: No external interconnecting are required.

The first FF is used as a binary element for the  $\div 2$  function. The B i/p is used to obtain binary divide by five operation at the QA o/p.



Count	$Q_A$	$Q_C$	$Q_B$	$Q_A$
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

Table 1: BCD Count Sequence

INPUT	QA	QB	QC	QD
0	L	L	L	L
1	L	L	L	H
2	L	L	H	L
3	L	L	H	H
4	L	H	L	L
5	H	L	L	L
6	H	L	L	H
7	H	L	H	L
8	H	L	H	H
9	H	H	L	L

Table 2: BCD Bi-Quinary (5-2)


 


Fig: Logic Diagram Ex 7490

<u>Reset i/p's</u>				<u>outputs</u>			
$R_Q(1)$	$R_Q(2)$	$R_Q(1)$	$R_Q(2)$	$Q_D$	$Q_C$	$Q_B$	$Q_A$
H	H	L	X	L	L	L	L
H	H	X	L	L	L	L	L
X	X	H	H	H	L	L	H
X	L	X	L		COUNT		
L	X	L	X		COUNT		
L	X	X	L		COUNT		
X	L	L	X		COUNT		

Table Reset/ count function table

$\Rightarrow$  MOD-20 Counter:

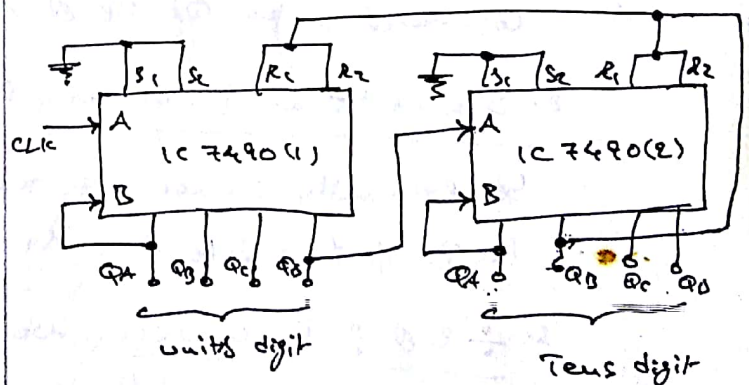

Divide by 20 Counter using 10 7490



The 7492 & 7493 are high speed 4-bit ripple type counters Partitioned into two sections. Each Counter has a divide-by-two section & either a divide-by-six (7492) or divide-by-eight (7493) section which are triggered by a High to low transition on the clock I/p.s. Each section can be used separately or tied together to form divide-by-twelve or divide-by-sixteen counters.

7492  $\rightarrow \div 12$  counter

7493  $\rightarrow \div 16$  counter

Each device consists of four master slave Flip Flops which are internally connected to provide a  $\div 2$  section.


7492:

  

Notes of 7492

- Mod-12: The B i/p must be Externally connected to two Q's of p. The A i/p receives the incoming count & Q0 produces a symmetrical  $\div 12$  square wave of p.
- $\div 2$  &  $\div 6$ : no External internal - connections are required, The first FF is used as a binary counter for the  $\div 2$  for. The B i/p is used to obtain the  $\div 3$  operation that the Q3 & Q0 o/p.s. & divided by six operation of the Q0 o/p.

7493

 



12	10	11	12
13	11	12	13
14	12	13	14
15	13	14	15
16	14	15	16
17	15	16	17

www.FirstRanker.com. The output must be externally connected to i/p 8. The i/p count pulses are applied to the i/p 1. Simultaneously divisions of 2, 4, 8 & 16 are performed at the Q<sub>A</sub>, Q<sub>B</sub>, Q<sub>C</sub> & Q<sub>D</sub> of 7493 as shown in the truth table.

2. 3-bit Ripple Counter: The i/p count pulses are applied to i/p A. Simultaneously frequency divisions of 2, 4, & 8 are available at the Q<sub>B</sub>, Q<sub>C</sub> & Q<sub>D</sub> with respect to the 3-bit ripple through counter.

7492 & 7493

Reset i/p		OBS			
R <sub>1</sub>	R <sub>2</sub>	Q <sub>A</sub>	Q <sub>B</sub>	Q <sub>C</sub>	Q <sub>D</sub>
H	H	L	L	L	L
L	H	Count			
H	L	Count			
L	L	Count			

7492

7493

Count	Q <sub>A</sub>	Q <sub>B</sub>	Q <sub>C</sub>	Q <sub>D</sub>	Count	Q <sub>A</sub>	Q <sub>B</sub>	Q <sub>C</sub>	Q <sub>D</sub>
0	L	L	L	L	0	L	L	L	L
1	H	L	L	L	1	H	L	L	L
2	L	H	L	L	2	L	H	L	L
3	H	H	L	L	3	H	H	L	L
4	L	L	H	L	4	L	L	H	L
5	H	L	H	L	5	H	L	H	L
6	L	L	L	H	6	L	L	H	L
7	H	L	L	H	7	H	L	H	L
8	L	H	L	H	8	L	H	L	H
9	H	H	L	H	9	H	H	L	H
10	L	L	H	H	10	L	L	H	H
11	H	L	H	H	11	H	L	H	H
					12	L	L	H	H
					13	H	L	H	H
					14	L	H	H	H
					15	H	H	H	H



## UNIT-6

### **Synchronous and Asynchronous Sequential Circuits**

#### **6.1 BASIC DESIGN STEPS**

The circuit has one input,  $w$ , and one output,  $z$ .

All changes in the circuit occur on the positive edge of a clock signal.

The output  $z$  is equal to 1 if during two immediately preceding clock cycles the input  $w$  was equal to 1. Otherwise, the value of  $z$  is equal to 0.

Thus, the circuit detects if two or more consecutive 1s occur on its input  $w$ . Circuits that detect the occurrence of a particular pattern on its input(s) are referred to as *sequence detectors*.

From this specification it is apparent that the output  $z$  cannot depend solely on the present value of  $w$ . To illustrate this, consider the sequence of values of the  $w$  and  $z$  signals during 11 clock cycles, as shown in Figure 8.2. The values of  $w$  are assumed arbitrarily; the values of  $z$  correspond to our specification. These sequences of input and output values indicate that for a given input value the output may be either 0 or 1. For example,  $w = 0$  during clock cycles  $t_2$  and  $t_5$ , but  $z = 0$  during  $t_2$  and  $z = 1$  during  $t_5$ . Similarly,  $w = 1$  during  $t_1$  and  $t_8$ , but  $z = 0$  during  $t_1$  and  $z = 1$  during  $t_8$ . This means that  $z$  is not determined only by the present value of  $w$ , so there must exist different states in the circuit that determine the value of  $z$ .

#### **6.2 STATE DIAGRAM**

The first step in designing a finite state machine is to determine how many states are needed and which transitions are possible from one state to another. There is no set procedure for this task. The designer must think carefully about what the machine has to accomplish. A good way to begin is to select one particular state as a *starting* state; this is the state that the circuit should enter when power is first turned on or when a *reset* signal is applied. For our example let us assume that the starting state is called state  $A$ . As long as the input  $w$  is 0, the circuit need not do anything, and so each active clock edge should result in the circuit remaining in state  $A$ . When  $w$  becomes equal to 1, the machine should recognize this, and move to a different state, which we will call state  $B$ . This transition takes place on the next active clock edge

after  $w$  has become equal to 1. In state  $B$ , as in state  $A$ , the circuit should keep the value of output  $z$  at 0, because it has not yet seen  $w = 1$  for two consecutive clock cycles. When in state  $B$ , if  $w$  is 0 at the next active clock edge, the circuit should move back to state  $A$ . However, if  $w = 1$  when in state  $B$ , the circuit should change to a third state, called  $C$ , and it should then generate an output  $z = 1$ . The circuit should remain in

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0

**Figure 6.2** Sequences of input and output signals.

state  $C$  as long as  $w = 1$  and should continue to maintain  $z = 1$ . When  $w$  becomes 0, the machine should move back to state  $A$ . Since the preceding description handles all possible values of input  $w$  that the machine can encounter in its various states, we can conclude that three states are needed to implement the desired machine.


Now that we have determined in an informal way the possible transitions between states, we will describe a more formal procedure that can be used to design the corresponding sequential circuit. Behavior of a sequential circuit can be described in several different ways. The conceptually simplest method is to use a pictorial representation in the form of a *state diagram*, which is a graph that depicts states of the circuit as nodes (circles) and transitions between states as directed arcs. The state diagram in Figure 8.3 defines the behavior that corresponds to our specification. States  $A$ ,  $B$ , and  $C$  appear as nodes in the diagram. Node  $A$  represents the starting state, and it is also the state that the circuit will reach *after* an input  $w = 0$  is applied. In this state the output  $z$  should be 0, which is indicated as  $A/z=0$  in the node. The circuit should remain in state  $A$  as long as  $w = 0$ , which is indicated by an arc with a label  $w = 0$  that originates and terminates at this node. The first occurrence of  $w = 1$  (following the condition  $w = 0$ ) is recorded by moving from state  $A$  to state  $B$ . This transition is indicated on the graph by an arc originating at  $A$  and terminating at  $B$ . The label  $w = 1$  on this arc denotes the input value that causes the transition. In state  $B$  the output remains at 0, which is indicated as  $B/z=0$  in the node.

---

When the circuit is in state  $B$ , it will change to state  $C$  if  $w$  is still equal to 1 at the next active clock edge. In state  $C$  the output  $z$  becomes equal to 1. If  $w$  stays at 1 during subsequent clock

cycles, the circuit will remain in state *C* maintaining  $z = 1$ . However, if  $w$  becomes 0 when the circuit is either in state *B* or in state *C*, the next active clock edge will cause a transition to state *A* to take place.

In the diagram we indicated that the *Reset* input is used to force the circuit into state *A*, which is possible regardless of what state the circuit happens to be in. We could treat

 

**Figure 6.3** State diagram of a simple sequential circuit

*Reset* as just another input to the circuit, and show a transition from each state to the starting state *A* under control of the input *Reset*. This would complicate the diagram unnecessarily. States in a finite state machine are implemented using flip-flops.



## 6.3 STATE TABLE

Although the state diagram provides a description of the behavior of a sequential circuit that is easy to understand, to proceed with the implementation of the circuit, it is convenient to translate the information contained in the state diagram into a tabular form. Figure 8.4 shows the *state table* for our sequential circuit. The table indicates all transitions from each *present state* to the *next state* for different values of the input signal. Note that the output  $z$  is specified with respect to the present state, namely, the state that the circuit is in at present time. Note also that we did not include the *Reset* input; instead, we made an implicit assumption that the first state in the table is the starting state.

We now show the design steps that will produce the final circuit. To explain the basic design concepts, we first go through a traditional process of manually performing each design step. This is followed by a discussion of automated design techniques that use modern computer aided design (CAD) tools.


## 6.4 STATE ASSIGNMENT

The state table in Figure 8.4 defines the three states in terms of letters  $A$ ,  $B$ , and  $C$ . When implemented in a logic circuit, each state is represented by a particular valuation (combination of values) of *state variables*. Each state variable may be implemented in the form of a flip-flop. Since three states have to be realized, it is sufficient to use two state variables. Let these variables be  $y_1$  and  $y_2$ .

Now we can adapt the general block diagram in Figure 6.5 to our example as shown in Figure 6.5, to indicate the structure of the circuit that implements the required finite state machine. Two flip-flops represent the state variables. In the figure we have not specified the type of flip-flops to be used; this issue is addressed in the next subsection.

Present state	Next state		Output  Z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	C	1

**Figure 6.4** State table for the sequential circuit

 

The signals  $y_1$  and  $y_2$  are also fed back to the combinational circuit that determines the next state of the FSM. This circuit also uses the primary input signal  $w$ . Its outputs are two signals,  $Y_1$  and  $Y_2$ , which are used to set the state of the flip-flops. Each active edge of the clock will cause the flip-flops to change their state to the values of  $Y_1$  and  $Y_2$  at that time. Therefore,  $Y_1$  and  $Y_2$  are called the *next-state variables*, and  $y_1$  and  $y_2$  are called the *present-state variables*. We need to design a combinational circuit with inputs  $w$ ,  $y_1$ , and  $y_2$ , such that for all valuations of these inputs the outputs  $Y_1$  and  $Y_2$  will cause the machine to move to the next state that satisfies our specification. The next step in the design process is to create a truth table that defines this circuit, as well as the circuit that generates  $z$ .

[www.FirstRanker.com](http://www.FirstRanker.com)



## 6.5 CHOICE OF FLIP-FLOPS AND DERIVATION OF NEXT-STATE AND OUTPUT EXPRESSIONS

From the state-assigned table in Figure 8.6, we can derive the logic expressions for the next-state and output functions. But first we have to decide on the type of flip-flops that will be used in the circuit. The most straightforward choice is to use D-type flip-flops, because in this case the values of  $Y_1$  and  $Y_2$  are simply clocked into the flip-flops to become the new values of  $y_1$  and  $y_2$ . In other words, if the inputs to the flip-flops are called  $D_1$  and  $D_2$ , then these signals are the same as  $Y_1$  and  $Y_2$ . Note that the diagram in Figure 8.5 corresponds exactly to this use of D-type flip-flops. For other types of flip-flops, such as JK type, the relationship between the next-state variable and inputs to a flip-flop is not as straightforward; we will consider this situation in section 8.7.

The required logic expressions can be derived as shown in Figure 8.7. We use Karnaugh maps to make it easy for the reader to verify the validity of the expressions. Recall that in Figure 8.6 we needed only three of the four possible binary valuations to represent the states. The fourth valuation,  $y_2y_1 = 11$ , should never occur in the circuit because the circuit is constrained to move only within states  $A$ ,  $B$ , and  $C$ ; therefore, we may choose to treat this valuation as a don't-care condition. The resulting don't-care squares in the Karnaugh maps are denoted by d's. Using the don't cares to simplify the expressions, we obtain

$$Y_1 = w y_1 y_2$$

$$Y_2 = w(y_1 + y_2)$$


$$z = y_2$$

Since  $D_1 = Y_1$  and  $D_2 = Y_2$ , the logic circuit that corresponds to the preceding expressions is implemented as shown in Figure 8.8. Observe that a clock signal is included, and the circuit is provided with an active-low reset capability. Connecting the clear input on the flip-flops to an external *Resetn* signal, as shown in the figure, provides a simple means

for forcing the circuit into a known state. If we apply the signal  $Resetn = 0$  to the circuit, then both flip-flops will be cleared to 0, placing the FSM into the state  $y_2y_1 = 00$ .
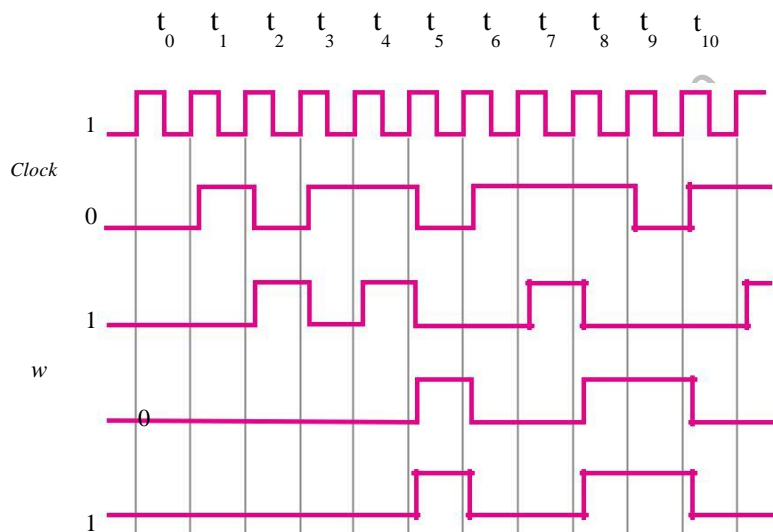
## 6.6 TIMING DIAGRAM

we are using positive-edge-triggered flip-flops, all changes in the signals occur shortly after the positive edge of the clock. The amount of delay from the clock edge depends on the propagation delays through the flip-flops. Note that the input signal  $w$  is also shown to change slightly after the active edge of the clock. This is a good assumption because in a typical digital system an input such as  $w$  would be just an output of another circuit that is synchronized by the same clock.



## 8.2 STATE-ASSIGNMENT PROBLEM

The basic concepts involved in the design of sequential circuits, we should revisit some details where alternative choices are possible. In section 6.1 we suggested that some state assignments may be better than others. To illustrate this we can reconsider the example in Figure 8.4. We already know that the state assignment in Figure 6.6 leads to a simple-looking circuit in Figure 8.8. But can the FSM of Figure 6.4 be implemented with an even simpler circuit by using a different state assignment.

In general, circuits are much larger than our example, and different state assignments can have a substantial effect on the cost of the final implementation. While highly desirable, it is often impossible to find the best state assignment for a large circuit. The exhaustive approach of trying all possible state assignments is not practical because the number of available state assignments is huge. CAD tools usually perform the state assignment using heuristic techniques. These techniques are usually proprietary, and their details are seldom published.

## 6.8 ONE-HOT ENCODING

Another interesting possibility is to use as many state variables as there are states in a sequential circuit. In this method, for each state all but one of the state variables are equal to 0. The variable whose value is 1 is deemed to be “hot.” The approach is known as the *one-hot encoding* method.

## 6.9 VHDL CODE FOR MOORE-TYPE FSMS

VHDL does not define a standard way of describing a finite state machine. Hence while adhering to the required VHDL syntax, there is more than one way to describe a given FSM. An example of VHDL code for the FSM of Figure 8.3 is given in Figure 8.29. For the convenience of discussion, the lines of code are numbered on the left side. Lines 1 to 6 declare an entity named *simple*, which has input ports *Clock*, *Resetn*, and *w*, and output port *z*. In line 7 we have used the name *Behavior* for the architecture body, but of course, any valid VHDL name could be used instead.

The TYPE keyword, which is a feature of VHDL that we have not used previously. The TYPE keyword allows us to create a user-defined signal type. The new signal type is named *State\_type*, and the code specifies that a signal of this type can have three possible values: *A*, *B*, or *C*. Line 9 defines a signal named *y* that is of the *State\_type* type. The *y* signal is used in the architecture body to represent the outputs of the flip-flops that implement the states in the FSM. The code does not specify the number of bits represented by *y*. Instead, it specifies that *y* can have the three symbolic values *A*, *B*, and *C*. This means that we have not specified the number of state flip-flops that should be used for the FSM. As we will see below, the VHDL compiler automatically chooses an appropriate number of state flip-flops when synthesizing a circuit to implement the machine. It also chooses the state assignment for states *A*, *B*, and *C*. Some CAD systems, such as Quartus II, assume that the first state listed in the TYPE statement (line 8) is the reset state for the machine. The state assignment that has all flip-flop outputs equal to 0 is used for this state. Later in this section, we will show



```
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
--
ENTITY simple IS
    PORT ( Clock, Resetn,
4      w      : IN  STD LOGIC ;
          : STD LOGIC )
5      Z      : OUT ; --
          :
END simple ;

ARCHITECTURE Behavior OF simple IS
    TYPE State type IS (A, B, C) ;
    SIGNAL y : State type ;
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
14      y <= A ;
        ELSIF (Clock'EVENT AND Clock = '1')
15      THEN
16      CASE y IS
17      WHEN A <=
18      IF w = '0' THEN
19      y <= A ;
```

```
20             ELSE
21                 y < B ;
22             END IF ;
23         WHEN B >
24             IF w = '0' THEN
25                 y < A ;
26             ELSE
27                 y < C ;
28             END IF ;
29         WHEN C >
30             IF w = '0' THEN
31                 y < A ;
32             ELSE
33                 y < C ;
34             END IF ;
35         END CASE ;
36
37     END IF ;
38
39     END PROCESS ;
40
41     z < '1' WHEN y = C ELSE '0' ;
42
43     END Behavior ;
```

## 6.9 SPECIFYING THE STATE ASSIGNMENT IN VHDL CODE

That the state assignment may have an impact on the complexity of the designed circuit. An obvious objective of the state-assignment process is to minimize the cost of implementation. The cost function that should be optimized may be simply the number of gates and flip-flops. But it could also be based on other considerations that may be representative of the structure of PLD chips used to implement the design. For example, the CAD software may try to find state

encodings that minimize the total number of AND terms needed in the resulting circuit when the target chip is a CPLD.

In VHDL code it is possible to specify the state assignment that should be used, but there is no standardized way of doing so. Hence while adhering to VHDL syntax, each CAD system permits a slightly different method of specifying the state assignment. The Quartus II system recommends that state assignment be done by using the attribute feature of VHDL. An *attribute* refers to some type of information about an object in VHDL code. All signals automatically have a number of associated *predefined* attributes. An example is the EVENT attribute that we use to specify a clock edge, as in Clock'EVENT.

In addition to the predefined attributes, it is possible to create a user-defined attribute. The *user-defined* attribute can be used to associate some desired type of information with an object in VHDL code. In Quartus II manual state assignment can be done by creating a user-defined attribute associated with the State\_type type. This is illustrated in Figure 8.34, which shows the first few lines of the architecture from Figure 8.33 with the addition of a user-defined attribute. We first define the new attribute called ENUM\_ENCODING, which has the type STRING. The next line associates ENUM\_ENCODING with the State\_type type and specifies that the attribute has the value "00 01 11". When translating the VHDL code, the Quartus II compiler uses the value of ENUM\_ENCODING to make the state assignment  $A = 00$ ,  $B = 01$ , and  $C = 11$ .

ARCHITECTURE Behavior OF simple IS

```
TYPE State TYPE IS (A, B, C) ;
-
ATTRIBUTE ENUM_ENCODING          : STRING ;
-
ATTRIBUTE ENUM_ENCODING OF State type : TYPE IS "00 01 11" ;
-
SIGNAL y present, y next          : State type ;
-
BEGIN
.
.
.
```



**Figure 8.34** A user-defined attribute for manual state assignment.

[www.FirstRanker.com](http://www.FirstRanker.com)

```

LIBRARY ieee ;

USE ieee.std logic 1164.all
;

ENTITY simple IS
    PORT ( Clock, Resetn,
          w          : INSTD LOGIC ;
          -          -
          -          : OUT STD LOGIC )
          Z          ;
END simple ;

ARCHITECTURE Behavior OF simple IS

    SIGNAL y presentz, y next : STD LOGIC VECTOR(1 DOWNT0
0);
    - - - -

    CONSTANT A : STD LOGIC VECTOR(1 DOWNT0 0) :    "00";
    -

    CONSTANT B : STD LOGIC VECTOR(1 DOWNT0 0) :    "01";
    -

    CONSTANT C : STD LOGIC VECTOR(1 DOWNT0 0) :    "11";
    -

BEGIN

    PROCESS ( w, y present )
    -

    BEGIN

        CASE y present IS
        -

        WHEN A >

            IF w = '0' THEN y next < A ;
  
```

```

                                -
ELSE y next < B ;
                                -
END IF ;
WHEN B >

    IF w  '0' THEN y next < A ;
                                -
    ELSE y next < C ;
                                -
    END IF ;
WHEN C >

    IF w  '0' THEN y next < A ;
                                -
    ELSE y next < C ;
                                -
    END IF ;
WHEN OTHERS >
    y next < A ;
END CASE ;

END PROCESS ;

PROCESS ( Clock, Resetn )

BEGIN

IF Resetn                                '0'
                                THEN

    y present <                                A ;
                                -

ELSIF (Clock'EVENT AND Clock                                '1') THEN

```



```
        y present < y next ;  
        -           -  
    END IF ;  
  
    END PROCESS ;  
  
    z < '1' WHEN y present C ELSE '0' ;  
        -  
    END Behavior ;
```

[www.FirstRanker.com](http://www.FirstRanker.com)

## 6.10 SPECIFICATION OF MEALY FSMS USING VHDL

A Mealy-type FSM can be specified in a similar manner as a Moore-type FSM. Figure 8.36 gives complete VHDL code for the FSM in Figure 8.23. The state transitions are described in the same way as in our original VHDL example in Figure 8.29. The signal  $y$  represents the state flip-flops, and `State_type` specifies that  $y$  can have the values  $A$  and  $B$ . Compared to the code in Figure 8.29, the major difference in the case of a Mealy-type FSM is the way in which the code for the output is written. In Figure 8.36 the output  $z$  is defined using a CASE statement. It states that when the FSM is in state  $A$ ,  $z$  should be 0, but when in state  $B$ ,  $z$  should take the value of  $w$ . This CASE statement properly describes the logic needed for  $z$ , but it may not be obvious why we have used a second CASE statement in the code, rather than specify the value of  $z$  inside the CASE statement that defines the state transitions. The reason is that the CASE statement for the state transitions is nested inside the IF statement that waits for a clock edge to occur. Hence if we placed the code for  $z$  inside this CASE statement, then the value of  $z$  could change only as a result of a clock edge. This does not meet the requirements of the Mealy-type FSM, because the value of  $z$  must depend not only on the state of the machine but also on the input  $w$ .

Implementing the FSM specified in Figure 8.36 in a CPLD chip yields the same equations as we derived manually in section 8.3. Simulation results for the synthesized circuit appear in Figure 8.37. The input waveform for  $w$  is the same as the one we used for the Moore-type machine in Figure 8.32. Our Mealy-type machine behaves correctly, with  $z$  becoming 1 just after the start of the second consecutive clock cycle in which  $w$  is 1.

In the simulation results we have given in this section, all changes in the input  $w$  occur immediately following a positive clock edge. This is based on the assumption stated in section 8.1.5 that in a real circuit  $w$  would be synchronized with respect to the clock that controls the FSM. In Figure 8.38 we illustrate a problem that may arise if  $w$  does not meet this specification. In this case we have assumed that the changes in  $w$  take place at the

```
LIBRARY ieee ;

USE ieee.std logic 1164.all
;

ENTITY mealy IS
    PORT ( Clock, Resetn,
          w          : INSTD LOGIC ;
          -          -
          Z          : OUT STD LOGIC )
          ;
END mealy ;

ARCHITECTURE Behavior OF mealy IS

    TYPE State type IS (A, B) ;
    -
    SIGNAL y : State type ;

BEGIN

    PROCESS ( Resetn, Clock )

    BEGIN

        IF Resetn  '0' THEN

            y <= A ;

        ELSIF (Clock'EVENT AND Clock '1')
            THEN CASE y IS

                WHEN A >

                    IF w  '0' THEN y <= A ;
```



```
ELSE y < B ;  
  
END IF ;  
  
WHEN B >  
  
IF w = '0' THEN y < A ;  
  
ELSE y < B ;  
  
END IF ;  
  
END CASE ;  
  
END IF ;  
  
END PROCESS ;  
  
PROCESS ( y, w )  
  
BEGIN  
CASE y IS  
WHEN A >  
  
z < '0' ;  
  
WHEN B >  
  
z < w ;  
  
END CASE ;  
  
END PROCESS ;  
  
END Behavior ;
```