

## **Pulse & Digital Circuits**

---

### **CONTENTS**

<b>S.NO</b>	<b>NAME OF THE TOPIC</b>	<b>Page.no</b>
<b>1.</b>	<b>Linear Wave Shaping</b>	<b>3</b>
<b>2.</b>	<b>Non-Linear Wave Shaping</b>	<b>35</b>
<b>3.</b>	<b>Multi vibrators</b>	<b>61</b>
<b>4.</b>	<b>Sweep Circuits</b>	<b>89</b>
<b>5.</b>	<b>Synchronization and frequency division</b>	<b>118</b>
<b>6.</b>	<b>Logic Gates</b>	<b>130</b>
<b>7.</b>	<b>Blocking Oscillator</b>	<b>147</b>

## Pulse & Digital Circuits

### 1. Linear Wave Shaping

#### SYLLABUS:

High Pass and Low Pass RC Circuits and their Response for Sinusoidal, Step Voltage, Pulse, Square Wave and Ramp Inputs. High Pass RC Circuit as a Differentiator. Low Pass RC Circuit as an Integrator. Attenuators and their application as CRO Probe. RL and RLC Circuits and their response for step input. Ringing circuit.

#### Linear wave shaping:

##### Introduction:

If a circuit is designed with components like R, L and C then it is called linear circuit. When sinusoidal signal is applied, the shape of the signal is preserved at the output with or without change in the amplitude and shape. But a non-sinusoidal signal alters the output when it is transmitted through a linear circuit. The process whereby the form of non-sinusoidal signals such as step, pulse, square wave, ramp and exponential is altered by transmission through a linear network is called linear wave shaping.

#### 1.1 High pass RC circuit:

Consider high pass RC circuit as shown in fig.1 below.

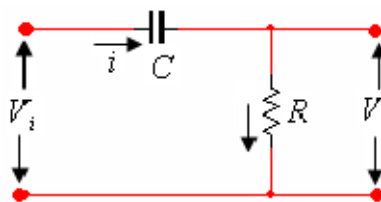


Fig.1 highpass rc circuit

The capacitor offers high reactance at low frequency and low reactance at high frequency. Hence low frequency components are not transmitted, but high frequencies are with less attenuation. Therefore the output is large and the circuit is called a high pass circuit.

Let us see now is, what will be the response if different types of inputs, such as, sinusoidal, step, pulse, square wave, exponential and ramp are applied to a high pass circuit.

## Pulse & Digital Circuits

### 1.2 Response of high pass RC for sinusoidal input:

**(i) sinusoidal input:**

First consider the response of a high pass RC circuit.

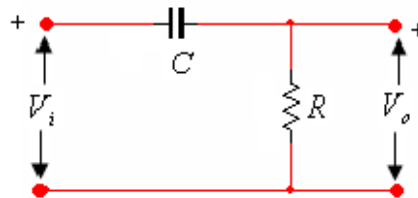


Fig.2 high pass RC circuit

$$V_o = V_i \frac{R}{R + 1/j\omega C}$$

$$\left| \frac{V_o}{V_i} \right| = \frac{R}{\sqrt{R^2 + \left( \frac{1}{\omega C} \right)^2}} = \frac{R}{R \sqrt{1 + \left( \frac{1}{\omega CR} \right)^2}} = \frac{1}{\sqrt{1 + \left( \frac{1}{\omega CR} \right)^2}}$$

$$\text{Let } \omega_1 = \frac{1}{CR}$$

$$\left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{1 + \left( \frac{\omega_1}{\omega} \right)^2}}$$

$$\text{At } \omega = \omega_1$$

$$\left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{2}} = 0.707$$

Hence,  $f_1$  is the lower cut-off frequency of the highpass circuit.

## Pulse & Digital Circuits

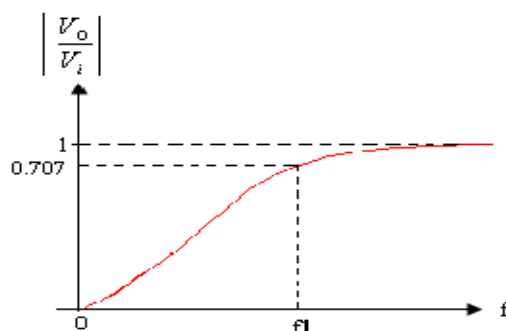


Fig.3 frequency response curve for sinusoidal input.

### 1.3 High Pass RC response for Step signal input.

#### (ii) Step input

A Step voltage is defined as,

$$V_i = 0 \quad \text{for } t < 0$$

and  $V_i = V \quad \text{for } t \geq 0$

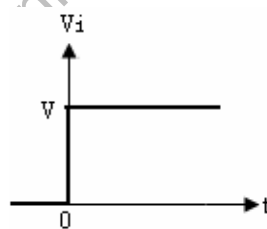


Fig.4 Step Voltage

The output voltage is of the form

$$V_o = B_1 + B_2 e^{-t/\tau}$$

Where  $\tau = RC$ , the time constant of the circuit.

$B_1$  is the steady state value as  $t \rightarrow \infty$ , and hence  $0 \rightarrow V \rightarrow B_1$

Let the final value be which we denote as  $V_f$ .

Then  $V_f = B_1$ .

## Pulse & Digital Circuits

---

B2 is determined by the initial output voltage.

$$\text{At } t = 0, V_i = V_o = B1 + B2$$

$$\text{Therefore, } B2 = V_i - B1$$

$$= V_i - V_f$$

Hence the general solution is

$$V_o = V_f + (V_i - V_f) e^{-t/\tau}$$

**Fall time  $t_f$ :** When a step is applied, the time taken for the output voltage to fall from 90% of its initial value to 10% of its initial value is the fall time. It indicates how fast the output reaches its steady state value.

The output voltage at any instant of time, in high pass circuit, is given by

$$V_o(t) = V e^{-t/\tau}, \quad \text{At } t = t_1, \quad V_o(t_1) = 90\% \text{ of } V = 0.9V$$

$$0.9 = e^{-t_1/\tau}$$

$$e^{t_1/\tau} = 1/0.9 = 1.11$$

$$t_1/\tau = \ln(1.11)$$

$$t_1 = \tau \ln(1.11) = 0.1 \tau$$

$$\text{At } t = t_2, \quad V_o(t) = 10\% \text{ of } V = 0.1V$$

$$0.1 = e^{-t_2/\tau}$$

$$e^{t_2/\tau} = 1/0.1 = 10$$

$$t_2 = \tau \ln(10) = 2.3 \tau$$

$$\text{fall time, } t_f = t_2 - t_1 = 2.3 \tau - 0.1 \tau = 2.2 \tau$$

The lower half power frequency of the highpass circuit is

$$f_1 = \frac{1}{2\pi RC}$$

$$\tau = RC = \frac{1}{2\pi f_1}$$

## Pulse & Digital Circuits

---


$$\text{Fall time} = t_f = 2.2 \tau = \frac{2.2}{2\pi f_1} = \frac{0.35}{f_1}$$

Hence, the fall time is inversely proportional to  $f_1$ , the lower cut-off frequency.

### 1.4 High Pass RC response for Square signal input.

- (iii) **Pulse input:** A pulse can be expressed combination of a positive (negative) step followed by negative(positive) step w.r.t. times i.e.  $V_i = V_u(t) - V_u(t - t_p)$  where  $t_p$  is the duration of the pulse as shown below in fig.5

## Pulse & Digital Circuits

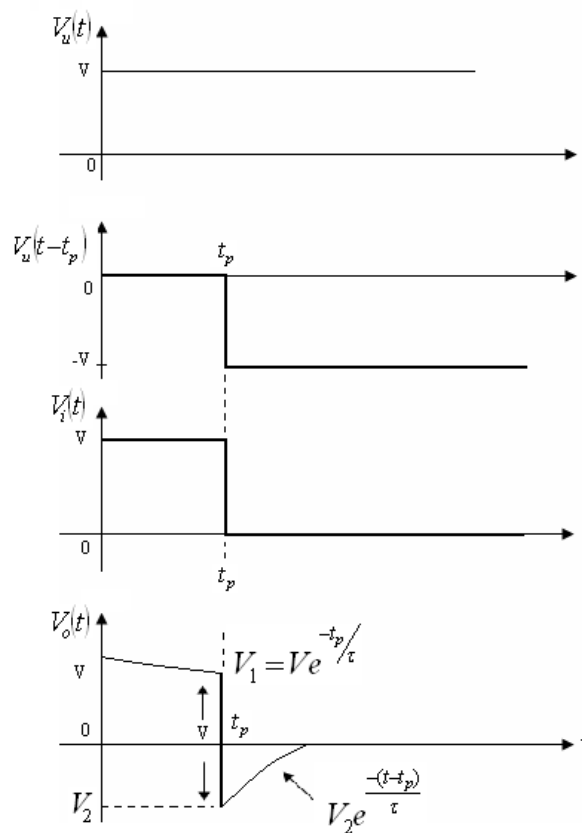

**Fig.5 Pulse input and output of a high pass circuit**

Consider a pulse signal is applied to the input of a high pass circuit.

At  $t=0$ ,  $V_i$  abruptly rises to  $V$ . As the capacitor is connected between the input and output, the output also changes by the same amount. As the input remains constant, the output decays exponentially to  $V_1$  at  $t = t_p$ .

Therefore,  $V_1 = Ve^{-t_p/\tau}$

At  $t = t_p$ , the input abruptly falls by  $V$ .  $V_o$  also falls by the same amount.

At  $t = t_p$ ,  $V_o = V_1 - V$

## Pulse & Digital Circuits

Since  $V_1$  is less than  $V$ ,  $V_o$  is negative and its value is  $V_2$  and this decays to zero exponentially.

For  $t > t_p$ ,


$$V_o = (V_1 - V) e^{-(t-t_p)/\tau}$$

But

$$V_1 = V e^{-t_p/\tau}$$

$$\therefore V_o = V(e^{-t_p/\tau} - 1) e^{-(t-t_p)/\tau}$$

The response of a high pass circuit with pulse input for different values of  $\tau$  is plotted in fig.1.6.

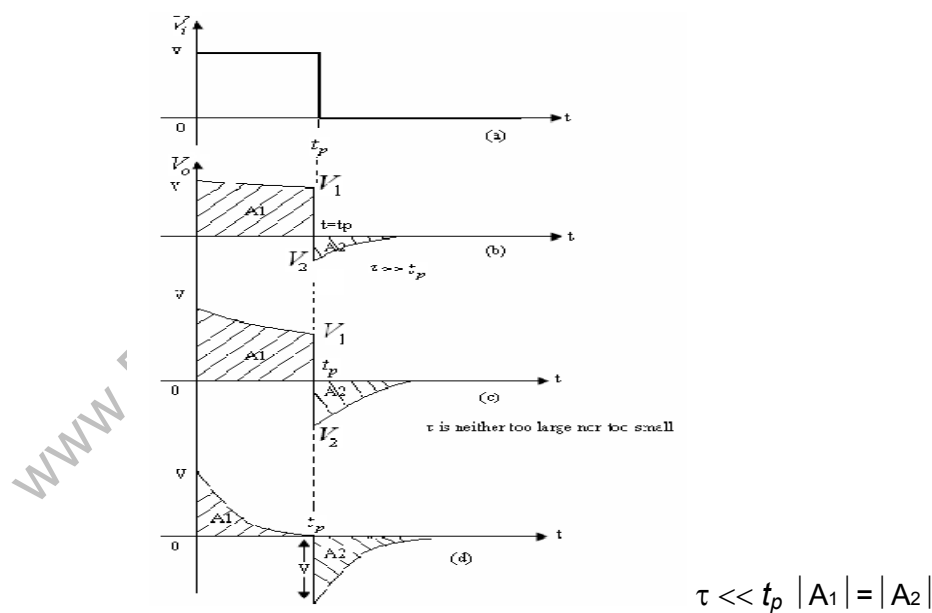

**Fig.6 Response of a high pass circuit for pulse input**

It is very clear that output has distortion when a pulse is passing through a high pass RC circuit. The shape of the pulse at the output is almost preserved when the time constant  $\tau$



## Pulse & Digital Circuits

is very large (fig.6b) whereas in fig.6c there is a tilt at the top of the pulse and an undershoot at the end of the pulse.

If  $\tau \ll t_p$  (fig.1.6d), the output consists of a positive spike at the beginning of the pulse and a negative spike at the end of the pulse, that means a highpass circuit converts a pulse into spikes called 'peaking'. To have a less distortion,  $\tau$  must be very much larger than the time period of the input pulse. In general, there is an undershoot at the end of the pulse. The area above the axis (A1) is always equal to the area below (A2).

### Area A1:

$$0 < t < t_p$$

$$V_o = V e^{-t/\tau}$$

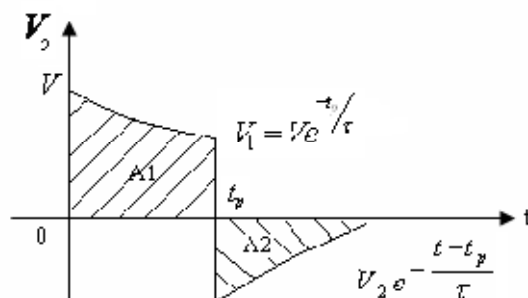


Fig.7 Calculation of A1 and A2

$$A_1 = \int_0^{t_p} V e^{-t/\tau} dt = \left[ -V \tau e^{-t/\tau} \right]_0^{t_p}$$

$$A_1 = \left[ -V \tau e^{-t_p/\tau} + V \tau \right] = V \tau (1 - e^{-t_p/\tau})$$

Similarly

$$A_2 = \int_{t_p}^{\infty} V (e^{-t_p/\tau} - 1) e^{-(t-t_p)/\tau} dt$$


## Pulse & Digital Circuits

$$\begin{aligned}
 &= \int_{t_p}^{\infty} \left[ V e^{-t/\tau} - V e^{-(t-t_p)/\tau} \right] dt \\
 &= \left[ \frac{V e^{-t/\tau}}{-1/\tau} \right]_{t_p}^{\infty} - \left[ V \frac{1}{-1/\tau} e^{-(t-t_p)/\tau} \right]_{t_p}^{\infty} \\
 A_2 &= \left[ V \tau e^{-t_p/\tau} - V \tau \right] = -V \tau (1 - e^{-t_p/\tau}) \\
 |A_1| &= |A_2|
 \end{aligned}$$

### (iv) Square wave-Average level

A waveform that has a constant amplitude 'V' for a time T<sub>1</sub> and has another constant Amplitude 'V' for a time T<sub>2</sub> and which is repetitive with a time T = (T<sub>1</sub> + T<sub>2</sub>) is called a square Wave. If T<sub>1</sub> = T<sub>2</sub> = T/2, then it is called a symmetric square wave and the typical input-output

Waveforms of the high pass circuit are shown in fig below.

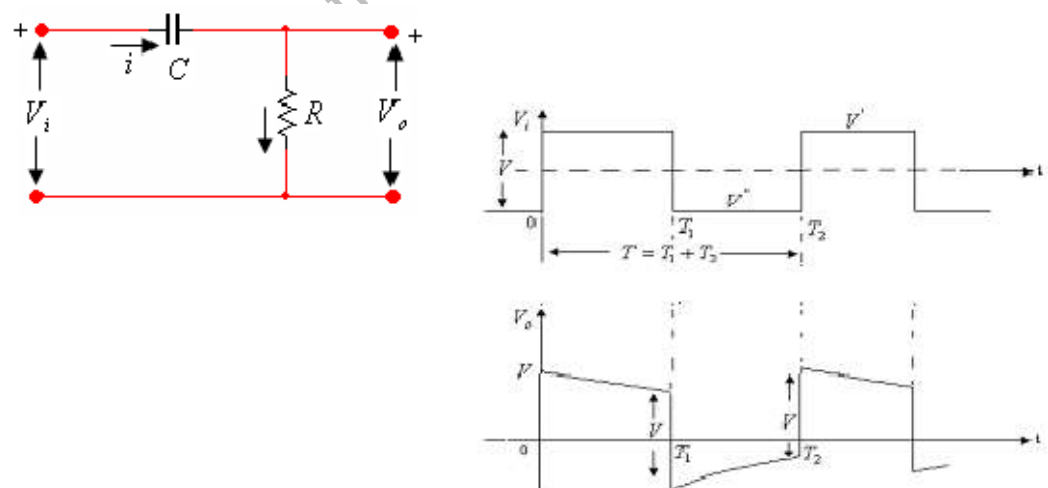

**Fig.8 output of a high pass for symmetric square wave input**

## Pulse & Digital Circuits

Whatever is the dc component associated with the periodic input, waveform the dc level of the Steady state output signal for the high pass circuit is always zero.

This can be verified by using KVL equation

$$V_i = \frac{q}{C} + V_o$$

where q is the capacitor charge

Differentiating with respect to t

$$\frac{dV_i}{dt} = \frac{1}{C} \frac{dq}{dt} + \frac{dV_o}{dt}$$

$$\text{But } i = \frac{dq}{dt}$$

Substituting above condition

$$\frac{dV_i}{dt} = \frac{i}{C} + \frac{dV_o}{dt}$$

since  $V_o = iR$ ,  $i = \frac{V_o}{R}$  and  $RC = \tau$

Multiplying by dt and integrating over the time period T we get

$$\therefore \frac{dV_i}{dt} = \frac{V_o}{\tau} + \frac{dV_o}{dt}$$

Multiplying by dt and integrating over the time period T we get

$$\int_0^T dV_i = [V_i]_0^T = V_i(T) - V_i(0)$$

$$\int_0^T \frac{V_o}{\tau} dt = \frac{1}{\tau} \int_0^T V_o dt$$

$$\int_0^T dV_o = [V_o]_0^T = V_o(T) - V_o(0)$$

From above equations

## Pulse & Digital Circuits

$$V_i(T) - V_i(0) = \frac{1}{\tau} \int_0^T V_o dt + [V_o(T) - V_o(0)]$$


Under steady-state conditions, the output and the input waveform are repetitive with a time period T. Therefore,

$$\int_0^T V_o dt = 0 \quad V_i(T) = V_o(T) \text{ and } V_i(0) = V_o(0)$$

Since this integral represents the area under the output waveform over one cycle, it is evident that the dc in the steady state is always zero.
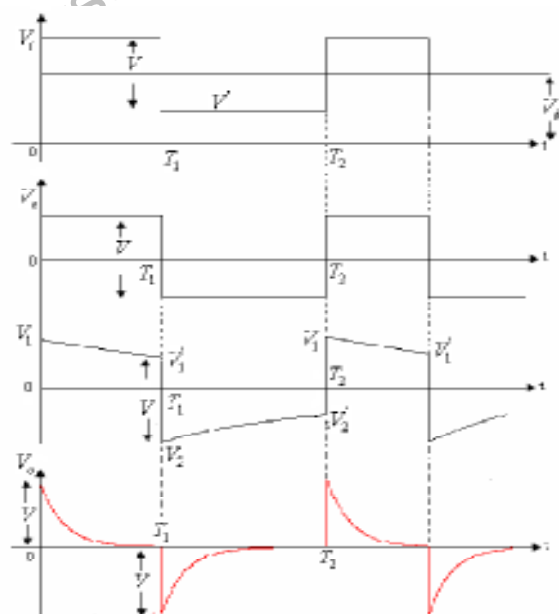
### 1.5 High pass RC response for Square wave input:

Now consider the response of the high pass RC circuit for a square wave input for different values of the time constant,  $\tau$ , fig below.




## Pulse & Digital Circuits

**Fig.9 Response of a highpass circuit for square input**

- a) Square Wave input
- (b) Response  $\tau \gg T_1$  and  $\tau \gg T_2$
- (c) Response when  $\tau$  is neither too large nor too small
- (d) Response when  $\tau$  is very small

Consider the typical response of the highpass circuit for square wave input, fig.10

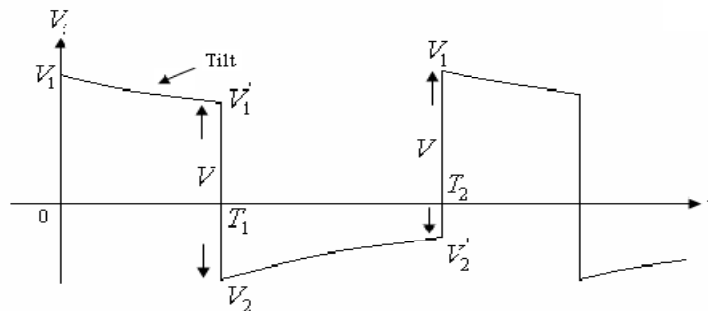

**Fig.10 response of a highpass RC circuit for squarewave input**

We know that  $V_1 = V_1 e^{-T_1/\tau}$  and  $V_1 - V_2 = V$

And  $V_2 = V_2 e^{-T_2/\tau}$  and  $V_1 - V_2 = V$

For a symmetric square wave

$$T_1 = T_2 = \frac{T}{2}$$

And because of symmetry'

$$V_1 = -V_2 \quad \text{and} \quad V_1' = -V_2'$$

From equation

$$V_1' - V_2 = V$$

But

$$V_1' = V_1 e^{-T_1/\tau}$$

Therefore

$$V_1 e^{-T_1/\tau} - V_2 = V$$

## Pulse & Digital Circuits

From

$$V_1 = -V_2$$

Substituting, we have

$$V_1 e^{-T/\tau} + V_1 = V$$

$$V_1 (1 + e^{-T/\tau}) = V$$

$$\text{Thus, } V_1 = \frac{V}{1 + e^{-T/\tau}}$$

For a symmetric squarewave as  $T_1 = T_2 = \frac{T}{2}$ ,

Therefore

$$V_1 = \frac{V}{1 + e^{-T/2\tau}}$$

But,  $V_1' = V_1 e^{-T/2\tau}$

$$V_1' = V \frac{e^{-T/2\tau}}{(1 + e^{-T/2\tau})}$$

There is a tilt in the output waveform. The percentage tilt is defined as

$$\begin{aligned} \% \text{ Tilt} = P &= \frac{V_1 - V_1'}{V/2} \times 100 \% \\ &= \frac{\frac{V}{1 + e^{-T/2\tau}} - \frac{V e^{-T/2\tau}}{1 + e^{-T/2\tau}}}{V/2} \times 100 \% \end{aligned}$$

## Pulse & Digital Circuits

If  $\frac{T}{2\tau} \ll 1$

$$P \cong \frac{T}{2\tau} \times 100\% \text{ since } \frac{T}{2\tau} \ll 1$$

$$P = \frac{T}{2\tau} \times 100\%, \text{ for a symmetrical squarewave}$$

---

The lower cut-off frequency,  $f_1 = \frac{1}{2\pi\tau}$

Therefore  $\frac{1}{2\tau} = \pi f_1$

$$P = \pi f_1 T \times 100\%$$

Therefore,  $P = \frac{\pi f_1}{f} \times 100\%$ , since  $T = \frac{1}{f}$

### 1.6 High Pass RC response for Ramp signal input.

- (v) **Ramp input:** Ramp waveform is one which increases linearly with time for  $t > 0$  and is zero for  $t < 0$ .

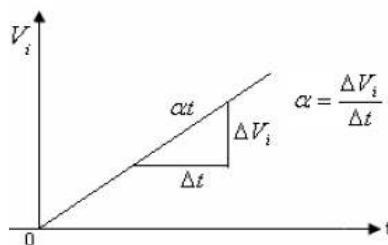


fig.13 ramp input

Let the input to the high pass circuit be  $V_i = \alpha t$  where  $\alpha$  is the slope fig.13

## Pulse & Digital Circuits

$$V_i = \frac{1}{\tau} \int V_o dt + V_o$$

$$\alpha t = \frac{1}{\tau} \int V_o dt + V_o$$

solving for  $V_o$

$$V_o(t) = \alpha \tau \left[ 1 - e^{-\frac{t}{\tau}} \right]$$

If  $\frac{t}{\tau} \ll 1$

$$e^{-\frac{t}{\tau}} = 1 - \frac{t}{\tau} + \frac{t^2}{2\tau^2}$$

$$\text{Therefore } V_o(t) = \alpha \tau \left[ 1 - 1 + \frac{t}{\tau} - \frac{t^2}{2\tau^2} \right]$$

$$V_o(t) = \alpha t \left[ 1 - \frac{t}{2\tau} \right]$$

The output falls away from the input, fig.

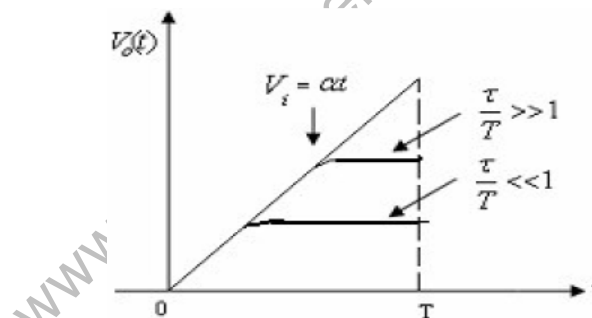


Fig. 14 Response of a highpass circuit to ramp input

Transmission error is defined as the deviation from linearity and is given by

$$e_t = \frac{V_i - V_o}{V_i}$$

$$V_i = \alpha t$$



## Pulse & Digital Circuits

$$\text{At } t = T, \quad V_i = \alpha T, \text{ And } V_o = \alpha T \left(1 - \frac{T}{2\tau}\right)$$

$$\text{Therefore } e_i = \frac{\alpha T - \alpha T \left(1 - \frac{T}{2\tau}\right)}{\alpha T} = \frac{\frac{\alpha T^2}{2\tau}}{\alpha T} = \frac{T}{2\tau}$$

$$\text{Thus, } e_i = \frac{T}{2\tau} = \Pi f_1 T \text{ as } \frac{1}{2\tau} = \pi f_1$$

### 1.7 HighPass RC Circuit as Differentiator

If the time constant of the RC highpass circuit is very much smaller than the time period of the input signal, then the circuit behaves as a differentiator. Then the voltage drop across R is very small when compared to the drop across C.

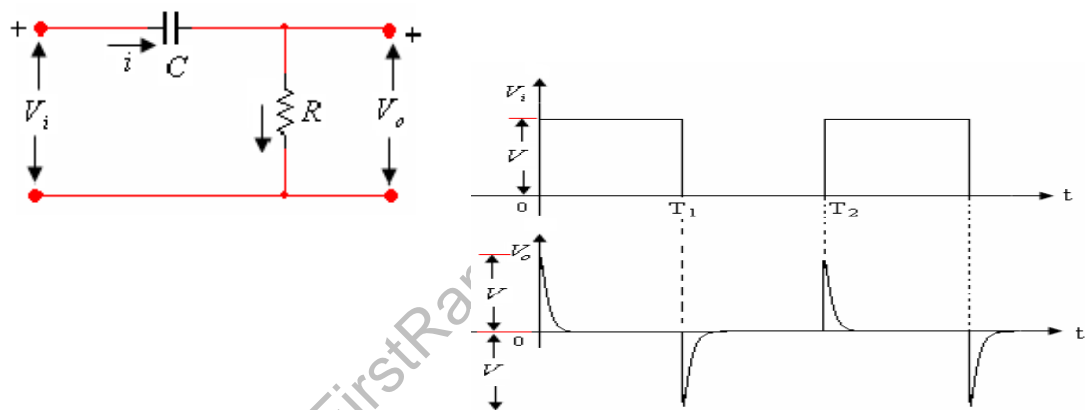


Fig.15 output of a differentiator

$$V_i = \frac{1}{C} \int i dt + iR$$

But  $iR = V_o$  is small

$$\text{Therefore } V_i = \frac{1}{C} \int i dt$$

$$i = \frac{V_o}{R}$$

$$\therefore V_i = V_i = \frac{1}{\tau} \int V_o dt = \frac{1}{\tau} \int V_o dt$$

## Pulse & Digital Circuits

Differentiating

$$\frac{dV_i}{dt} = \frac{V_o}{\tau}$$
$$V_o = \tau \frac{dV_i}{dt}$$
$$\therefore V_o \propto \frac{dV_i}{dt}$$

The output is proportional to the differential of the input signal.

### LOWPASS CIRCUITS:

#### Introduction:

Low pass circuit is one which allows low frequencies with less attenuation and high frequencies with maximum attenuation. This is because capacitance offers high reactance at low frequencies and hence there is an output.

**1.8 LOWPASS RC CIRCUIT:** Following is the low pass RC circuit.

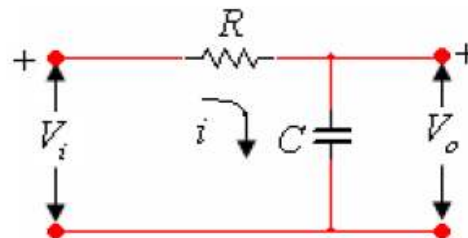


Fig.16 Low pass RC Circuit

## Pulse & Digital Circuits

At low frequencies the reactance of C is large and as frequency increases its Reactance decreases. Hence the output is larger for smaller frequencies and is smaller for larger frequencies. Hence this circuit is called a low pass circuit.

Consider the response of this circuit for different types of inputs.

### 1.9 Low Pass RC response for Sine signal input.

**i) SINUSOIDAL INPUT:** For the circuit shown above, if sinusoidal signal is applied as an input, the output  $V_o$  is given by

$$V_o = V_i \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$

$$\frac{V_o}{V_i} = \frac{1}{1 + j\omega CR}$$

$$\left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{1 + (\omega CR)^2}} = \frac{1}{\sqrt{1 + \left( \frac{\omega}{\omega_2} \right)^2}} \quad \text{, where } \omega_2 = \frac{1}{CR}$$

$$\text{At } \omega = \omega_2, \quad \left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{2}} = 0.707$$

Hence,  $f_2$  is the upper cut-off frequency as shown in the response curve below.

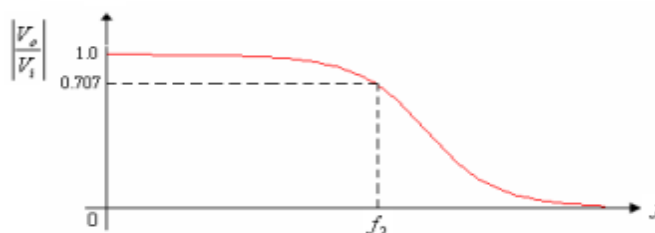


Fig.17 Response of low pass circuit to sinusoidal input

### 1.10 Low Pass RC response for Step signal input.

## Pulse & Digital Circuits

(ii) **STEP INPUT:** When a step voltage is applied as input to the lowpass circuit the output will be appeared as shown in fig. below.

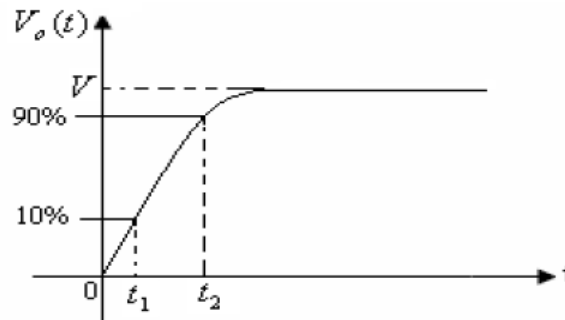


Fig.18 Response of lowpass circuit to step input

We have  $RC = \tau$

$$V_o = V_f + (V_i - V_f)e^{\frac{-t}{\tau}}$$

Here,  $V_f = V$  and  $V_i = 0$

$$\therefore V_o(t) = V - Ve^{\frac{-t}{\tau}} = V\left(1 - e^{\frac{-t}{\tau}}\right)$$

As  $t \rightarrow \infty$ ,  $V_o(t) \rightarrow V$

On the other hand, the output can be obtained by solving the differential equation.

## Pulse & Digital Circuits

---

$$V = V_i = Ri + \frac{1}{C} \int i dt$$

We know that  $\frac{1}{C} \int i dt = V_o$

$$\frac{i}{C} = \frac{dV_o}{dt}$$

$$i = C \frac{dV_o}{dt}$$

$$V = RC \frac{dV_o}{dt} + V_o$$

$$V = \tau \frac{dV_o}{dt} + V_o \quad \text{Solving for}$$

$$V_o(t) = V_o = V - Ve^{\frac{-t}{\tau}} = V \left( 1 - e^{\frac{-t}{\tau}} \right)$$

**Rise time:** The time taken for the output to reach from 10% of its final value to 90% of its final value is called rise time.

From equation

$$0.9 = 1 - e^{\frac{-t}{\tau}}$$

$$e^{-t_2/\tau} = 0.1$$

$$t_2 = 2.3\tau$$

$$\text{Rise time } t_r = t_2 - t_1 = 2.3\tau - 0.1\tau = 2.2\tau$$

$$\text{Also } f_2 = \frac{1}{2\pi RC}$$

$$RC = \tau = \frac{1}{2\pi f_2}$$

## Pulse & Digital Circuits

### 1.11 Low pass RC response for pulse input:

Let the input of low pass rc is a pulse signal with pulse width  $T$  the response of low pass RC for pulse input under different conditions will be as follows.

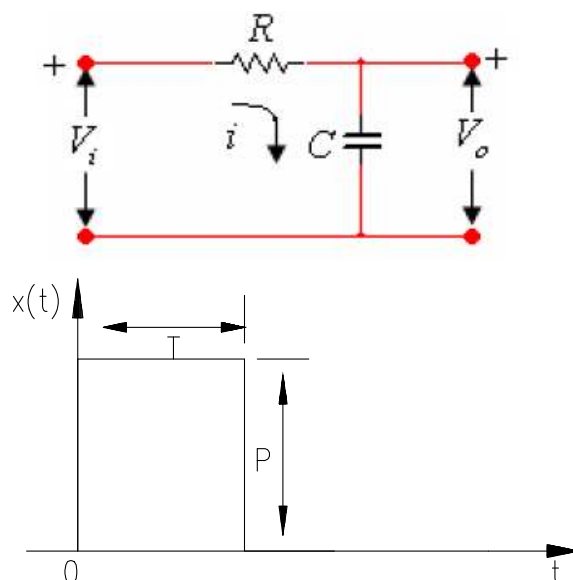


Fig.19 Input pulse to low pass RC

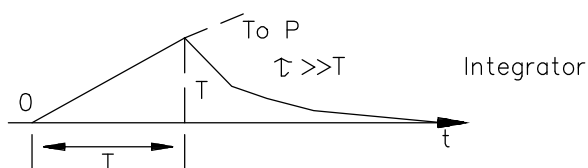
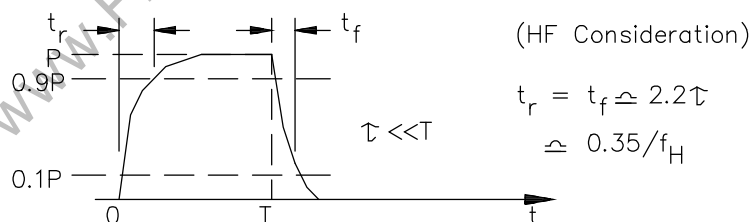
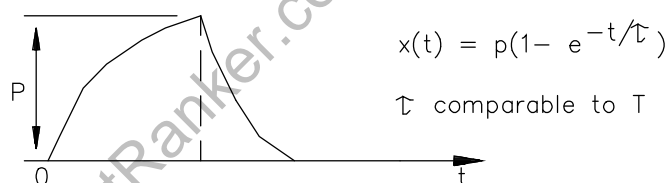


Fig.20 Response of low pass RC for pulse input under different conditions

## Pulse & Digital Circuits

### 1.12 Response of low pass RC for square input:

The shape of the output waveform of an RC low-pass circuit depends upon the value of the circuit time constant  $T$  (as compared to pulse duration  $t_p$ ). For a pulse waveform of the low-pass circuit may be short, long or medium as compared to  $t_p$ , the pulse duration of the input pulse wave. The output wave form for three different conditions for square wave input will be as follows. The conditions are  $T \ll t_p$ ,  $T = t_p$ ,  $T \gg t_p$ .

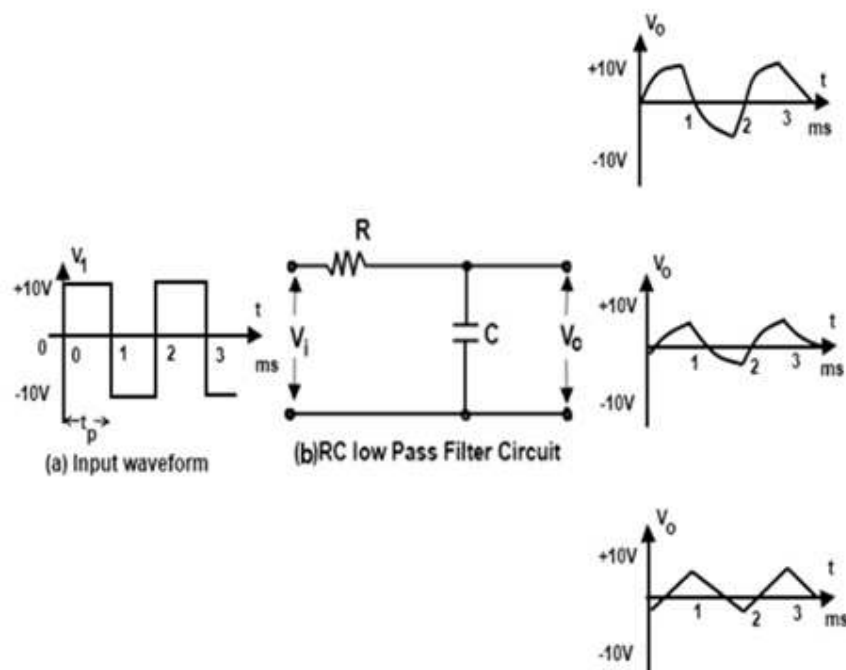


Fig.21 Response of low passes RC for square input

### 1.13 Response of Low pass circuit for ramp input:

When a ramp is applied as input to a lowpass circuit, the output deviates from the input which is defined as transmission error  $e_t$ . Mathematically it can be written as

## Pulse & Digital Circuits

The input is a ramp  
i.e.  $V_i = \alpha t$

We have  $V_i = \tau \frac{dV_o}{dt} + V_o$

$\therefore \alpha t = \tau \frac{dV_o}{dt} + V_o$

solving for output, we have

$$V_o(t) = -\alpha\tau + \alpha t + \alpha\tau e^{-t/\tau}$$

$$V_o(t) = \alpha \left[ t - \tau(1 - e^{-t/\tau}) \right]$$

At  $t = T$

$$V_o(T) = \alpha \left[ T - \tau(1 - e^{-T/\tau}) \right]$$

**Case 1 :** If  $\tau \ll T$ , then the deviation of the output from the input is very small since

$$e^{-T/\tau} \approx 0$$



$$V_o(t) = \alpha(T - \tau)$$

**Case 2:** If  $\tau \gg T$ , then  $e^{-T/\tau}$  can be expanded as series

$$V_o(t) = \alpha \left[ T - \tau \left( \frac{T}{\tau} - \frac{T^2}{2\tau^2} \right) \right]$$

$$= \alpha \left[ T - T + \frac{T^2}{2\tau} \right] = \frac{\alpha T^2}{2\tau} \quad \text{-----} \quad 2.36$$

The response is plotted in fig. below

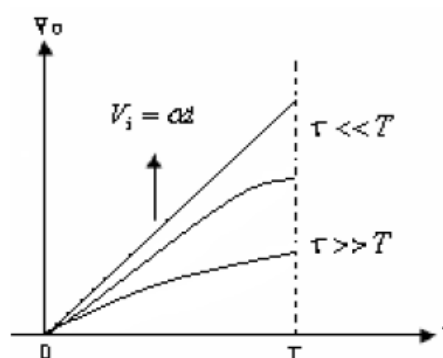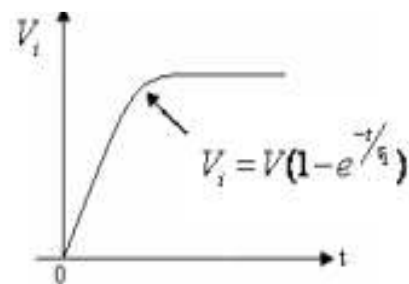



## Pulse & Digital Circuits

$$e_i = \frac{V_i - V_0}{V_i}$$

$$= \frac{\alpha T - \alpha(T - \tau)}{\alpha T}$$

$$e_i = \frac{\tau}{T}$$

$$f_2 = \frac{1}{2\pi\tau}$$

$$\tau = \frac{1}{2\pi f_2}$$


### 1.14 Low pass circuit as an integrator

For the low pass circuit to behave as an integrator  $\tau \gg T$  then the voltage Variation in C is very small

$$V_i = iR + \frac{1}{C} \int i dt$$

$$V_i \cong iR$$
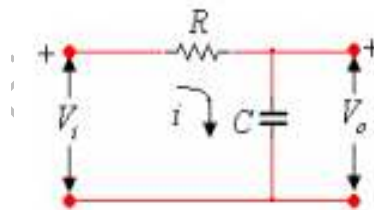
$$\text{Since, } \frac{1}{C} \int i dt \ll iR$$



$$i = \frac{V_i}{R}$$

$$\text{Therefore } V_o = \frac{1}{C} \int i dt = \frac{1}{RC} \int V_i dt = \frac{1}{\tau} \int V_i dt$$

The output is proportional to the integral of the input signal.

Hence a low pass circuit with large time constant produces an output that is proportional to the integral of the input.

## Pulse & Digital Circuits

### 1.15 Attenuators:

An attenuator is a circuit that reduces the amplitude of the signal by a finite amount. A simple resistance attenuator is as shown below.


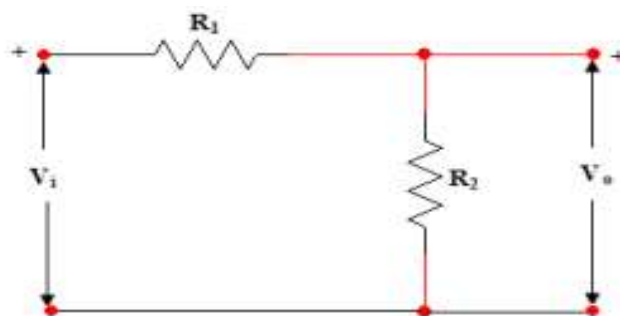


Fig.22 Resistive Attenuator

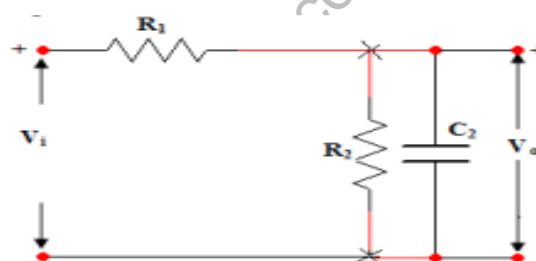The output is reduced depending on the choice of  $R_1$  and  $R_2$ . The output of this attenuator can be connected as input to an amplifier having a stray capacitance  $C_2$  and input resistance  $R_i$ . If  $R_i \gg R_2$ , then the effective value of resistance will be smaller than  $R_2$ . The attenuator circuit will be now as



Reducing the two loop network into a single loop network by Thevenizing


$$V_{th} = V_1 \times \frac{R_2}{R_1 + R_2} = \alpha V_1 \quad \text{where } \alpha = \frac{R_2}{R_1 + R_2}$$

and

$$R_{th} = R_1 \parallel R_2$$

Hence the above circuit reduces to

## Pulse & Digital Circuits

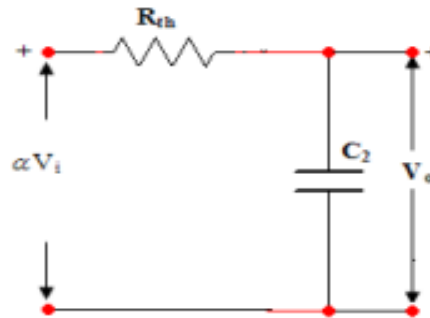

When the input  $\alpha V_i$  is applied to this low pass RC circuit, the output will not reach the steady-state value instantaneously. For e.g. in the above circuit,  $R_1=R_2=1\text{M}$  and  $C_2 = 20\text{nF}$ . Then the rise time  $t_r = 2.2R_{th}C_2 = 2.2 \times 0.5 \times 10^6 \times 20 \times 10^{-9}$ ,  $t_r = 22\text{msec}$ . which says that approximately after a time interval of 22 msec. after the application of the input  $\alpha V_i$  to the circuit, the output reaches the steady state value. Obviously this is an abnormally long time delay. An attenuator of this type is called an uncompensated attenuator and the response is depending on frequency. To make the response of the attenuator independent of frequency, capacitor  $C_1$  is shunted across  $R_1$ . This attenuator now is called a compensated attenuator as shown in fig.a, and the same is redrawn as in fig.b

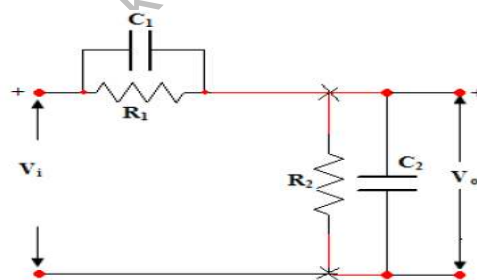


fig.a Compensated Attenuator

## Pulse & Digital Circuits


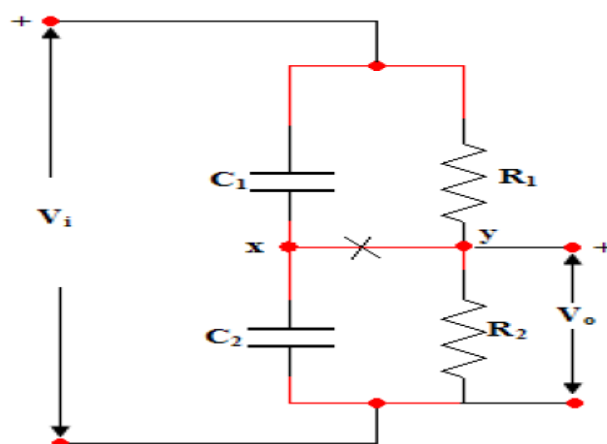


fig.b Compensated attenuator

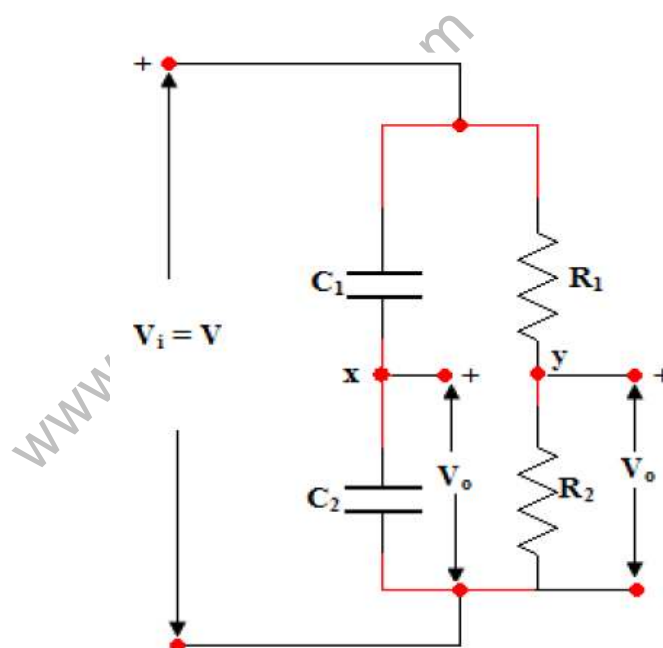$R_1, R_2, C_1, C_2$  form four arms of the bridge. The bridge is said to be balanced when  $R_1 C_1 = R_2 C_2$ . Then no current flows in the branch  $xy$ . Hence for the purpose of computing the output, branch  $xy$  is omitted. The resultant circuit is



**When a step voltage  $V_i = V$  is applied as input, the output is calculated as follows:**

At  $t=0+$ , as the capacitors will not allow any sudden changes in voltage, as the Input changes the output also should change abruptly, depending on the values of  $C_1$  and  $C_2$ .

## Pulse & Digital Circuits

$$V(0^+) = V \frac{C_1}{C_1 + C_2}$$

Thus, the initial output voltage is determined by  $C_1$  and  $C_2$ .

As  $t \rightarrow \infty$ , the capacitors are fully charged and they behave as open circuits for dc.

Hence the resultant output is

$$V_0(\infty) = V \frac{R_2}{R_1 + R_2}$$

Perfect compensation is obtained if,  $V_0(0^+) = V_0(\infty)$

$$\frac{C_1}{C_1 + C_2} V = V \frac{R_2}{R_1 + R_2}$$

From this we get


$$C_1 R_1 = C_2 R_2, \text{ or } C_1 = (R_2/R_1) C_2 = C_p$$

and the output is  $\propto V_i$

Hence following conditions (cases) arise.

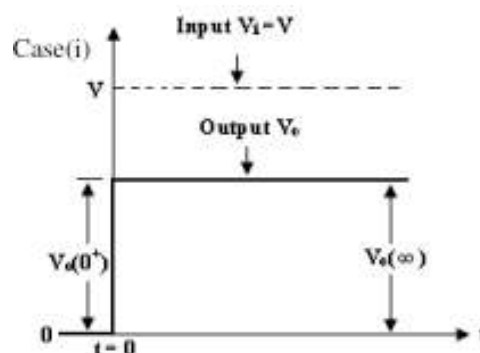
- (i) When  $C_1 = C_p$ , the attenuator is a perfectly compensated attenuator.
- (ii) When  $C_1 > C_p$ , it is an over-compensated attenuator and
- (iii) When  $C_1 < C_p$ , it is an under-compensated attenuator.

The responses of the attenuator for step input are shown in the following fig.




## Pulse & Digital Circuits

Case(ii)

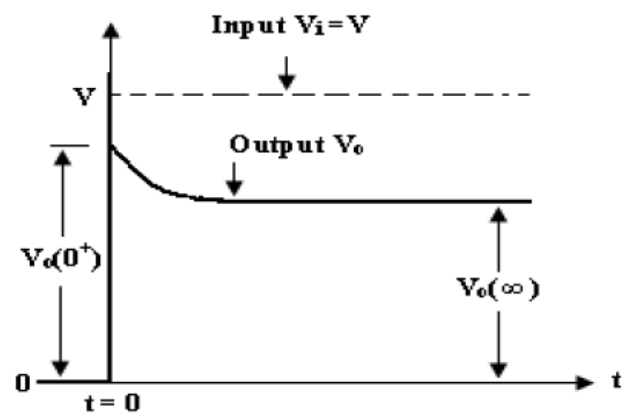


case(iii)

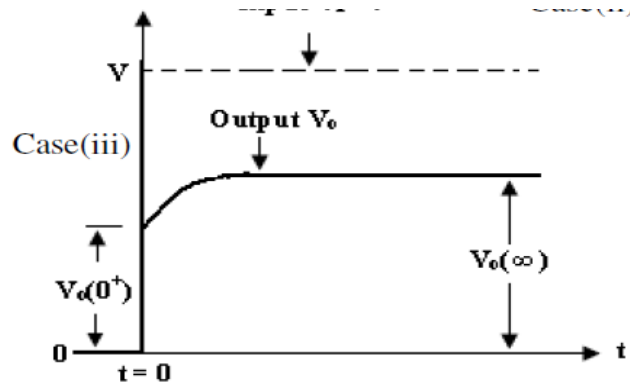

## Pulse & Digital Circuits
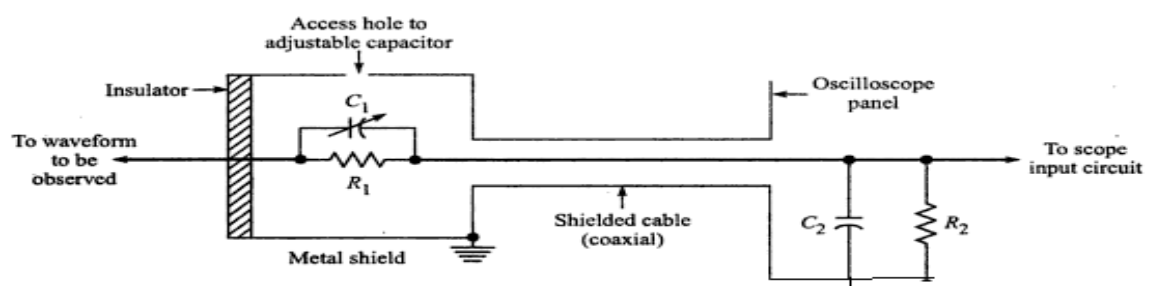
### 1.16 Application of attenuator as a CRO probe:


To measure the signal at a point in the circuit, the input terminals of the oscilloscope are connected to the signal point. Normally the point at which the signal is available will be at some distance from the oscilloscope terminals and if the signal appears at a high impedance level, a shielded cable is used to connect the signal to the oscilloscope. The shielding is necessary in this case to isolate the input lead from stray fields such as those of the ever-present power line. The capacitance seen looking into several feet of cable may be as high as 100 to 150 pF. This combination of high input capacitance together with the high output impedance of the signal source will make it impossible to make faithful observations of waveforms. A probe assembly, which permits the use of shielded cable and still keeps the capacitance low, is indicated in Figure 1.64.



### 1.17 RL and RLC Circuits and their response for step input.
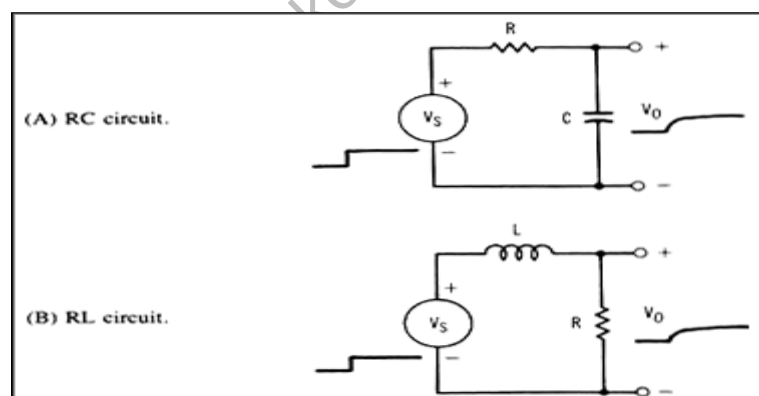
#### RL circuit:


RL circuit is similar to RC circuit the circuit diagram represents RL circuit will be as follows it can be acts as high pass RL and low pass RL also.



## Pulse & Digital Circuits
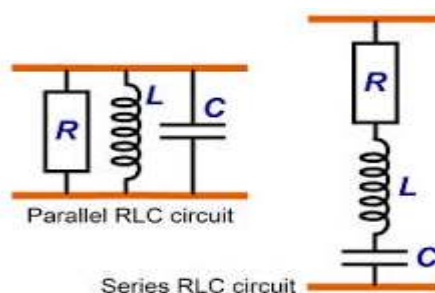
### RLC circuits:

There are two types of RLC circuits series RLC and parallel RLC will be as follows.



### Step response of RL and RLC circuits:

$$V_{in}(t) \rightarrow \tilde{V}_{in}(s) \rightarrow \tilde{V}_{out}(s) \rightarrow V_{out}(t)$$

$$T(s) = \frac{\tilde{V}_{out}(s)}{\tilde{V}_{in}(s)} \bigg|_{\substack{Z=0 \\ I_C}} = \frac{\frac{1}{sC}}{sL + R + \frac{1}{sC}} = \frac{1}{LC} \cdot \frac{1}{s^2 + s \cdot \frac{R}{L} + \frac{1}{LC}}$$

poles of  $s^2 + s \cdot \frac{R}{L} + \frac{1}{LC} = 0$        $p_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$

case1:  $\frac{R^2}{4L^2} > \frac{1}{LC}$ , i.e.  $R > 2\sqrt{\frac{L}{C}}$       poles are real and different

case2:  $\frac{R^2}{4L^2} = \frac{1}{LC}$ , i.e.  $p_1 = p_2 = -\frac{R}{2L}$       poles are real and equal


case3:  $\frac{R^2}{4L^2} < \frac{1}{LC}$ , i.e.  $R < 2\sqrt{\frac{L}{C}}$       poles are imaginary

By solving above three cases we get the output as the waveforms which are under damped, critical damped and overdamped waveforms.

The output waveforms will be as follows.



## Pulse & Digital Circuits

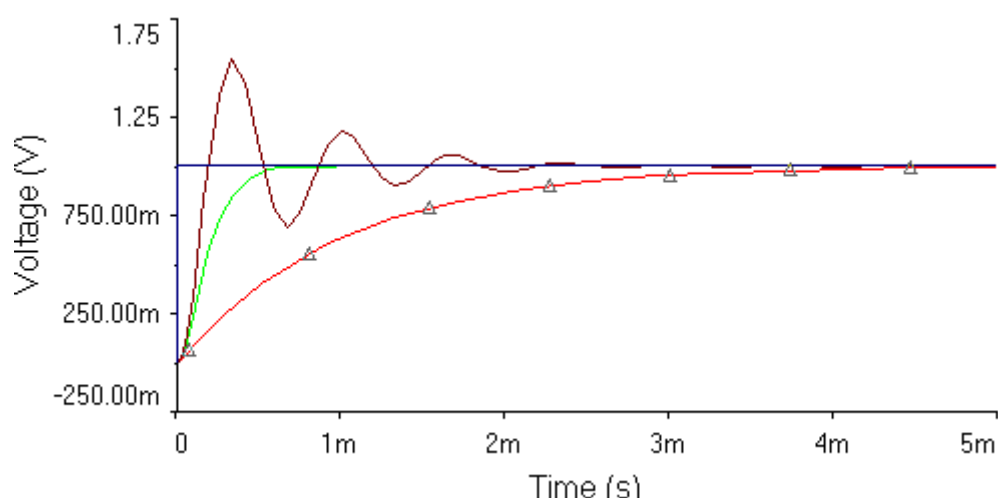

**Fig. Response of RLC for step input.**

### 1.18 Ringing circuit:

A circuit which provides un damped oscillations is called ringing circuit. If the damping is very small circuit rings for many cycles. for this circuit  $Q = \pi N$ . if  $Q = 12$ , circuit will ring for 4 cycles

### Important Questions:

1. What is linear wave shaping?
2. What are linear elements give suitable examples?
3. What are linear wave shaping circuits?
4. What is high pass RC? explain how it acts as differentiator?
5. What is low pass RC? explain how it acts as integrator?
6. What is the time constant of RC circuit?
7. Draw the responses of high pass RC for STEP, PULSE, SQUARE inputs?
8. Draw the responses of low pass RC for STEP, PULSE, SQUARE inputs?
9. What is transmission error? how it can be defined?
10. What is attenuator? give its applications?

## Pulse & Digital Circuits

### 2. Non-Linear Wave Shaping


#### Syllabus:

Diode clippers. Transistor Clippers. Clipping at two independent levels. Comparator – Applications of voltage Comparators – Diode Comparator. Clamping Operation. Clamping Circuits using Diode with Different Inputs. Clamping Circuit Theorem. Practical Clamping circuits. Effect of diode Characteristics on Clamping Voltage.


#### 2.1 Diode clippers:
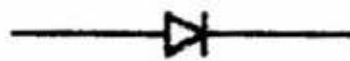
##### Basic Description

As you know, diodes can be used as switches depending on the biasing type, reverse or forward. The clipping circuit also referred to as clipper, clips off some of the portions of the input signal and uses the clipped signal as the output signal.



Forward turning-on

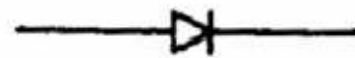

Reversely turning-off



Switch is closed



Switch is opened

Ideal Diode – Switch Terminology


#### 2.1. a Clipper Circuits

There are two types of clipper circuits, the series and parallel diode clipping circuits.

##### 2.1 a.1 Series Diode Clipping Circuit


In these types of circuits, the diode is connected between the input and output voltage terminals

## Pulse & Digital Circuits

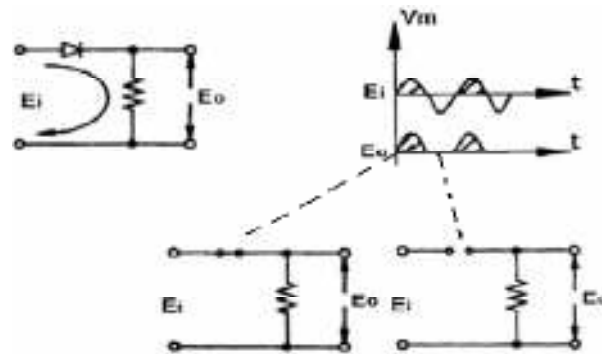


**Fig: series negative clipper**

As **Fig** reveals, the negative cycle of the input voltage can be clipped off by this type of series clippers. Reverse of the diode pins yields to a positive cycle clipping circuit as shown in **Fig**.

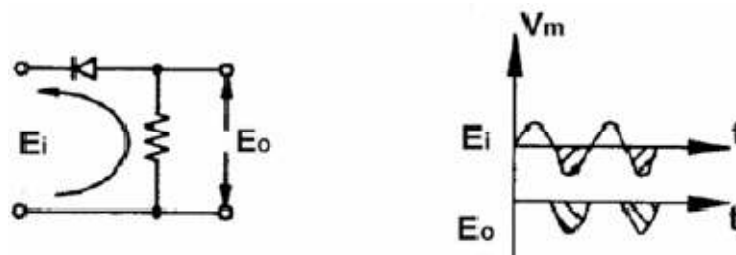

**Fig. series positive clipper**

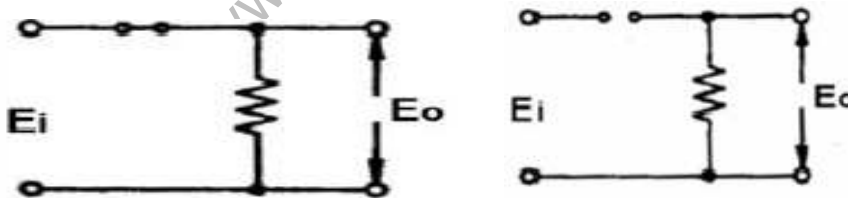


**Diode operation as short and open circuits**

## Pulse & Digital Circuits
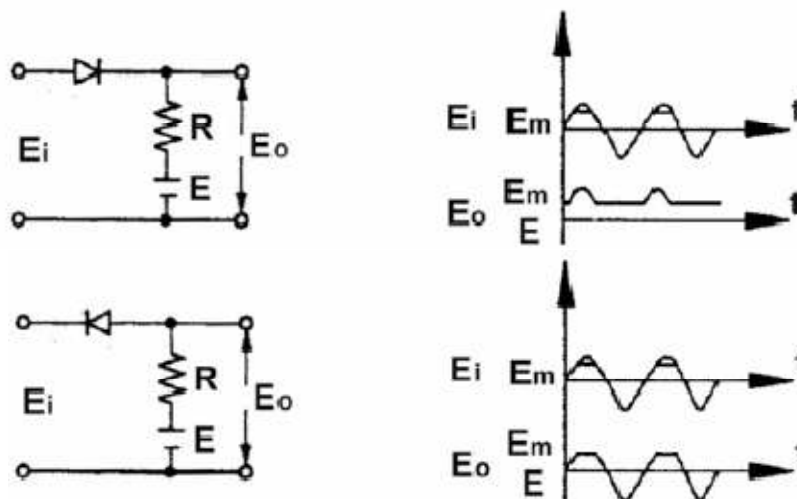
### Diode clippers using bias

Previous circuits clip the values larger or smaller than zero voltage. This voltage, technically called “threshold voltage” and can be changed to a desired value by inserting a D.C. voltage source. This is achieved in two different ways.

**In the first type**, the voltage source of  $E_m$  (positive or negative) is connected through output terminals as in Fig. Depending on the diode connection (normal or reverse), the values smaller or greater than  $E_m$  is clipped and assigned as  $E_m$ .




Note that if  $E_m$  is negative, (where the voltage source is reversely connected) again the values smaller or larger than this negative value are clipped.
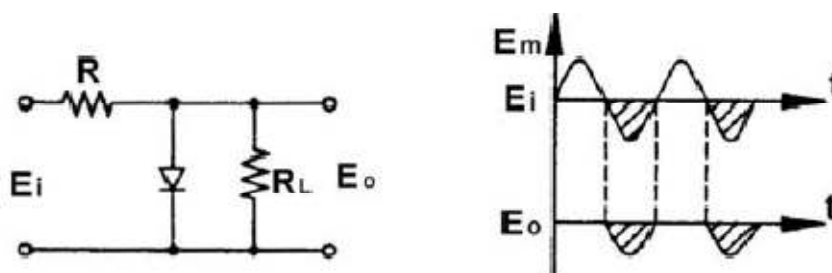
### Parallel Diode Clipping Circuit

In this type of clippers, the diode is connected between output terminals. The on/off state of diode directly affects the output voltage. These types of clippers may also have a non-zero threshold voltage by addition of a voltage series with diode.

Following figures illustrate the clipping process



## Pulse & Digital Circuits

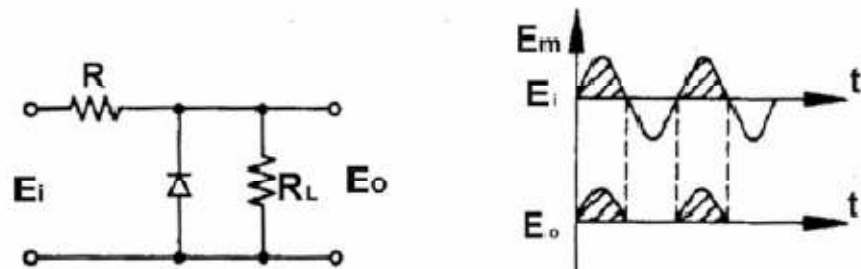


Fig. Zero Threshold Parallel Clippers

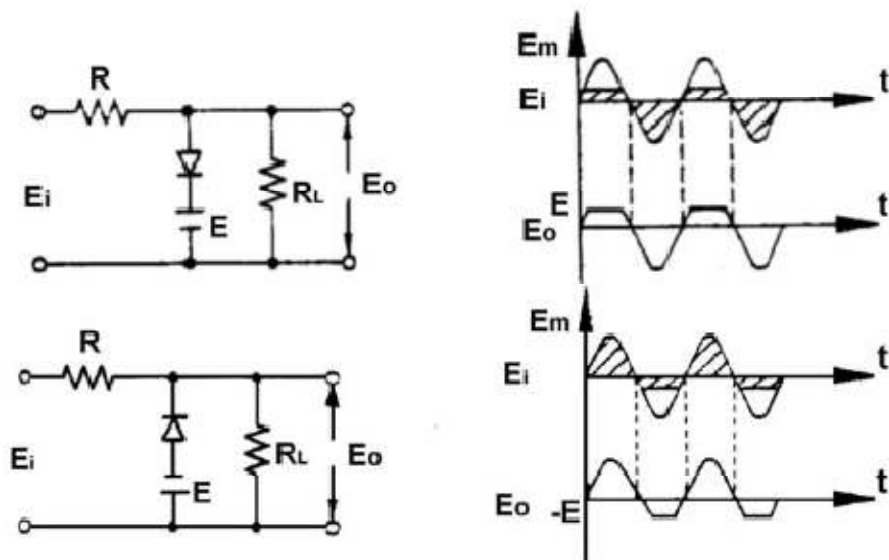



Fig. Threshold Parallel Clippers

### 2.2 Double Diode Clipping

In single diode clipping circuit, the wave form is selected either above or below (but not on both sides) reference level. Two diode clippers may be used in parallel, series, or series-parallel to limit the output at two independent levels.

Consider the circuit in Fig. side


## Pulse & Digital Circuits

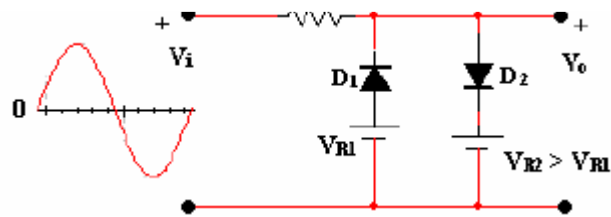


The transfer curve has two break points, one at  $V_o = V_i = V_{R1}$  and a second at  $V_o = V_i = V_{R2}$  has the following characteristics  $V_o$

Input voltage	Output voltage	Diode states
$V_i > V_{R2}$ ,	$V_o = V_{R1}$	D1 is OFF and D2 is ON,
$V_i < V_{R1}$ ,	$V_o = V_i$	D1 is ON D2 is OFF,
$V_{R1} < V_i < V_{R2}$ ,	$V_o = V_{R2}$	D1 and D2 are OFF.

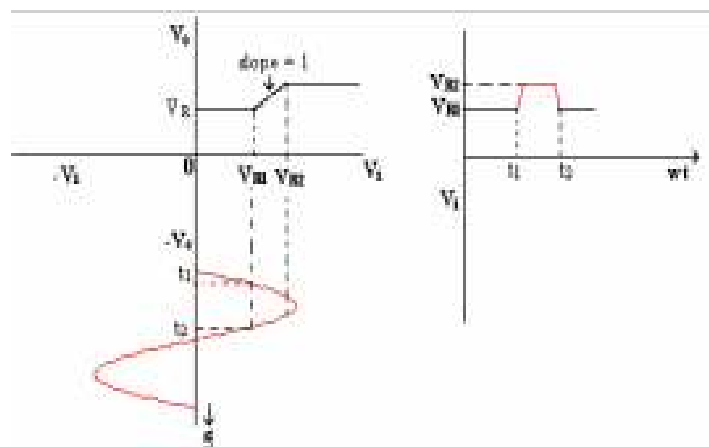Transfer characteristic of the slicer with input and output




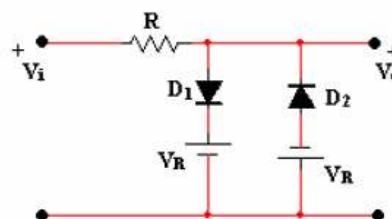A combination of a positive peak clipper and a negative peak clipper, clipping the input symmetrically at the top and the bottom is called a limiter





## Pulse & Digital Circuits

The resultant transfer characteristic is as shown below.

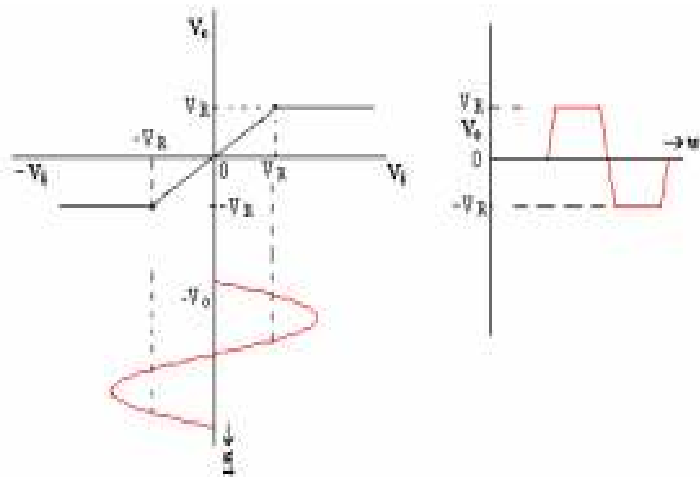

**Fig. Transfer characteristic of a Limiter with input and output**

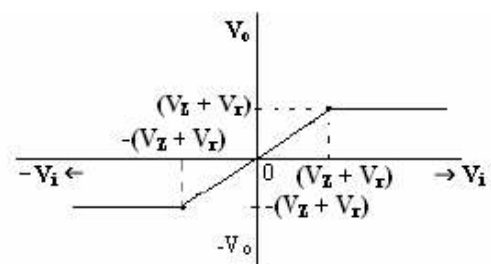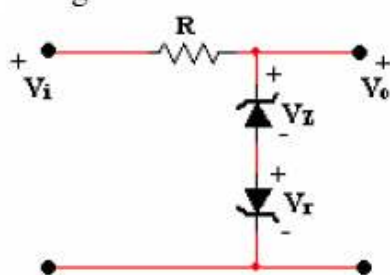Two avalanche diodes in series opposing, as indicated in fig below constitutes another form of double-ended clipper. If the diodes have identical characteristics then a symmetrical limiter is obtained. If the breakdown (zener) voltage is  $V_Z$  and if the cut in voltage in the forward direction is  $V_f$ , then the transfer characteristic is as shown below. Transfer characteristic




**Transfer characteristic**

## Pulse & Digital Circuits

### 2.3 Transistor clippers:


#### Emitter-coupled transistor clipper:

Consider initially that the input voltage  $V_i$  is negative enough to ensure that  $Q_1$  is in cutoff. Then only  $Q_2$  is carrying current. Consider that  $V_{BB}$  has been adjusted so that  $Q_2$  is in its active region. As  $V_i$  increases  $Q_1$  will eventually come out of cutoff, both transistors will be carrying current and the input signal will appear at the output, amplified but not inverted. As  $V_i$  continues its excursion in the positive direction the common emitter will follow the base of  $Q_1$ . The base of  $Q_2$  is fixed, a point will be reached when the rising emitter cuts off  $Q_2$ . Finally, the input signal is amplified but twice limited, once by the cutoff of  $Q_1$  and once by the onset of cutoff in  $Q_2$ .

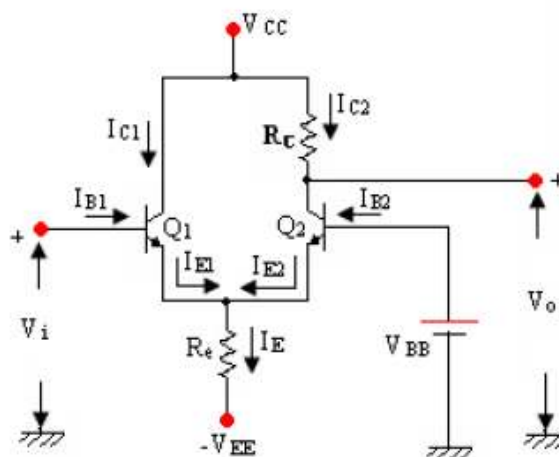

**Fig.A two-level transistor clipper**

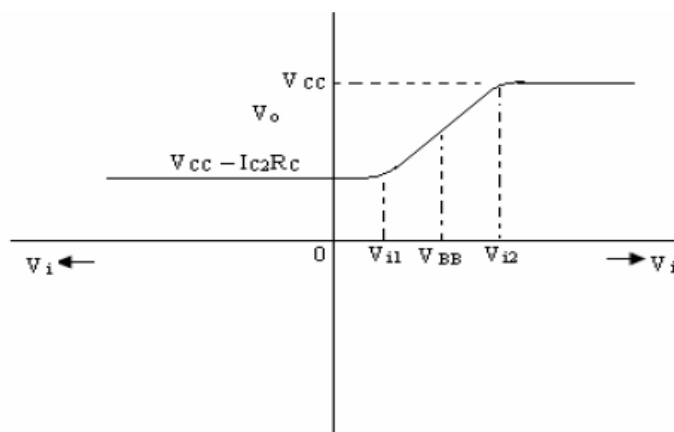The transfer characteristic is shown in fig below. Thus this circuit behaves as a two-level clipper. The region of linearity can be controlled by the choice of  $V_{BB}$ .





## Pulse & Digital Circuits


### 2.4 COMPARATORS:

A comparator circuit is one which may be used to mark the instant when an Arbitrary waveform attains some reference level. Consider the simple clipping circuit for comparison operation.

For the sake of explanation let the input signal be a ramp as shown below.

This input crosses the voltage level  $v_i = V_R$  at time  $t = t_1$ .

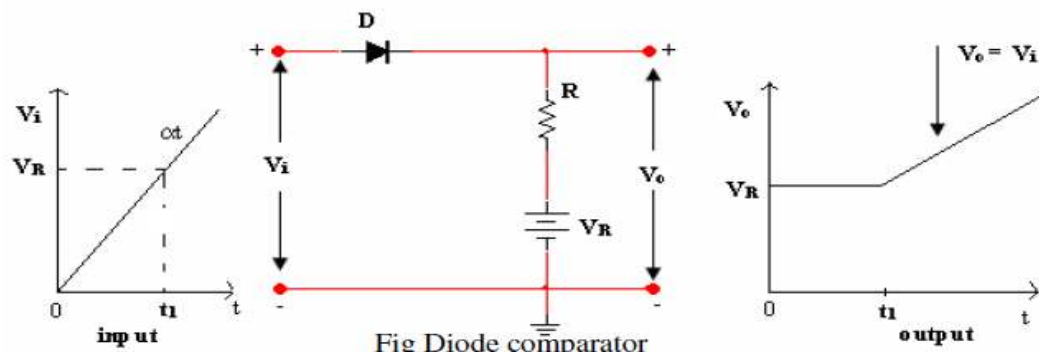
The output remains quiescent at  $v_o = V_R$  until  $t = t_1$  after which it rises with the input Signal



There is a sudden change in the slope of the output at the instant the input reaches  $V_R$ .

But due to ageing and due to temperature variations the diode, may not switch from OFF to ON at exactly  $t = t_1$ . It may switch state at any instant after  $t_1$  and before  $t_2$ .

## Pulse & Digital Circuits

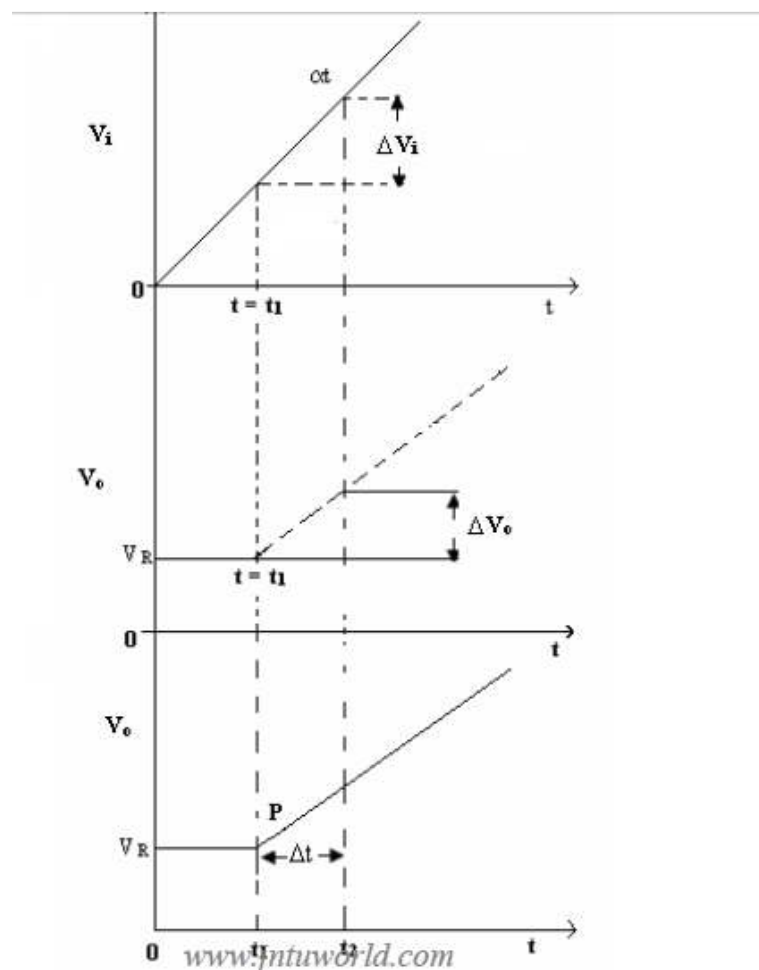

### Input and output of the diode comparator

Hence, the break point (point at which device  $D$  changes state) may not exactly be at  $t_1$  but instead, there is a break region ( $t_1$  to  $t_2$ ).. Hence, there is a region of uncertainty which also, after the break point, the output follows the input i.e. has the same slope of the input. If this region of uncertainty is to be reduced, the response after the break point should be sharp. To achieve this amplifier may be placed before or after the comparator.

Consider the comparator circuit the response. To the left of the break point, the diode is OFF then the reverse incremental resistance of the diode,  $R_r$  is very much larger when compared to  $R$ . To the right of the break point the forward incremental resistance of the diode,  $R_f$  is very much smaller than  $R$ . If the break point is located at a point where  $r = R$ .

## Pulse & Digital Circuits

$$\Delta V_o = \Delta V_i \frac{R}{r+R} \approx V_i \quad \text{if } R \gg r$$

$$\text{As } \Delta V_o = \Delta V_i \frac{R}{r+R}$$

if  $r = R$

$$\therefore \frac{\Delta V_o}{\Delta V_i} = \frac{R}{R+R} = \frac{1}{2}$$

So the improvement is only half.


If a device is connected at the output of the comparator, this is required to be activated when the diode current is say,  $I$  and has a drop across  $R$  as  $IR$ .

If now an amplifier is connected at the output of the comparator so that this amplifier output activates the device.

Let the amplifier have a gain  $A$ . During  $\Delta t = t_2 - t_1$ , the output changes by

$\Delta V_o = V_2 - V_R$ , the delay in response is reduced to
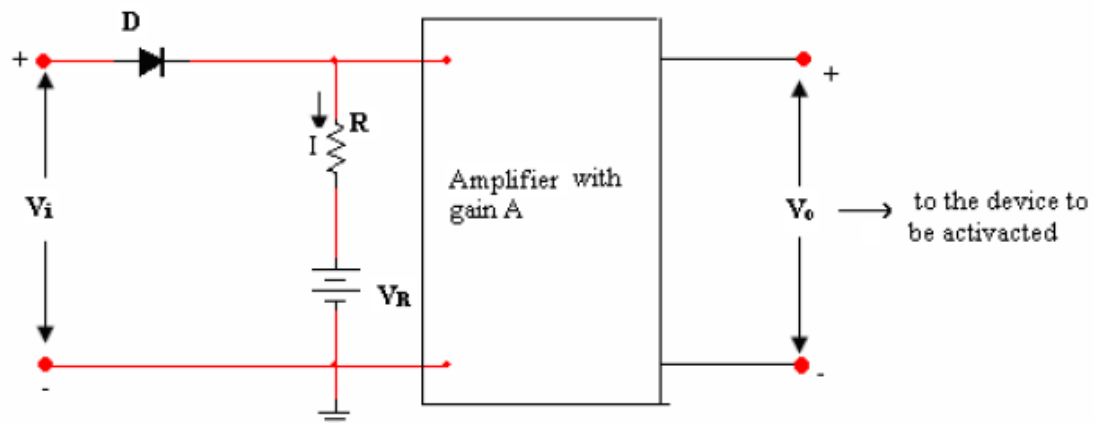
$$\frac{\Delta t}{A} \text{ or } \frac{(t_2 - t_1)}{A}$$



Output of the comparator connected to an amplifier

□—

Let the amplifier only amplify the change in the comparator input but not the reference voltage. The device to be activated is activated only when the drop across  $R$  is  $IR$ . But now  $I = I/A$ , Hence the device is activated when the drop across  $R$  is  $RI/A$  since the diode current is amplified by  $A$  and the diode resistance i.e the dynamic resistance which varies inversely with current. Therefore it is evident that, the device to be activated by the

## Pulse & Digital Circuits

comparator will respond at a current such that  $r = RA$

$$\therefore \frac{\Delta V_o}{\Delta V_i} = A \frac{R}{r + R} = \frac{AR}{R + RA} = \frac{A}{1 + A}$$

$$\text{As } A \rightarrow \infty, \frac{\Delta V_o}{\Delta V_i} \rightarrow 1$$

Without an amplifier  $\frac{\Delta V_o}{\Delta V_i}$  the transmission gain) was  $\frac{1}{2}$  and with an amplifier connected,

$\frac{\Delta V_o}{\Delta V_i}$  is 1. Which says that there is no marked improvement in the response of the comparator arrangement.

### 2.5 Some applications of comparators:

#### (i) Measurement of time delays:


In the comparator shown before, if  $V_{R1}$  is the reference level in the first comparator (double differentiator) then a pulse is generated with a peak at  $t = t_1$ . If  $V_{R2}$  is the reference level set in a second comparator then the pulse is generated with peak at  $t = t_2$ .

Then the time difference between the two pulses is simply

$$t_2 - t_1 = (V_{R2} - V_{R1})/\alpha$$

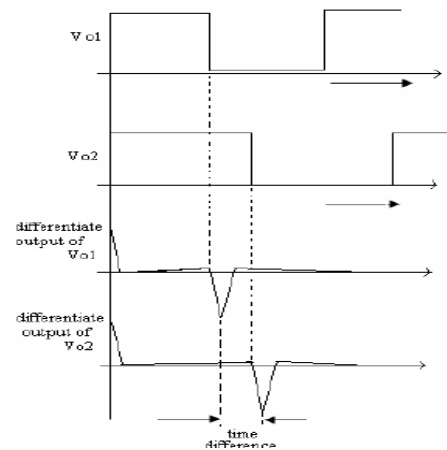
#### (ii) Timing markers generated from sine wave:

If a sine wave is applied as input, when the input reaches  $V_R$  output of the comparator is high till again the input reaches  $V_R$ . Differentiate and clip negative spikes. We have positive spikes which can be implemented as timing markers.



(iv) **Square waves from sine waves:** In regenerative comparator (Schmitt trigger) if the reference voltage is  $+V_{ref}$ , the output goes to  $+V$  or  $-V$

## Pulse & Digital Circuits

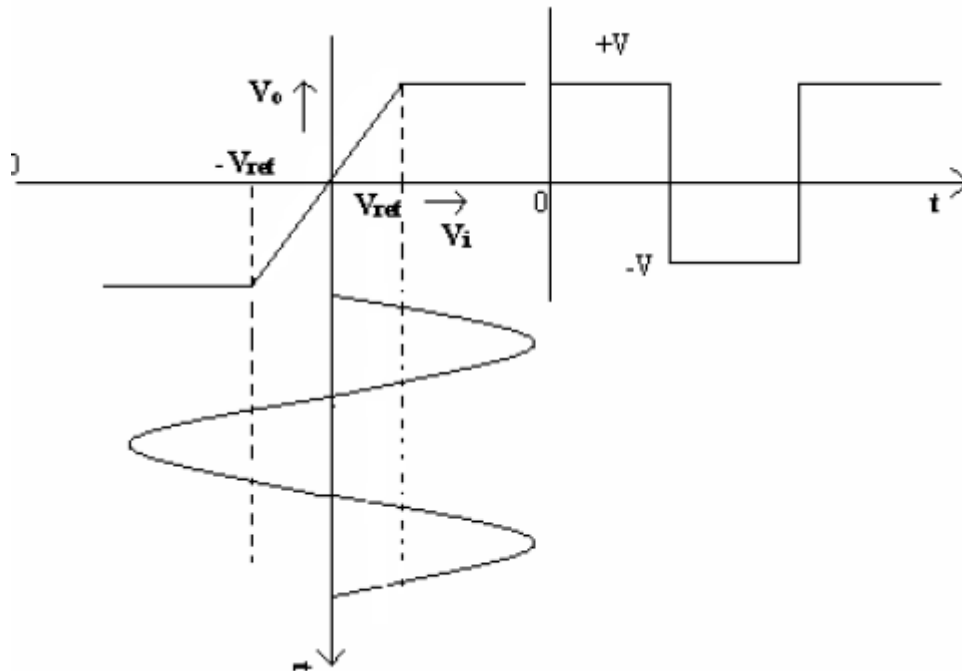


## NON-LINEAR WAVESHAPING - CLAMPING CIRCUITS

### 2.6 clamping operation:

#### Introduction:


The establishment of extremity of positive or negative signal excursion at some reference level  $V_R$  is called Clamping. Clamping circuits introduce the dc component lost during transmission through a capacitive coupled network. Circuits that clamp the positive peak of the signal to zero level are called negative clampers and those that clamp the negative peak of the signal to zero level are called positive clampers. If a non-sinusoidal periodic signal is transmitted through a network having capacitive coupling, the dc component in the output is lost since the capacitor blocks the dc. If there arises the need once again that dc component is to be restored, this is done by a clamping circuit. A clamping circuit is, therefore, called a dc restorer or dc reinserted. As such, the output can be referenced to any arbitrarily chosen reference level.

## Pulse & Digital Circuits

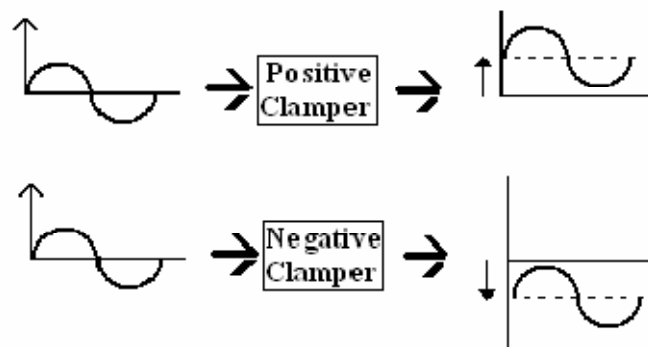

### The clamping circuit:

The circuit in fig below is the basic clamping circuit.

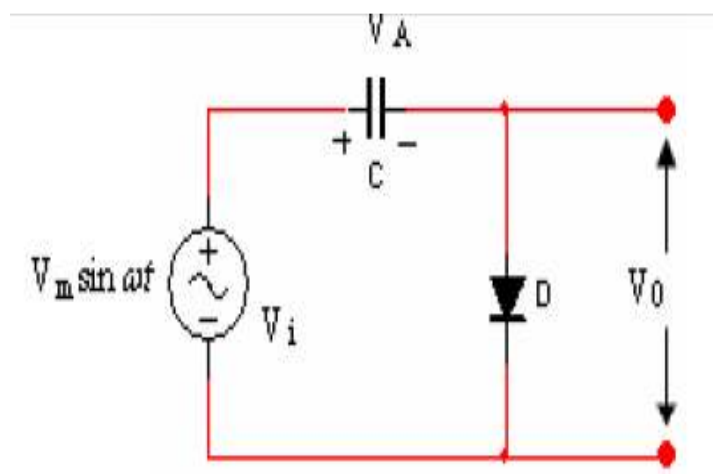

**Fig. Negative Clamping circuit**

As the input rises from 0 to  $V_m$  in the first quarter cycle fig.4.2a,  $C$  charges to  $V_m$ . During this period,  $V_0 = 0$ . i.e. the output is zero for the first quarter cycle since  $D$  conducts. The input falls after the first quarter cycle.  $V_i < V_m$ , the charge on the capacitor. As a result the diode is reverse biased by a voltage  $(V_i - V_m)$ . Hence  $D$  is OFF.

$$V_0 = V_i - V_m \quad \text{----- 1}$$


The voltage across  $C$  remains unchanged.

From equation .1----.If  $V_i = 0$ ,  $V_0 = -V_m$

And if,  $V_i = -V_m$ ,  $V_0 = -V_m - V_m = -2V_m$


## Pulse & Digital Circuits

During the next cycle, the positive peak of the output just reaches the zero level. Hence in the output, the positive peak is clamped to zero level and this is repeated for succeeding cycles. The input, output waveforms are represented in fig.2

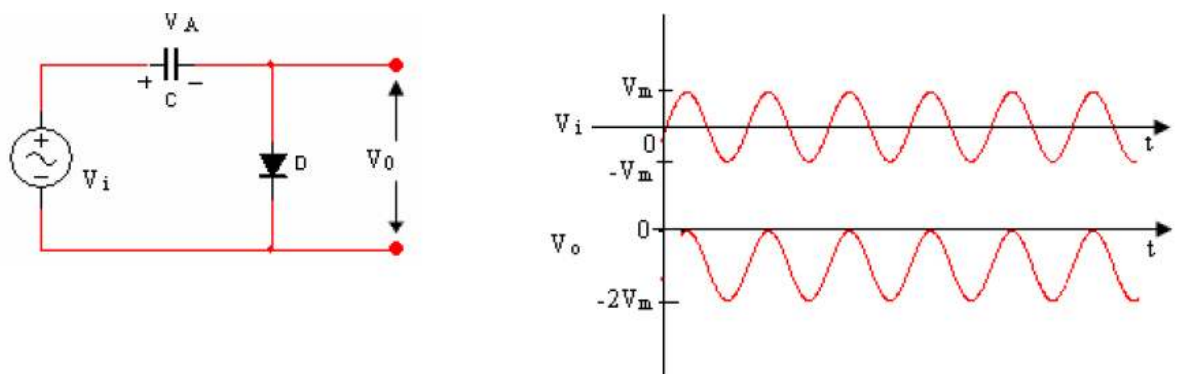

**Fig.2 input – output waveforms of negative clamp**

The input to this circuit is a sinusoidal with zero reference level. The output is referenced to  $-V_m$  and the positive peak is clamped to zero. When the input decreases, to clamp the positive peak to zero level, the voltage across the capacitor should change to the peak amplitude of the new input. But there is no discharge path for the capacitor to discharge. For this a resistance  $R$  is provided in shunt with the diode  $D$  fig.3

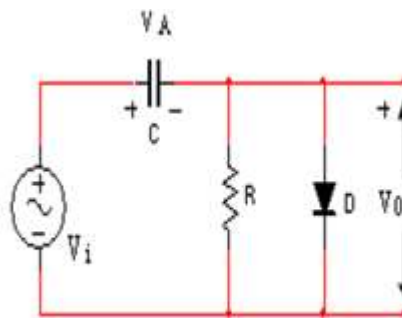

**Fig. clamping circuit with  $R$  shunted across diode  $D$**



## Pulse & Digital Circuits


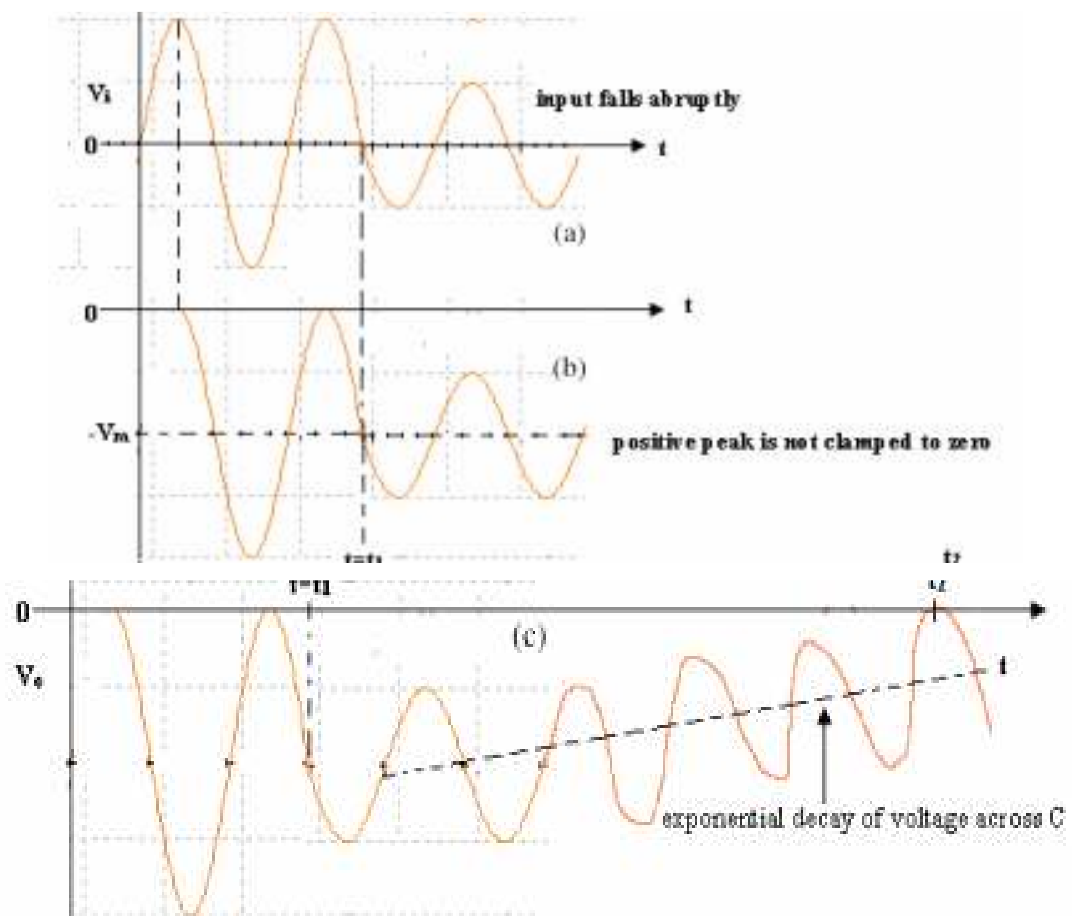
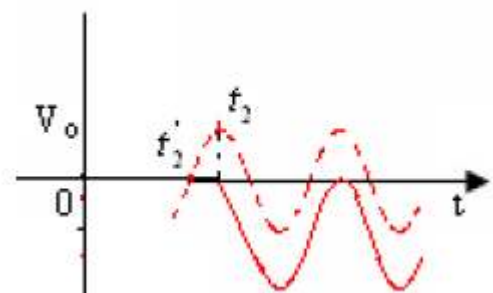


Fig. a) input b) Output when  $R = \infty$  c) output with finite  $R$

At  $t = t_1$ , if the input amplitude is abruptly reduced, as the voltage across the capacitor cannot change instantaneously, the positive peaks will not reach zero level. But now as the charge on  $C$  is going to discharge, as the voltage across the capacitor varies exponentially with a time constant  $\tau = RC$ , the output reaches zero level at  $t = t_2$ , the positive peak is again clamped to zero, after few cycles

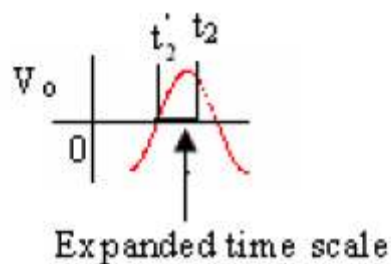

## Pulse & Digital Circuits

### Fig. Output with expanded time scale in the neighborhood of a positive peak

In the vicinity of a positive peak  $D$  conducts and at  $t = t_1$ ,  $V_0 = 0$ . If there were to be no diode, the output should have followed the dashed line with the peak at  $t = t_2$ . But because of the diode, the output is zero from  $t_1$  to  $t_2$  and in the subsequent cycles the positive peaks of the sinusoidal are clamped to zero.

### 2.7 Clamping circuit theorem:

Under steady state conditions the area under the forward biased condition and the area under the reverse biased condition are related as  $A_f/A_r = R_f/R$

#### proof:

for forward biased condition charging of capacitor can be done and charge stored on capacitor is  $Q_1 = A_f/R_f$


for reverse biased condition discharging of capacitor can be done and CHARGE LOST BY capacitor is  $Q_2 = A_r/R$ .

under steady state conditions charge gained by the capacitor equal to charge lost hence we can get

$$A_f/A_r = R_f/R$$
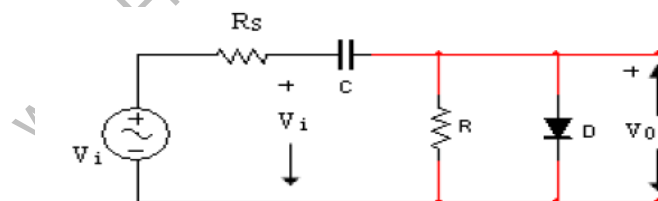
### 2.8 Clamping circuit with diode and source resistances:

Consider now the internal resistance of the source,  $R_s$ , as shown in Fig.



When the input is applied, the output reaches the steady-state value after a few cycles and the positive peaks are clamped to zero. Consider the equivalent circuits

- (i) When the diode is ON,

## Pulse & Digital Circuits

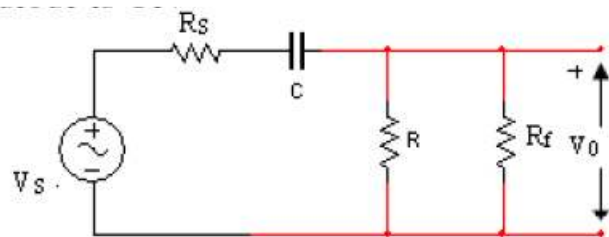


Fig.ii) Circuit when the diode is ON

(i) When the diode is ON

As  $R_f \ll R$ , this circuit reduces to


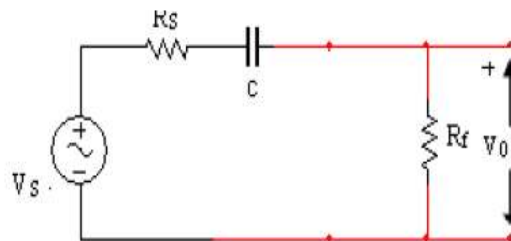


Fig.ii) Circuit when the diode is ON


This circuit, for the purpose of computing the output may be redrawn as fig.iv

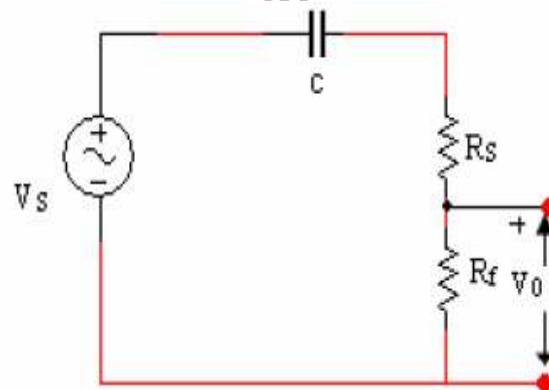

**Fig.Circuit to calculate the output when the diode is ON**


(ii) when the diode is OFF

## Pulse & Digital Circuits

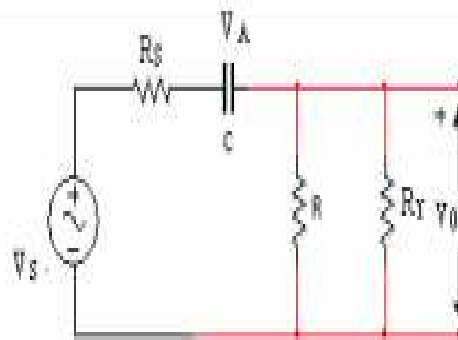

circuit when D is OFF

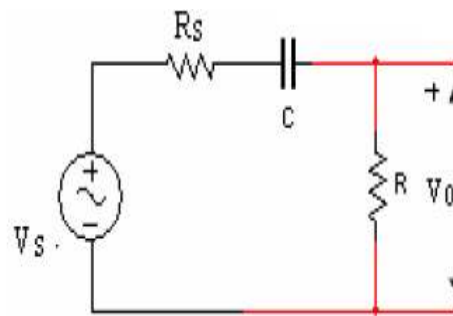As  $R_Y \gg R$ , this circuit reduces to



Again, for computing the output this circuit is redrawn as in Fig

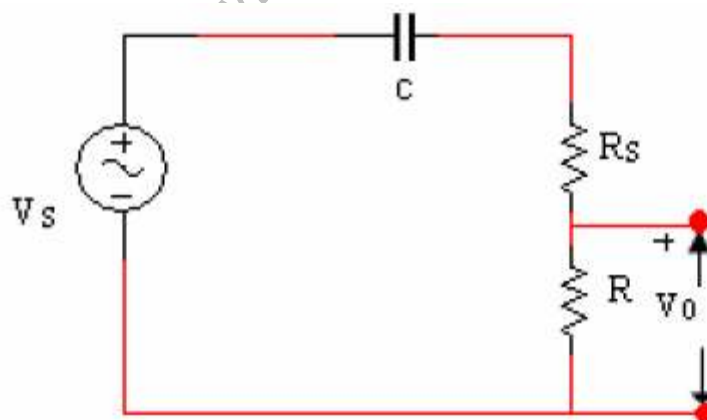



Fig.Circuit to calculate the output when the diode is OFF

## Pulse & Digital Circuits
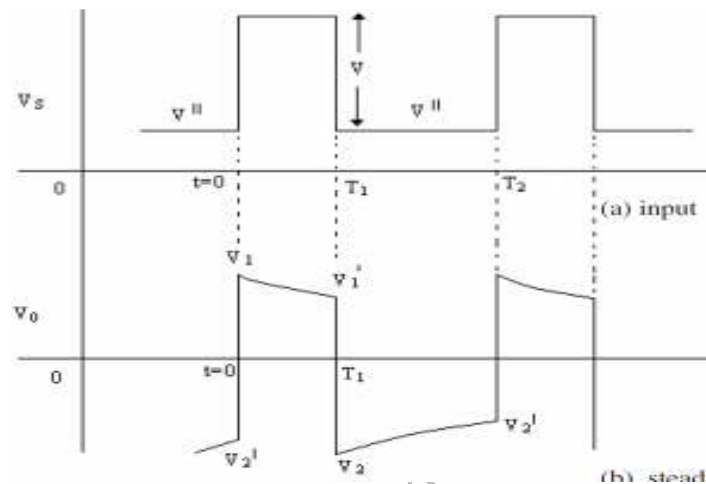
### 2.9 Practical clamping circuits

If a square wave is applied as input to a clamping circuit, the output reaches the steady state value after a few cycles.

Hence for the input in Fig.(a) the output of the clamping circuit is given in (b).




(a) input

(b) steady-state output
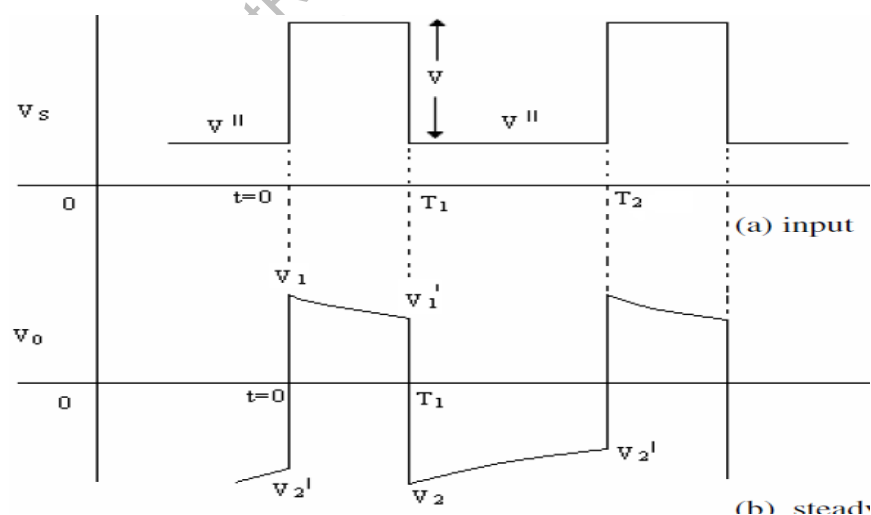
#### Input and steady-state output of the clamping circuit

The output at steady-state is as in figure above with voltage levels  $V_1$ ,  $V^H$ ,  $V_2$  and



## Pulse & Digital Circuits


Input and steady-state output of the clamping circuit

The output at steady-state is as in figure above with voltage levels  $V_1$ ,  $V_1^1$ ,  $V_2$  and  $V_2^1$ . This output can be plotted to scale if the voltages  $V_1$ ,  $V_1^1$ ,  $V_2$  and  $V_2^1$  are calculated. To calculate these four unknowns, we need four equations and these four equations are obtained as follows.fig.

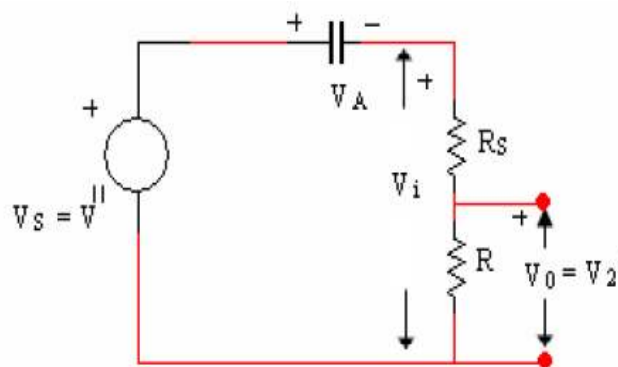(a) consider the situation at  $t = 0^-$

At  $t = 0^-$ ,  $V_s = V_1^1$  and  $V_0 = V_2^1$

The diode is reverse biased and the corresponding equivalent circuit is



The voltage across the capacitor terminals at  $t=0^-$  is

$$V_A(0^-) = V_s - V_i \quad \text{-----} \quad 2$$

$$V_s = V_1^1 \quad \text{and} \quad V_2^1 = V_i \frac{R}{R_s + R}$$

$$\therefore V_i = V_2^1 \frac{(R_s + R)}{R}$$


Substituting the values of  $V_s$  and  $V_i$  in equation 2

$$\therefore V_A(0^-) = V_1^1 - V_2^1 \frac{(R_s + R)}{R} \quad \text{-----} \quad 3$$

(b) Consider the situation at the instant  $t = 0^+$

At  $t = 0^+$ ,  $V_s = V_1^1$  and  $V_0 = V_1$ . the diode is ON and the corresponding equivalent circuit is

## Pulse & Digital Circuits

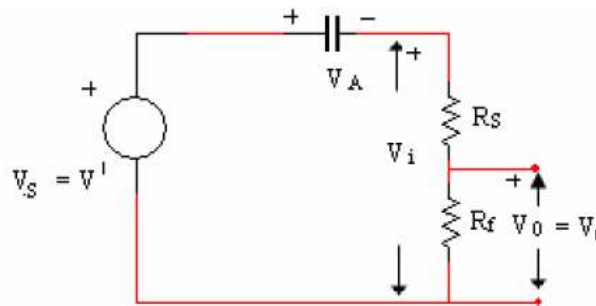

The voltage across the capacitor terminals at  $t = 0+$  is

$$\begin{aligned} V_A(0+) &= V_s - V_i \\ &= V^1 - V_i \end{aligned}$$

$$V_1 = V_i \frac{R_f}{R_s + R_f},$$

$$\therefore V_i = \frac{(R_s + R_f)}{R_f} V_1$$

$$\therefore V_A(0+) = V^1 - \frac{(R_s + R_f)}{R_f} V_1 \quad \text{-----} \quad 4$$

Since the voltage across the capacitor cannot change instantaneously

$$V_A(0-) = V_A(0+)$$

Hence, from equations 3 and 4

$$V^{11} - \frac{R + R_s}{R} V_2^1 = V^1 - V_1 \frac{R_s + R_f}{R_f} \quad \text{-----} \quad 5$$


The peak-to-peak amplitude of the input is  $V$ . Therefore

$$V = V^1 - V^{11}$$

$$\text{From equation 5, } V = V^1 - V^{11} = V_1 \frac{R_s + R_f}{R_f} - \frac{R + R_s}{R} V_2^1 \quad \text{-----} \quad 6$$

Once again consider the situation at  $t = T_1^-$ ,  $V_s = V^1$  and  $V_0 = V_1^1$  and the diode is ON

$$V_A(T_1^-) = V_s - V_i$$

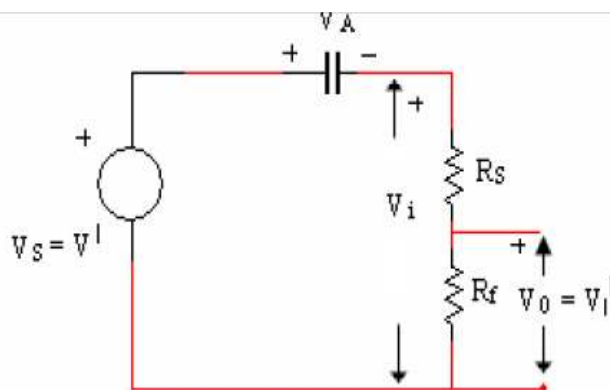



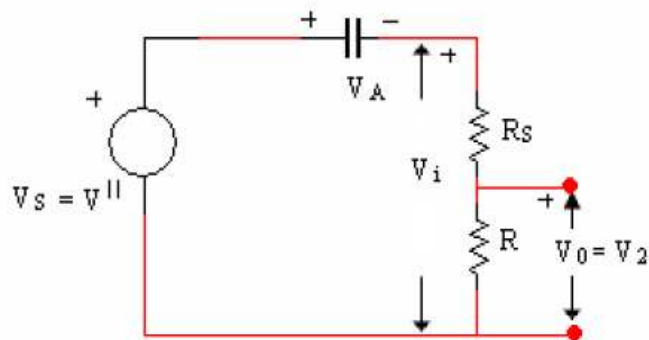
## Pulse & Digital Circuits

$$= V^1 - \frac{R_f + R_s}{R_f} V_1^1 \quad \text{-----} \quad 7$$

Similarly, at  $t = T_1 +$  from the equivalent circuit, since D is OFF



$$\begin{aligned} \therefore V_A(T_1+) &= V_s - V_i \\ &= V^{11} - \frac{R + R_s}{R} V_2 \quad \text{-----} \quad 8 \end{aligned}$$

Again as  $V_A(T_1-) = V_A(T_1 +)$ , from equations 7 and 8

$$\begin{aligned} V^1 - \frac{R_f + R_s}{R_f} V_1^1 &= V^{11} - \frac{R + R_s}{R} V_2 \\ V &= V^1 - V^{11} = \frac{R_f + R_s}{R_f} V_1^1 - \frac{R + R_s}{R} V_2 \quad \text{-----} \quad 9 \end{aligned}$$

Further at  $t = 0+$ ,  $V_0 = V_1$  and in the interval 0 to  $T_1$ ,  $V_0$  decays with a time constant  $(R_f + R_s)C$

$$\text{Hence, } V_1^1 = V_1 e^{\frac{-T_1}{(R_f + R_s)C}} \quad \text{-----} \quad 10$$

Similarly in the interval  $T_1$  to  $T_2$ , the diode is reverse biased and the circuit time constant is  $(R_s + R)C$

The voltage  $V_2$  decays to  $V_2^1$

$$V_2^1 = V_2 e^{\frac{-(T_2 - T_1)}{(R_s + R)C}} \quad \text{-----} \quad 11$$



## Pulse & Digital Circuits

---

Equations 6, 9, 10 and 11 will enable us to determine the voltage  $V_1$ ,  $V_1^1$ ,  $V_2$  and  $V_2^1$ . If in the above circuit  $R_s = 0$ .

Equations 6 and 9 reduce to

$$V = V_1 - V_2^1 = V_1^1 - V_2 \quad \text{-----} \quad 12$$

It is evident from the above discussion that the output is independent of the levels  $V^1$  and  $V^{11}$  associated with the input and is only determined by the amplitude  $V$ .

Subtracting equation 9 from equation 6

$$\frac{R_f + R_s}{R_f} (V_1 - V_1^1) - \frac{R + R_s}{R} (V_2^1 - V_2) = 0 \quad \text{-----} \quad 13$$

If  $V_1 - V_1^1 = \Delta_f$  and  $V_2^1 - V_2 = \Delta_r$

From Equation 13

$$\frac{R_f + R_s}{R_f} \Delta_f = \frac{R + R_s}{R} \Delta_r$$

$$\Delta_f = \frac{R_f}{R_s + R_f} \cdot \frac{R + R_s}{R} \Delta_r$$

If  $R_s \ll R$

$$\Delta_f = \frac{R_f}{R_s + R_f} \Delta_r,$$

where  $\Delta_f$  is the tilt in the forward direction and  $\Delta_r$  is the tilt in the reverse direction

Let  $R_s \ll R_f$

Then  $\Delta_f \approx \Delta_r$

## Pulse & Digital Circuits

**A clamping circuit that clamps the output to a reference voltage  $V_R$ :**

The following clamping circuit similar to that we have studied earlier, except for the fact that a reference voltage  $V_R$  is included.



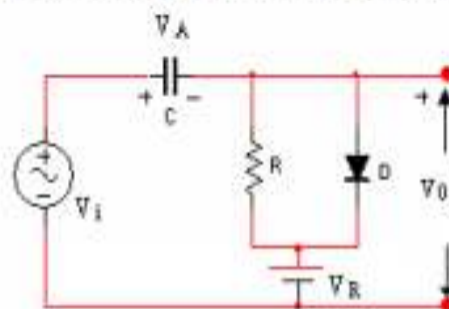


Fig.1 Circuit that clamps the positive peak of the input to  $V_R$

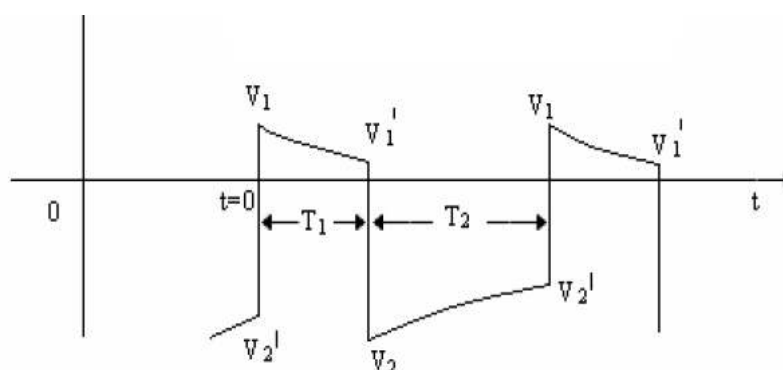To obtain the steady-state response of the circuit, first assume that  $V_R$  is zero. Then this circuit is clamping circuit that clamps the positive peak of the input signal to  $V_g$ . Now the steady-state response for the input of an unsymmetrical square wave, will be as follows,



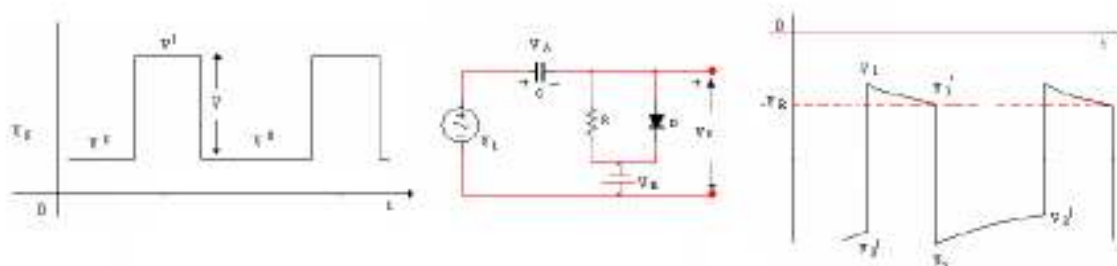Solving four equations (we have discussed earlier) the values of  $V_1$ ,  $V_1'$ ,  $V_2$  and  $V_2'$  can be evaluated. To each of these values calculated add  $V_R$ . With the result, the positive peak in the output is clamped to  $V_R$ .



The positive peak of the input clamped to  $-V_R$

## Pulse & Digital Circuits

### 2.10 Effect of diode characteristics on clamping voltage:

The diode characteristics will also effect the voltage as diode voltage is the clamping voltage,

$I_{cl} = I_o e^{V_{cl}/\eta V_T}$  will be the diode current. For charging of capacitor resistor voltage is equal to

$$R = V_A - V'' = V - V_{cl}$$

$$V_{cl} \ll V. \text{ Hence } V - V_{cl} = V$$

Charging current=discharging current

$$I_{cl} = \frac{V}{R} = I_o e^{(V_{cl}/\eta V_T)}$$

$$\frac{V}{I_o R} = e^{(V_{cl}/\eta V_T)}$$

$$V_{cl} = \eta V_T \ln \frac{V}{R I_o}$$

$$dV_{cl} = \eta V_T \frac{dV}{V}$$

From the above equation we can say that the diode will effect the voltage as diode voltage is the clamping voltage,


### Important Questions:

- 1.what is clipping?what are the types of clippers?
- 2.what is non linear wave shaping?
- 3.what is clamping ?what are the types of clamping?
- 4.explain the effect of diode charecterestics on clamping voltage?
- 5.state clamping circuit theorem?

## Pulse & Digital Circuits

### 3. SWITCHING CHARACTERISTICS OF DEVICES SYLLABUS:

Transistor and diode as a Switch - Switching times of a transistor. Transistor acts as a switch, Breakdown voltage consideration of transistor, saturation parameters of transistor and their variation with temperature, design of transistor switch, transistor switching times.

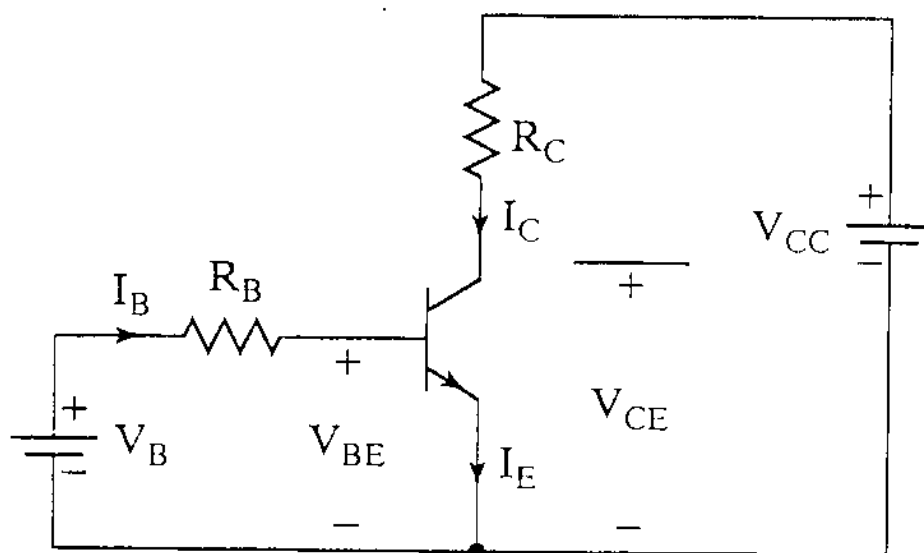

**Fig. Transistor as a switch**

Above diagram represents the operation of transistor as a switch.

The transistor operates as a switch in two regions mainly

- 1. Saturation region:** In this region transistor acts as closed switch.
- 2. Cut-off region:** In this region transistor acts as closed switch

By applying KCL to above circuit,

## Pulse & Digital Circuits

$$I_B = \frac{V_B - V_{BE}}{R_B}$$

$$V_{CE} = V_{CC} - I_C R_C$$


$$V_{CE} = V_{CB} + V_{BE}$$

$$V_{CB} = V_{CE} - V_{BE}$$

### 3.2 Switching characteristics of devices
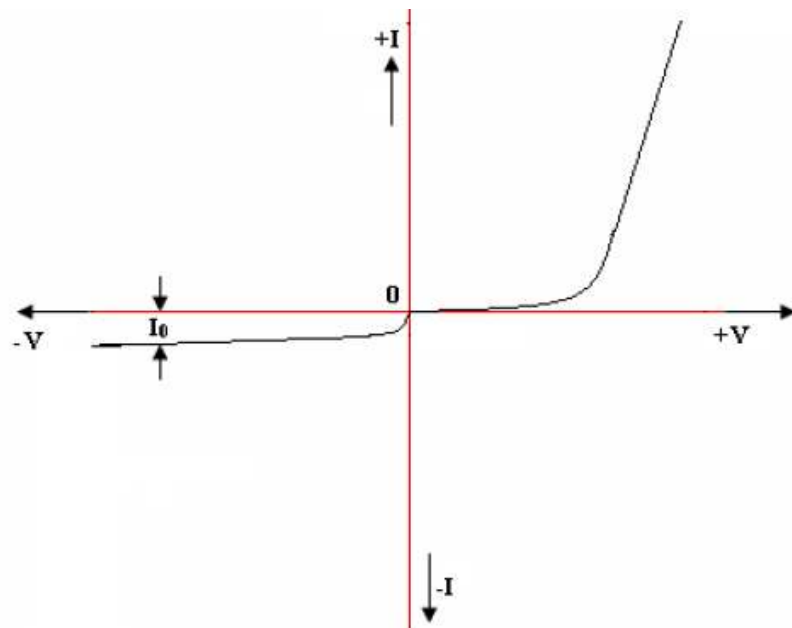
#### Diode as a switch:

A PN junction diode can be used as a switch. When diode is forward biased, the switch is said to be in the ON state and in reverse-bias, the switch is in the OFF state. The V-I Characteristic of a PN junction diode is shown here.



V-I characteristic of a PN diode

The diode current is given by the relation

$$I = I_0 \left( e^{\frac{V}{\eta V_T}} - 1 \right)$$

Where V is the bias voltage,  $\eta = 1$  or  $2$  depending on whether the diode is Ge or Si and

$V_T$  is the Volt-equivalent for temperature and at room temperature  $V_T = 26\text{mV}$ .

## Pulse & Digital Circuits

If 
$$e^{\frac{V}{\eta V_T}} \gg 1,$$

equation 5.1 reduces to

$$I = I_0 e^{\frac{V}{\eta V_T}}$$


When the diode is forward biased  $V$  is positive and  $I$  is a positive current which varies exponentially with the variation of  $V$ . When the diode is reverse-biased  $V$  is a negative voltage and the current  $I$  now flows in the opposite direction.  $I = -I_0$ , the reverse saturation current gets doubled for every 100C rise in temperature.

When a diode is used as a switch, the device should be ON or OFF depending on the polarity of the signal applied to change state.

**Junction diode switching times:**

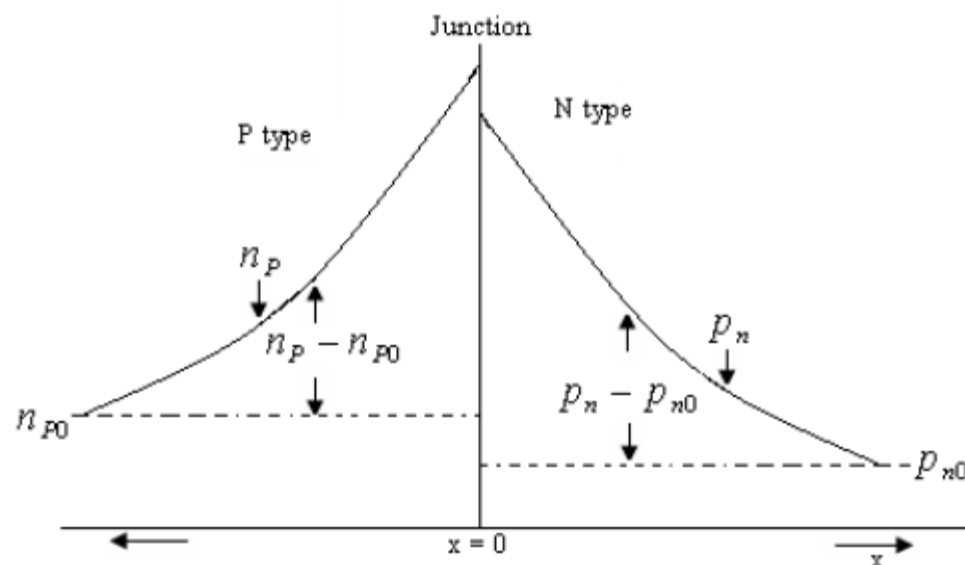**Reverse recovery time of the diode:**

Let the diode be ON for some time, as a result there is a large current due to injected hole or electron density.



## Pulse & Digital Circuits

**Fig.a Minority carrier density distribution as a function of  $x$ , the distance from the junction when the diode is ON**

$p_{n0}$  = density of holes on the n-side at equilibrium


$n_{p0}$  = density of electrons on the P-side at equilibrium

$n_p$  = density of electrons on the P-side when forward biased

$p_n$  = density of holes on the n-side when forward biased

$p_n - p_{n0}$  = injected or excess hole density on the n-side


$n_p - n_{p0}$  = injected or excess electron density on the P-side

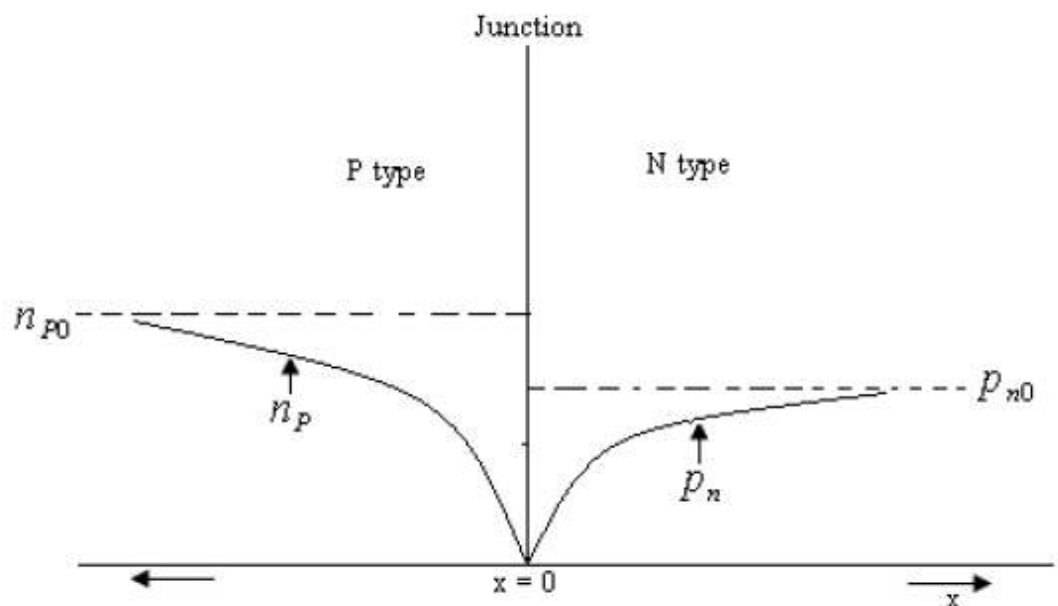

**Fig.b Minority carrier density distribution as a function of  $x$ , the distance from the junction when the diode is OFF**

When the diode is ON the number of minority carriers is large fig (a). When the polarity of the external voltage is suddenly reversed, the diode forward current when ON being large is to be reduced to reverse current which is very small. But this is not happened as it takes a finite time delay for the minority carrier density distribution to take the form shown in fig. During this period the injected minority carrier density will drop to zero and the minority carrier density reaches the equilibrium value.

## Pulse & Digital Circuits

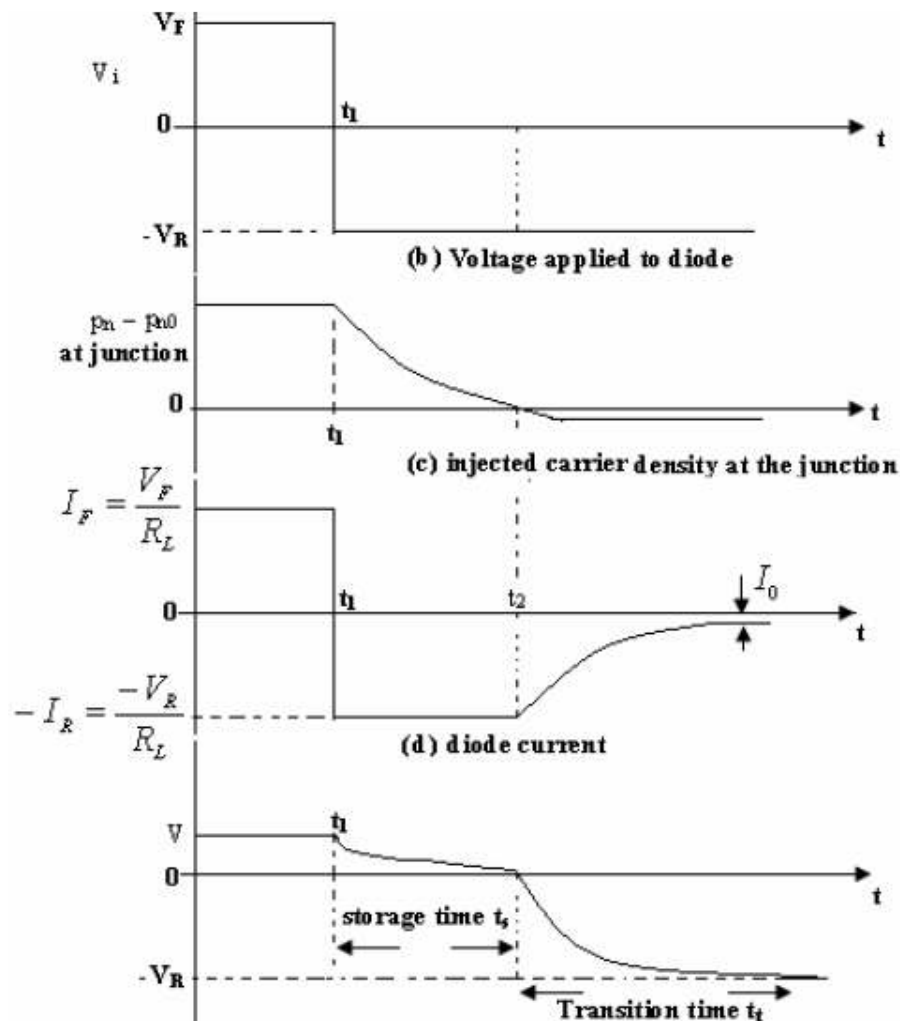

As long as the voltage  $V_i = V_F$  till  $t_1$ , the diode is ON. The forward resistance of the diode being negligible when compared to  $R_L$ , therefore

$$I_F = \frac{V_F}{R_L}$$

At  $t = t_1$ , the polarity of  $V_i$  is abruptly reversed, i.e.  $V_i = -V_R$  and  $-I_R = \frac{-V_R}{R_L}$  until  $t = t_2$  at which time minority carrier density  $p_n$  at  $x = 0$  has reached the equilibrium value  $p_{n0}$ .

At  $t = t_2$  the charge carriers have been swept, the polarity of the diode voltage reverses, the diode current starts to decrease. The time duration,  $t_1$  to  $t_2$ , during which period the stored minority charge becomes zero is called the **storage time  $t_s$** .



## Pulse & Digital Circuits

The time interval from  $t_2$  to the instant that the diode has recovered ( $V = -V_R$ ) is called the **transition time,  $t_T$** .


The sum total of the storage time,  $t_s$  and the transition time,  $t_t$  is called the reverse recovery time of the diode,  $t_{rr}$ .

$$\therefore t_{rr} = t_s + t_t$$

### Transistor switching times

Let the input to the transistor switch be a pulse of duration  $T$ .

When a pulse is applied, because of stray capacitances, collector current will not reach the steady state value instantaneously. To know exactly when the device switches into the ON state and also into the OFF state we define the following switching times of the transistor.

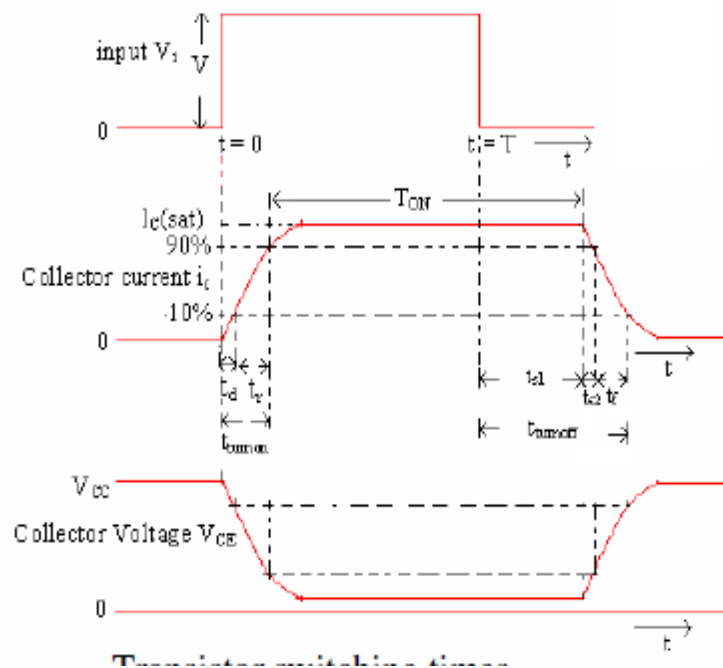

**Fig. Transistor switching times**

**Delay Time,  $t_d$ :** It is the time taken for the collector current to reach from its initial value to 10% of its final value, If the rise of the collector current is linear, the time required to rise to 10%  $I_C(\text{sat})$  is  $1/8$  the time required for the current to rise from 10% to 90%  $I_C(\text{sat})$ .

It is given as

## Pulse & Digital Circuits

---

$$t_d = \frac{1}{8} t_r$$

where  $t_r$  is the rise time

**Rise Time,  $t_r$  :** It is the time taken for the collector current to reach from 10% of its final value to 90% of its final value.

However, because of the stored charges, the current remains unaltered for sometime interval  $t_{s1}$  and then begin to fall. The time taken for this current to fall from its initial value at  $t_{s1}$  to 90% of its initial value is  $t_{s2}$ . The sum of these  $t_{s1}$  and  $t_{s2}$  is approximately  $t_{s1}$  and is called the storage time.

**Storage time,  $t_s$  :** It is the time taken for the collector current to fall from its initial value to 90% of its initial value. Storage time

$$t_s \cong \tau_s \ln \frac{I_{B1} - I_{B2}}{I_{B \min} - I_{B2}}$$

$I_{B1}$  is the base current when the pulse amplitude is  $V (=12 \text{ V})$  and  $I_{B2}$  is the base current when the pulse amplitude is zero.

**Fall time,  $t_f$  :** It is the time taken for the collector current to fall from 90% of its initial value to 10% of its initial value.

## Pulse & Digital Circuits

### UNIT III & IV

#### Multivibrators

Multi vibrators are cross-coupled two-stage regenerative amplifiers acting as switching circuits. Multi vibrators are broadly classified as

1. Bistable multi or binary or Flip-Flop
2. Monostable multi or One shot multi or univibrator
3. Astble multi or Freerunning multi

Multivibrators are extensively used in digital and switching applications. A bistable multivibrator remains in one of the stable states until we are asked to change. Hence this circuit is essentially used as a memory element in digital circuits..

A monostable multi has only one stable state and one quasi-stable state. Initially the multi is in stable state. After the application of a trigger, the multi goes into the quasi-stable state and stays there for a finite time and will return back to the initial stable state. Such a circuit is used as a gate. Other type of multivibrator is an Astable multi which has two quasi-stable states. This means that change of state occurs in the multi simultaneously. So, the output of this multi is a square wave. The output of an astable multi is normally used as a clock signal in digital circuits.

#### Bistable multivibrators

##### Introduction:

This circuit has two devices Q1 and Q2. Let initially be Q1, OFF and Q2 ON. On the application of a trigger Q1 goes to ON and Q2 goes to OFF. When next trigger is applied Q1 goes OFF and Q2 goes ON. If the ON device is driven in to saturation, the Binary is called saturating Binary. If on the other hand, the ON device is held in the active region, the binary is called a non-saturating binary.


Consider two types of Bistable multivibrator circuits.

1. Fixed bias binary
2. Self bias binary

##### Fixed bias binary:

The circuit shown in fig. below is a fixed-bias binary

## Pulse & Digital Circuits

 


Let initially Q1 be OFF and Q2 be in ON. Then the voltage at the first collector is  $V_{CC}$  and the voltage at the second collector is  $V_{CE(sat)}$ . If a negative trigger is applied at the base of the ON device (Q2), Q2 goes into the OFF i.e. its collector voltage rises to  $V_{CC}$ . Consequently Q1 goes into the ON state and its collector voltage falls to  $V_{CE(sat)}$ .

### Design of a fixed bias binary:

Design a fixed bias binary with supply voltages +12V, NPN silicon devices having  $V_{CE(sat)} = 0.2V$ ,  $V_{BE(sat)} = 0.7V$  and  $h_{FEmin} = 50$  are used.

Assume  $I_C = 5mA$ .

## Pulse & Digital Circuits

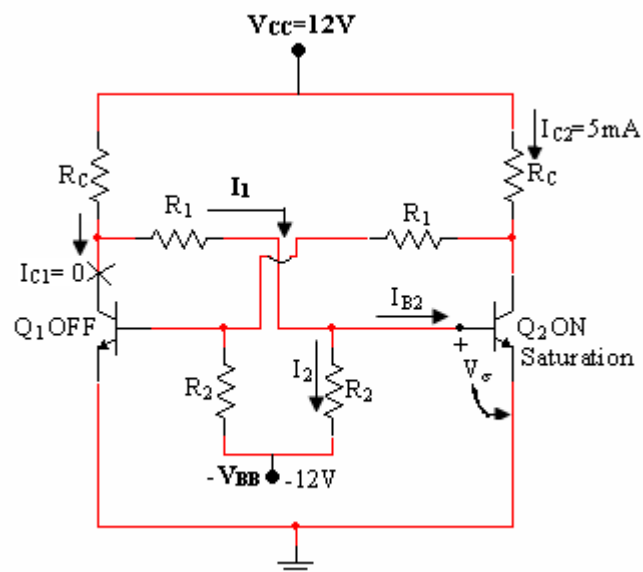

$$R_C = \frac{V_{CC} - V_{CE(sat)}}{I_{C2}} = \frac{12 - 0.2V}{5mA} = \frac{11.8V}{5mA}$$

$$= 2.36K\Omega$$

$$\approx 2.2K \text{ (standard resistance)}$$

$$R_2 = \frac{V_{ce} - (-V_{BB})}{I_2}$$

$$\text{Choose } I_2 \approx \frac{1}{10} I_{C2}$$

$$= 0.5mA$$

$$\therefore R_2 = \frac{0.7 + 12}{0.5} = \frac{12.7V}{0.5mA} = 25.4K\Omega$$

$$\approx 22K\Omega$$

If Q2 is in saturation

## Pulse & Digital Circuits

$$I_{B2} = 1.5 I_{B2 \min}$$

$$= 0.15 \text{ mA}$$

$$I_1 = I_2 + I_{B2}$$


$$= 0.5 \text{ mA} + 0.15 \text{ mA} = 0.65 \text{ mA}$$

$$R_C + R_1 = \frac{V_{CC} - V_{CE}}{I_1} = \frac{12 - 0.7}{0.65 \text{ mA}} = \frac{11.3 \text{ V}}{0.65 \text{ mA}} = 17.38 \text{ K}\Omega$$

$$R_1 = (R_C + R_1) - R_C$$

$$= 17.38 - 2.36 = 15.02 \text{ K}\Omega$$

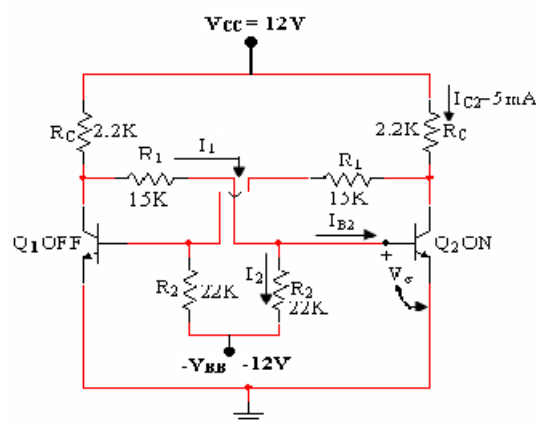The circuit, so designed, with component values indicated is shown below:



$$= 0.94 \text{ mA}$$

$$I_{B2} = I_1 - I_2$$

$$= 0.94 \text{ mA} - 0.58 \text{ mA}$$

$$= 0.36 \text{ mA}$$

$$I_{B2} \geq I_{B2 \min}$$

Hence  $Q_2$  is in saturation

$$V_{B1} = V_{CE}(\text{sat}) \frac{R_2}{R_1 + R_2} - V_{BB} \frac{R_1}{R_1 + R_2}$$

$$= 0.2 \times \frac{22}{10 + 22} - 12 \times \frac{10}{10 + 22}$$

$$= 0.137 - 3.75$$

$$= -3.613 \text{ V}$$

Hence  $Q_1$  is OFF

### 3.4 Resolution time of a binary:

## Pulse & Digital Circuits

It is the sum of settling time and transition time of a binary is called resolution time.

### 3.5 Methods of improving resolution time:

1. By reducing stray capacitances.
2. By not allowing transistors to go into saturation.


### 3.6 Methods of triggering a binary:

To change the binary from one stable state to the other, a pulse of short duration with sufficient amplitude (called trigger) of proper polarity should be applied at the input(output) of an active device the circuit. The trigger can be a dc trigger or it can be a pulse trigger. There are two triggering methods to change the state of multivibrator.

1. Unsymmetrical triggering
2. Symmetrical triggering.
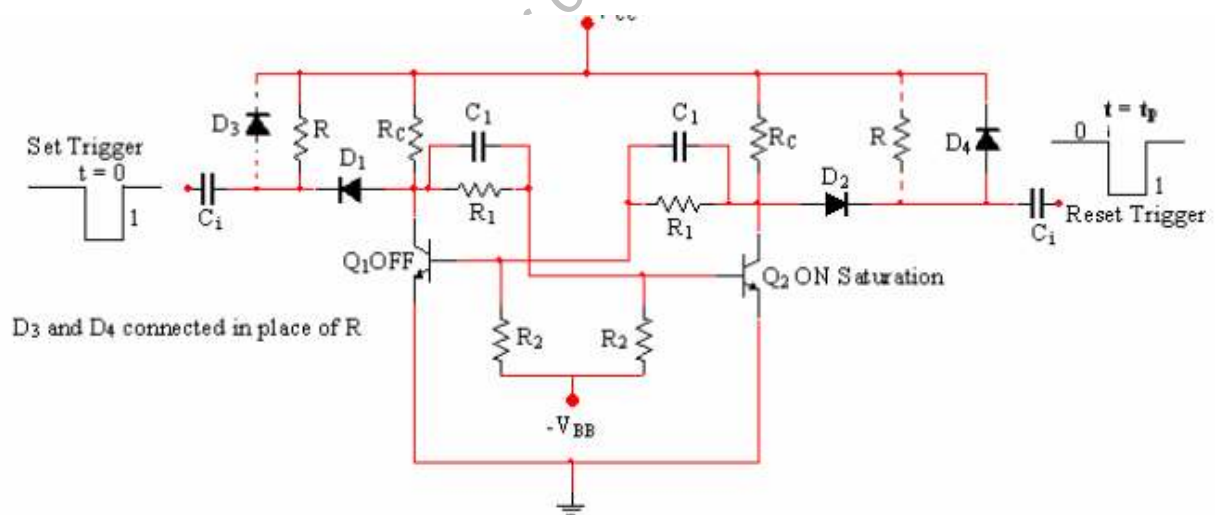
#### Unsymmetrical triggering:

In unsymmetrical triggering, one trigger pulse, taken from a source, is applied at one point in the circuit. The next trigger pulse taken from a different source is applied at a different point in the circuit as shown below.



#### Unsymmetrical triggering of a binary


Let the trigger be applied to the collector C1 of the circuit at  $t=0$ . If Q1 is OFF, D1 is ON and this negative pulse appears at the base of Q2 as the first collector and second base are connected. Q2 goes into the OFF state and Q1 into the ON state. The next through C1 trigger pulse, i.e. the Reset pulse, is applied through D2 at the second collector C2 which is coupled

## Pulse & Digital Circuits

to the first base through  $C_1$ .  $Q_1$  now goes into the OFF state and  $Q_2$  into the ON state. Unsymmetrical triggering is used to generate a gated output, the width of this gate must be at least equal to the spacing between two successive triggers. To prevent the loading down problem from the trigger source,  $R$  should be large. But when a trigger is applied, a charge is built up on the condenser  $C_i$ . If the charge is to be quickly removed before the application of the next trigger signal at this terminal,  $R$  should be small. So while choosing the value of resistance  $R$  a compromise is necessary single resistance cannot simultaneously satisfy these two requirements. Hence in place of  $R$ , diodes  $D_3$  and  $D_4$  are used. When a pulse appears, the diode is OFF ( $D_3$  or  $D_4$ ), a large reverse resistance of the diode appears in place of  $R$ . Otherwise the diode is ON offering negligible resistance so that the charge on the capacitance can be quickly removed.
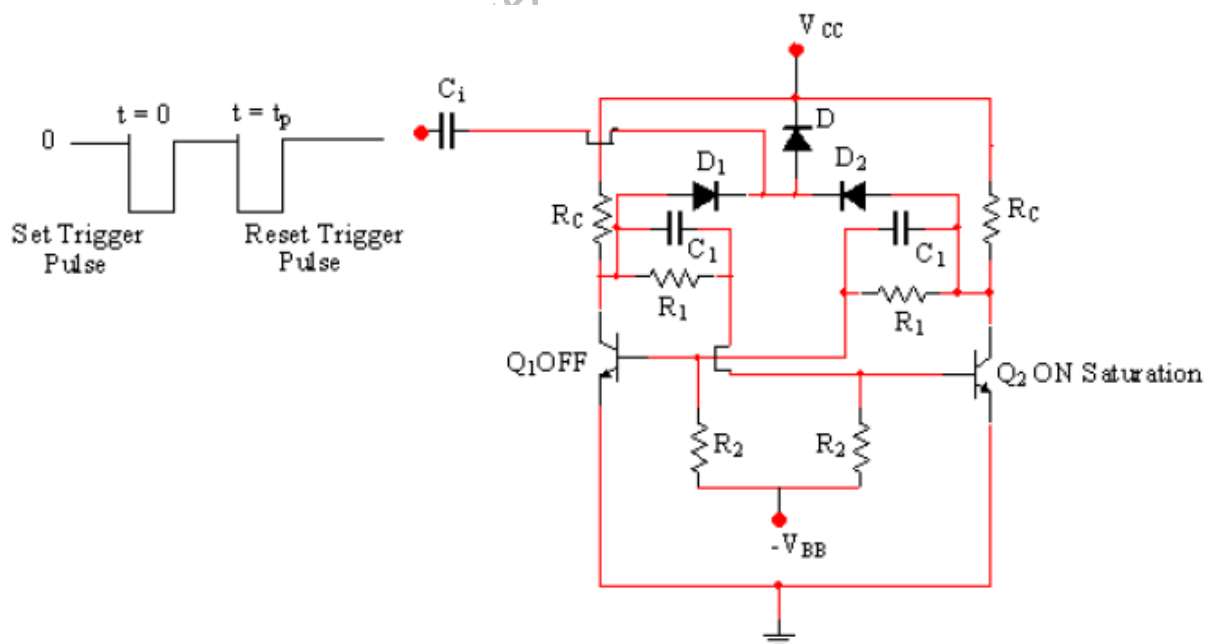
### Symmetrical triggering:

In symmetrical triggering, one triggering pulse generator is taken to change from one stable state to the other in one direction. The same is used to change the state in reverse direction also. This method of triggering is normally used in counters.






## Pulse & Digital Circuits

**Fig. Symmetric triggering of binary**

The purpose of D is similar to the diodes D3 and D4 used earlier. The first trigger pulse makes D1 conduct and this pulse is coupled to the base of Q2 and drives Q2 into the OFF state and Q1 into the ON state. The next trigger pulse applied at  $t = t_p$  is coupled to the base of Q1 as D2 is now ON. Hence Q1 again goes into the OFF state and Q2 into the ON state. D1 and D2 are called steering diodes as these diodes steer the trigger pulse train.
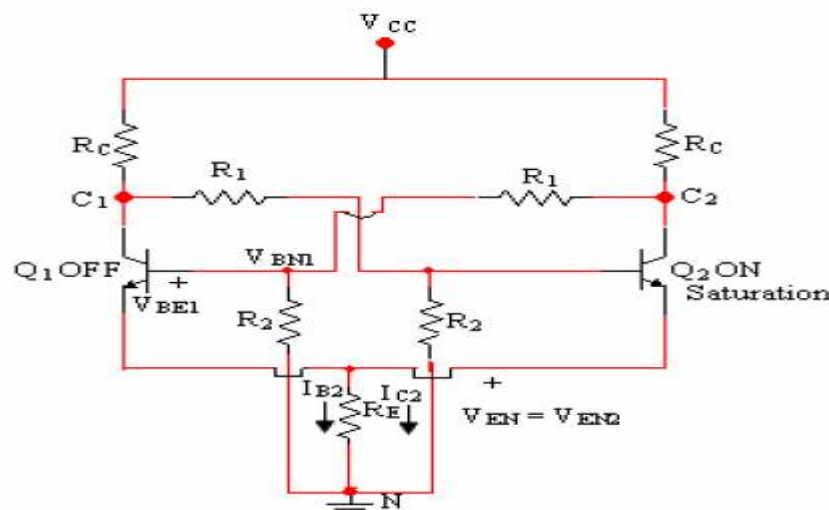
### Self-bias binary :

In a fixed bias binary there are two separate sources, VCC and VBB. Instead two we can design a binary with one power supply using self-bias method.



**Self-bias Binary**


Let Q2 be ON and in saturation, in the initial stable state. As a result  $I_{B2}$  and  $I_{C2}$  flow through  $R_E$  developing a voltage  $V_{EN}$ . The voltage between the base emitter terminals of Q1 is  $V_{BE1}$  and it is  $V_{BE1} = V_{BN1} - V_{EN}$

If this voltage reverse biases the emitter diode of Q1, then Q1 is indeed in the OFF state. To calculate the stable state currents and voltages consider a practical circuit.

In npn silicon transistors are used.  $V_{BE(sat)} = 0.7V$ ,  $V_{CE(sat)} = 0.4V$  and  $h_{FEmin} = 50$ ,  
 $V_{CC} = 20V$ ,  $R_C = 6.7K$ ,  $R_1 = 30K$  and  $R_E = 400\Omega$

Let Q1 be OFF and Q2 be ON. As Q1 is OFF,  $I_{E1} = 0$ . To verify whether Q2 is in Saturation or not, draw the collector loop and base loop of the circuit by theveninising at the collector and base terminals.

## Pulse & Digital Circuits

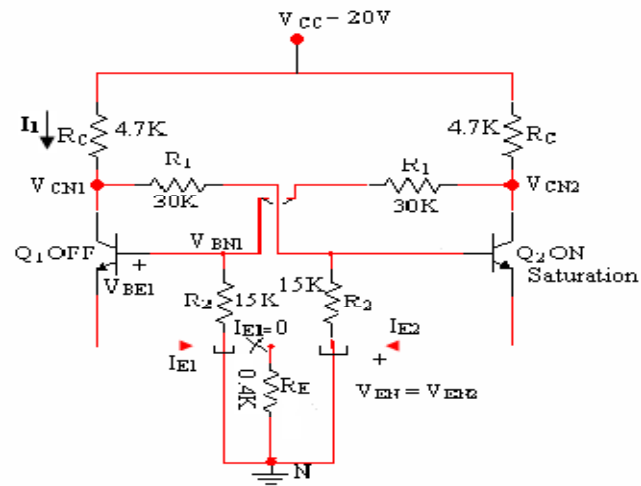

$$V_{thb} = V_{CC} \times \frac{R_2}{R_C + R_1 + R_2}$$

$$= 20 \times \frac{15}{4.7 + 30 + 15}$$

$$= 6.03V$$

and

$$R_{thb} = R_2 // (R_C + R_1) = \frac{R_2 (R_C + R_1)}{R_2 + R_C + R_1}$$

$$= \frac{(15)(30 + 4.7)}{4.7 + 30 + 15}$$

$$= 10.47K$$

$$V_{thc} = V_{CC} \times \frac{(R_1 + R_2)}{R_C + R_1 + R_2}$$

$$= \frac{20 \times (30 + 15)}{4.7 + 30 + 15}$$


$$= 18.10V$$

$$R_{thc} = (R_1 + R_2) // R_C$$

## Pulse & Digital Circuits

$$= \frac{(30 + 15)(4.7)}{30 + 15 + 4.7}$$

$$= 4.25K$$

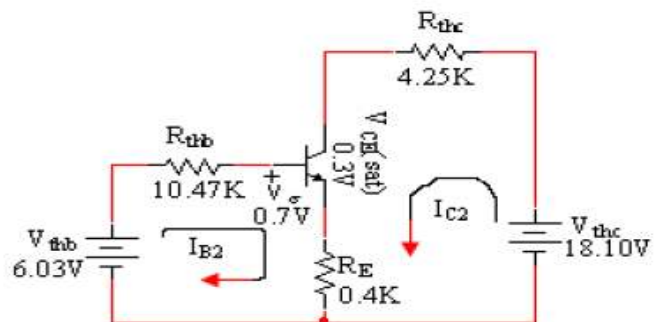

Using KVL at the input and output loops

$$6.03 - 0.7 = (10.47 + 0.4) I_{B2} + 0.4 I_{C2} \quad \text{----- (1)}$$

$$18.10 - 0.3 = 0.4 I_{B2} + (6.25 + 0.4) I_{C2} \quad \text{----- (2)}$$

i.e.

$$5.33V = 10.87 I_{B2} + 0.4 I_{C2}$$

$$17.80V = 0.4 I_{B2} + 6.65 I_{C2}$$

From which

$$I_{B2} = 0.35mA$$

$$I_{C2} = 3.79mA$$

$$I_{B2min} = \frac{I_{C2}}{h_{FE}} = \frac{3.79mA}{50}$$

$$= 0.076mA$$

$$I_{B2} \gg I_{B2min}$$

Hence  $Q_2$  is saturation

$$\therefore V_{EN} = V_{EN2} = (I_{B2} + I_{C2}) R_E$$

$$V_{CN2} = V_{EN2} + V_{CE(sat)}$$

$$= (1.66V + 0.4V) = 2.06V$$

$$V_{BN2} = V_{EN2} + V_{\sigma}$$

$$= (1.66V + 0.7V) = 2.36V$$

$$V_{BN1} = V_{CN2} \times \frac{R_2}{R_1 + R_2}$$

$$= \frac{2.06 \times 15}{15 + 30}$$

$$= 0.69V$$

$$V_{BE1} = V_{BN1} - V_{EN2}$$

$$= (0.69V - 1.66V) = -0.97V$$

As this voltage reverse biases the emitter diode,  $Q_1$  is OFF.

## Pulse & Digital Circuits

$$I_1 = \frac{V_{CC} - V_{BN2}}{R_C + R_1}$$

$$= \frac{20 - 2.36}{4.7 + 30}$$

$$= 0.51 \text{mA}$$

$$V_{CN1} = V_{CC} - I_1 R_C$$

$$= 20 - (0.51)(4.7)$$

$$= 17.6 \text{V}$$

The stable state voltages are


$$V_{CN1} = 17.6 \text{V}, \quad V_{BN1} = 0.69 \text{V}$$

$$V_{CN2} = 2.06 \text{V} \quad V_{BN2} = 2.36 \text{V}$$

$$V_{EN} = 1.66 \text{V}$$
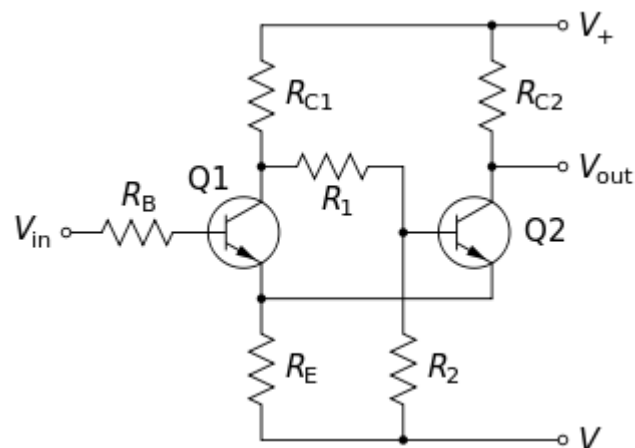
### 3.7 Schmitt trigger:

It is an emitter coupled binary it is also called inverter. The following circuit represents Schmitt trigger.



## Pulse & Digital Circuits

---

**Fig 1 .schmitt trigger**

Schmitt trigger belongs to a class of bistable multivibrator circuits. In a bistable, there exist two D.C. couplings from each output to input of the other. But in Schmitt trigger circuit, there exists only one coupling. It can be recalled that if in the emitter coupled bistable the feedback network from the collector of [transistor](#)  $Q_2$  to the base of transistor  $Q_1$  is removed, it becomes a Schmitt trigger circuit.

The Schmitt trigger is used for wave shaping circuits. It can be used for generation of a square wave from a sine wave input. Basically, the circuit has two opposite operating states like in all other multivibrator circuits. However, the trigger signal is not, typically, a pulse waveform but a slowly varying A.C. Voltage. The Schmitt trigger is level sensitive and switches the output state at two distinct trigger levels. One of the triggering levels is called a lower trigger level (abbreviated as L.T.L) and the other as upper trigger level (abbreviated as U.T.L).

Above Figure1 shows the circuit of a Schmitt trigger, the circuit of Schmitt trigger contains of two identical transistors  $Q_1$  and  $Q_2$  coupled through an emitter  $R_E$ . The [resistors](#)  $R_1$  and  $R_2$  form a voltage divider across the  $V_{CC}$  supply and ground. These resistors provide a small forward bias on the base of transistor  $Q_2$ .

Let us suppose that initially there is no signal at the input. Then as soon as the power supply  $V_{CC}$  is switched on, the transistor  $Q_2$  starts conducting. The flow of its current through resistor  $R_E$  produces a voltage drop across it. This voltage drop acts as a reverse bias across the emitter junction of transistor  $Q_1$  due to which it cuts-off. As a result of this, the voltage at its collector rises to  $V_{CC}$ . This rising voltage is coupled to the base of transistor  $Q_2$  through the resistor  $R_1$ . It increases the forward bias at the base of transistor  $Q_2$  and therefore drives it into saturation and holds it there. At this instant, the collector voltage, level are  $V_{C1} = V_{CC}$  and  $V_{C2} = V_{CE(sat)}$  as shown in Figure 2.

## Pulse & Digital Circuits

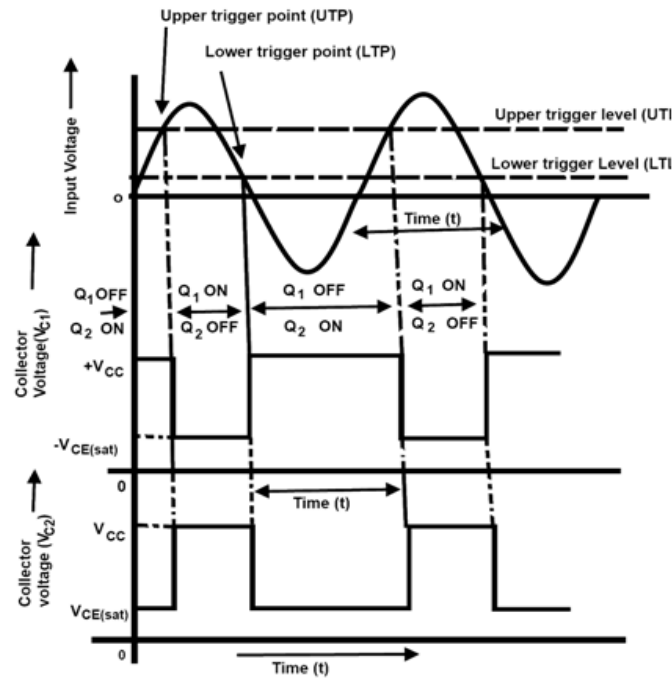


Figure 2: Waveforms at the input and collector of transistor Q1 and Q2

suppose an A.C. signal is applied at the input of the Schmitt trigger (i.e. at the base of the transistor  $Q_1$ ). As the input voltage increases above zero, nothing will happen till it crosses the upper trigger level (U.T.L). As the input voltage increases, above the upper trigger level, the transistor  $Q_1$  conducts. The point, at which it starts conducting, is known as upper trigger point (U.T.P). As the transistor  $Q_1$  conducts, its collector voltage falls below  $V_{CC}$ . This fall is coupled through resistor  $R_1$  to the base of transistor  $Q_2$  which reduces its forward bias. This in turn reduces the current of transistor  $Q_2$  and hence the voltage drop across the resistor  $R_E$ . As a result of this, the reverse bias of transistor  $Q_1$  is reduced and it conducts more. As the transistor  $Q_1$  conducts more heavily, its collector further reduces due to which the transistor  $Q_1$  conducts near cut-off. This process continues till the transistor  $Q_1$  is driven into saturation and  $Q_2$  into cut-off. At this instant, the collector voltage levels are  $V_{C1} = V_{CE(sat)}$  and  $V_{C2} = V_{CC}$  as shown in the figure.

## Pulse & Digital Circuits

---

The transistor  $Q_1$  will continue to conduct till the input voltage falls below the lower trigger level (L.T.L). It will be interesting to know that when the input voltage becomes equal to the lower trigger level, the emitter base junction of transistor  $Q_1$  becomes reverse biased. As a result of this, its collector voltage starts rising toward  $V_{CC}$ . This rising voltage increases the forward bias across transistor  $Q_2$  due to which it conducts. The point, at which transistor  $Q_2$  starts conducting, is called lower trigger point (L.T.P). Soon the transistor  $Q_2$  is driven into saturation and  $Q_1$  to cut-off. This completes one cycle. The collector voltage levels at this instant are  $V_{C1} = V_{CC}$  and  $V_{C2} = V_{CE(sat)}$ . No change in state will occur during the negative half cycle of the input voltage.

### 3.8 Monostable Multivibrator

#### Introduction:

This circuit consists of two active devices  $Q_1$  and  $Q_2$ , one is in the OFF state, say ( $Q_1$ ) and the other,  $Q_2$  in the ON state. These devices remain in the same state forever. Only on the application of a trigger, the multi goes into the quasi stable state ( $Q_1$  ON and  $Q_2$  OFF) and after a time interval  $T$ , will return to the stable state ( $Q_1$  OFF and  $Q_2$  ON). Thus this circuit generates a gate pulse of duration  $T$  either output of this circuit is high for a time duration  $T$  called the pulse duration, pulse width or gate width.


#### Collector-Coupled monostable multivibrator:

The collector coupled monostable multivibrator is shown below.

**www.FirstRanker.com**




## Pulse & Digital Circuits

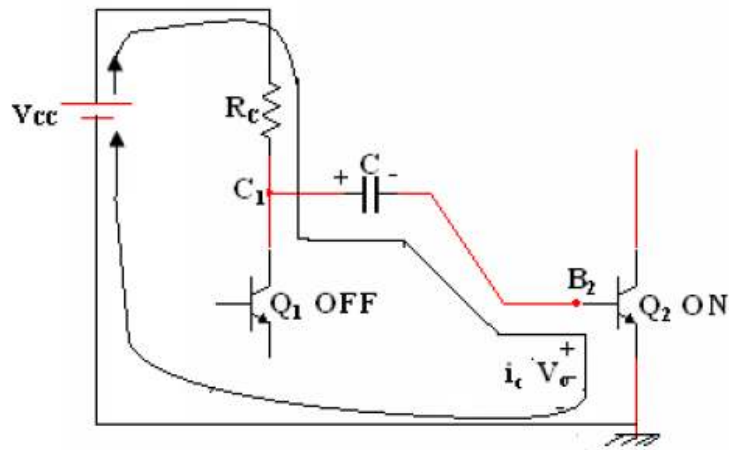


**Fig. Charging of C**

C now tries to charge to  $V_{CC}$  through  $R_C$  of  $Q_1$  and small input resistance of  $Q_2$ . As  $t \rightarrow \infty$ , this voltage reaches  $V_{CC}$ . On the application of a trigger at  $t=0$ , (a negative pulse at  $B_2$ ),  $Q_2$  goes into the OFF state and  $Q_1$  is driven into the ON state and preferably into saturation. Hence there is a current  $I_1$  in  $Q_1$ .  $V_{C1}$  is  $V_{CE(sat)}$ , if  $I_1 = I_{C(sat)}$ .

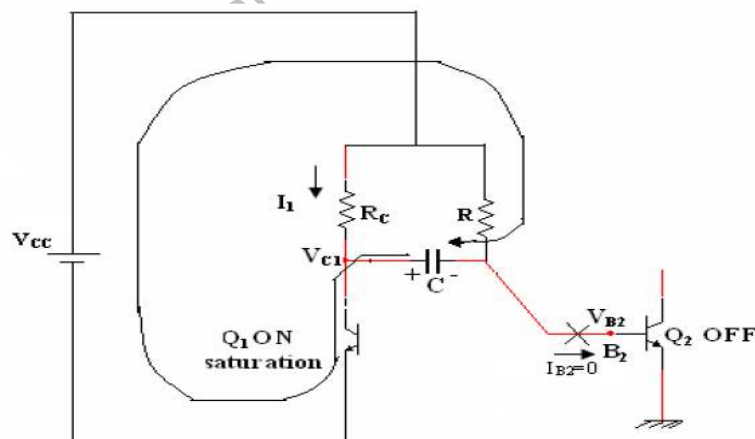

**Fig. discharging of c**

## Pulse & Digital Circuits

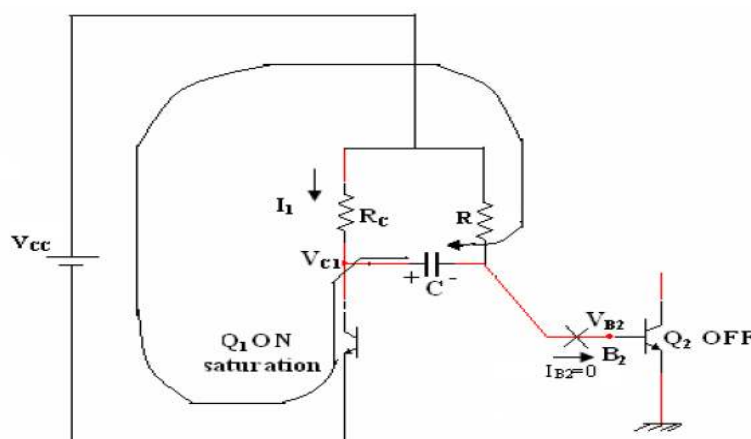

The charge on C now discharges with a time constant  $\tau = RC$ . As a result the voltage at  $B_2$  changes as a function of time. When this voltage  $V_{B2}$  at  $B_2$  reaches  $V_\gamma$  after a time interval  $T$ ,  $Q_2$  is switched ON and  $Q_1$  is switched OFF due to regeneration, thus ending the quasi stable state.

The voltage variation at  $B_2$  of  $Q_2$

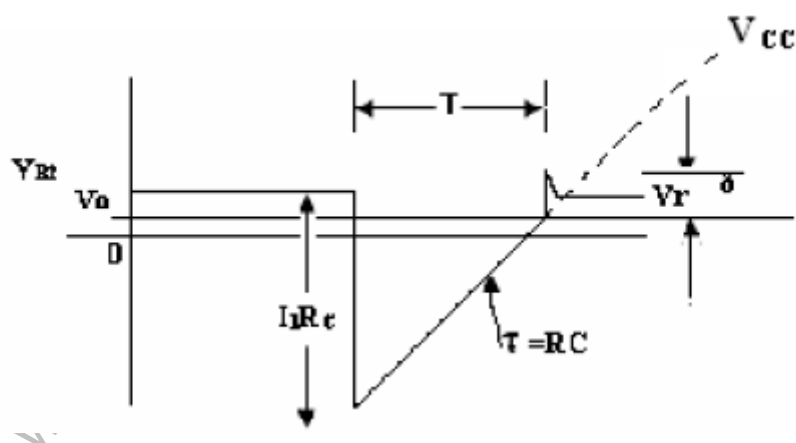



Fig. Voltage variation at the base of  $Q_2$  in the quasi stable state.

The time period  $T$  can be calculated as  $T = 0.69RC$ , if  $Q_1$  in the quasi stable state is in saturation, since  $I_1 RC = V_{CC} - V_{CE(sat)}$

### Gate width of a collector coupled mono stable:

A mono stable multi can be used as a voltage to time converter as shown in Fig


## Pulse & Digital Circuits

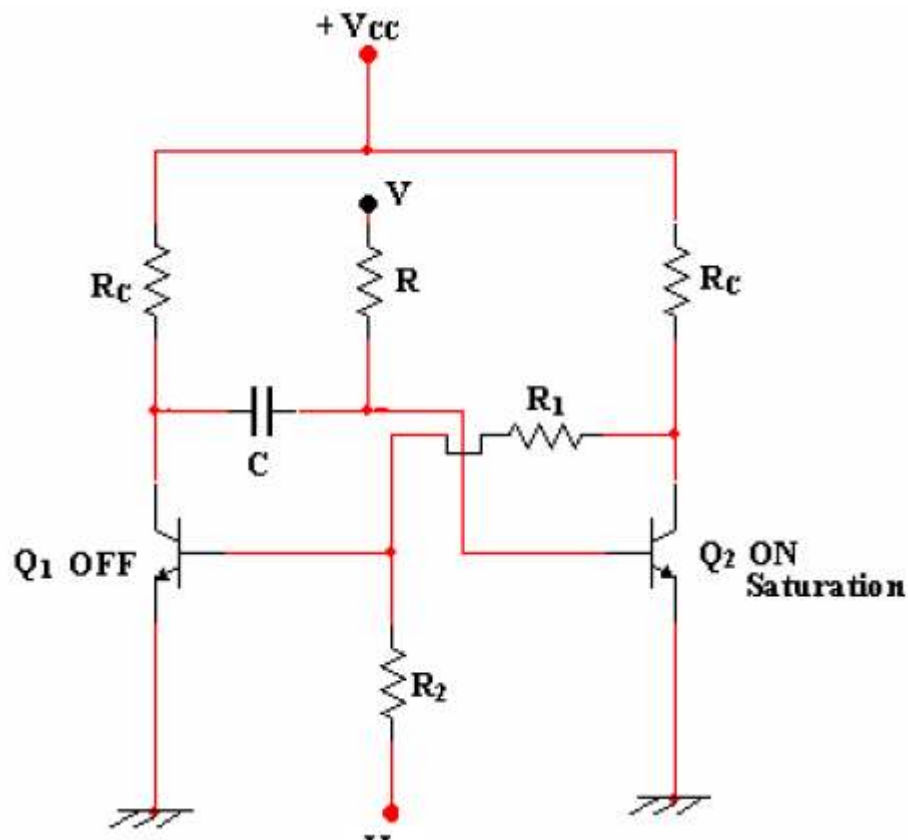

**Fig. . Monostable as a voltage to time converter**

The time  $T$  for which  $Q_1$ , in the quasi stable state, is ON and  $Q_2$  is OFF is calculated.

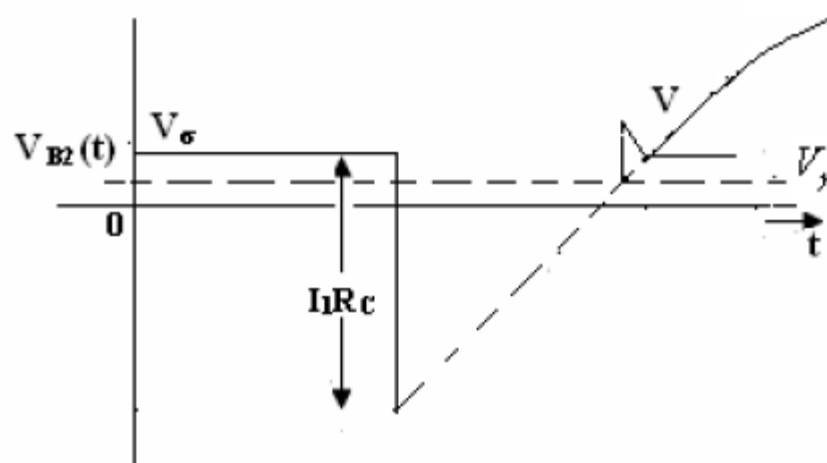Consider the voltage variations at B2, fig.7.17



## Pulse & Digital Circuits

---

$$V_{B2}(t) = V_f - (V_f - V_i)e^{\frac{-t}{\tau}}$$

$$V_f = V$$

$$V_i = V_{\sigma} - I_1 R_C$$

If  $Q_1$  is in saturation

$$I_1 R_C = V_{CC} - V_{CE(sat)}$$

$$V_i = V_{\sigma} - V_{CC} + V_{CE(sat)}$$

$$V_{B2}(t) = V - (V - V_{\sigma} + V_{CC} - V_{CE(sat)})e^{\frac{-t}{\tau}}$$

At  $t = T$

$$V_{B2}(t) = V_{\gamma}$$

$$V_{\gamma} = V - (V - V_{\sigma} + V_{CC} - V_{CE(sat)})e^{\frac{-T}{\tau}}$$

As  $V_{\gamma}$ ,  $V_{\sigma}$  and  $V_{CE(sat)}$  are small when compared to  $V$  and  $V_{CC}$

$$\therefore 0 = V - (V + V_{CC})e^{\frac{-T}{\tau}}$$

$$T = \tau \ln \frac{(V + V_{CC})}{V}$$

$$T = \tau \ln \left(1 + \frac{V_{CC}}{V}\right)$$

Thus, to change  $T$ ,  $V$  can be varied.

### 3.9 Astable multivibrator

#### Introduction:

Two cross-coupled switching circuits are connected in this arrangement. The devices in this Multivibrator will not remain in one state (either ON or OFF) forever. Change of state in the devices occurs continuously after a finite time interval depending on the circuit components used. Hence this circuit has two quasi stable states.


Let  $Q_1$  and  $Q_2$  be two transistors used. If  $Q_1$  is ON, then  $Q_2$  is OFF. These will remain in this state only for a fixed time duration after which  $Q_1$  switches into the OFF state and  $Q_2$  into the ON state without applying triggering pulse and this process is repeated. Therefore it

## Pulse & Digital Circuits

is also called Free running multivibrator. The output of the circuit is a squarewave, having two time periods,  $T_1$  and  $T_2$ . If  $T_1 = T_2 = T/2$ , then the circuit is a symmetric astable multivibrator. If  $T_1 \neq T_2$ , then it is called an unsymmetrical astable multi-vibrator. The astable multivibrator is essentially a square wave generator

### Collector Coupled astable multi:


Collector coupled astable multi is shown below.

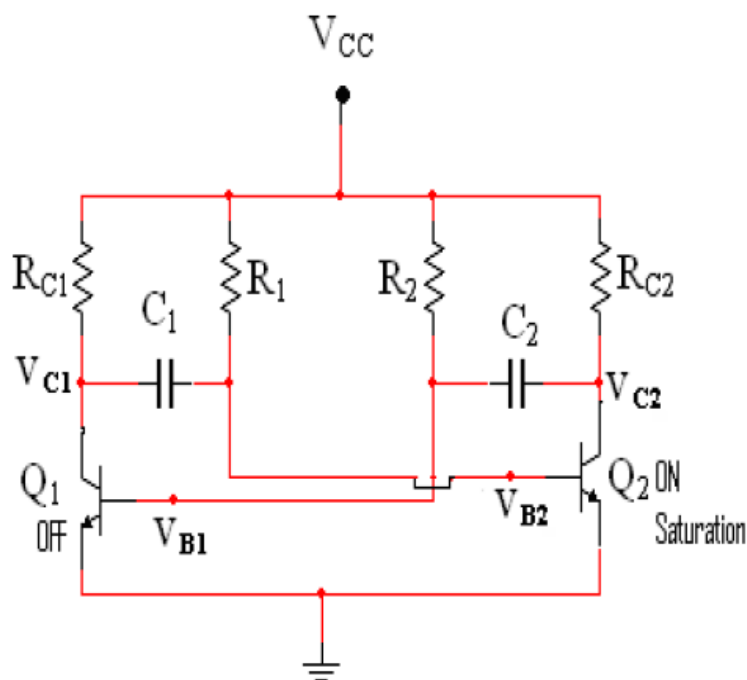

**Fig. astable multi vibrator**


Assume that transistor  $Q_1$  is OFF and  $Q_2$  is ON initially. Then  $V_{B2} = V_{\sigma}$ ,  $V_{C2} = V_{CE(sat)}$  and  $V_{C1} = V_{CC}$ . With  $Q_1$  OFF and  $Q_2$  ON,  $C_1$  will try to charge to the supply voltage through the collector resistance  $R_{C1}$  and through the base and emitter terminals of  $Q_2$ .

## Pulse & Digital Circuits

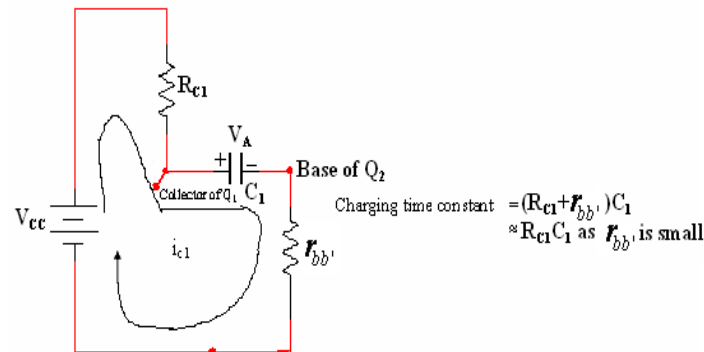

**Fig. Charging of capacitor C1**

Prior to this condition, Q2 must have been in the OFF state and Q1 must have been in the ON state. As a result C2 must have been charged through  $R_{c2}$ . Between the base and emitter terminals of Q1,

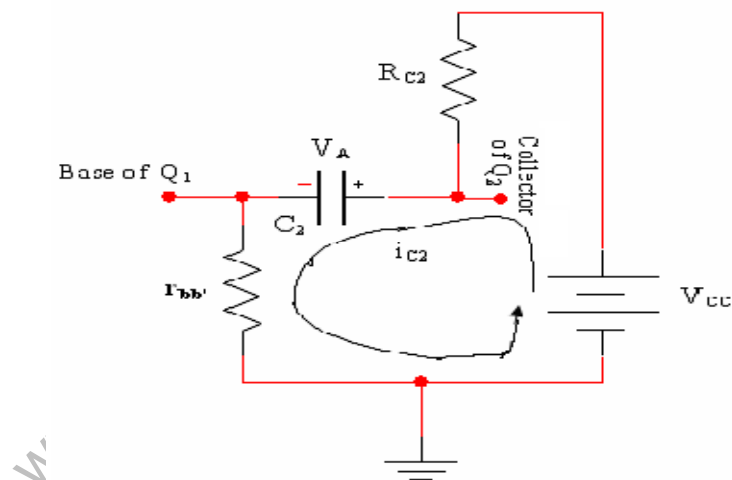


**Fig. charging of capacitor C2**

When Q2 suddenly changes from the OFF state to ON state, the voltage between its collector and emitter terminals is  $V_{CE}$ . Hence the collector of Q2 is at ground potential i.e. the positive end of the capacitor C2 is at the ground potential and its negative terminal is connected to base of Q1. As a large negative voltage is now coupled to base of Q1, Q1 is indeed in the OFF state.

## Pulse & Digital Circuits

But Q1 is not going to remain in the OFF state forever. Now, with Q2 ON, the charge on the capacitor C2 discharges with a time constant  $\tau_2 = R_2C_2$ .

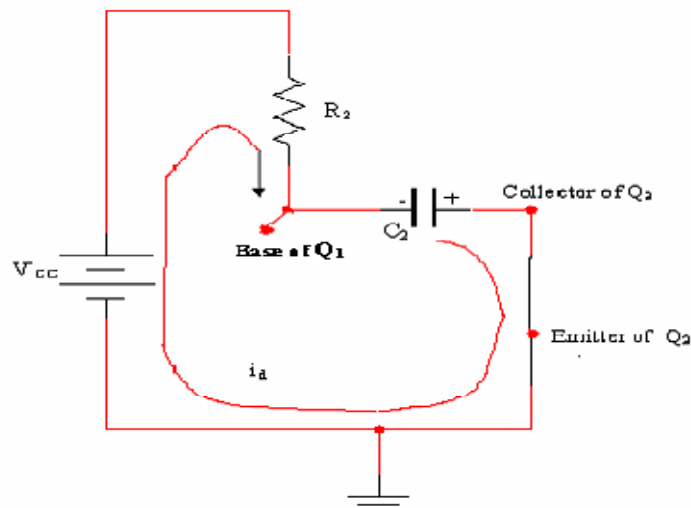


**Fig. discharge of C2 through R2**

As a result, the voltage at the base of Q1 goes on changing as a function of time. Once this voltage is  $V_\gamma$ , Q1 draws base current. Hence there is a collector current; there is a voltage drop across  $R_{C1}$  and the voltage at the collector of Q1 falls. Earlier this voltage was  $V_{CC}$  and now it is smaller than  $V_{CC}$ . Therefore, the negative step at this collector is coupled to the base of Q2 through  $C_1$ . As the collector of Q1 and the base of Q2 are connected through  $C_1$  and as a capacitor will not allow any sudden changes in voltage, whatever is the change that has taken place at the first collector an identical change takes place at the base of Q2. As a result the base current of Q2 is reduced, its collector current is reduced and the voltage at its collector rises. This positive step change is coupled to the base of Q1. Its base current further increases. The collector current increases, the voltage at the collector of Q1 further falls and this change is coupled to the base Q2 and this process is repeated. Thus a regenerative action takes place and Q2 switches into the OFF state and Q1 goes into the ON state.

The waveforms at the base and collectors of Q1 and Q2 are shown below.

## Pulse & Digital Circuits

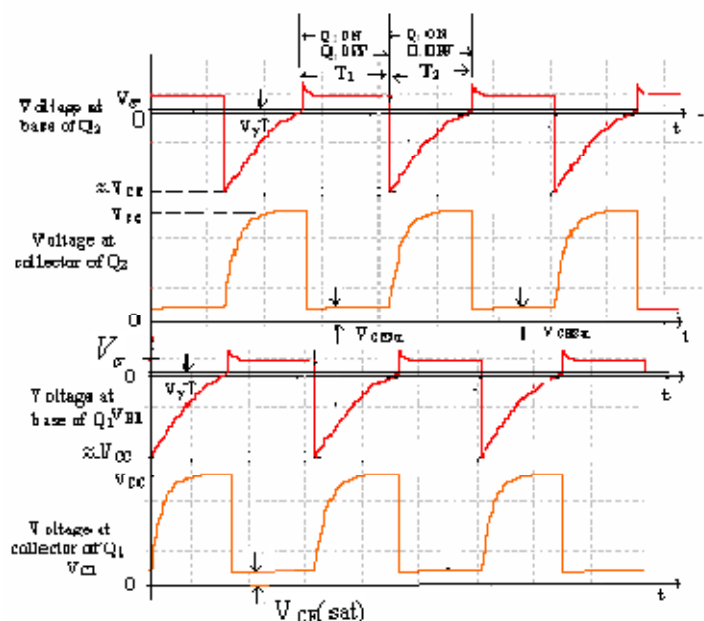

**Fig. Waveforms of collector-coupled astable multi**

When suddenly the transistor changes from the OFF state to the ON state there could be a small overshoot at this base and at the collector of the other transistor. Further, it is seen that when a transistor changes from the ON state into OFF state, say Q1, its collector voltage is required to abruptly rise to  $V_{CC}$ . But when Q1 is OFF and Q2 is ON, there is a charging current of capacitor C1. As a result the voltage  $V_{C1}$  will not suddenly rise to  $V_{CC}$ . Only when this charging current is zero, the collector voltage reaches  $V_{CC}$ . Hence, there is rounding off of the rising edge of the pulse.

### Important Questions:

1. What is a multivibrator? what are the types of it?
2. What are types of triggering?
3. What is the resolution time? how it can be improved?
4. Explain operation of bistable multivibrator? calculate pulse width?
5. Explain operation of Monostable multivibrator? calculate pulse width?
6. Explain operation of astable multivibrator? calculate pulse width?
7. Explain operation of Schmitt trigger?



## Pulse & Digital Circuits

### UNIT-V

### TimeBase Generators

#### 4.1 Voltage Sweep Generators

##### Introduction:

A linear time-base generator is one that provides an output waveform a portion of which Exhibits a linear variation of voltage or current with time. Earlier, this waveform is used to sweep the electron beam horizontally across the screen. Because of this reason it is called **sweep voltage**.


#### 4.2 Errors that define deviation from linearity

Quality of a sweep is specified by three errors that define deviation from linearity.

Errors that define deviation from linearity are three types.

- i) The slope error or speed error  $e_s$
- ii) Displacement error  $e_d$
- iii) Transmission error  $e_t$
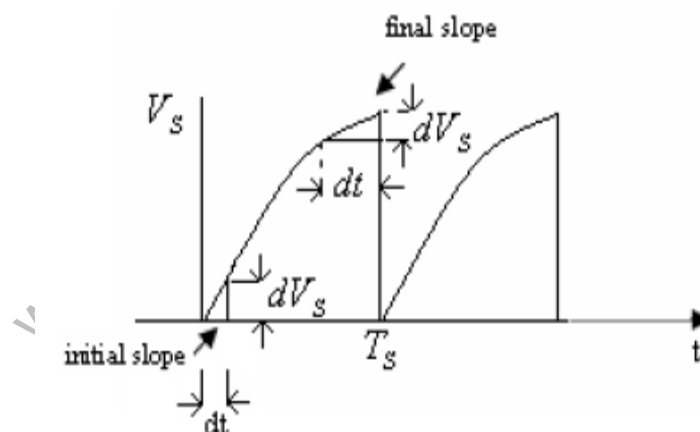
##### (a) Slope or sweep speed error, $e_s$



$$e_s = \frac{\text{initial slope} - \text{final slope}}{\text{initial slope}}$$


$$= \frac{\left. \frac{dV_s}{dt} \right|_{t=0} - \left. \frac{dV_s}{dt} \right|_{t=T_s}}{\left. \frac{dV_s}{dt} \right|_{t=0}}$$

##### (b) Displacement error, $e_d$ :
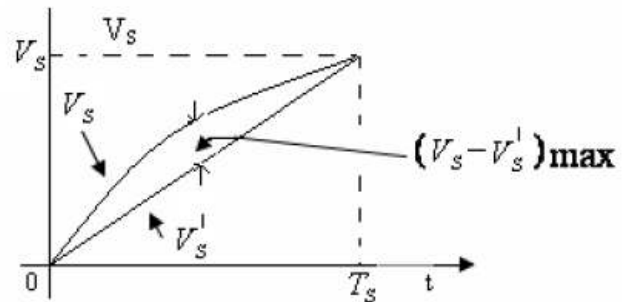
## Pulse & Digital Circuits

It is the maximum difference between the actual sweep voltage and the linear sweep which passes through the beginning and end points of the a sweep.

$$e_d = \frac{(V_s - V_s')_{\max}}{V_s}$$




### (c) Transmission error, $e_t$ :

If a ramp voltage is transmitted through a highpass RC circuit, the output falls away from the input.

$$e_t = \frac{(V_s' - V_s)}{V_s'}$$

$V_s$  is the actual output



$V_s'$  is the input

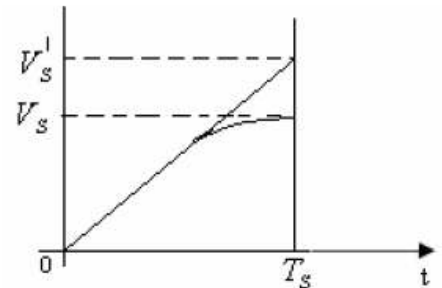

### 4.3 Exponential sweep generator:

A simple exponential sweep generator and its output are shown in Figs. a) and b) respectively. If initially the capacitor is uncharged and  $t = 0$  the switch  $S$  is open, the capacitor charges to the supply voltage  $V$ .
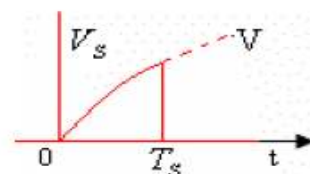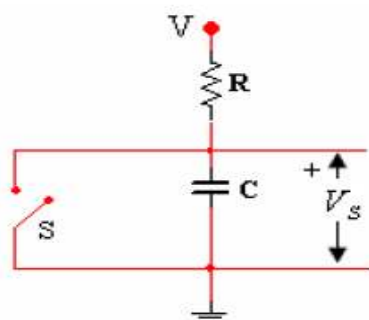
## Pulse & Digital Circuits

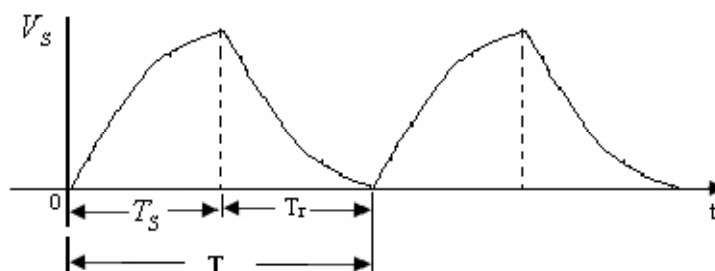


**Fig.a) A simple exponential sweep generator**

**Fig.b) Output of the sweep generator**

If the resistance offered by the switch is ideally not zero there is a finite time delay before the signal reaches its initial value. This time delay is called fly back time, restoration time or retrace tie.

Normally  $T_r \ll T_s$ , so  $T = T_s$



**Fig. output waveform of exponential sweep**

The voltage variation in the capacitor C is

$$\begin{aligned} v_c(t) &= V_f - (V_f - V_i)e^{-t/\tau} \\ &= V - (V - 0)e^{-t/\tau} \\ v_c(t) &= v_s = V(1 - e^{-t/\tau}) \end{aligned}$$

## Pulse & Digital Circuits

Assume that after an interval  $T_s$  when  $v_s = V_s$ , the switch closes. The charge on the capacitor discharges with a negligible time constant and the voltage abruptly falls to zero at  $t = T_s$ .

$$v_s = V(1 - e^{-t/\tau})$$

$$\frac{dv_s}{dt} = -Ve^{-t/\tau} \left(-\frac{1}{\tau}\right) = \frac{V}{\tau} e^{-t/\tau}$$

$$\left. \frac{dv_s}{dt} \right|_{t=0} = \frac{V}{\tau}$$

$$\left. \frac{dv_s}{dt} \right|_{t=T_s} = \frac{V}{\tau} e^{-T_s/\tau}$$

$$\therefore e_s = \frac{\frac{V}{\tau} - \frac{V}{\tau} e^{-T_s/\tau}}{\frac{V}{\tau}} = \left[ 1 - e^{-T_s/\tau} \right]$$

$$\text{at } t = T_s, v_s = V_s$$

$$\text{Hence } V_s = V \left( 1 - e^{-T_s/\tau} \right)$$

$$\therefore 1 - e^{-T_s/\tau} = \frac{V_s}{V}$$

Substituting, we have

$$e_s = \frac{V_s}{V}$$

From above equation it is evident that  $e_s$  is small when  $V \gg V_s$  . i.e. the linearity improves if  $V$  is large when compared to  $V_s$  . Therefore, a simple exponential sweep suffers from the disadvantage that a linear sweep is generated only when the sweep amplitude is very much small when compared to the applied d.c. voltage,  $V$

If

## Pulse & Digital Circuits

---

$$\frac{t}{\tau} \ll 1$$

$$e^{-t/\tau} = 1 - \frac{t}{\tau} + \frac{t^2}{2\tau^2} - \frac{t^3}{6\tau^3} + \Lambda$$

$$v_s = V \left( 1 - e^{-t/\tau} \right)$$

$$= V \left[ 1 - 1 + \frac{t}{\tau} - \frac{t^2}{2\tau^2} + \frac{t^3}{6\tau^3} \Lambda \right]$$

$$= \frac{Vt}{\tau} \left[ 1 - \frac{t}{2\tau} + \frac{t^2}{6\tau^2} \right]$$

Since  $v = V_s$  at  $t = T_s$

To first approximation

As this is a linear sweep

$$V_s' = \frac{VT_s}{\tau}$$

Hence, for  $e_s$  to be small  $\tau \gg T_s$

If the actual sweep is non-linear, consider the first two terms

$$v_s = \frac{Vt}{\tau} \left( 1 - \frac{t}{2\tau} \right)$$

$$\therefore V_s = \frac{VT_s}{\tau} \left( 1 - \frac{T_s}{2\tau} \right)$$

This is a non-linear sweep

Therefore the transmission error  $e_t$  is

## Pulse & Digital Circuits

---

$$\begin{aligned}e_i &= \frac{V_s' - V_s}{V_s'} \\&= \frac{\frac{VT_s}{\tau} - \frac{VT_s}{\tau} \left(1 - \frac{T_s}{2\tau}\right)}{\frac{VT_s}{\tau}} \\e_i &= \frac{T_s}{2\tau}\end{aligned}$$

Now,

$$e_s = \frac{T_s}{\tau}$$

If we relate

$e_s$  and  $e_i$

$$e_i = \frac{T_s}{2\tau} = \frac{e_s}{2}$$

Displacement error,  $e_d$  is

## Pulse & Digital Circuits

$$e_d = \frac{(v_s - v_s') \max}{V_s}$$

From equation 6.12

$$v_s = \frac{Vt}{\tau} \left( 1 - \frac{t}{2\tau} \right)$$

$$v_s' = \frac{Vt}{\tau}$$

$$(v_s - v_s') = \frac{Vt}{\tau} \times \frac{t}{2\tau}$$

The deviation is maximum at  $t = \frac{T_s}{2}$

$$(v_s - v_s')_{\max} = \frac{VT_s}{2\tau} \times \frac{T_s}{4\tau}$$

$$v_s = \frac{Vt}{\tau}$$


At  $t = T_s$   $v_s = V_s$

$$\therefore V_s = \frac{VT_s}{\tau}$$

$$\therefore e_d = \frac{(v_s - v_s')_{\max}}{V_s} = \frac{\frac{VT_s}{2\tau} \times \frac{T_s}{4\tau}}{\frac{VT_s}{\tau}}$$

$$= \frac{T_s}{8\tau} = \frac{T_s}{8\tau}$$

$$e_d = \frac{1}{8} e_s$$

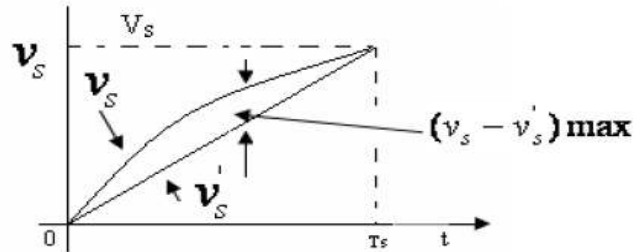

The interrelationship between the three types of errors is given below

$$e_d = \frac{1}{8} e_s = \frac{1}{4} e_t$$

If we know one type of error, we can calculate the other types of errors

$$C = \frac{I}{C} t$$

If the capacitor is charged with a constant current  $I$  then the voltage across  $t$ . hence, the rate of change of voltage with time is called sweep speed.


## Pulse & Digital Circuits

Sweep speed

$$= \frac{I}{C}$$
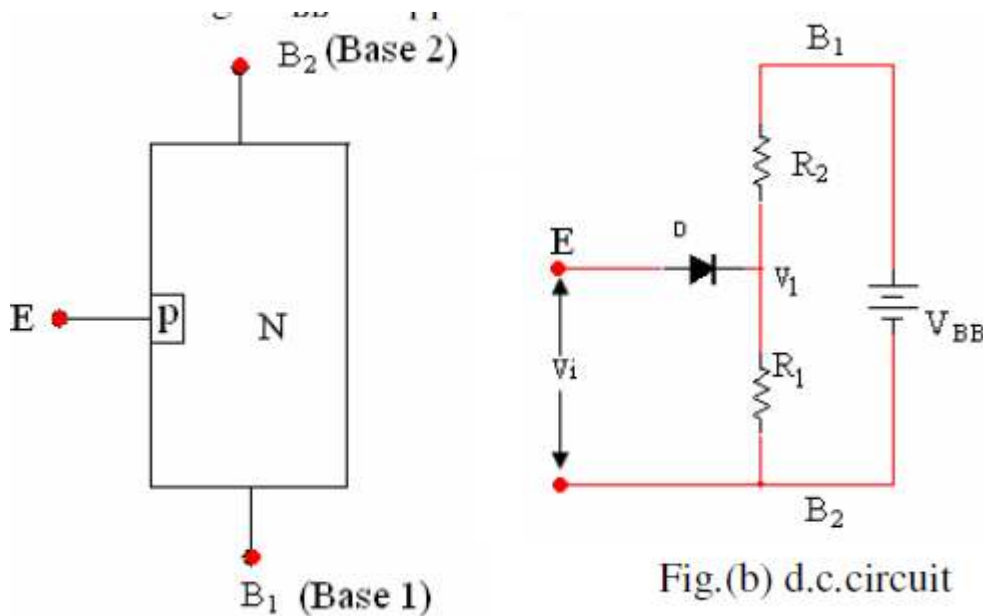
### 4.4 UJT sweep generator:

In the exponential sweep generator, a UJT can be used as switch S. The UJT and its d.c. circuit are shown in figs. below. A UJT consists of an N-type semiconductor bar with leads  $B_1$  and  $B_2$  drawn. Emitter is a P-type material and it is heavily doped. Let the bias voltage  $V_{BB}$  be applied.



$$\begin{aligned} \text{We have, } V_1 &= V_{BB} \frac{R_1}{R_1 + R_2} \\ &= V_{BB} \frac{R_1}{R_{BB}} = \eta V_{BB} \end{aligned}$$



## Pulse & Digital Circuits

Where  $\eta$  = Intrinsic stand-off ratio (lies around 0.7)

As long as  $V_i \ll \eta V_{BB}$  D is OFF.

When  $V_i > \eta V_{BB}$  D is ON and a large number of charge carriers exist on the N-side, reducing the resistance and the device conducts heavily, switch S is closed. The V-I characteristic of a UJT is shown in fig.c

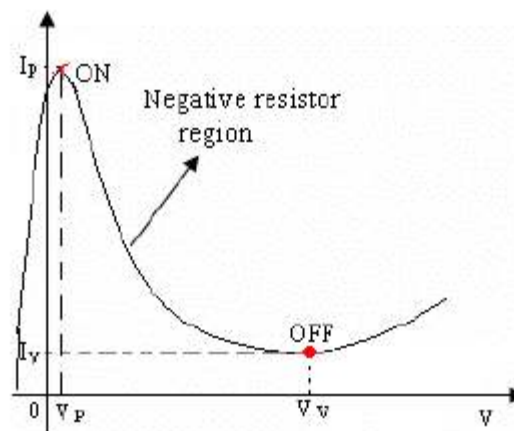


Fig.c. V-I characteristic of UJT

An exponential sweep generator using UJT is shown in fig below

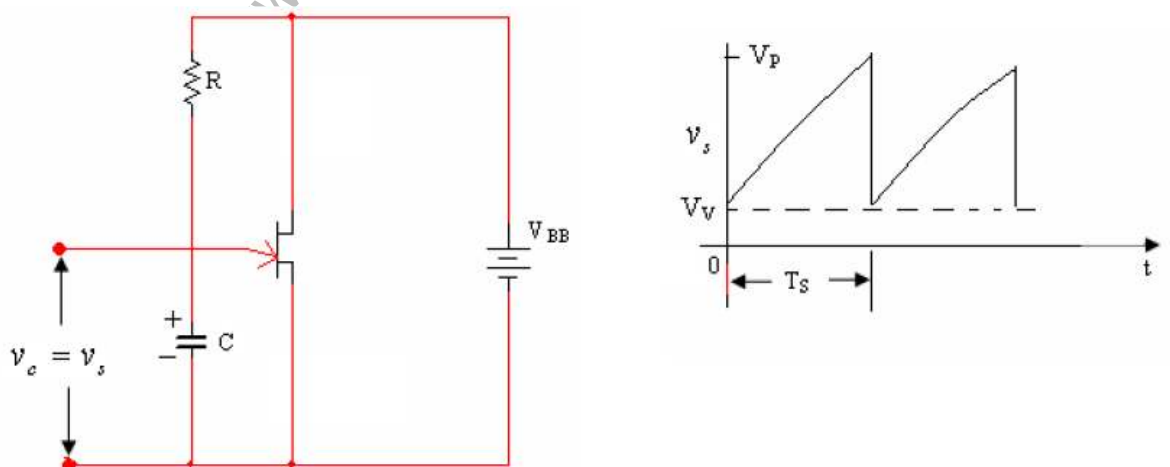


Fig.c A practical UJT sweep generator and its output

## Pulse & Digital Circuits

$$v_s = V_{BB} \left( 1 - e^{-t/\tau} \right)$$

$$\text{At } t = T_s, v_s = \eta V_{BB}$$

$$\eta V_{BB} = V_{BB} \left( 1 - e^{-T_s/\tau} \right)$$

$$V_{BB} e^{-T_s/\tau} = V_{BB} (1 - \eta)$$

$$V_{BB} e^{-T_s/\tau} = V_{BB} (1 - \eta)$$

$$T_s = \tau \ln \frac{1}{(1 - \eta)}$$

Alternately

$$\begin{aligned} v_s &= V_f - (V_f - V_i) e^{-t/\tau} \\ &= V_{BB} - (V_{BB} - V_v) e^{-t/\tau} \end{aligned}$$

$$\text{At } t = T_s, v_s = V_s = V_p$$

$$V_p = V_{BB} - (V_{BB} - V_v) e^{-T_s/\tau}$$

$$T_s = \tau \ln \frac{(V_{BB} - V_v)}{(V_{BB} - V_p)}$$

### 4.5 Time-base generators-general considerations:

A simple exponential sweep generator essentially produces a nonlinear sweep voltage. Consider an auxiliary generator  $v$ . If  $V$  always kept equal to the volt across  $C$  Then net voltage in the loop is  $V$ . Then

## Pulse & Digital Circuits

$$i = \frac{V}{R}$$

i.e. the capacitor charging current is constant and perfect linearity is achieved. Let us identify three nodes X, Y and Z. In a circuit one terminal is chosen as a reference terminal or ground terminal. Ground in a circuit is an arbitrarily chosen reference terminal.

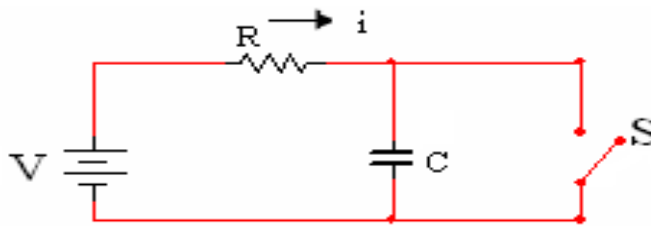


Fig. Method to linearize a non-linear sweep

### Miller Sweep:

Now let Z be the ground terminal, and redrawing the above circuit

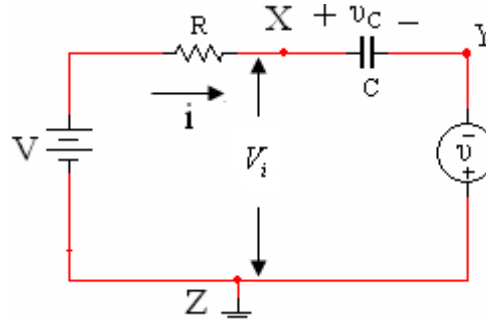


Fig. The sweep generator with Z as the ground terminal

## Pulse & Digital Circuits

Since  $v_C = v$  and  $v_i = 0$ . Hence if the auxiliary generator is replaced by an amplifier with X and Z as input terminals and Y and Z as output terminals, then the gain of the amplifier A should be infinity. The above circuit reduces to that shown in fig. below which is called Miller Sweep.


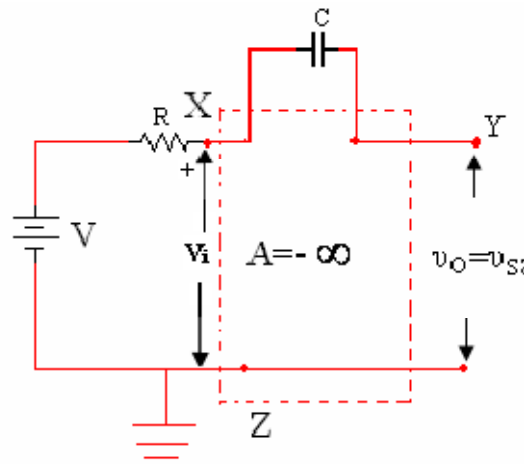


Fig. equivalent circuit.


**Bootstrap Sweep:** Let Y be the ground terminal redrawing the above circuit and replacing the auxiliary generator by an amplifier with X and Y as input terminals the amplifier should have a gain of unity as  $v = V_c$

## Pulse & Digital Circuits

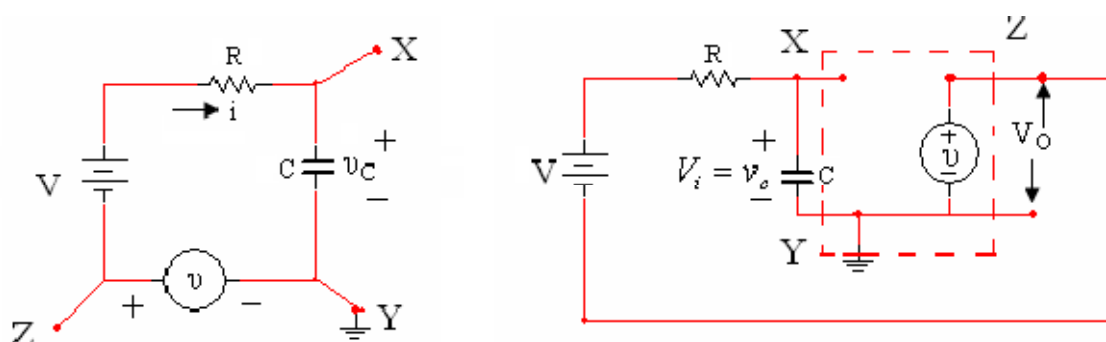

**Fig. the sweep generator, with Y as the ground terminal**


Replacing the generator by amplifier, the circuit is redrawn as in fig. below

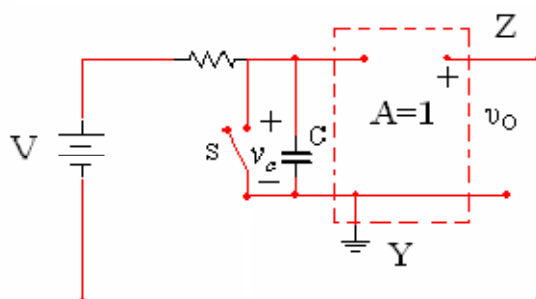

**fig. Bootstrap sweep generator**

This type of sweep generator is called a Bootstrap sweep generator

**Slope error of a Miller's sweep:**

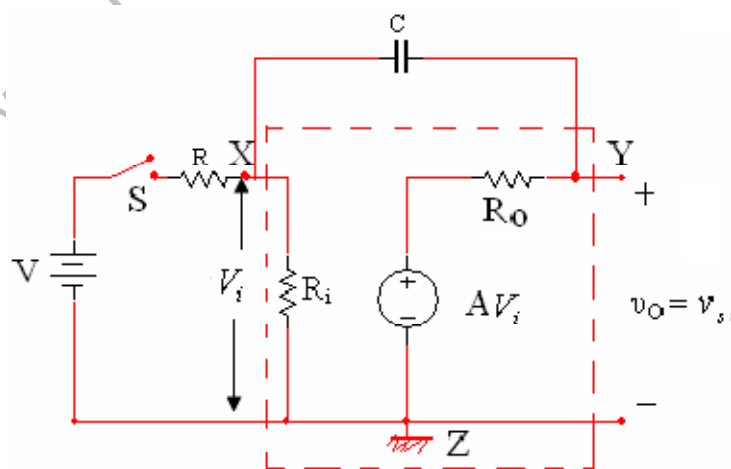


**Fig. equivalent circuit**

$R_i$  = Input resistance of the amplifier

## Pulse & Digital Circuits

$R_o$  = Output resistance of the amplifier

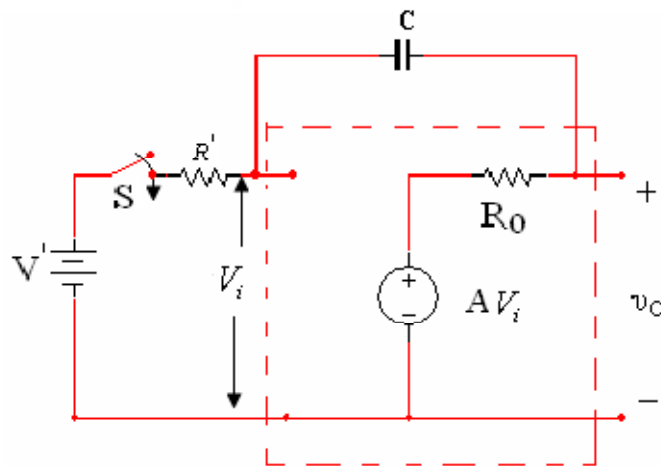

**Fig. Thevenin's equivalent circuit**

Thevenising the circuit at the input

$$V' = V \frac{R_i}{R + R_i} = V \frac{1}{1 + \frac{R}{R_i}}$$

$$R' = \frac{R \times R_i}{R + R_i}$$

## Pulse & Digital Circuits

Let  $R_0 = 0$

At  $t = 0$  the voltage across the capacitor is zero

$$\therefore v_i - Av_i = 0, \quad v_i(1 - A) = 0, \quad v_i = 0$$

$$v_i = AV_i = V_0 = 0$$

As  $t \rightarrow \infty$ , the capacitor is fully charged no current flows in it and hence can be replaced by an open circuit for

the purpose of finding out the output voltage. The resultant circuit is


$$\text{At } t = \infty, \quad V_i = V'$$

$$\text{Hence } V_0 = AV'$$

$$\text{We know that } e_s = \frac{V_s}{V}$$

where  $V_s$  = sweep amplitude

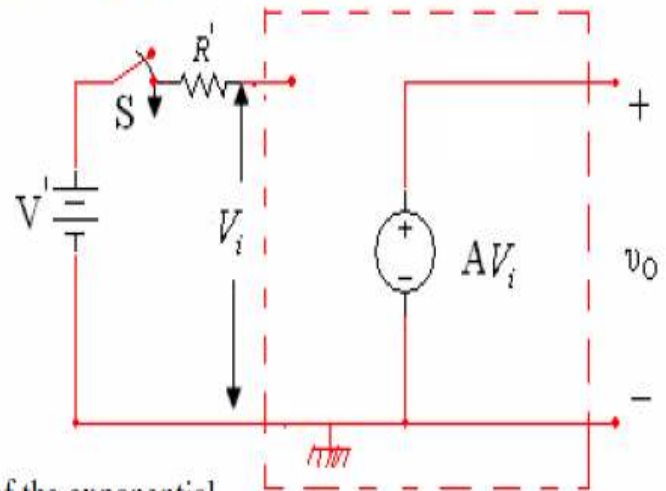$V$  = total peak to peak excursion of the exponential



$$\text{Hence, } e_{s_{\text{Miller}}} = \frac{V_s}{V_0} = \frac{V_s}{|A|V'} = \frac{V_s}{|A|} \times \frac{1}{V'}$$

$$\text{Substituting, } e_{s_{\text{Miller}}} = \frac{V_s}{|A|} \times \frac{1 + R/R_i}{V}$$

$$= \frac{V_s}{V} \times \frac{1 + R/R_i}{|A|}, \text{ where } \frac{V_s}{V} \text{ is the slope error of the exponential sweep.}$$

$$\therefore e_{s_{\text{Miller}}} = e_s \times \frac{1 + R/R_i}{|A|}. \text{ Even if } R_i \text{ is small, as } A \text{ is large, the slope error of a Miller's}$$

sweep is very small. Hence, for all practical purposes this sweep generator produces a near linear sweep.

## Pulse & Digital Circuits

### Slope error of Bootstrap sweep generator:

Consider the Bootstrap sweep generator in fig I)

If initially the capacitor is uncharged and if S is closed at  $t = 0$

$$V_o = -V \times \frac{R_o}{R + R_o} \quad \text{from fig.ii)}$$

And as  $R_o$  of emitter follower is very small.

$$V_o \approx 0$$

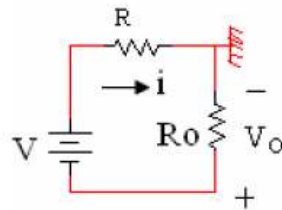


Fig ii) Circuit to calculate the output at  $t = 0$

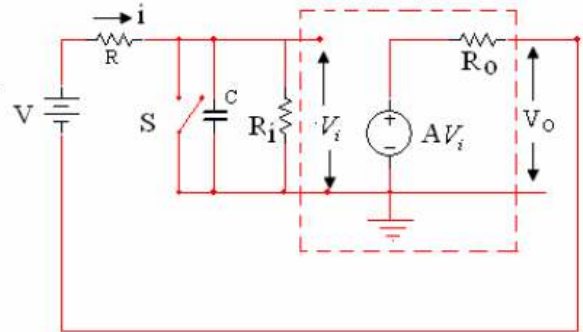


Fig.i) Bootstrap sweep generator

As  $t \rightarrow \infty$ , C is fully charged and is open circuited, fig.6.20

$$V_o(t \rightarrow \infty) = \frac{V(AR_i - R_o)}{R_o + R + R_i(1 - A)}$$

Dividing by  $R_i$

$$V_o(t \rightarrow \infty) = \frac{V(A - R_o/R_i)}{(1 - A) + \frac{R}{R_i} + \frac{R_o}{R_i}}$$

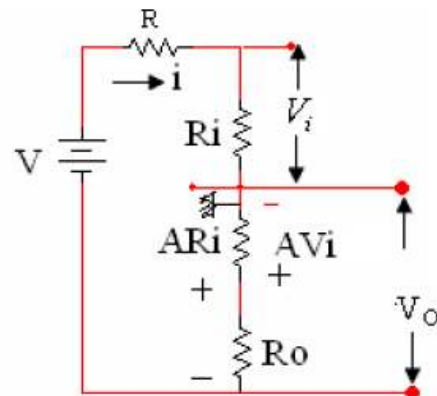


Fig 6.20 circuit to calculate the output as  $t \rightarrow \infty$

$$V_o(t \rightarrow \infty) \approx \frac{V}{(1 - A) + R/R_i}$$

$R_o$  is the output resistance which is small and  $R_i$  is its input resistance which is large.

$$\therefore \frac{R_o}{R_i} \text{ is negligible and } A \approx 1$$



## Pulse & Digital Circuits


Equation reduces to

$$\therefore e_{s\text{Bootstrap}} = \frac{V_s}{V} (1 - A + R/R_i)$$

$$\cong e_s \frac{R}{R_i}$$

If  $R=R_i$ ,  $e_{s\text{Bootstrap}} = e_s$ . That is the Bootstrap circuit will not provide any improvement in linearity. For this sweep to be linear  $R_i \gg R$


**Transistor Miller Sweep:** Consider the working of the triggered transistor Miller's sweep generator as shown below.

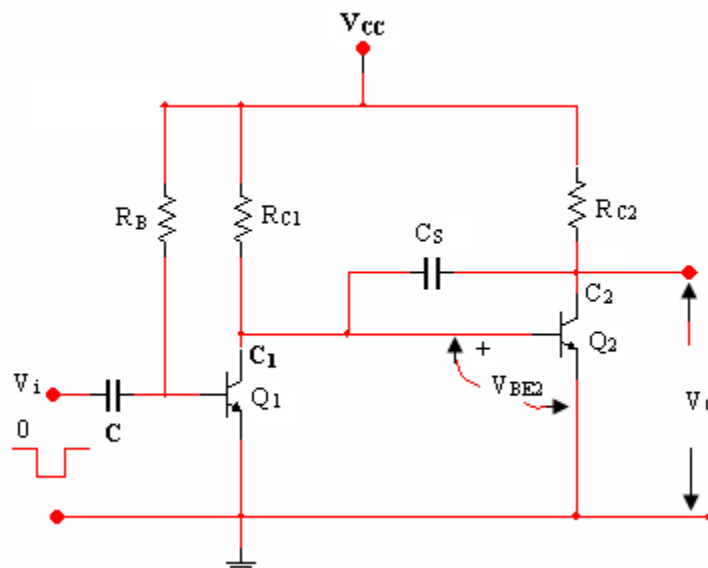

**Fig. Transistor Miller sweep**


The circuit conditions are adjusted such that when the input is zero  $Q1$  is ON and is in saturation. Therefore the voltage at  $C1$  (collector of  $Q1$ ) is  $V_{sat}$   $CE=0$ . Transistor  $Q2$  is OFF since  $v_{be2}=0$ . The voltage at  $C2$  (collector of  $Q2$ ) is  $V_{cc}$ . The voltage across the capacitor  $C$  is  $V_{cc}$ . When the input signal goes negative,  $Q1$  is OFF and the voltage at  $C1$  rises and  $Q2$  goes ON. The charge on the capacitor  $C2$  discharges. Hence the output is a negative going ramp. Again at the end of the input pulse,  $Q1$  goes ON,  $Q2$  goes OFF and the output again reaches  $V_{CC}$ . The waveforms are shown in fig

## Pulse & Digital Circuits

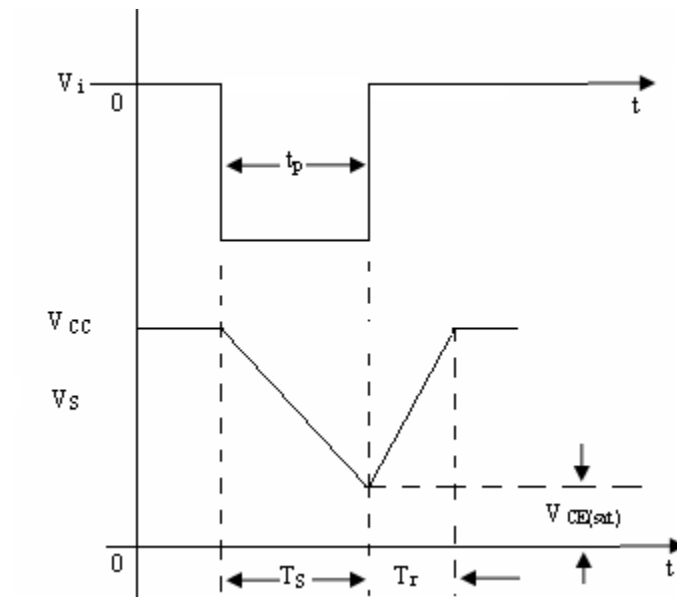

**Fig Waveforms of a transistor Miller sweep**

**Bootstrap circuit:** The circuit of a Bootstrap sweep generator is shown in fig. below.

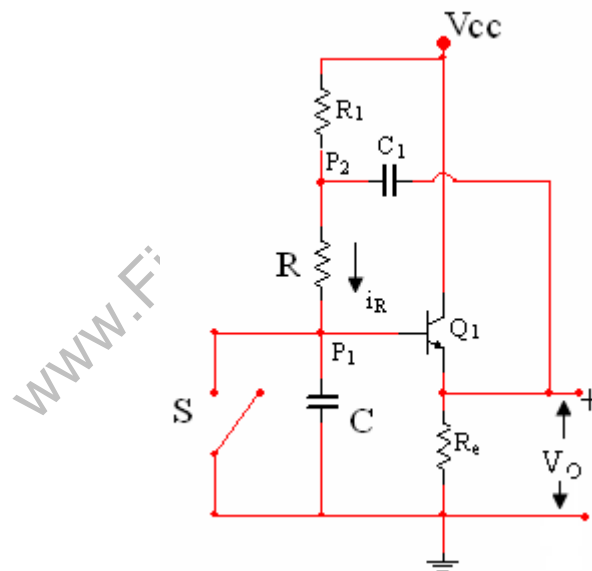


**Fig. Bootstrap sweep generator**

At  $t = 0$ , the switch  $S$  is open and the capacitor charges.  $C_1$  is very large. Therefore, it is assumed that the voltage across  $C_1$  remains unaltered during the sweep period. Let the

## Pulse & Digital Circuits

voltage gain of the emitter follower remain constant. Then the voltage at  $P_2$  (output of the emitter follower) follows  $P_1$  (input of the emitter follower). The voltage between  $P_2$  and  $P_1$  will remain invariant and the current  $R_1$  through  $R$  is constant. As the capacitor charges with a constant current, the resultant sweep is linear.

The circuit of a practical Bootstrap ramp generator is shown.

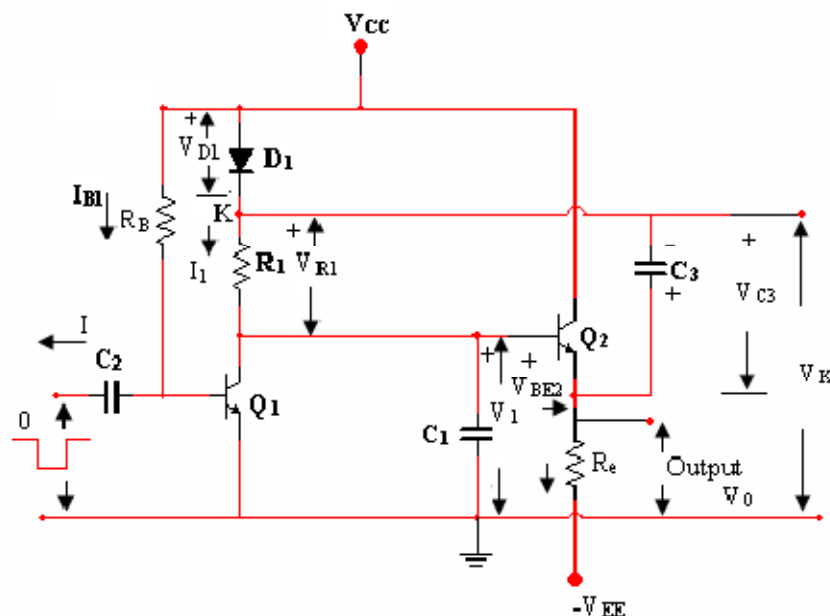

**Fig. A practical Bootstrap sweep generator**

The ramp is generated across capacitor  $C_1$  which is charged from the current through  $R_1$ . The discharge transistor  $Q_1$  when ON keeps the  $V_1$  at  $V_{(sat) CE}$  until a negative input pulse is applied.  $Q_2$  is an emitter follower with low output resistance. Emitter resistance  $R_e$  is connected to a negative supply  $V_{ee}$  instead of referencing to ground to ensure that  $Q_2$  remains conducting even when its base voltage  $V_1$  is close to ground. Capacitor  $C_3$ , called bootstrapping capacitance, has a much higher capacitance than  $C_1$ .  $C_3$  is meant to maintain a constant voltage across  $R_1$  and thus maintain the charging current constant.

## Pulse & Digital Circuits

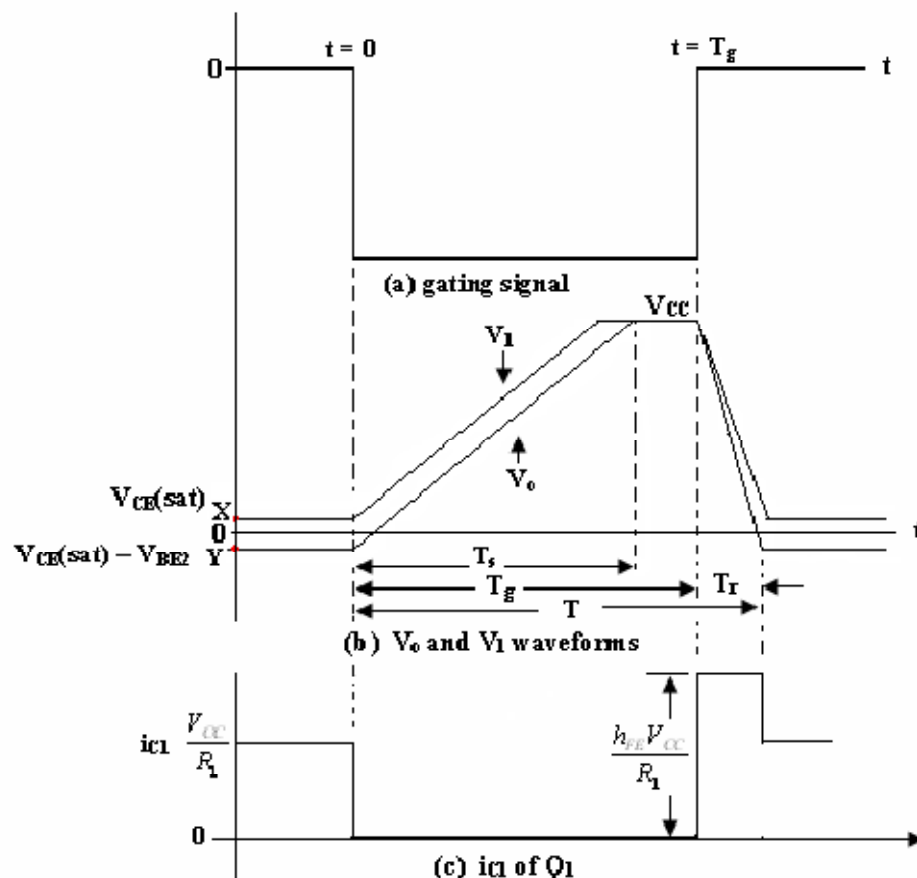


Fig.6.27 waveforms of the bootstrap circuit

### Circuit operation:

#### Quiescent conditions:

As long as the input trigger signal is zero,  $Q_1$  has sufficient base current. So  $Q_2$  goes into saturation. Therefore the voltage  $V_1$  across the capacitor  $C_1$  is  $V_{CE(sat)}$ .  $V_1 = V_{CE(sat)}$

$Q_2$  is an emitter follower for which input is  $V_1$  and its output  $V_0$  is  $V_0 = V_1 - V_{BE2}$  which is very less

For all practical purposes both  $V_1$  and  $V_0$  are zero. The voltage across  $R_1$  is

$$V_{R1} = V_{CC} - V_{D1} - V_{CE(sat)} \approx V_{CC}$$

Also, the voltage across  $C_3$  is  $V_{C3} = V_{CC}$ .

Hence the current  $I_1$  in  $R_1$  is

## Pulse & Digital Circuits

$$I_1 = \frac{V_{CC}}{R_1}$$

As the base current of Q2 is smaller than the collector current of Q1

$$i_{C1} \approx I_1 = \frac{V_{CC}}{R_1} \quad \text{and} \quad I_{B1} = \frac{V_{CC}}{R_B}$$

For Q1 to be in saturation,  $i_{B1(sat)} > i_{B1(active)}$

$$\therefore \frac{V_{CC}}{R_B} > \frac{V_{CC}}{h_{FE} R_1}, \quad \text{or } R_B < h_{FE} R_1$$

### Sweep generation:

At  $t=0$ , when voltage at the base of Q1 goes negative, Q1 is OFF. There is no current into the collector lead of Q1 and instead this current flows through  $C_1$  charging it. As the voltage across the capacitor  $C_1$  varies as  $t$

$$\frac{i}{C} t$$

and so does the output.

$$V_0 = \frac{V_{CC}}{R_1} \cdot \frac{t}{C_1}$$

When the sweep starts, D1 is reverse biased and is an open circuit. The changing current  $I_1$  to  $C_1$  through  $R_1$  is supplied by  $C_3$  which is charged to  $V_{CC}$ .

It is known that the output  $V_0$  varies linearly only when the duration of the gate signal ( $T_g$ ) is small so that in this period  $V_0$  does not reach  $V_{CC}$ . However, if  $T_g$  is large, the output  $V_0$  may reach  $V_{CC}$  even before  $T_g$ . When  $V_0 = V_{CC}$ , the voltage  $V_{CE2}$  of Q2 is practically zero

## Pulse & Digital Circuits

---

(saturation). Q2 no longer behaves as an emitter follower.  $V_0$  and  $V_1$  therefore remain at  $V_{CC}$ . The current  $V_{CC}/R_1$  now flows through  $C_3$ ,  $R_1$  and through the base emitter diode of Q2. thereby changing voltage across  $C_3$  by a small amount.

If  $T_s < T_g$ , Then at  $t = T_s$ ,  $V_s = V_{CC}$

Hence

$$V_{CC} = \frac{V_{CC} T_s}{RC}, \text{ or } T_s = RC$$

On the other hand if  $V_s < V_{CC}$ , the maximum ramp voltage is

$$V_s = \frac{V_{CC} T_g}{RC}$$

### 4.6 Current Sweep Generators

#### Introduction:

Application of electromagnetic deflection is used in these current sweep generators.


When a voltage is applied to a coil of inductance  $L$ , the current in  $L$  increases linearly with time. Usually a coil or set of coils called yoke is mounted external to the gun structure of the tube and the current in yoke produces a magnetic field that causes deflection of the electron beam.

If at a time  $t = 0$ , a voltage  $V$  is applied to a coil of inductance  $L$  in which the current is initially zero, then the inductor current  $L$

$$i_L = \frac{V}{L}t$$

A time base circuit using this principle is shown in fig.a

## Pulse & Digital Circuits

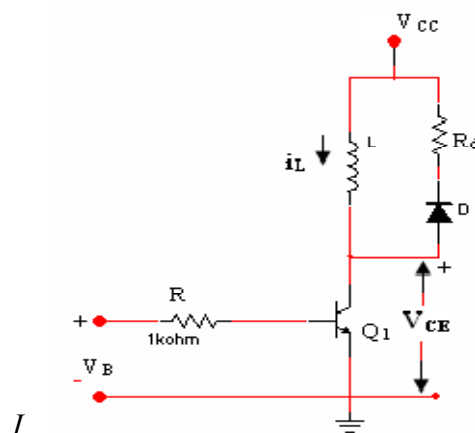

**Fig.a Current sweep generator**

The gating waveform  $V_b$  operates between two levels. The lower level keeps the transistor in cut off while the upper level drives the transistor into saturation. As long as the input is negative Q1 is biased OFF and the inductor current is zero. At  $t=0+$  as the input goes positive Q1 is driven into saturation. The current  $i_L$  increases linearly with time. During the sweep period the diode D does not conduct since it is reverse-biased. The sweep terminates at  $t=T_s$  when the trigger signal drives the transistor to cut off. The inductor current then continues to flow through the diode D and the resistance  $R_d$  till it decays to zero. This decay is exponential with a time constant

$$\tau = \frac{L}{R_d}$$

Where  $R_d$  is the sum of the damping resistance and the diode forward resistance.

The inductor current attains a maximum value of  $I_L$  in fig b.

Before the transistor is turned ON, and sometime after it has been turned OFF,  $V_{CE}$

$$V_{CE} = V_{CC} \cdot \text{When the transistor is ON,}$$

$$V_{CE} = V_{CE}(sat),$$

Is very low. At  $t=T_s$  Q1 is turned OFF. A spike of amplitude  $I R$  appears across the inductance L. This peak voltage must be limited to make sure that it would not exceed the

## Pulse & Digital Circuits

break down voltage of the collector base junction.  $I_L$  is normally chosen on deflection requirements, and a spike of magnitude  $I_L R$  is generated. Thus there is an upper limit to the size of  $R$ . The spike decays with the same time constant as the inductor current. Thus we see that the spike duration depends on  $L$ , whereas the spike amplitude does not. So far we have neglected the resistance of the inductor  $R_L$  and the collector saturation resistance of the transistor,  $R_{CS}$ .

Taking  $R_L$  and  $R_{CS}$  into account

$$i_L = \frac{V_{CC}}{R_L + R_{CS}} \left( 1 - e^{-\frac{(R_L + R_{CS})t}{L}} \right)$$

Expanding it in to series

$$i_L \approx \frac{V_{CC}}{R_L + R_{CS}} \left[ 1 - \frac{(R_L + R_{CS})t}{L} + \frac{(R_L + R_{CS})^2 t^2}{2L^2} \right]$$

$$i_L = \frac{V_{CC}}{L} t \left[ 1 - \frac{(R_L + R_{CS})t}{2L} \right]$$

The slope error  $e_s$  is 
$$e_s = \frac{I_L}{V_{CC}/(R_L + R_{CS})} = \frac{(R_L + R_{CS})I_L}{V_{CC}}$$

The current sweep is linear if the slope error is small. Therefore, to ensure linearity the Voltage must be small when compared with the supply voltage  $V_{CC}$ .

$$(R_L + R_{CS})I_L$$


As this simple current sweep may not produce a linear output, we may think of methods that help in linearising the sweep. One simple method to produce a linear current sweep is by adjusting the driving waveform.



## Pulse & Digital Circuits

### 4.7 Linearity correction through adjustment of the driving waveform:

The non-linearity encountered in this circuit results from the fact that as the yoke current increases the current in the series resistance also increases. Consequently the voltage across the yoke decreases and the rate of change of current decreases. We may compensate for the voltage developed across the resistance as shown in fig.c

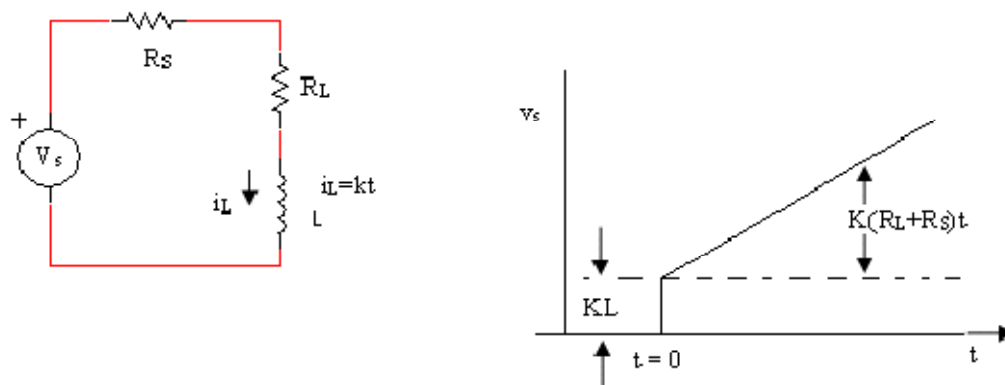

**Fig.c Driving waveform for generating a linear current sweep**

Let  $R_s$  be the internal resistance of the source  $V_s$ . The total circuit resistance  $(R_s + R_L)$ . we want the inductor current to vary linearly

i.e.  $i_L = Kt$ , where  $K$  is the constant of proportionality.

If  $i_L = Kt$ , then the source voltage  $V_s$  is

$$V_s = L \frac{di_L}{dt} + (R_s + R_L)i_L$$

$$\text{If } i_L = Kt, \quad \frac{di_L}{dt} = K$$

$$\therefore V_s = LK + (R_s + R_L)Kt$$


This waveform consists of a step by followed by a ramp  $(R_s + R_L)Kt$ . Such a waveform is called a trapezoidal waveform.

The Norton representation of the driving source, using above equation

$$i_s = \frac{V_s}{R_s} = \frac{LK}{R_s} + \left(1 + \frac{R_L}{R_s}\right)Kt$$

## Pulse & Digital Circuits

This waveform consists of a step by followed by a ramp

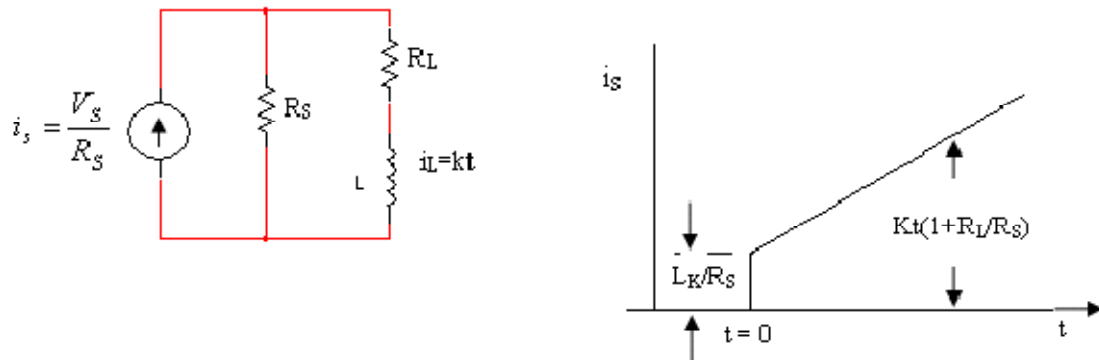

**Fig.d Trapezoidal current source and the wave form**

Thus a trapezoidal driving waveform generates a linear current sweep. At the end of the sweep the current once again will return to zero exponentially with a time constant

$$\tau = \frac{L}{R_s + R_L}.$$

Generally,

$$R_s \gg R_L \text{ hence } \tau \approx \frac{L}{R_s}$$

If  $R_s$  is small the current will decay slowly and a long period will have to elapse before another sweep is possible. But the advantage is that, the peak voltage developed across the current source (transistor) will be small. Alternately, if  $R_s$  is large, the current will decay rapidly, but a large peak voltage will appear across the source.

Generally, one has to strike a compromise such that the spike amplitude is not appreciably large and at the time the inductor current decays in a smaller time interval. To achieve this normally a damping resistance  $R_d$  is connected across the yoke to limit the peak voltage. Let  $R$  be the parallel combination of  $R_s$  and  $R_d$ . Then the retrace time constant is

## Pulse & Digital Circuits

$$\tau_r = L/R.$$

Now, how to generate this trapezoidal waveform which when applied as a driving source will result in the linearity of the current sweep.

The trapezoidal waveform required is generated using the circuit in fig below.

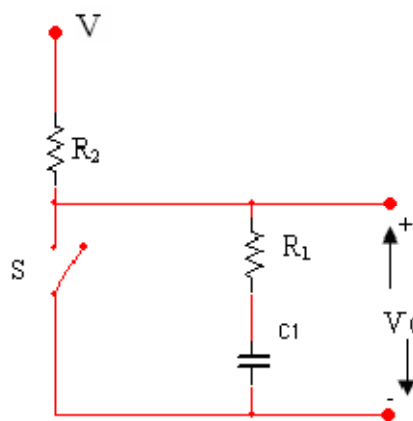


Fig . Generation of trapezoidal waveform

$$v_o = V - \frac{R_2}{R_1 + R_2} V e^{-t/(R_1 + R_2)C_1}$$

Generally

$$R_2 \gg R_1$$

$$v_o = \frac{V(R_1 + R_2) - R_2 V e^{-t/(R_1 + R_2)C_1}}{R_1 + R_2}$$

## Pulse & Digital Circuits

---

Dividing by  $R_2$

$$v_o = \frac{V(1 + \frac{R_1}{R_2}) - Ve^{-t/(R_1+R_2)C_1}}{R_1/R_2 + 1}$$

$$\approx \frac{VR_1}{R_2} + V - Ve^{-t/R_2C_1}$$

$$= \frac{VR_1}{R_2} + V(1 - Ve^{-t/R_2C_1})$$

$$v_o = V \frac{R_1}{R_2} + \frac{Vt}{R_2C_1} (1 - \frac{t}{2R_2C_1})$$

If  $\frac{t}{2R_2C_1} \ll 1$

$$v_o = V \frac{R_1}{R_2} + \frac{Vt}{R_2C_1}$$

Thus  $v_o$  is a step followed by ramp.

### Important Questions:

1. Explain the operation of UJT Sweep Generator?
2. What is a Sweep waveform and what are three types of errors that define deviation from linearity?
3. Explain miller Sweep circuit?
4. Explain Bootstrap Sweep circuit?
5. Explain simple exponential Sweep generator circuit?

## Pulse & Digital Circuits

### UNIT - VI

#### Logic Families & Sampling Gates



##### Logic circuits:

##### Introduction :

In large scale digital systems such as in a digital computer, data processing, control or digital communication system a few basic operations are needed. These are four circuits known as OR, AND, NOT and flip-flop. These are called logic gates or circuits because their operations uses logic algebra or Boolean algebra.
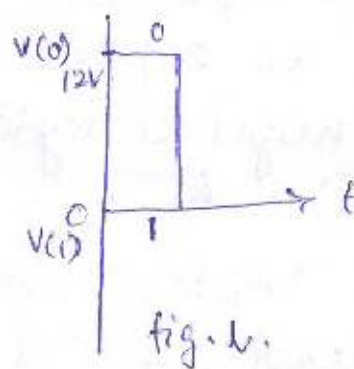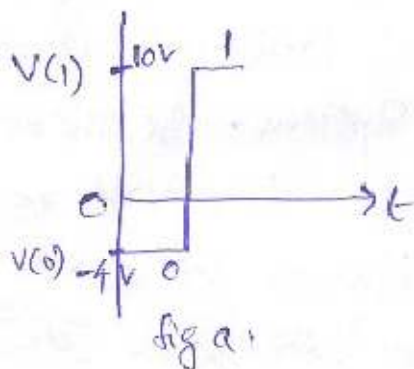
##### Logic System :

In a de-or level-logic system a bit is implemented as one of two voltage levels as shown below.




In fig (a) more positive voltage is the level 1 and the other is the level 0. this is called as de-positive logic. In fig(b) more negative voltage state is represented with 1 and more positive with 0, which is known as negative logic.

In a dynamic or pulse logic system of bit is recognized by the presence or absence of a pulse. In a dynamic positive logic system, positive pulse indicates 1 and its absence or no pulse signifies 0. Similarly a negative pulse indicates 1 in a dynamic negative system and no pulse or absence specifies 0.

## Pulse & Digital Circuits
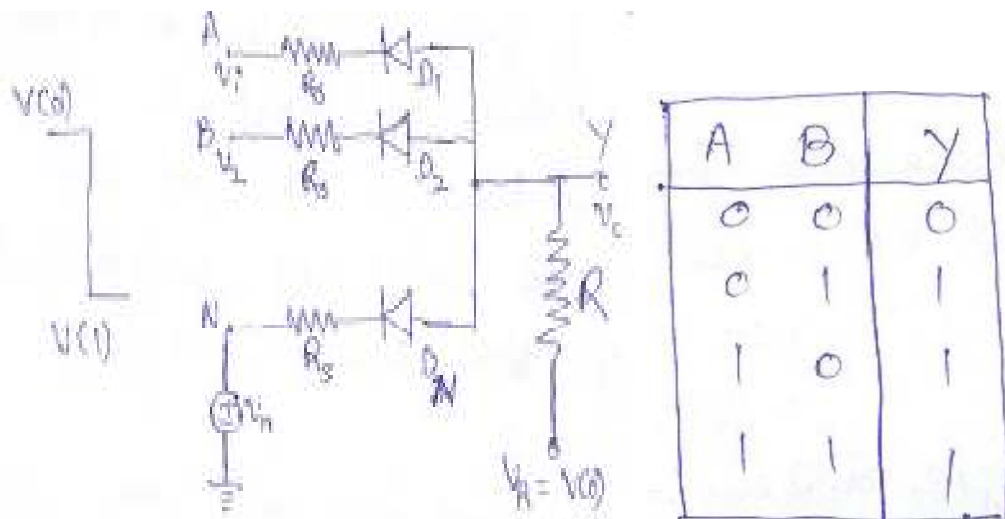
### OR gate :

The output of an OR assumes 1 state if any one of the inputs assumes 1 state. The N input logic circuit with output y is represented as shown below. Truth table for 2 input circuit is mentioned to understand simply.



In the circuit, since the diodes only are used, it is called diode logic (DL) system. Here upper and lower voltages are represented with  $V(0)$  and  $V(1)$  respectively, it is a negative logic system. If all inputs are applied by  $V(0)$ , the the voltage across each diode is  $V(0) - V(0) = 0$ . Hence no diode is forward biased by at least the cut voltage  $V_\gamma$  and none of the diode conducts. Therefore the output voltage is  $V_0 = V(0)$  and so the gate is said to be in the 0 state. If one of the inputs, say A, is changed to 1 state and for negative logic system, the level  $V(1)$  makes that diode forward bias. So diode  $D_1$  conducts and hence current flows in the resistance R. Therefore the output is given by

$$V_0 = V(0) \left[ \frac{V(0) - V(1) - V_\gamma}{R + R_s + R_f} \right]$$

Where  $R_f$  is the forward resistance and  $S R$  is the source resistance.

As  $R_f$  and  $R_s$  are smaller than R,

The above expression can be reduced to

## Pulse & Digital Circuits


$$V_0 = V(1) + V_\gamma$$

So the output voltage exceeds the more negative level  $V(1)$  by  $V_\gamma$  that means output voltage is smaller by  $V_\gamma$  than the change in input voltage. If for any reason the level  $V(1)$  is not identical for all inputs then the most negative value of  $V(1)$  (for negative logic) appears at the output. A positive logic OR gate can also be designed but this is same as above circuit except all diodes must be reversed.

**AND gate :**

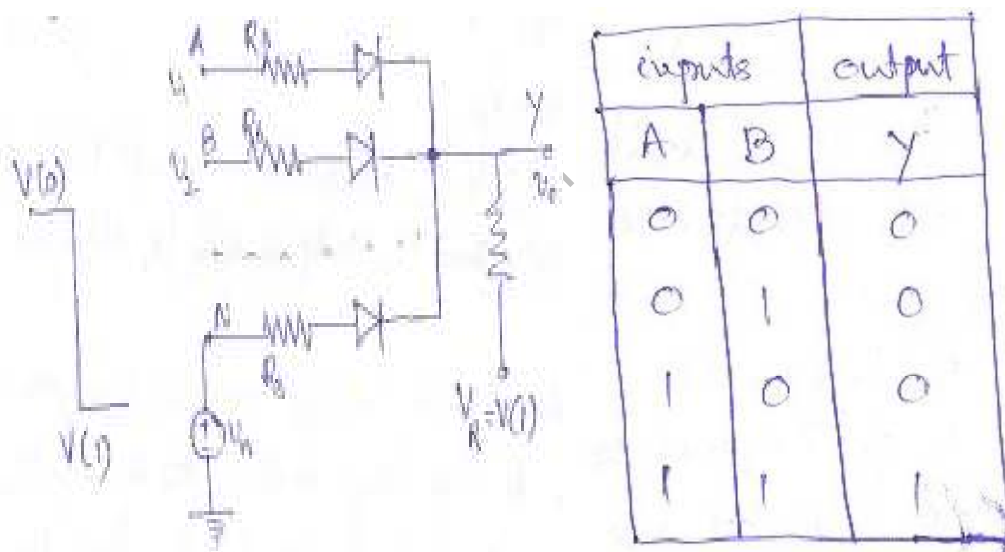**Definition :**

The output an AND assumes the 1 state if and only if all the inputs assume the 1 state. A diode (DL) configuration for a negative AND gate is shown below with truth table for 2 inputs.



To understand the operation simply, assume that all source resistances  $R_S$  are zero and that the diodes are ideal. If any input is at the 0 level  $V(0)$ , the diode connected to this input conducts and the output is clamped at the voltage  $V(0)$  or  $Y = 0$ .

If all the inputs are at the 1 level  $V(1)$ , then all diodes are reverse biased and output voltage is  $V(1)$

or  $y = 1$

## Pulse & Digital Circuits

Taking source resistance  $R_S$  and diode forward resistance  $R_F$  into account, we can determine the output of the circuit for positive logic system. Assume in inputs out of  $n$  are at  $V(1)$  and hence in diodes are reverse biased. The remaining  $n-m$  diodes conduct and hence the effective circuit of these diodes in parallel consists of


$$(R_S + R_f)/(n-m) \text{ in}$$

series with a voltage  $V_\gamma$ . Then the output is

$$V_o = V(1) - [V(1) - V(0) - V_\gamma] \left[ \frac{R}{R + \frac{(R_S + R_f)}{n-m}} \right]$$
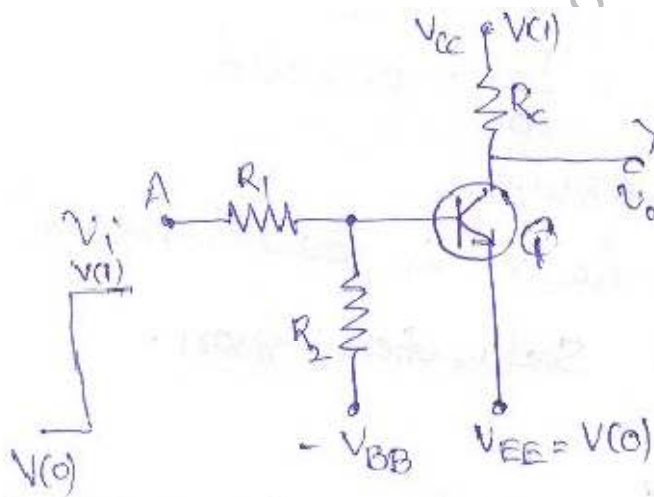
### NOT or INVERTER Circuit

The NOT logic circuit has a single input and single output. It is defined as the output of a NOT circuit takes on the 1 state if and only if the input does not take on the 1 state. The following transistor circuit performs the logic NOT operation in the dc positive logic system.



\_ If the input is low then the parameters are chosen so that in Q is OFF and hence output is high.

\_ When the input is changed to high state, then the circuit parameters are picked so that the transistor Q is in saturation and then output is zero. the saturation voltage will be very low i.e., a few tenths of a volt and that can be neglected.



## Pulse & Digital Circuits

### NAND Gate

A negation following an AND gate is called a NOT-AND or NAND gate. A positive NAND circuit is implemented by a cascade of diode AND and a transistor NOT as shown in the circuit.

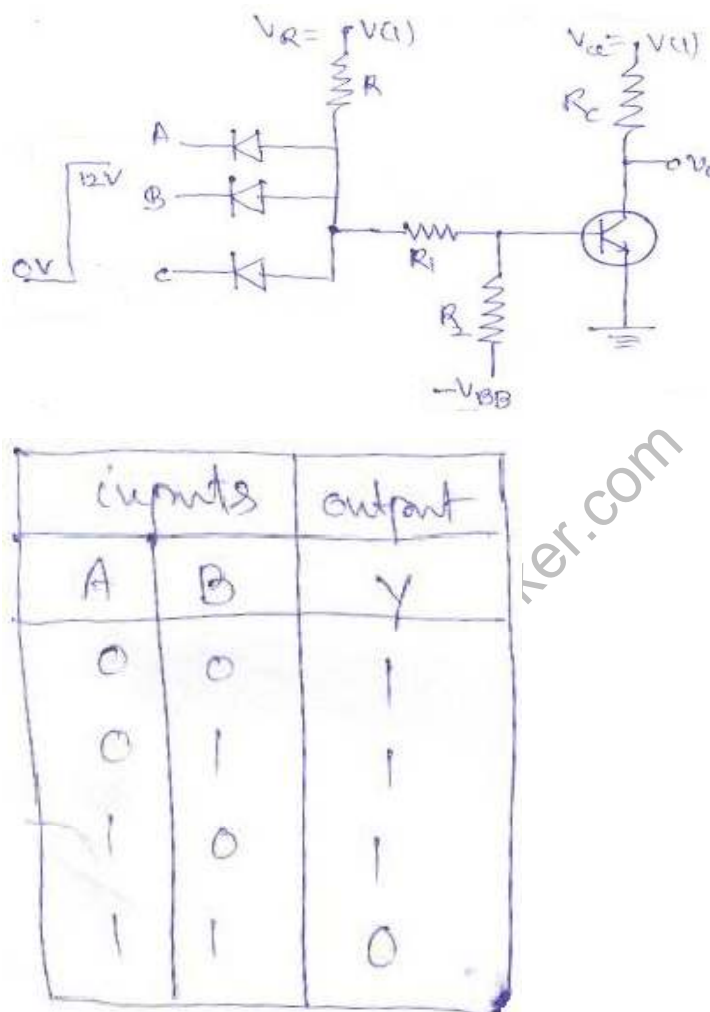


Fig.3 input NAND gate

## Pulse & Digital Circuits

Truth table for two input NAND circuit is mentioned. Similarly a NOR circuit can also be designed by cascading a diode NOT with a resistance OR. But the positive NAND gate is same as that of a negative NOR. These NAND and NOR circuits are involving with diodes and transistors, these are also called as Diode-Transistor logic (DTL) gates.


In the above DTL configurations, the same can be implemented by omitting the diodes. Then logic gates are called transistor resistor logic TTL or Resistor-Transistor Logic RTL. If these resistors are shunted with capacitors then they are called as Resistor- Capacitor-Transistor (RCTL) logic circuits.

### 6.1 Logic IC families:

- Most of logic gates, flip-flops, counters, shift registers, encoders, and decoders are available in several logic families.
- TTL, ECL, IIL, MOS, CMOS are the various logic families.

 
### 6.2 TTL two input NAND gate:

The following circuit diagram represents the TTL NAND gate with multi emitter transistor.



By the above operation we can say that TTL acts as NAND gate.

The following circuit diagram represents the ECL NOR GATE with three inputs.

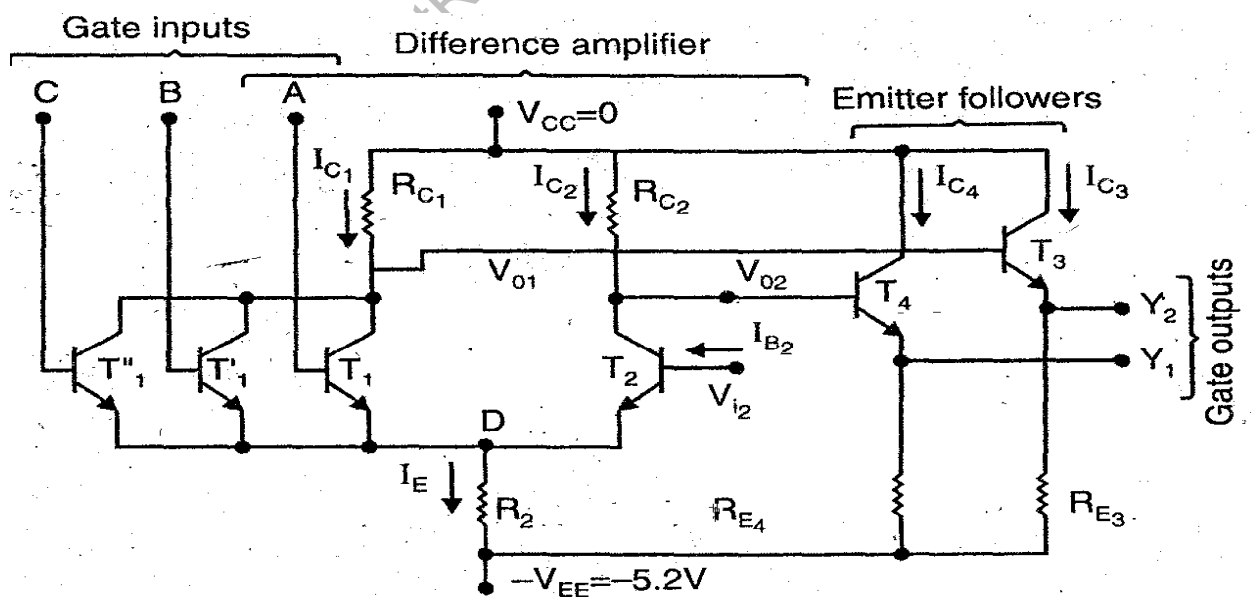

**Fig. (A) A 3-input ECL OR/NOR Gate**

## Pulse & Digital Circuits

### Circuit description:

The above diagram contains the inputs as A, B, C through the transistors  $T_1$ ,  $T_1'$ ,  $T_1''$  of which emitters are coupled and the combination of  $T_1$ ,  $T_1'$ ,  $T_1''$  and  $T_2$  will act as differential amplifier. The two collector currents in this configuration are  $I_{C1}$  and  $I_{C2}$  respectively. If one current increases another will get decrease. The two transistors  $T_2$ ,  $T_3$  are emitter followers.

### Circuit operation:

When A, B, C are low the transistors  $T_1$ ,  $T_1'$ ,  $T_1''$  will be off and the transistor  $T_2$  will be ON. Because of  $T_3$  will be ON output of nor gate is HIGH and because of  $T_4$  is OFF output is LOW at or output.

When any one of the inputs high, corresponding transistor is ON and the transistor  $T_2$  will be OFF. Because of  $T_3$  will be OFF output of nor gate is LOW and because of  $T_4$  is ON output is HIGH at or output.

When all of the inputs high, corresponding transistors  $T_1$ ,  $T_1'$ ,  $T_1''$  will be ON and the transistor  $T_2$  will be OFF. Because of  $T_3$  will be OFF output of nor gate is LOW and because of  $T_4$  is ON output is HIGH at or output.

### MOS (metal oxide semiconductor) logic:

This logic uses MOSFETS instead of Bipolar junction Transistors.

### Advantages:

- Easy to fabricate.
- Inexpensive.
- Require less power.
- Less chip area and high fan-out

## Pulse & Digital Circuits

---

### NFET and PFET Transistors:


- N channel device: built directly in the P substrate with N-doped source and drain junctions and normally N-doped gate conductor
  - Requires positive voltage applied to gate and drain (with respect to source) for electrons to flow from source to drain (thought of as positive drain current)
- P channel device: built in an N-well (a deep N-type junction diffused into the P substrate) with P-doped source and drain junctions and N or P-doped gate
  - Requires negative voltage applied to gate and drain (with respect to source) for electrons to flow from drain to source (thought of as negative drain current)

### 6.4 CMOS logic family

- CMOS stands for *Complementary Metal Oxide Semiconductor*
  - **Complementary:** there are N-type and P-type transistors. N-type transistors use electrons as the current carriers. P-type transistors use holes as the current carriers.
  - **Metal:** the gate of the transistor was made of aluminum metal in the early days, but is made of polysilicon today.
  - **Oxide:** silicon dioxide is the material between the gate and the channel
  - **Semiconductor:** the semiconductor material is silicon, a type IV element in the periodic chart. Each silicon atom bonds to four other silicon atoms in a tetrahedral crystal structure.

## Pulse & Digital Circuits

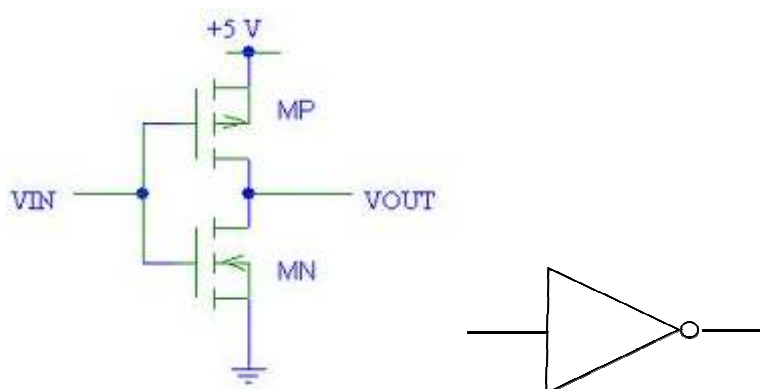
### Simple CMOS Circuits: *The Inverter Gate*



- **The simplest complementary MOS (CMOS) circuit is the inverter:**
  - NFET & PFET gates are connected together as the input
  - NFET & PFET drains are connected together as the output
  - NFET & PFET sources are connected to Gnd and  $V_{dd}$ , respectively.
  - NFET substrate is normally connected to Gnd for all NFET devices in the circuit
  - PFET well is normally connected to  $V_{dd}$  (most positive voltage in circuit) for all PFET devices
- **Operation:**
  - If  $V_{in}$  is down (0 volts), NFET is OFF and PFET is ON pulling  $V_{out}$  to  $V_{dd}$  (high = 1)
  - If  $V_{in}$  is up (at  $V_{dd}$ ), NFET is ON hard and PFET is OFF pulling  $V_{out}$  low to Gnd ("0")
  - With  $V_{in}$  at 0 or  $V_{dd}$ , no dc current flows in inverter

### CMOS Circuits: *2-way NAND*

## Pulse & Digital Circuits

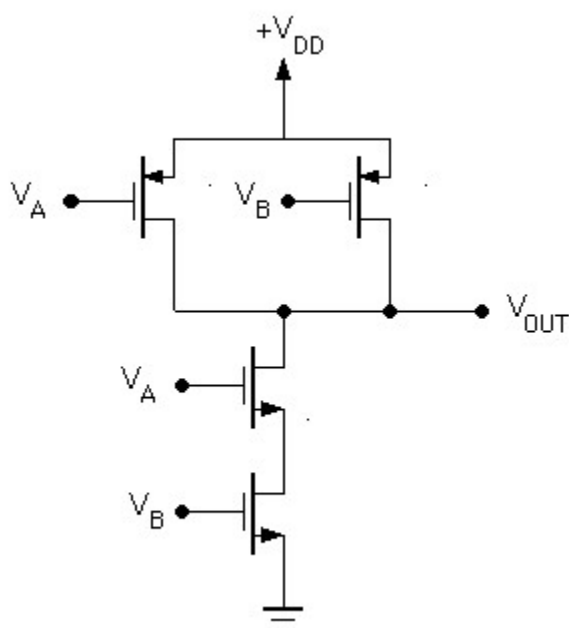

- **Circuit Topology:**

- T1 and T2 are N-FET devices connected in series; T3 and T4 are P-FET devices connected in parallel with their sources at V<sub>dd</sub> and their drains at V<sub>out</sub>.
- Inputs A and B are connected to the gates of T1 & T3 and T2 & T4, respectively.
- T2, T3, & T4 operate as “grounded source” devices, but T1 has its source generally above Gnd potential.



- **Operation:**

- If both A and B are high (at V<sub>dd</sub>), both T1 and T2 are ON hard, therefore pulling V<sub>out</sub> low (to zero volts). Both T3 and T4 are OFF due to their gate-to-source voltages (V<sub>gs</sub>) being at 0 volts, thus preventing any dc current.

## Pulse & Digital Circuits

- If either A or B (or both) are low (at 0 volts), either T1 or T2 (or both) are OFF; T3 or T4 (or both) are ON hard, thus pulling  $V_{out}$  high to  $V_{dd}$  (a “1” output).

### CMOS Circuits: 2-way NOR

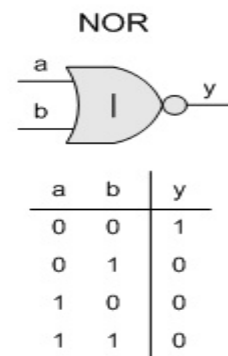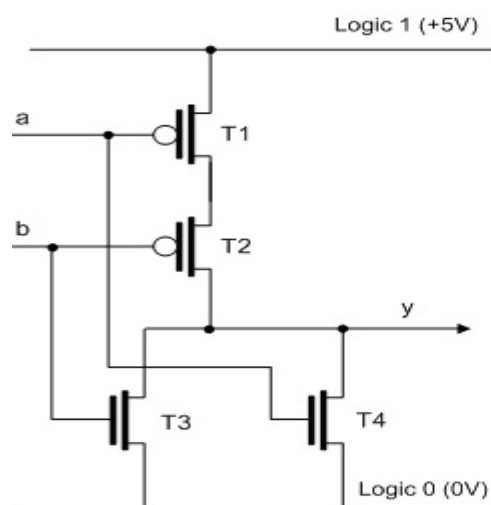

- **Circuit Topology:**

- T1 and T2 are N-FET devices connected in parallel with their sources at Gnd and drains at  $V_{out}$ ; T3 and T4 are P-FET devices connected in series.
- Inputs A and B are connected to the gates of T1 & T3 and T2 & T4, respectively.
- Operation:
  - If either A or B is high, T1 and/or T2 are ON hard and either T3 or T4 (or both) are OFF, pulling  $V_{out}$  to gnd. No dc current flows.
  - If both A and B are low (at gnd), both T1 and T2 are OFF and both T3 and T4 are ON hard, thus pulling  $V_{out}$  to  $V_{dd}$  (a “1” output).



## Pulse & Digital Circuits

---

- T1, T2, and T3 operate as common source, but T4's source potential will drop below  $V_{dd}$ .


### Important Questions:

1. What are two logic levels represented by logic system? How they can be represented?
2. Explain how TTL acts as NAND gate?
3. What is a totem pole configuration?
4. Explain how ECL acts as NOR gate?
5. Explain CMOS Inverter circuit?
6. Explain the operation of D-FlipFlop?

## Pulse & Digital Circuits

---

[www.FirstRanker.com](http://www.FirstRanker.com)

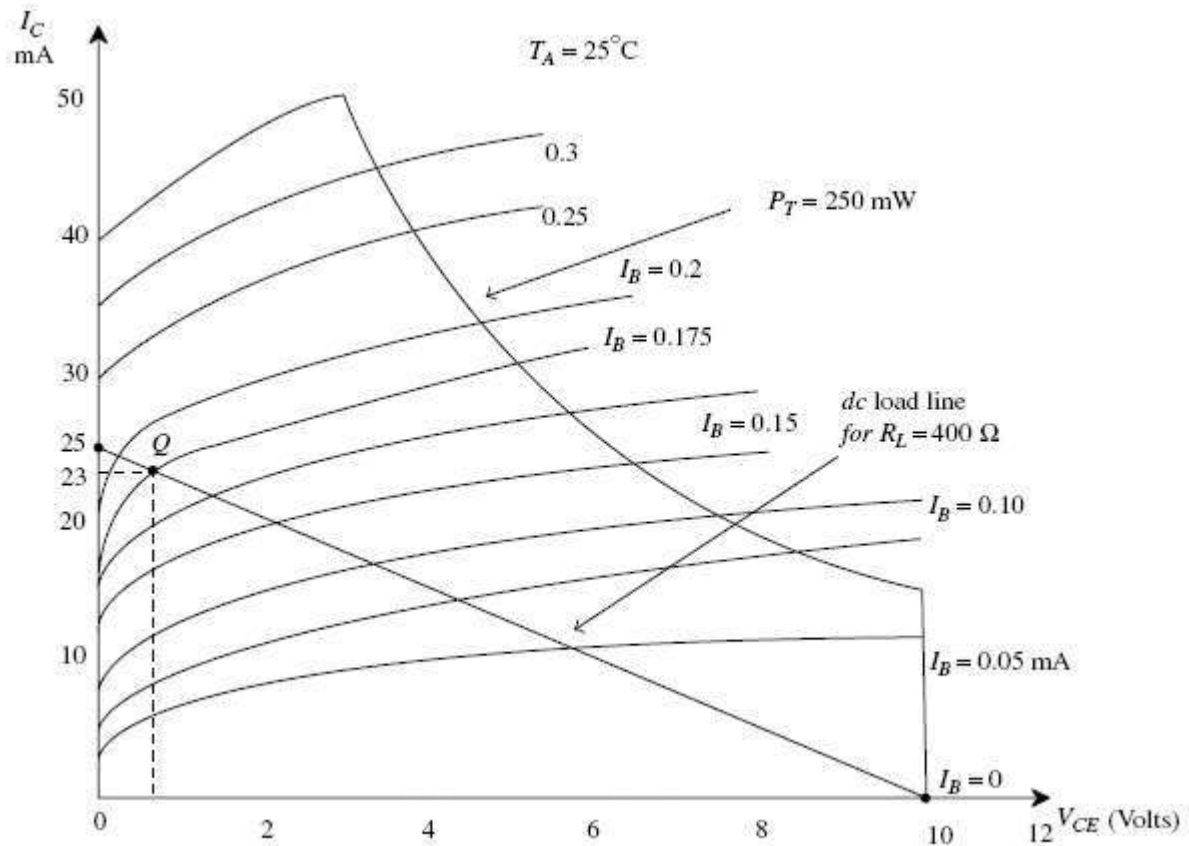

**FIGURE 6.36** Typical output characteristics of an  $n-p-n$  transistor in the CE mode

## UNIT-IV - b

### Sampling gates

#### INTRODUCTION


A sampling gate is a transmission circuit that faithfully transmits an input signal to the output for a finite time duration which is decided by an external signal, called a gating signal (normally rectangular in shape), as shown in Fig. 11.1.

The input appears without a distortion at the output, but is available for a time duration  $T$  and afterwards the signal is zero. They can transmit more number of signals. The main applications of


the sampling gates are: (i) multiplexers; (ii) choppers; (iii) D/A converter; (iv) sample and hold circuits, etc. Sampling gates can be of two types:

1. Unidirectional gates: These gates transmit the signals of only one polarity.
2. Bidirectional gates: These gates transmit bidirectional signals (i.e., positive and negative signals).

Earlier, we had seen logic gates in which the output, depending on the input conditions, is either a 1 level or a 0 level. That is, the inputs and outputs are discrete in nature. In a sampling gate, however, the output is a faithful replica of the input. Hence, sampling gates are also called linear gates, transmission gates or time selection circuits. Linear gates can use either a series switch, as shown in Fig. 11.2(a) or a shunt switch, as shown in Fig. 11.2(b). In Fig. 11.2(a), only when the switch closes, the input signal is transmitted to the output. In Fig. 11.2(b), only when the switch is open the input is transmitted to the output.

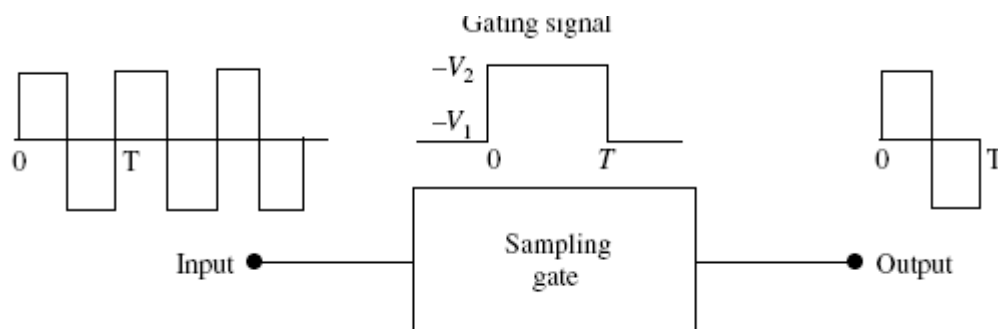

**FIGURE 11.1** A sampling gate

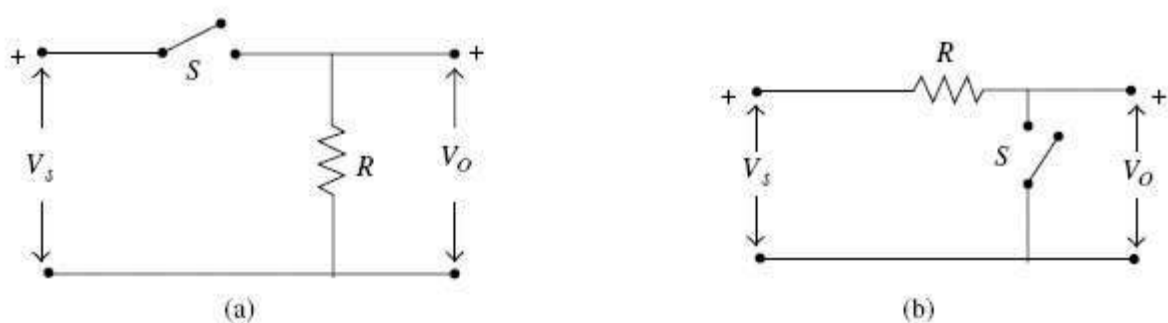

**FIGURE 11.2** A linear gate (a) using a series switch; and (b) using a shunt switch

### UNIDIRECTIONAL DIODE GATES

A unidirectional gate can transmit either positive or negative pulses (or signals) to the output. It means that this gate transmits pulses of only one polarity to the output. The signal to be

transmitted to the output is the input signal. This input signal is transmitted to the output only when the control signal enables the gate circuit. Therefore, we discuss two types of unidirectional diode gates, namely, unidirectional diode gates that transmit positive pulses and unidirectional diode gates that transmit negative pulses.


### Unidirectional Diode Gates to Transmit Positive Pulses

In order to transmit positive pulses, the unidirectional gate shown in Fig. 11.3 can be used. The gating signal is also known as a control pulse, selector pulse or an enabling pulse. It is a negative signal, whose magnitude changes abruptly between  $-V_2$  and  $-V_1$ .


Consider the instant at which the gating signal is  $-V_1$ , which is a reasonably large negative voltage. As a result,  $D$  is OFF. Even if a positive input pulse is present when the gating signal with value  $-V_1$  is present, the diode  $D$  remains OFF since the input may not be sufficiently large to forward-bias it. Hence, the output is zero.

Now consider the duration when the gate signal has a value  $-V_2$  (smaller negative value) and when the input is also present (coincidence occurs). Assume that the control signal has peak-to-peak swing of 25 V and the signal has peak-to-peak swing of 15 V.

1. Let, for example,  $-V_1 = -40$  V,  $-V_2 = -15$  V and the signal amplitude be 15 V, as shown in Fig. 11.4(a). The net voltage at the anode of the diode, when the input is present for the duration of the gating signal, is 0. The diode is OFF and the output in this case is zero.

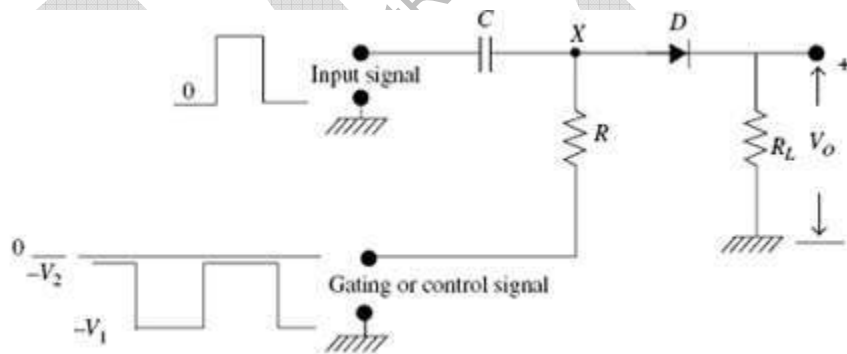


**FIGURE 11.3** The unidirectional gate to transmit positive pulses

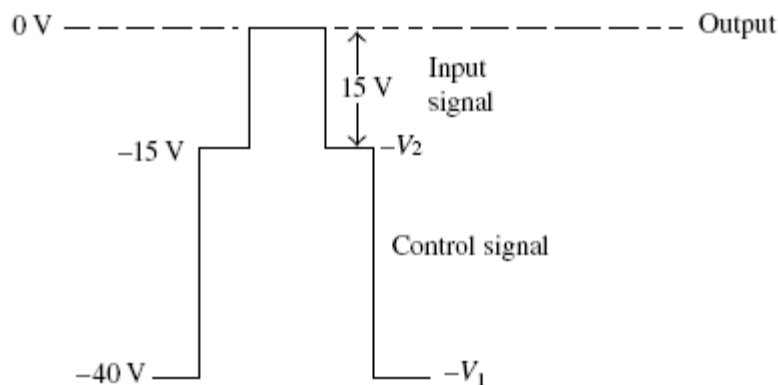


**FIGURE 11.4(a)** The control signal with  $-V_1 = -40$  V,  $-V_2 = -15$  V and the input amplitude 15 V


2. Now, change the levels to  $-V_1 = -35$  V,  $-V_2 = -10$  V and the signal amplitude remains constant at 15 V, as shown in [Fig. 11.4\(b\)](#). Only when the input forward-biases the diode, there is an output. The output in this case is a pulse of amplitude 5 V (assuming an ideal diode). The duration of the output is the same as the duration of the input signal.
3. Now let  $-V_1 = -30$  V,  $-V_2 = -5$  V and the signal amplitude be 15 V, as shown in [Fig. 11.4\(c\)](#). As the signal above the zero level is 10 V, the output is a pulse of amplitude 10 V and has the same duration as the input.
4. Let  $-V_1 = -25$  V,  $-V_2 = 0$  V and the signal amplitude be 15 V, as shown in [Fig. 11.4\(d\)](#). The output in this case is 15 V and has the same duration as the input.
5. Let  $-V_2 = +5$  V and  $-V_1 = -20$  V, as shown in [Fig. 11.4\(e\)](#). In this case, the output not only contains the input but also a portion of the control signal. The desired signal at the output is seen to be riding over a pedestal. We see that the output of the gate changes by adjusting  $-V_2$  and in the last case it is seen that the output is superimposed on a pedestal of 5 V. Thus, the output is influenced by the control signal.

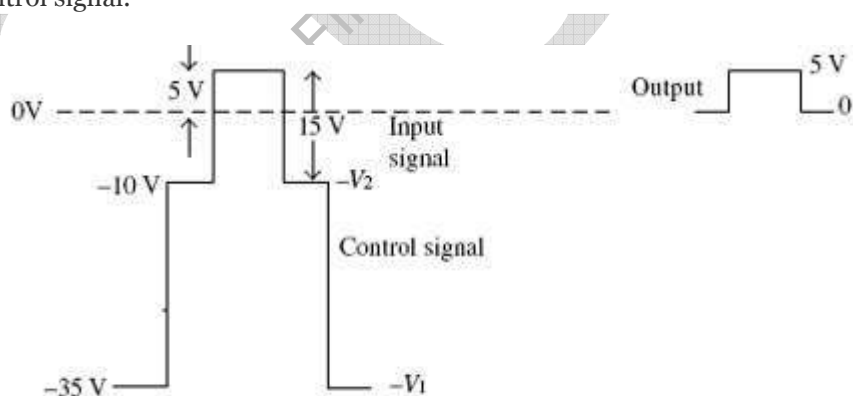


**FIGURE 11.4(b)** The control signal with  $V_1 = -35$  V,  $-V_2 = -10$  V and the input amplitude 15 V

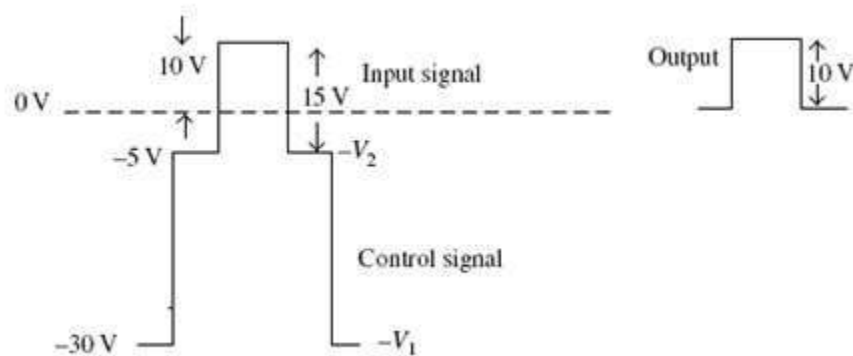

**FIGURE 11.4(c)** The control signal with  $V_1 = -30$  V,  $-V_2 = -5$  V and the input amplitude 15 V

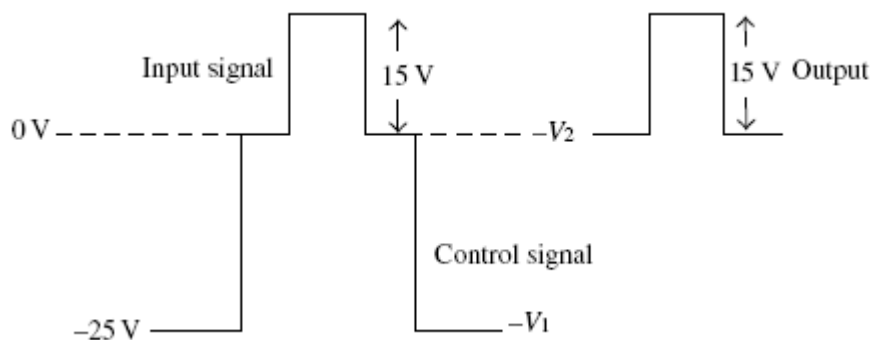

**FIGURE 11.4(d)** The control signal with  $V_1 = -25$  V,  $-V_2 = 0$  V and the input amplitude 15 V

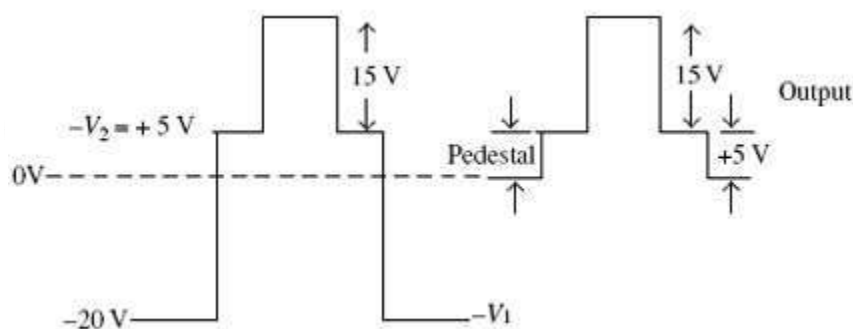


**FIGURE 11.4(e)** The control signal with  $V_1 = -20$  V,  $-V_2 = 5$  V and the input amplitude 15 V


For a gating signal, the  $RC$  network behaves as an integrator. Hence, the gate signal is not necessarily a rectangular pulse but rises and falls with a time constant  $RC$ . As a result, there is a distortion in the gate signal. However, if the duration of the input signal (a pulse) is much smaller than the duration of the gate, this distortion associated with the gating signal is not necessarily

transmitted to the output; and the output is a sharp pulse as desired, provided the pedestal is eliminated, as shown in Fig. 11.4(f). On the contrary, if there is a pedestal, there is a corresponding distortion in the output, as shown in Fig. 11.4(g).

The advantages of unidirectional diode gates are: (i) they are simple to implement; (ii) have a negligible transmission delay; (iii) the gate draws no current in the quiescent condition; and (iv) by the proper modification of the circuit, more than one input signal can be transmitted through the gate circuit. However, there are two disadvantages of this arrangement. As the control signal and the input signal are directly connected at  $X$  (see Fig. 11.3), there could be an interaction between these two sources. The time constant  $RC$ , if properly not chosen, can cause the distortion of the gate signal. A two-input unidirectional diode gate is shown in Fig. 11.5(a).

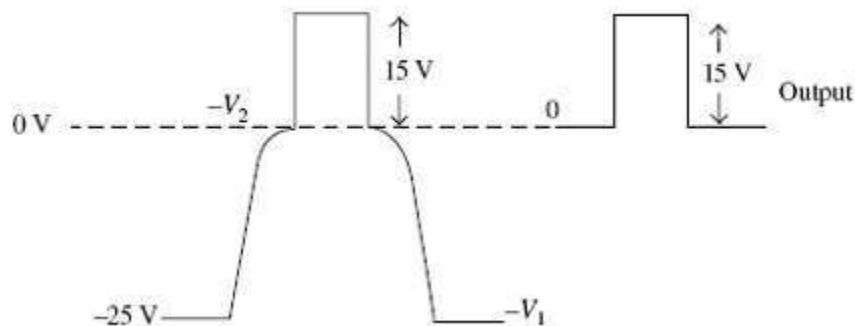

**FIGURE 11.4(f)** There is no distortion in the output though the control signal is distorted

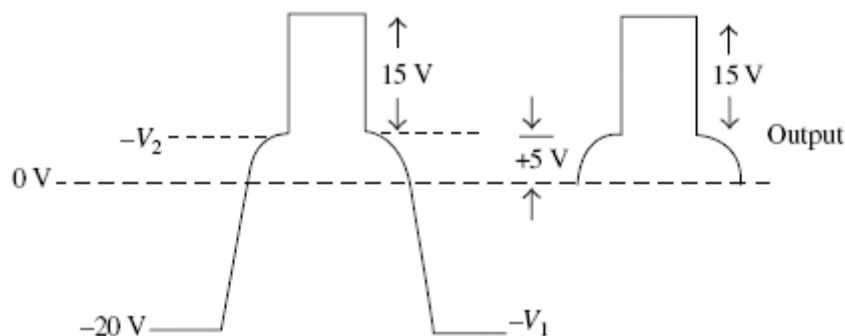


**FIGURE 11.4(g)** The distorted gate signal giving rise to a distorted pedestal


Let  $V_{s1}$  and  $V_{s2}$  be the pulses of amplitude  $5\text{ V}$ . When both these signals appear at the input simultaneously, having the same duration, the output is shown in Fig. 11.5(b), when  $-V_1 = -25\text{ V}$  and  $-V_2 = 0$ .




When the control signal is at  $-V_2 (= 0 \text{ V})$ , and if both the inputs are 0 the output is zero. When the inputs are above 0, the output is 5 V. However, when the control input is at  $-V_1 (-25 \text{ V})$ , no output is available. This negative control signal inhibits the gate. Hence, this circuit is a two-input OR gate with  $-V_1 (-25 \text{ V})$  and inhibiting the gate operation. The waveforms shown in [Fig. 11.5\(b\)](#) suggest that time division multiplexing can be employed to simultaneously transmit a number of signals. The limitation of this arrangement is that signal sources may load the control input. To overcome this disadvantage, an arrangement in which the signal sources avoid loading the control input is suggested in [Fig. 11.6](#). Here, the input signals are connected to point X through diodes  $D_1$  and  $D_2$  whereas the control source is connected at X directly to avoid interference and loading.

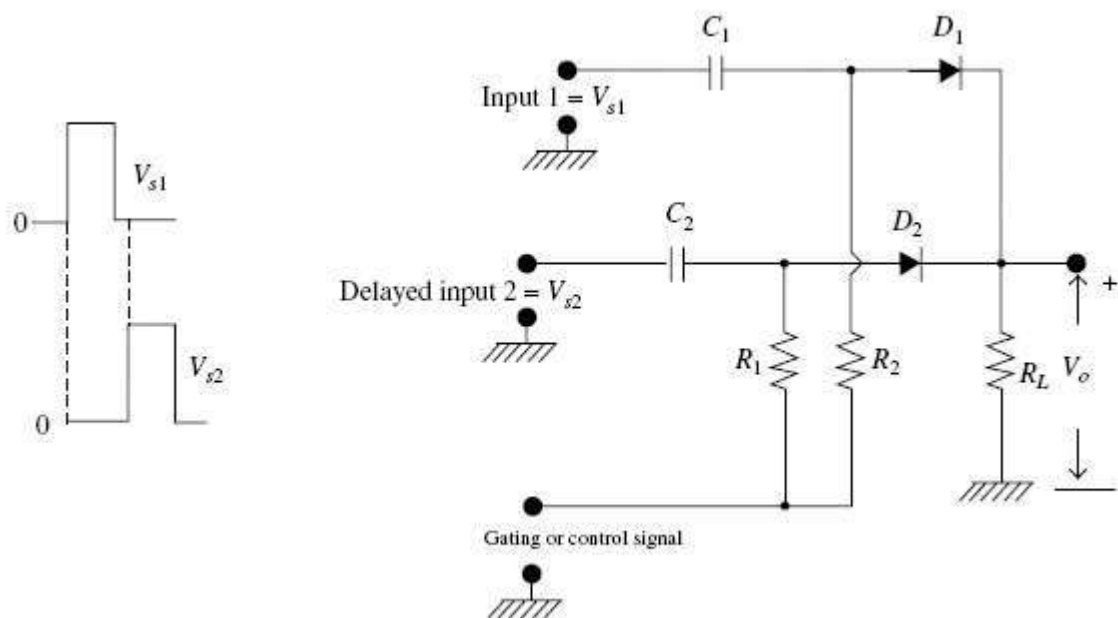

**FIGURE 11.5(a)** A unidirectional two-input diode gate

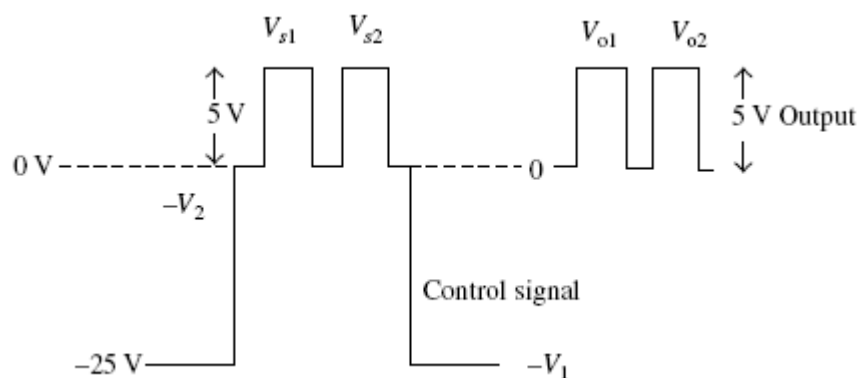

**FIGURE 11.5(b)** The waveforms of a two-input unidirectional gate

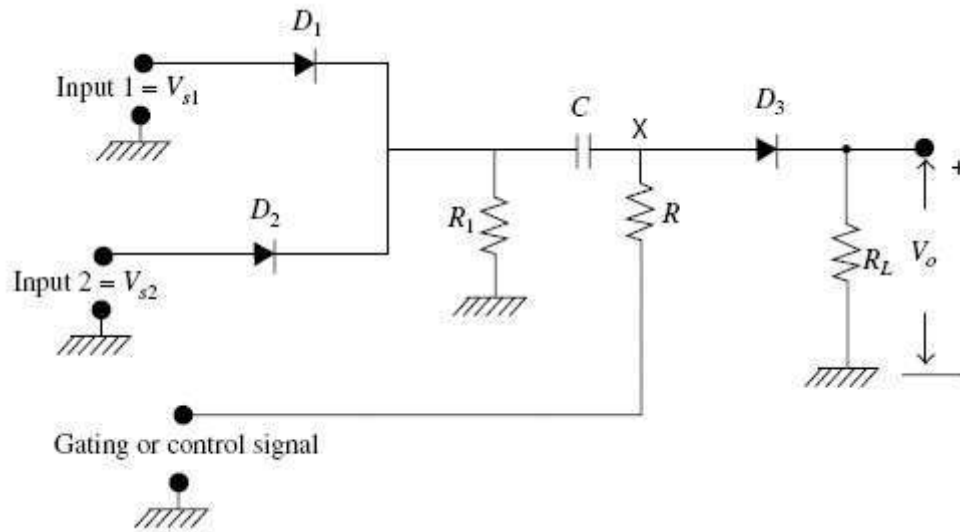


**FIGURE 11.6** A two-input diode gate that avoids loading on the control signal


### Unidirectional Diode Gates

1. **A unidirectional diode coincidence gate (AND gate):** In certain applications, it may become necessary that the input be transmitted to the output only when a set of conditions are simultaneously satisfied. In such cases, a coincidence gate is employed. A unidirectional diode coincidence (AND) gate is shown in Fig. 11.7(a).

When any of the control voltages is at  $-V_1$  ( $-25$  V), point X is at a larger negative voltage, even if the input pulse  $V_s$  ( $15$  V) is present.  $D_0$  is reverse-biased. Hence, there is no signal at the output.

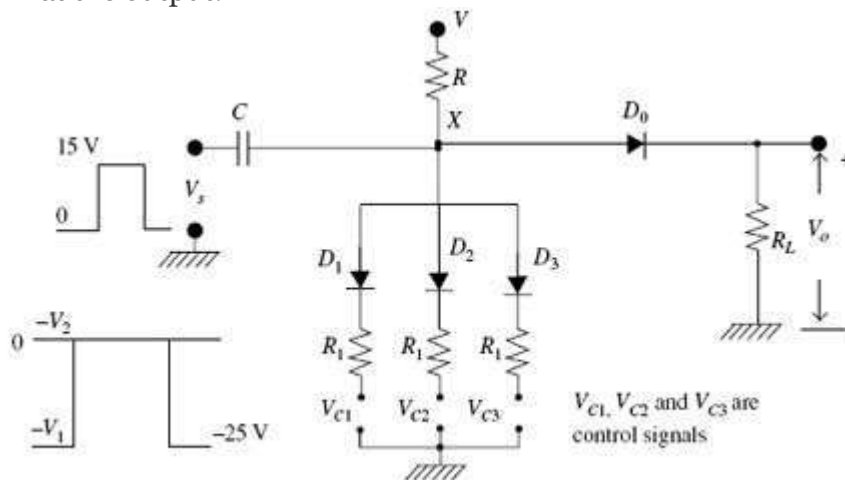

**FIGURE 11.7(a)** A unidirectional diode AND gate with multiple control signals

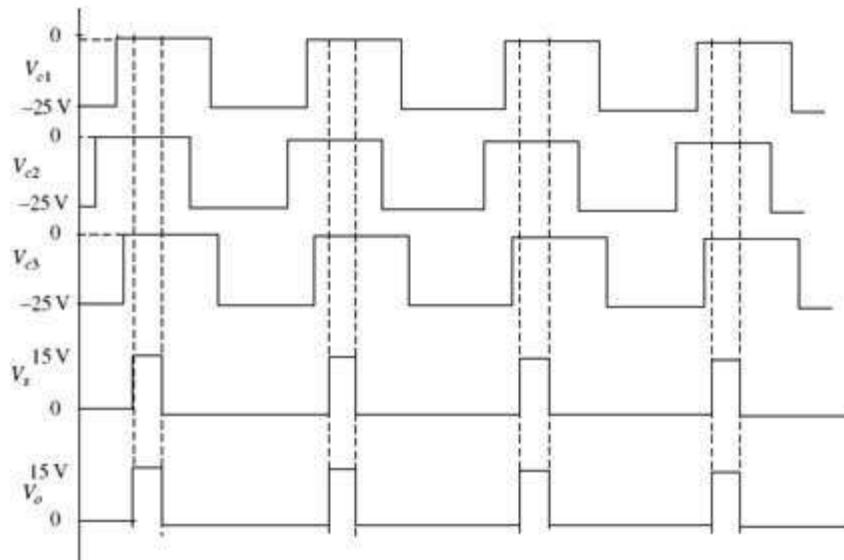


**FIGURE 11.7(b)** The waveforms of the coincidence (AND) gate


When all the control voltages, on the other hand, are at  $-V_2$  (0 V), if an input signal  $V_s$  (15 V) is present,  $D_o$  is forward-biased and the output is a pulse of 15 V. Thus, only when all the control signals are at 0 V (1 level) and if an input signal is present, then it is transmitted to the output. Hence, this circuit is a coincidence circuit or AND circuit, as shown in [Fig. 11.7\(b\)](#).

2. **A unidirectional diode OR gate:** Consider the gate circuit shown in [Fig. 11.8\(a\)](#). Let the control voltages vary from  $-50$  V to  $0$  V. If any control signal  $V_C$  (say  $V_{C1}$ ) is at  $0$  V,  $D_1$  conducts and behaves as a short circuit. Then the resultant circuit is shown in [Fig. 11.8\(b\)](#). If  $R_s$  is  $1$  k $\Omega$  and if  $I$  is specified as  $1$  mA then  $R = 149$  k $\Omega$ . The voltage at  $X$  is now at  $-1$  V.

Hence,  $D_o$  is reverse-biased and is an open circuit; and so the output is zero. Now, if a pulse  $V_s (= 10$  V) is applied at the input,  $D_o$  is forward-biased and  $D_1$  and  $D_2$  are reverse-biased. The output is  $10$  V.

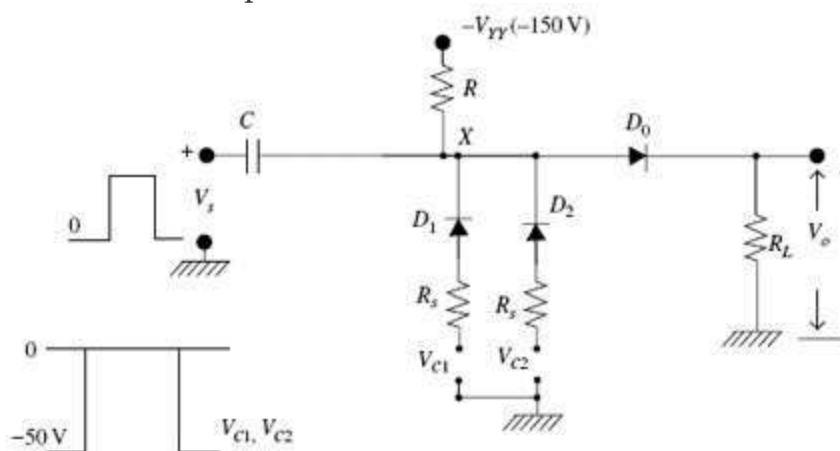

**FIGURE 11.8(a)** An OR sampling gate

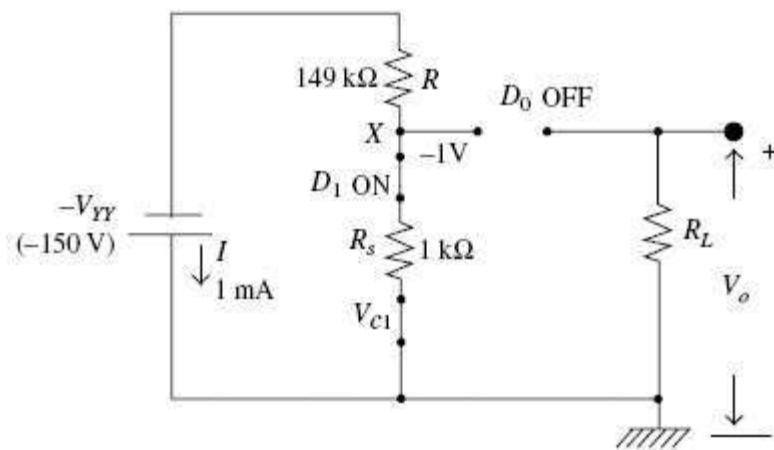

**FIGURE 11.8(b)** The circuit of Fig. 11.8(a) when any of the control signals and inputs is zero


Thus, the circuit shown in Fig. 11.8(a) is a gate that transmits the input signals to the output when any one of the control inputs is 0 V (1 level). This circuit is an OR circuit. The waveforms are shown in Fig. 11.8(c). The truth table, given in Table. 11.1 with control signals as logical inputs, verifies the OR operation. We see from the waveforms shown in Fig. 11.8(c) and Table.11.1 that the output is 0 V (0 level) for input pulses 4 and 8, for which both the control signals are -50 V (0 level).

3. **Unidirectional diode gate that eliminates pedestal:** In the unidirectional gates discussed till now, if the upper level of the gating signal ( $-V_2$ ) is exactly zero volts, the gate is enabled and an input is faithfully transmitted to the gate output terminals. The output can also be derived if  $-V_2$  is a positive voltage (say 5 V). In this case, the output will have a pedestal and the signal is superimposed on it. To ensure that the output is a faithful replica of the input even if the upper level of the control signal is positive (i.e., to eliminate pedestal), the circuit shown in Fig. 11.9(a) is employed.


1. If the input  $V_s$  is zero and if the enabling control signal is not present,  $D_1$  conducts and the negative voltage at X reverse-biases  $D_0$  and  $V_o = 0$ , shown in Fig. 11.9(b).

**TABLE 11.1** The truth table of the OR gate with control signals as logical inputs


Input pulse number	State of $V_{C1}$	State of $V_{C2}$	Output $V_o$
1	0 V (1 level)	0 V (1 level)	10 V (1 level)
2	-50 V (0)	0 V (1)	10 V (1)
3	0 V (1)	-50 V (0)	10 V (1)
4	-50 V (0)	-50 V (0)	0 V (0)
5	0 V (1)	0 V (1)	10 V (1)
6	-50 V (0)	0 V (1)	10 V (1)
7	0 V (1)	-50 V (0)	10 V (1)
8	-50 V (0)	-50 V (0)	0 V (0)
9	0 V (1)	0 V (1)	10 V (1)
10	-50 V (0)	0 V (1)	10 V (1)
11	0 V (1)	-50 V (0)	10 V (1)

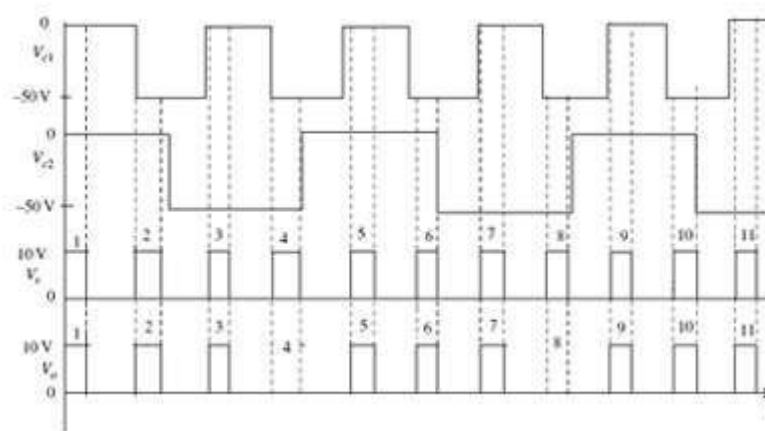


**FIGURE 11.8(c)** The waveforms of the OR gate shown in [Fig. 11.8\(a\)](#).

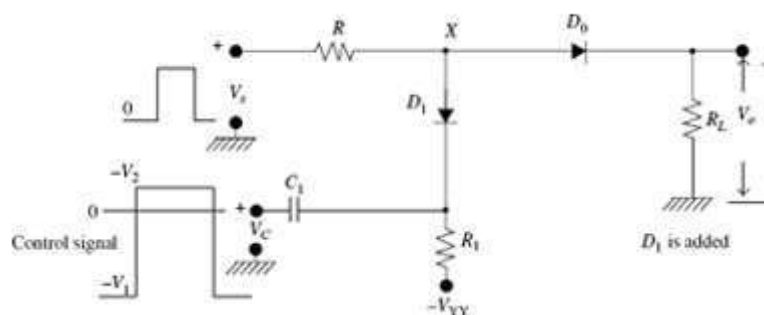

**FIGURE 11.9(a)** A sampling gate that is insensitive to the upper level ( $-V_2$ ) of the control signal

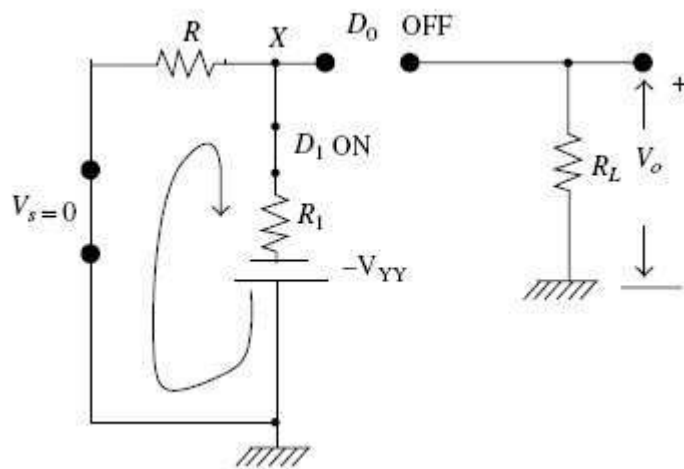

**FIGURE 11.9(b)** The circuit of Fig. 11.9(a) when  $V_s = 0$  and the control signal is absent

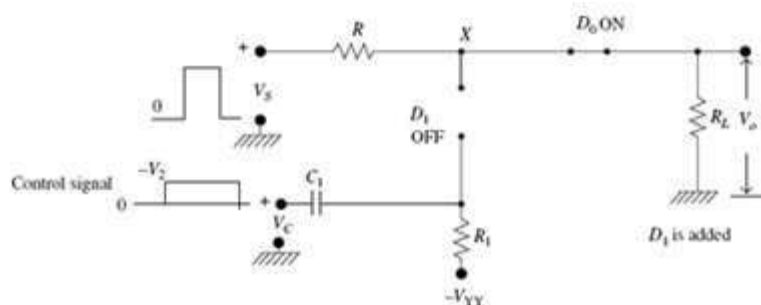

**FIGURE 11.9(c)** The circuit when the control signal is positive and the input is present

2. If the control voltage is now positive,  $D_1$  is reverse-biased and is OFF, as shown in Fig. 11.9(c). An input signal  $V_s$  (a positive pulse) ensures conduction of  $D_0$  and hence, the input signal is present at the output for the duration of the control signal. There is no pedestal in the output even though the control signal has a positive voltage as its upper level.

### A Unidirectional Diode Gate to Transmit Negative Pulses


A unidirectional diode gate is shown in Fig. 11.3, to transmit the positive pulses when the gating signal is present. Similarly, a unidirectional diode gate to transmit negative pulses can be constructed as shown in Fig. 11.10. The difference between these two gates is that the input signals are negative pulses and the gating signal varies between  $V_1$  and  $V_2$  as shown in Fig. 11.10 and the diode is connected in the opposite direction.

When the gating signal is at  $V_1$ , the voltage at  $X$  is a large positive voltage as a result  $D$  is reverse-biased. If an input signal is now present until the magnitude of the input is more negative than the

positive voltage at  $X$ , the diode will not conduct, i.e., for the diode to conduct and thus transmit the signal to the output, the input is required to have a large negative value. Even if the diode conducts only the peak of the input will be transmitted to the output, but not the entire input signal. On the other hand, when the amplitude of the gating signal is  $V_2$ , a small positive voltage, if a negative pulse is present at the input it can make the diode conduct. As such the output is present when the gating signal is at  $V_2$ .

### BIDIRECTIONAL SAMPLING GATES


Till now we have considered gates that pass only unidirectional signals. Bidirectional sampling gates transmit both positive and negative signals. These gates can be derived using diodes, BJTs, FETs, etc. We are going to consider some variations of the bidirectional gates.

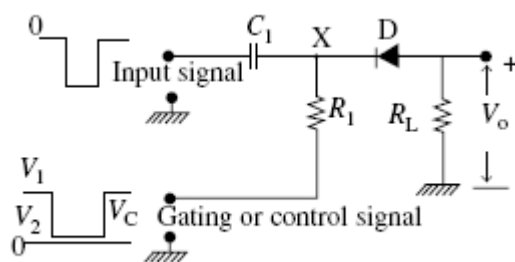

**FIGURE 11.10** The unidirectional diode gate to transmit negative pulses

### SINGLE-TRANSISTOR BIDIRECTIONAL SAMPLING GATES

A bidirectional sampling gate using a single transistor is shown in [Fig. 11.11](#). The control signal and the input are applied to the base of  $Q$ . The control signal is a pulse whose amplitude varies between  $V_1$  and  $V_2$  and has a duration  $t_p$  sufficient enough for a signal transmission. As long as  $V_c$  is at the lower level  $V_1$ ,  $Q$  is OFF and at the output we only have a dc voltage  $V_{cc}$ . However, when  $V_c$  is at its upper level  $V_2$ ,  $Q$  is ON for the duration  $t_p$  and if the input signal is present during this period, it is amplified and transmitted to the output with phase inversion but referenced to a dc voltage  $V_{dc}$ . At the end of  $t_p$ ,  $Q$  is again OFF and the dc voltage at its collector jumps to  $V_{cc}$ . Thus, the signal is transmitted when the gating signal is at  $V_2$ . However, the output contains a pedestal.

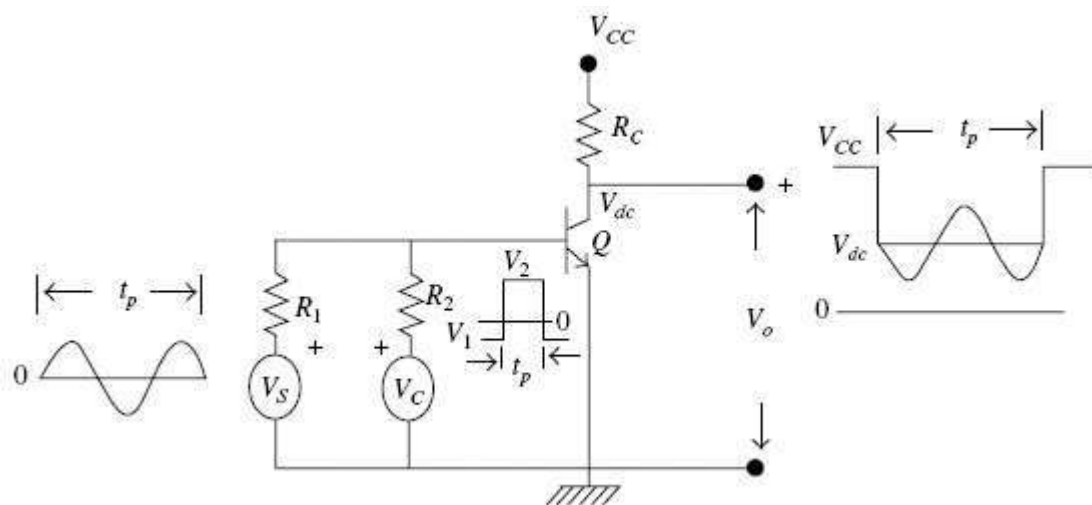

**FIGURE 11.11** A bidirectional transistor gate


### Two-transistor Bidirectional Sampling Gates

The [Fig. 11.12\(a\)](#) shows another bidirectional transistor gate where two devices  $Q_1$  and  $Q_2$  are used and the control signal and the input signal are connected to the two separate bases.


There is no external dc voltage connected to the base of  $Q_1$ , only the gating signal  $V_C$  is connected. Let the control voltage be at its upper level,  $V_2$ . Then,  $Q_1$  is ON and there is sufficient emitter current  $I_{E1}$  which results in  $V_{EN1}$  across  $R_E$ .  $Q_2$  is biased to operate in the active region using  $R_1$  and  $R_2$ . The voltage at the base of  $Q_2$  with respect to its emitter ( $V_{BE2}$ ) is  $(V_{BN2} - V_{EN1})$ . If this voltage is sufficient enough to reverse-bias the base emitter diode of  $Q_2$ , then  $Q_2$  is OFF. There is no output signal, but only a dc voltage  $V_{CC}$  is available. However, when the gating signal is at its lower level  $V_1$ ,  $Q_1$  is OFF and  $Q_2$  operates in the active region and can also operate as an amplifier. If an input signal is present, there is an amplified output  $V_o$ . The presence of  $R_E$  increases the input resistance  $R_i$  and thus, the signal source is not loaded.

From the waveforms shown in [Fig. 11.12\(b\)](#) it is seen that the output is  $V_{CC}$  when  $Q_2$  is OFF. When the gating signal drives  $Q_1$  OFF and  $Q_2$  ON, the dc voltage at the collector of  $Q_2$  falls to  $V_{dc}$  (a voltage much smaller than  $V_{CC}$ ). During the period of the gating signal, the input signal is amplified and phase inverted by  $Q_2$  and is available at the output. Again at the end of the gating signal  $Q_2$  goes OFF and  $V_o$  jumps to  $V_{CC}$ . Hence, the signal is superimposed on a pedestal.



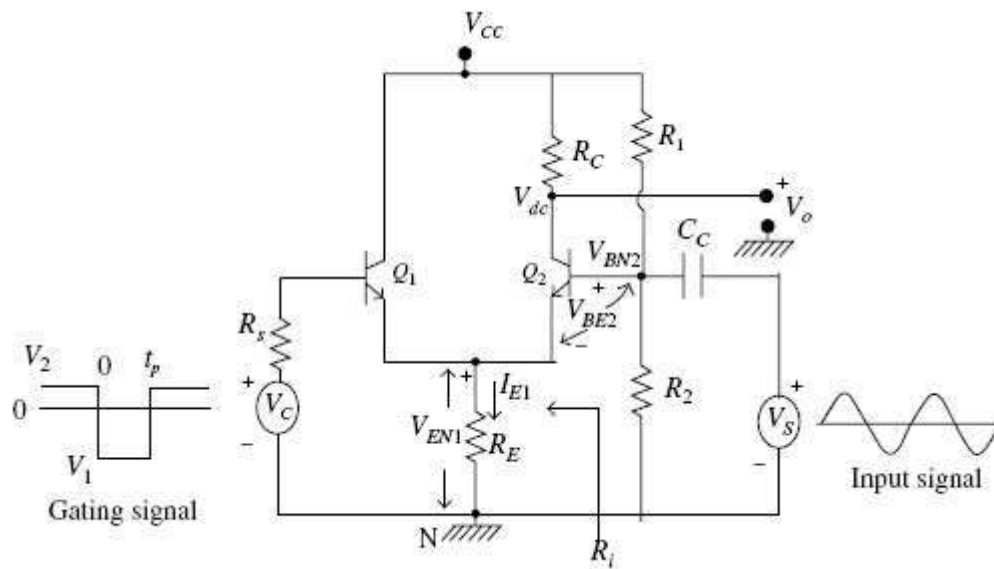

**FIGURE 11.12(a)** A bidirectional transistor gate

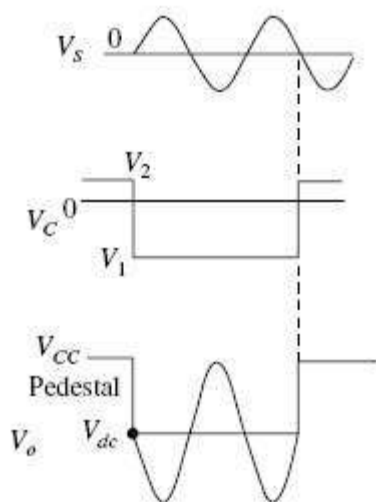


**FIGURE 11.12(b)** The waveforms

### 11.3.3 A Two-transistor Bidirectional Sampling Gate that Reduces the Pedestal


A circuit arrangement that reduces the pedestal is shown in [Fig. 11.13](#). The control signals applied to the bases of  $Q_1$  and  $Q_2$  may have the same amplitude but are of a opposite polarity. When the gating signal is connected to  $Q_1$  at  $T = 0^-$ , it is negative (at level  $V_1$ ). The net voltage at the base of  $Q_1$  is  $-(V_{BB1} + V_1)$ . Therefore,  $Q_1$  is OFF. At the same time the gating signal connected to  $Q_2$  is positive and is  $V_2$ . The net voltage at the base of  $Q_2$  is  $(V_{BB2} + V_2)$  and is positive and therefore, drives  $Q_2$  ON.  $Q_2$  draws a collector current  $I_C$ . As a result, there is a dc voltage  $V_{dc}$  at its collector and  $V_o = V_{dc}$ . However, when the gating voltage at the base of  $Q_1$  drives  $Q_1$  ON and into the active

region, at  $t = 0+$ ,  $Q_2$  goes OFF as the gating signal is . During this period when  $Q_1$  is ON, if the input signal is present, it is amplified and is available at the output, with phase inversion. The bias voltages  $V_{BB1}$  and  $V_{BB2}$  are adjusted such that the quiescent current in  $Q_1$  and  $Q_2$  when ON is the same ( $= I_C$ ) and consequently the quiescent dc voltage at the output is  $V_{dc}$ . Therefore, the dc reference level practically is  $V_{dc}$ . At the end of the time period  $t_p$ ,  $Q_1$  once again goes into the OFF state and  $Q_2$  into the ON state and the dc voltage at the output is  $V_{dc}$ . As such the pedestal can be eliminated. However, our assumption is that the gating signals are ideal pulses (with zero rise time). In this case, the instant  $Q_1$  switches ON,  $Q_2$  switches OFF, as shown in [Fig. 11.14\(a\)](#). However, in practice the gating signals may not be ideal pulses but have a finite rise time and fall time; these may then give rise to spikes in the output shown in [Fig. 11.14\(b\)](#).


Let  $V_{BE}$  be the voltage between the base and emitter terminals of a transistor when the device is in the active region. If the gating pulse is at its lower level ( , negative), the net voltage as we have seen at the base of  $Q_2$  is far below the cut-off. As a result,  $Q_2$  goes OFF at  $t = t_2$ . At the same instant,  $Q_1$  is required to go into the ON state, as the gating signal at its base is positive. However, because of the finite rise time associated with the gating signal at the base of  $Q_1$ , it may not necessarily go into the ON state at the instant  $Q_2$  has gone into the OFF state ( $t_2$ ) and may go into the ON state at  $t = t_1$ . The result is that the output is nearly  $V_{CC}$  during the interval  $t_2$  to  $t_1$ . This voltage, however, falls to  $V_{dc}$  when eventually  $Q_1$  is ON. A spike is developed at the output. Similarly, at the end of the gating signal  $Q_1$  goes OFF (at  $t = t_4$ ) before  $Q_2$  goes ON (at  $t = t_3$ ). Another spike develops at the output. It is seen that the gating signals themselves give rise to spikes in the output. If the rise time of the gating signal is large, these spikes are of larger duration as shown in [Fig. 11.14\(b\)](#), whereas if the rise time of the gating signal is small, these output spikes are of smaller duration as shown in [Fig. 11.15](#). If the rise time of the gating signal is small when compared to the duration of the gating signal, even though the spikes may occur in the output, as the duration of the signal is smaller than the spacing between the spikes, these spikes will not cause any distortion of the signal and hence, are not objectionable, as shown in [Fig. 11.15](#).

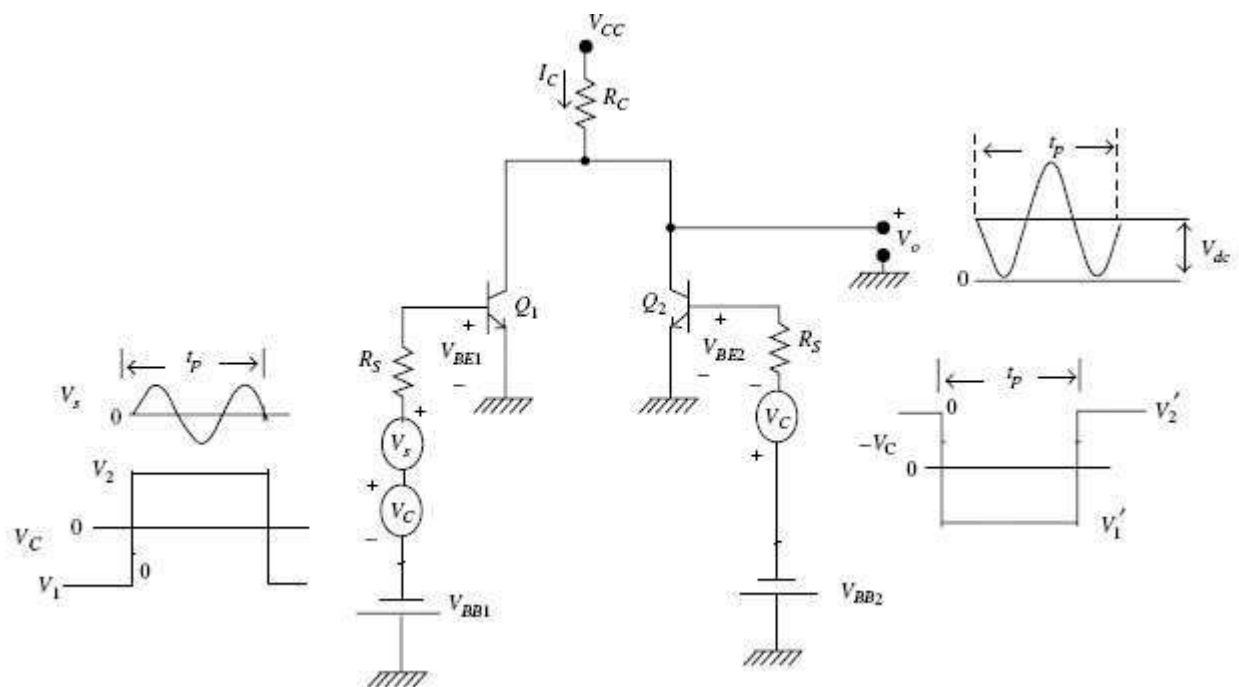

**FIGURE 11.13** Circuit that reduces the pedestal

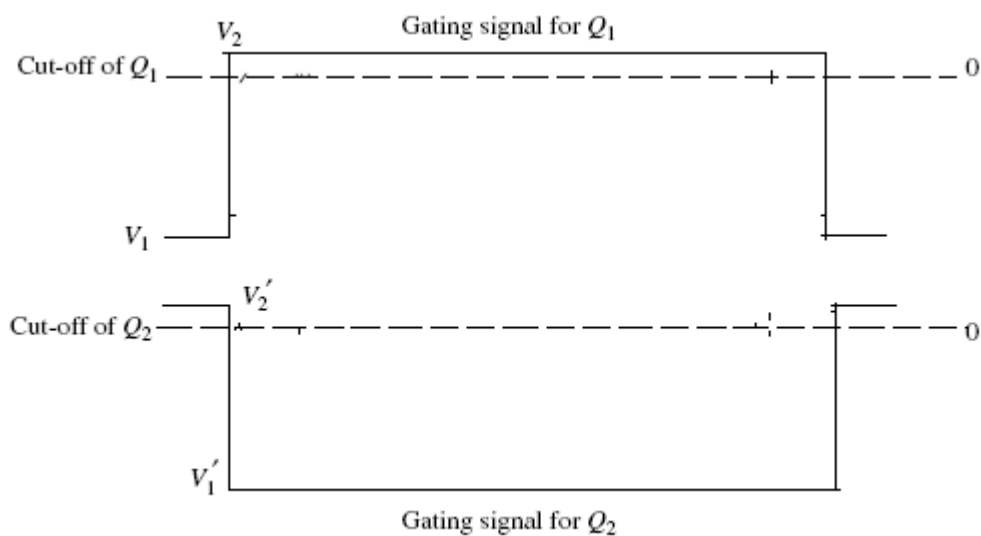

**FIGURE 11.14(a)** There are no spikes in the output when the gating signals are ideal

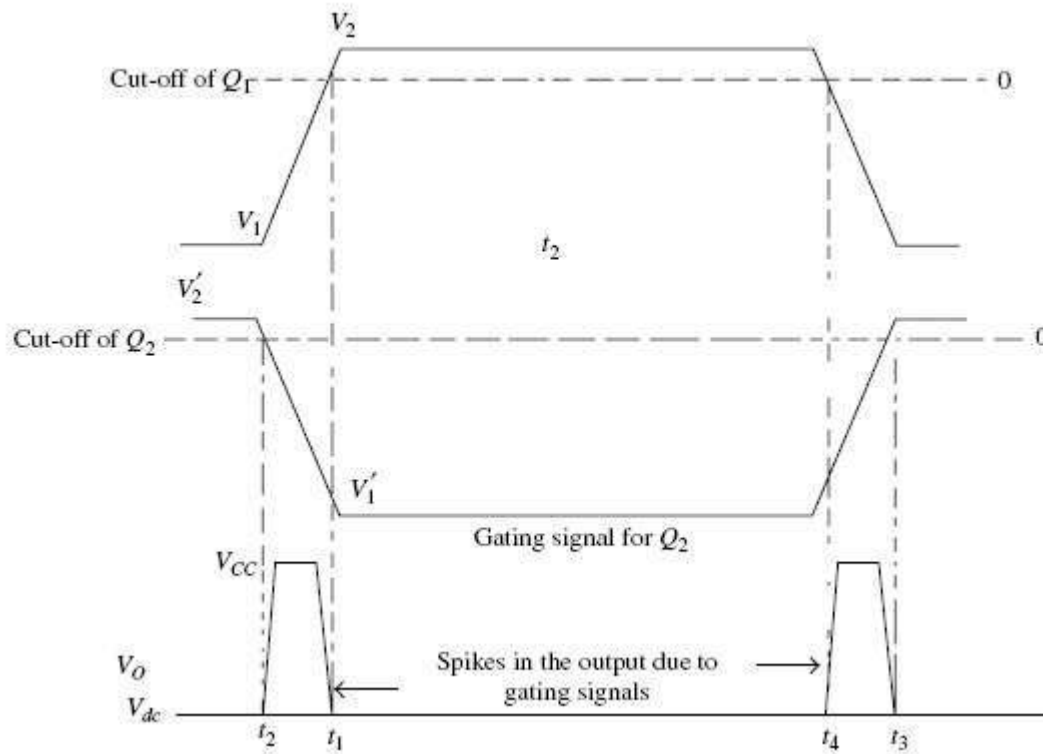


**FIGURE 11.14(b)** The spikes of a longer duration if the rise time of the gating signal is large

### A Two-diode Bridge Type Bidirectional Sampling Gate that Eliminates the Pedestal


A bidirectional diode gate that eliminates the pedestal is shown in [Fig. 11.16\(a\)](#).

$R_1$ ,  $R_2$ ,  $D_1$  and  $D_2$  form the four arms of the bridge. When the control signals are at  $V_1$ ,  $D_1$  and  $D_2$  are OFF and no input signal is transmitted to the output. However, when the control signals are at  $V_2$ , diode  $D_1$  conducts if the input ( $= V_s$ ) are positive pulses and diode  $D_2$  conducts if the input are negative pulses. Hence, these bidirectional inputs are transmitted to the output. This arrangement because of the circuit symmetry eliminates a pedestal. Consider one half of the circuit that transmits the positive pulses to the output when  $D_1$  conducts (because of symmetry), as shown in [Fig. 11.16\(b\)](#).

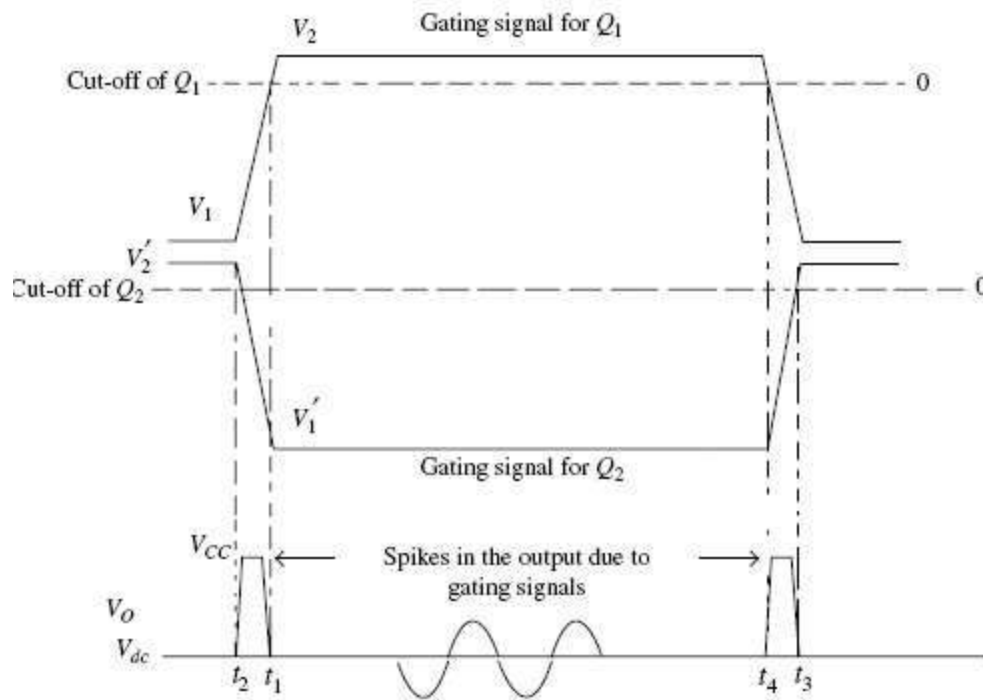


**FIGURE 11.15** The spikes of relatively smaller duration when the rise time of the gating signals is small


Thévinizing the circuit shown in [Fig. 11.16\(b\)](#) at node A, the Thévenin voltage source magnitude due to  $V_s$  (shorting  $V_C$  source, considering one source at a time) and its internal resistance are calculated using the circuit shown in [Fig. 11.16\(c\)](#).

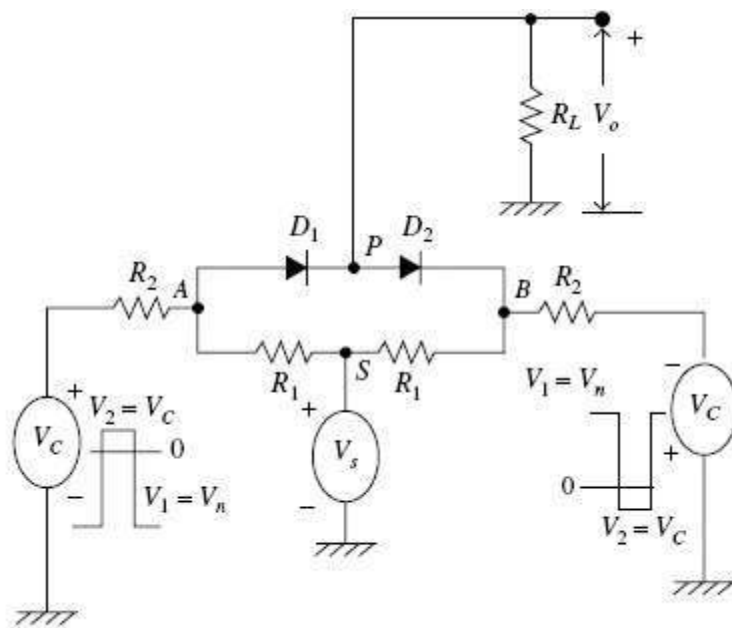


**FIGURE 11.16(a)** A bidirectional gate in the form of a bridge circuit

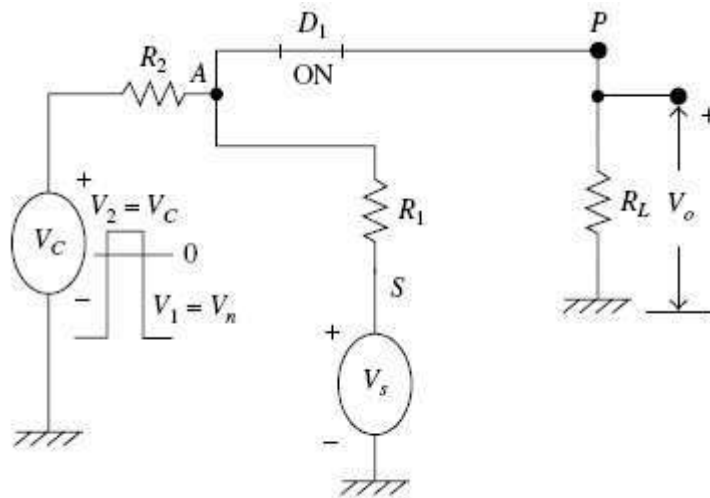

**FIGURE 11.16(b)** The circuit that transmits the positive pulses to the output

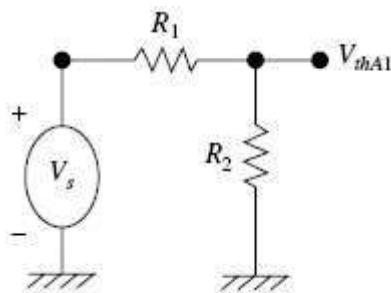

**FIGURE 11.16(c)** The equivalent circuit to calculate voltage at node A due to  $V_s$  source

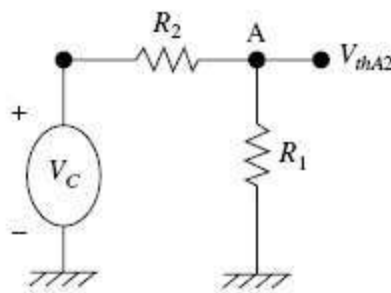

**FIGURE 11.16(d)** The equivalent circuit to calculate voltage at node A due  $V_C$  source

$$V_{thA1} = \frac{R_2}{R_1 + R_2} V_s = \alpha V_s$$

$$\text{where } \alpha = \frac{R_2}{R_1 + R_2} \quad \text{and} \quad R_{th1} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

Similarly, Thevenizing the circuit shown in [Fig. 11.16\(b\)](#) at node A, the Thévenin source due to  $V_C$  is (shorting  $V_S$ ), shown in [Fig. 11.16\(d\)](#).

$$V_{thA2} = \frac{R_1}{R_1 + R_2} V_C \quad R_{th2} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$


$$V_{thA2} = \frac{R_1}{R_1 + R_2} V_C = (1 - \frac{R_2}{R_1 + R_2}) V_C = (1 - \alpha) V_C$$

We have  $R_{th1} = R_{th2}$ .

Redrawing the circuit shown in [Fig. 11.16\(b\)](#) and replacing the diode by its linear model (a battery of value  $V_\gamma$  in series with  $R_f$ , the forward resistance of the diode), results in the circuit shown in [Fig. 11.16\(e\)](#).

Similarly, considering the circuit when a negative signal is transmitted to the output when  $D_2$  is ON and combining the equivalent circuits of the two halves, we finally have the circuit shown in [Fig. 11.16\(f\)](#).

$$R_3 = R + R_f \text{ where } R = R_{th1} = R_{th2}$$

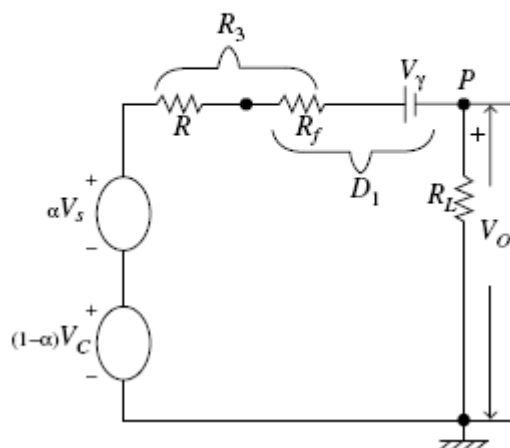

**FIGURE 11.16(e)** The equivalent circuit of the circuit shown in [Fig. 11.16\(b\)](#)

$R_f$  is the diode forward resistance


$V_\gamma$  is its cut-in voltage

We shall now define the gain of the transmission gate  $A$  (strictly speaking this is attenuation) as the ratio of  $V_o/V_s$  during transmission period. The control and small diode voltages do not contribute to any current in  $R_L$ , the resultant simplified circuit is shown in [Fig. 11.16\(g\)](#). The open circuit voltage between  $P$  and the ground is  $\alpha V_s$  and the Thévenin resistance is  $R_3/2$ , as shown in [Fig. 11.16\(h\)](#).

$$V_o = \alpha V_s \frac{R_L}{R_L + \frac{R_3}{2}} \quad A = \frac{V_o}{V_s} = \alpha \frac{R_L}{R_L + \frac{R_3}{2}}$$

But

$$\alpha = \frac{R_2}{R_1 + R_2}$$

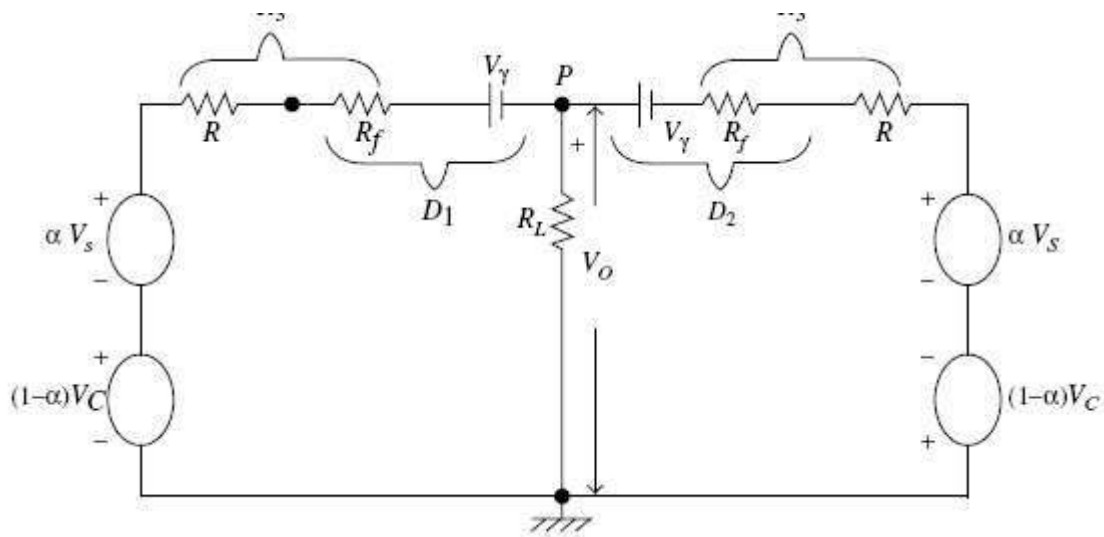


**FIGURE 11.16(f)** The equivalent circuit of [Fig. 11.16\(a\)](#)


$R_f$  is the diode forward resistance

$V_\gamma$  is its cut-in voltage



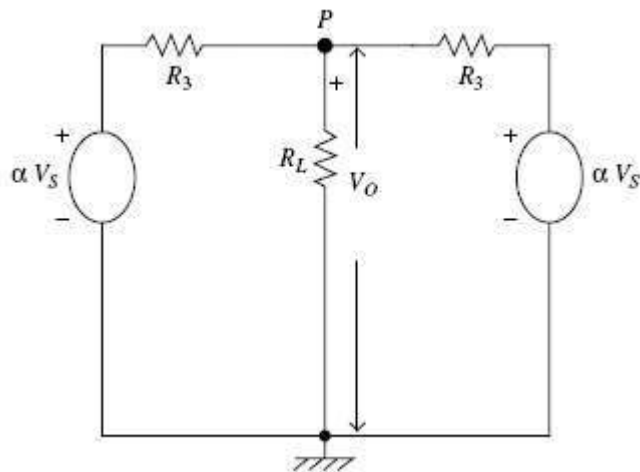

**FIGURE 11.16(g)** The simplified circuit of Fig. 11.16(f)

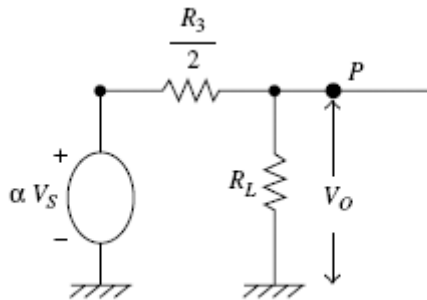

**FIGURE 11.16(h)** The circuit that enables the calculation of gain  $A$

Therefore,


$$A = \frac{R_2}{R_1 + R_2} \times \frac{R_L}{R_L + \frac{R_3}{2}} \quad (11.1)$$

**a) Minimum control voltage  $V_c(\text{min})$  required to keep both the**


**diodes  $D_1$  and  $D_2$  ON:** Let only the gating signals be present. The amplitude and polarity of the gating signals are such that both the diodes  $D_1$  and  $D_2$  conduct, and equal currents flow in these two diodes. When these equal and opposite currents flow in  $R_L$ , the net voltage drop is zero and there is no pedestal.

Let  $V_s$  be a positive signal. As the amplitude of the signal goes on increasing, the current in  $D_1$  goes on increasing and that in  $D_2$  goes on decreasing. As  $V_s$  increases further, the current in  $D_2$  becomes zero (i.e.,  $D_2$  is OFF). Thus, there is a minimum control voltage  $V_c$  that will keep both the diodes

ON. To calculate this  $V_{C(\min)}$ , let it be assumed that  $D_2$  has just stopped conducting i.e., the diode current has become zero; the drop across  $R_3$  is zero. Therefore, the output voltage across  $R_L$  is the open circuit voltage, as shown in Fig. 11.17(a).

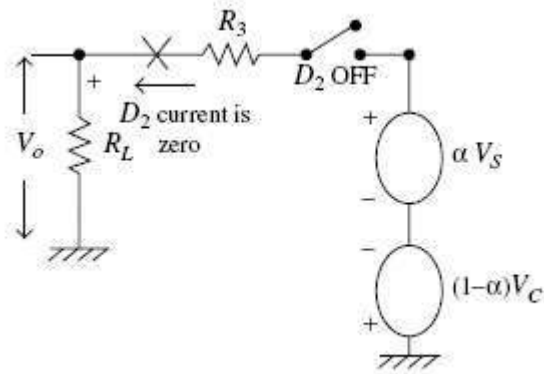

**FIGURE 11.17(a)** The voltage  $V_o$  when  $D_2$  is OFF

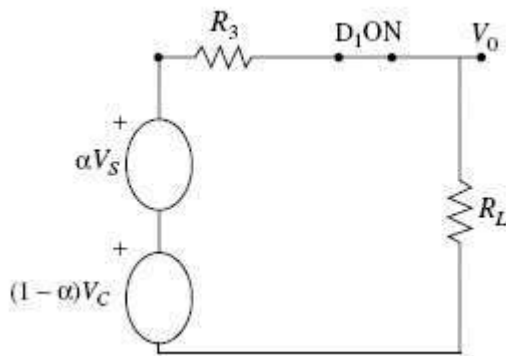

**FIGURE 11.17(b)** The voltage  $V_o$  when  $D_1$  is ON

Now, calculating the output due to the left hand side signal source  $V_s$  and control signal  $(1 - \alpha)V_c$ , with the assumption that  $V_y \ll V_s$  (i.e.,  $V_r \approx 0$ ), as shown Fig. 11.17(b).

$$V_o = [\alpha V_s + (1 - \alpha)V_c] \frac{R_L}{R_L + R_3} \quad (11.3)$$

Eqs. (11.2) and (11.3) represent  $V_o$  hence,

$$[\alpha V_s + (1 - \alpha)V_C] \frac{R_L}{R_L + R_3} = \alpha V_s - (1 - \alpha)V_C$$

$$\alpha V_s \left(1 - \frac{R_L}{R_L + R_3}\right) = (1 - \alpha)V_C \left(\frac{R_L}{R_L + R_3} + 1\right) \quad \alpha V_s \left(\frac{R_3}{R_L + R_3}\right) = (1 - \alpha)V_C \left(\frac{R_3 + 2R_L}{R_L + R_3}\right)$$

$$\alpha V_s R_3 = (1 - \alpha)V_C(R_3 + 2R_L)$$


$$\alpha = \frac{R_2}{R_1 + R_2} \text{ and } 1 - \alpha = 1 - \frac{R_2}{R_1 + R_2} = \frac{R_1}{R_1 + R_2}$$

$$\frac{R_2 R_3}{R_1 + R_2} V_s = \frac{R_1}{R_1 + R_2} (R_3 + 2R_L) V_C$$


$$V_{C(\min)} = \frac{R_2}{R_1} \times \frac{R_3}{R_3 + 2R_L} V_s \quad (11.4)$$

$V_{C(\min)}$  decreases with increasing  $R_L$ .

b) **Minimum control voltage  $V_n(\min)$  to ensure that  $D_1$  and  $D_2$  are reverse-biased:** We have calculated the minimum control voltage  $V_{C(\min)}$  i.e., needed to keep both the diodes,  $D_1$  and  $D_2$  ON. Similarly we calculate the minimum control voltage  $V_{n(\min)}$  i.e., required to keep  $D_1$  and  $D_2$  OFF when no transmission takes place. If both the diodes are reverse-biased, the output voltage at point  $P$  is zero and  $P$  is at the ground potential, shown in [Fig. 11.18\(a\)](#). As  $D_1$  is reverse-biased, it behaves as an open circuit. As a result, the input appears at the output.

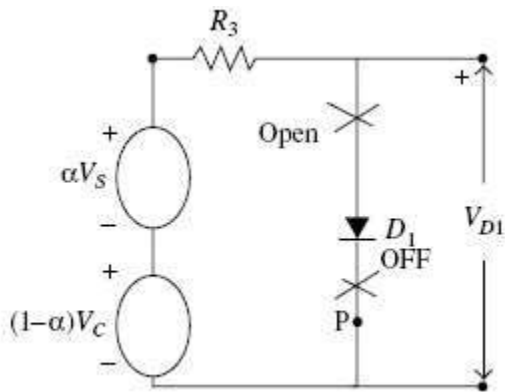

**FIGURE 11.18(a)** The gate circuit when  $D_1$  and  $D_2$  are reverse-biased

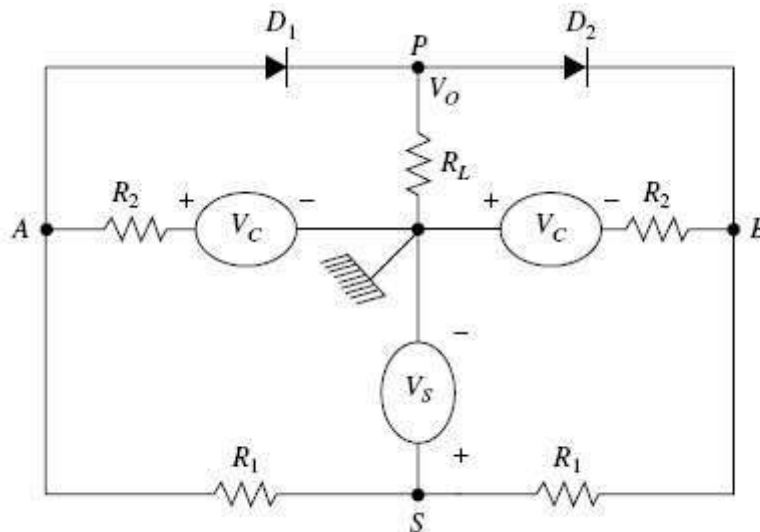

**FIGURE 11.19(a)** The bidirectional gate redrawn in the form of a bridge

$$V_{D1} = \text{Voltage across } D_1 = [\alpha V_s + (1 - \alpha) V_c]$$

If  $V_n$  is the magnitude of  $V_c$  at the lower level,

$$V_{D1} = [\alpha V_s + (1 - \alpha) V_n]$$

For  $D_1$  to be OFF,  $V_{D1}$  must be either zero or negative. If  $V_{D1}$  is zero,

$$[\alpha V_s + (1 - \alpha) V_n] = 0 \quad V_n = V_{n(\min)} = \frac{-\alpha V_s}{1 - \alpha} \quad \frac{\alpha}{1 - \alpha} = \frac{R_2}{R_1}$$

Therefore,

$$V_{n(\min)} = \frac{-R_2}{R_1} V_s \quad (11.5)$$

In practice  $V_{C(\min)}$  and  $V_{n(\min)}$  are larger by 25 per cent. The bidirectional diode gate shown in Fig. 11.16(a) is redrawn as shown in Fig. 11.19(a). If the two control voltages are equal in magnitude but opposite in polarity the pedestal is not present in the output.


c) **Input resistance:** The purpose of the control signal is to enable the gate and the current drawn from the signal source does not depend on the control voltage. This current depends on the state of the diodes, whether they are ON or OFF. Here we assume that  $D_1$  and  $D_2$  as ideal diodes.

When the diodes  $D_1$  and  $D_2$  are OFF from Fig. 11.19(a) the equivalent circuit is as shown in Fig. 11.19(b) (obtained by open circuiting the diodes  $D_1$  and  $D_2$  and short circuiting  $V_C$  sources). The input resistance is calculated using the circuit shown in Fig. 11.19(b).


(i) When  $D_1$  and  $D_2$  are OFF

$$R_i = (R_1 + R_2) || (R_1 + R_2) \quad (11.6)$$


$$R_i = \frac{(R_1 + R_2)}{2}$$

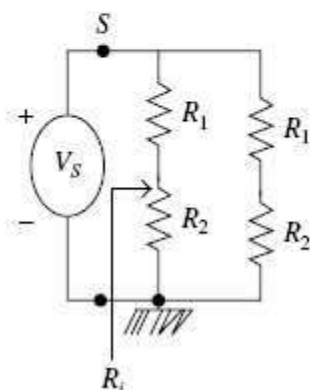

**FIGURE 11.19(b)** The circuit of Fig. 11.19(a) when  $D_1$  and  $D_2$  are OFF

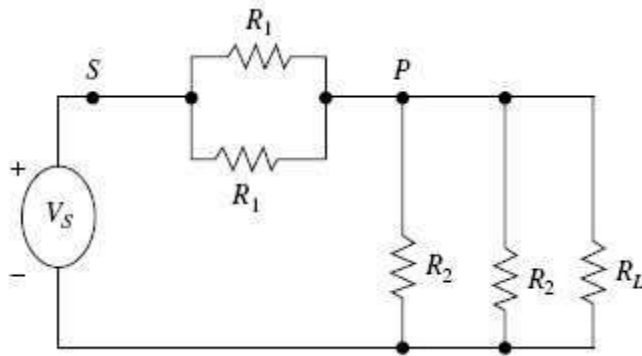

**FIGURE 11.19(c)** The circuit of Fig. 11.19(a) when  $D_1$  and  $D_2$  are ON

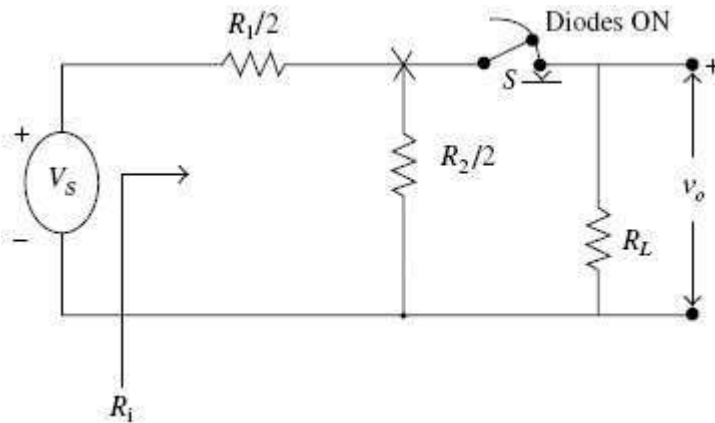

**FIGURE 11.19(d)** The simplified circuit of Fig. 11.19(c)

When the diodes are ON, the equivalent circuit is as shown in Fig. 11.19(c). The circuit of Fig. 11.19(c) after simplification is redrawn as shown in Fig. 11.19(d).

From the circuit in Fig. 11.19(d), input resistance  $R_i$  when the diodes are conducting is,


$$R_i = \frac{R_1}{2} + \frac{\frac{R_2}{2} R_L}{\frac{R_2}{2} + R_L}$$

$$R_i^1 = \frac{R_1}{2} + \frac{R_2 R_L}{R_2 + 2R_L} \quad (11.7)$$

Now to calculate the gain of the transmission gate,  $A$ , let us calculate the Thévenin voltage source magnitude and its internal resistance. The circuit in [Fig. 11.19\(d\)](#) now reduces to that shown in [Fig. 11.19\(e\)](#).

$$V_{th} = V_s \times \frac{\frac{R_2}{2}}{\frac{R_1}{2} + \frac{R_2}{2}} = V_s \times \frac{R_2}{(R_1 + R_2)} = \alpha V_s$$

$$R_{th} = \frac{R_1}{2} \parallel \frac{R_2}{2} = \frac{R_1 R_2}{2(R_1 + R_2)} = \alpha \frac{R_1}{2}$$

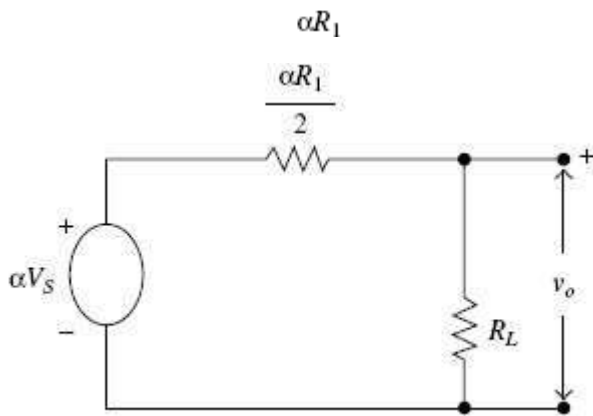

**FIGURE 11.19(e)** The simplified circuit of [Fig. 11.19\(d\)](#)


$$V_o = \frac{\alpha V_s R_L}{R_L + \alpha \frac{R_1}{2}}$$

$$A = \frac{V_o}{V_s} = \frac{\alpha R_L}{R_L + \alpha \frac{R_1}{2}} = \frac{\alpha}{1 + \alpha \frac{R_1}{2R_L}} \quad (11.8)$$

[Eq. \(11.8\)](#) gives the expression for the transmission gain.

### Four-diode Gates

The main disadvantages with two-diode gates are (i) although  $A$  is called the gain, the circuit actually offers a large attenuation to the signal since  $A$  is small (much less than 1); (ii) the two control voltages  $V_C$  and  $-V_C$  should be equal in magnitude and opposite in polarity, failing which, there could be a pedestal in the output and (iii)  $V_{n(\min)}$  can be appreciably large, as seen in [Example 11.1](#). These limitations can be overcome in a four diode gate shown in [Fig. 11.20\(a\)](#). The differences seen in the four diode gate as compared to a two diode gate shown in [Fig. 11.16\(a\)](#) are (i) instead of connecting control signals at points A and B, sources  $+V$  and  $-V$  are connected at these points and (ii) the control signals are connected through the two additional diodes  $D_3$  and  $D_4$  to points  $P_1$  and  $P_2$ .

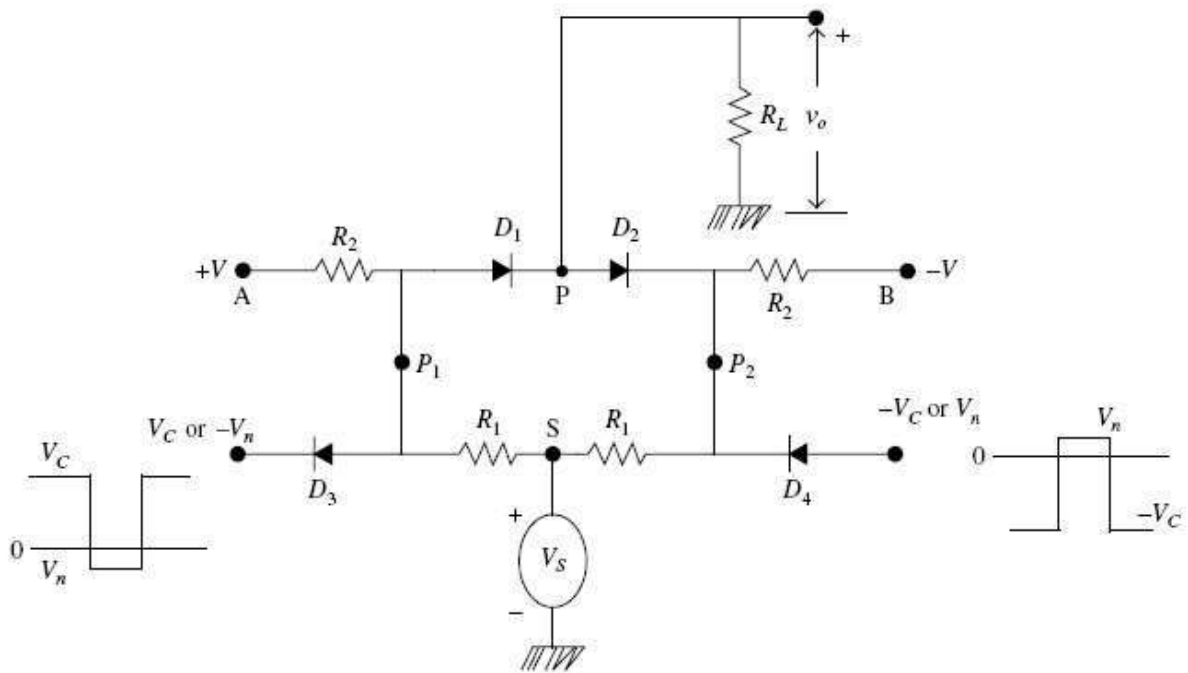

**FIGURE 11.20(a)** A four-diode gate

When the control voltages are  $V_C$  and  $-V_C$ ,  $D_3$  and  $D_4$  are reverse-biased and are OFF. However,  $D_1$  and  $D_2$  are ON because of  $+V$  and  $-V$ . The signal is connected to the load through  $R_1$  and the conducting diodes, as shown in [Fig. 11.20\(b\)](#).

When the signal is transmitted, as  $D_3$  and  $D_4$  are OFF, even if there is a slight imbalance in the two control voltages  $+V_C$  and  $-V_C$ , there is no pedestal at the output. Alternately, if the control voltages are at  $-V_n$  and  $V_n$  respectively,  $D_3$  and  $D_4$  conduct. As a result,  $D_1$  and  $D_2$  are OFF and now the output is zero. When  $D_3$  and  $D_4$  are OFF, the circuit is similar to a two diode gate and  $A$  is the



same as given in Eq. (11.1) except for the fact that  $V_C$  and  $-V_C$  are replaced by  $V$  and  $-V$ . Also, the minimum value of voltage  $V_{(\min)}$  is the same as  $V_{C(\min)}$  in Eq. (11.4).

Therefore,

$$V_{\min} = \frac{R_2}{R_1} \times \frac{R_3}{R_3 + 2R_L} \times V_s \quad (11.9)$$


Let us now compute  $V_{C(\min)}$ . If  $R_f \ll R_L$ , for a positive  $V_s$  the voltage at  $P_1$  is  $AV_s$ . If  $D_3$  is to be OFF,  $V_C$  must at least be equal to  $AV_s$ .

$$\text{ie., } V_{C(\min)} \approx AV_s \quad (11.10)$$


$V_{n(\min)}$  is calculated to satisfy the condition that  $D_2$  is OFF and  $D_4$  is ON. Then we calculate the voltage at the cathode of  $D_4$  ( $K_2$ ) due to sources  $-V$  and  $V_s$  using the superposition theorem, as shown in Fig. 11.20(c). The minimum voltage  $V_{n(\min)}$  should at least be equal to  $V_{K_2}$ .

Therefore,

$$V_{n(\min)} = V_s \times \frac{R_2}{R_1 + R_2} - V \times \frac{R_1}{R_1 + R_2} \quad (11.11)$$

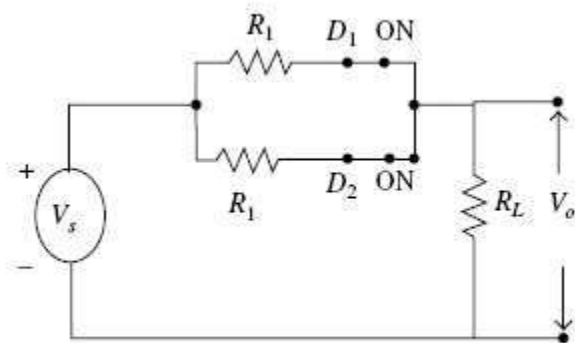

**FIGURE 11.20(b)** The circuit of Fig. 11.20(a) when  $D_1$  and  $D_2$  are ON and  $D_3$  and  $D_4$  are OFF

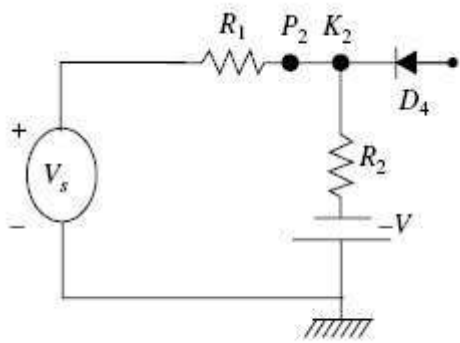

**FIGURE 11.20(c)** The circuit to calculate the voltage at the cathode of  $D_4$

### Six-diode Gates

For the four-diode gate shown in [Fig. 11.20\(a\)](#), the voltages  $+V$  and  $-V$  need to be large and have to be balanced to avoid pedestal. This gate circuit is insensitive to slight variations in the control voltages. Also, for the four diode gate [see [Fig. 11.21\(a\)](#)], the control voltages tend to become large and further there is a need for balanced control voltages, which is difficult. However, in the former case it is easy to choose large desired values for  $+V$  and  $-V$  and also easy to balance these two voltages as these are dc sources. For the circuit shown in [Fig. 11.21\(a\)](#),  $R_L$  is connected through a parallel path with the result the current is shared by these two parallel branches. The transmission gain  $A$  in both the cases, however, is approximately unity. A six diode gate is shown in [Fig. 11.22](#), and it combines the features of the gate circuits shown in [Figs. 11.20\(a\)](#) and [11.21\(a\)](#).

When no signal is transmitted,  $D_5$  and  $D_6$  conduct while  $D_1$  to  $D_4$  remain OFF. During the transmission,  $D_5$  and  $D_6$  are OFF and this six diode gate is equivalent to the four diode gate seen in [Fig. 11.21\(a\)](#), earlier. If the diodes  $D_5$  and  $D_6$  remain OFF for the signal amplitude  $V_s$ , then,


$$V_{C(\min)} = V_s \quad (11.18)$$

The minimum required value of  $V_n$  is  $V_{n(\min)}$  and is equal to  $V_s$  since the transmission diodes  $D_1$  to  $D_4$  will not conduct unless  $V_s$  exceeds  $V_n$ .

Hence,

$$V_{n(\min)} = V_s \quad (11.19)$$

The expression for  $A$  is given by Eq. (11.16).

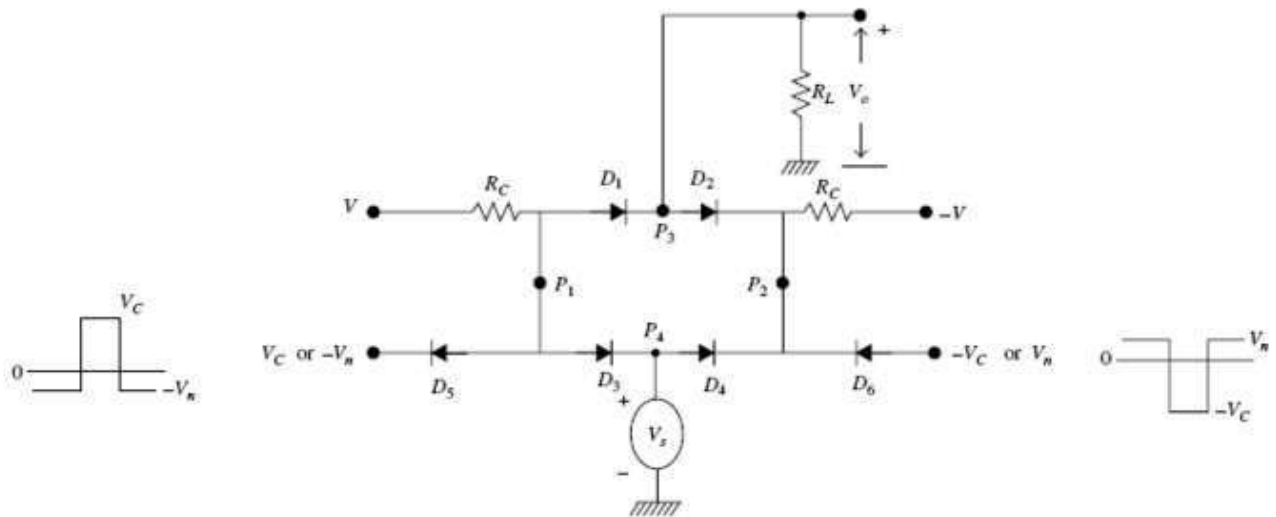


**FIGURE 11.22** A six-diode gate

## APPLICATIONS OF SAMPLING GATES

Sampling gates find applications in many circuits. Sampling gates are used in multiplexers, D/A converters, chopper stabilized amplifiers, sampling scopes, etc. Here, the three specific applications of the sampling gates in: chopper stabilized amplifier; sampling scope and time division multiplexer are discussed.

### Chopper Stabilized Amplifiers

Sometimes it becomes necessary to amplify a signal  $v$  that has a very small  $dv/dt$  and that the amplitude of the signal itself is very small, typically of the order of milli-volts. Neither, ac amplifiers using large coupling condensers nor dc amplifiers with the associated drift would be useful for such an application. A chopper stabilized amplifier employing sampling gates can be a useful option in such an application, as shown in Fig. 11.27(a).

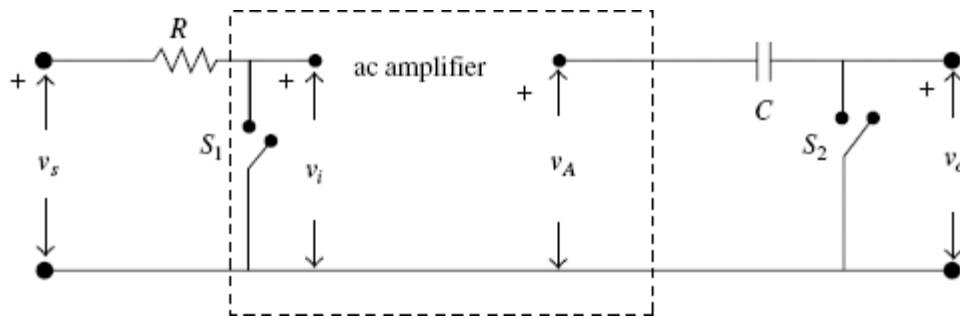

**FIGURE 11.27(a)** A chopper stabilized amplifier


Let the input  $v_s$  to the amplifier be a slowly varying sinusoidal signal. Switch  $S_1$  and  $S_2$  open and close synchronously at a fast rate i.e., the switching frequency is significantly larger than the signal frequency. When  $S_1$  is open,  $v_i$  is the same as  $v_s$ . When  $S_1$  is closed,  $v_i = 0$ . As the switching frequency is large, the samples are taken at smaller time intervals. With the result, the signal  $v_i$  contains pulses with almost flat tops and have the same amplitude of the input signal as is available at the instant of sampling. As a result, the input of the amplifier  $v_i$  is a chopped signal— $R$  and  $S_1$  constitute the chopper. Hence,  $v_i$  can be described as a square wave at the switching frequency (if  $dv/dt$  is small), i.e., amplitude modulated by the input signal and superimposed on a signal (dashed line) that is proportional to  $v_s$ . The waveform  $v_A$  at the amplifier output is an amplitude modulated square wave, as shown in [Fig. 11.27\(b\)](#). Hence, a chopper is also called a modulator.

Let  $S_1$  and  $S_2$  operate in synchronism. During  $t = T_1$ , the negative going component of  $v_A$  is zero and during  $t = T_2$  the positive going component is zero. Also, because of the amplifier,  $v_o$  is greater than  $v_i$  in amplitude. Except for this change,  $v_A$  is similar to  $v_i$ , as shown in [Fig. 11.27\(c\)](#). This signal is passed through a low pass filter which eliminates the squarewave and retrieves the original signal. If  $S_2$  opens when  $S_1$  is closed, the output is shifted in phase by  $180^\circ$ , as shown in [Fig. 11.27\(d\)](#).  $C$  and  $S_2$  constitute a synchronous detector. The chopper eliminates the need for a dc stabilized amplifier. This amplifier is called a chopper stabilized amplifier.


### Sampling Scopes

Another application of a sampling gate is in a sampling scope used to display very fast periodic waveforms, having a rise time of the order of nano-seconds. A general purpose CRO may be used for displaying such waveforms. However, a CRO needs a wideband amplifier. A sampling scope eliminates the use of the high gain wideband amplifier. The basic principle of

a sampling scope is explained with the aid of a block diagram shown in Fig. 11.28(a) and the waveforms are shown in Fig. 11.28(b).

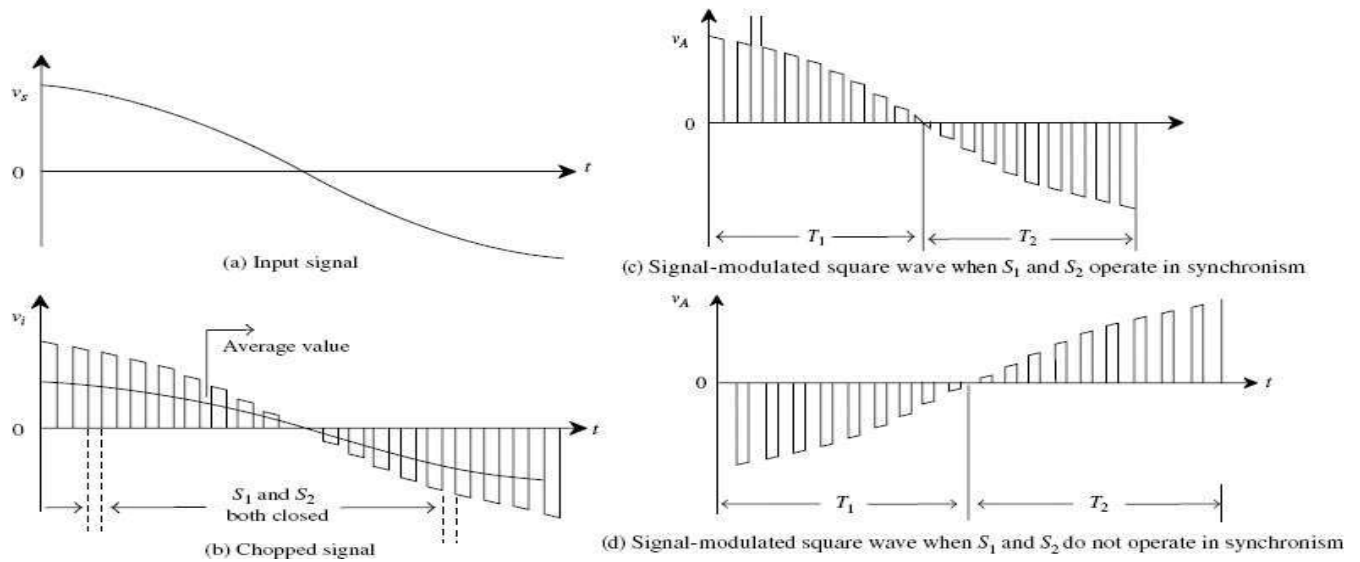

**FIGURE 11.27(b)** The waveforms of the chopper stabilized amplifier

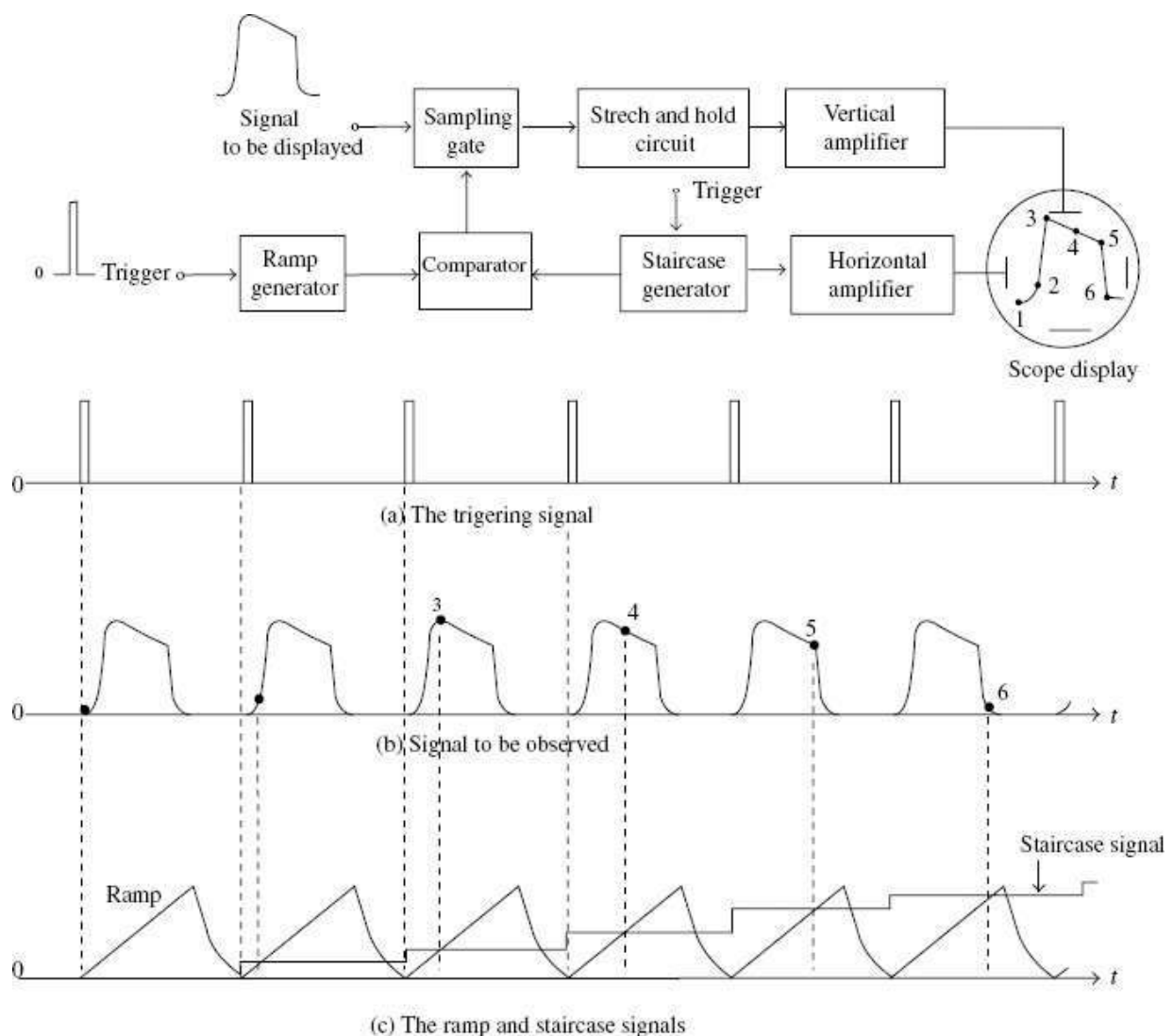


**FIGURE 11.28(a)** The waveforms that explain the principle of sampling-scope

Let the trigger signals shown in [Fig. 11.28\(a\)](#) occur slightly prior to the occurrence of the pulses that are to be displayed on the screen. These trigger signals trigger ramp and staircase generators. The staircase generator has constant amplitude between the triggers and its amplitude jumps to a higher level at the instant the trigger is present. The amplitude of the staircase generator remains the same till the presence of the next trigger. The inputs to the comparator are the staircase and ramp signals. The instant the ramp reaches the amplitude of the staircase signal; a pulse is produced at the output of the comparator. This pulsed output of the comparator is used as the control signal for the sampling gate. When a control signal is present, the gate transmits a sample of the signal to the vertical amplifier whose amplitude is the same as that of the signal at the instant of sampling and has the same duration as the control signal. Points 1, 2..., 6 are the instants at which the samples are taken. The output of the staircase generator is connected to the horizontal deflecting plates.


When one sample is taken, say at instant 1, to go to the next sample, i.e., sample 2, the amplitude of sample 1 should be held constant till the next trigger pulse arrives. Therefore, it becomes necessary to hold the amplitude of the input signal between successive triggers and hence, the need for a stretch and hold circuit. The staircase generator moves the spot horizontally across the screen in steps and at each step the spot is deflected vertically proportional to the signal amplitude. The CRT beam is blanked normally and is un-blanked only at the time of display of the sample. Thus, the signal is represented by a series of dots.

### Multiplexers

An analog time division multiplexer using a sampling gate is shown in [Fig. 11.29\(a\)](#). In the FET  $Q_1$ ,  $Q_2$  and  $Q_3$  are ON when the control voltages  $V_{C1}$ ,  $V_{C2}$  and  $V_{C3}$  are at 0 V. The voltage  $V$  is more negative than the pinch off voltage of the FET. As such the FET is OFF when the gate voltage is  $V$ . During the period 0 to  $T_1$ ,  $V_{C1}$  is such that  $Q_1$  is ON. At the same time  $Q_2$  and  $Q_3$  are OFF. Hence, input  $V_{s1}$ , which is the sinusoidal signal is present at the output during this period. During the period  $T_1$  to  $T_2$ ,  $Q_2$  is ON and  $Q_1$  and  $Q_3$  are OFF. Hence, only  $V_{s2}$  is present at the output during this period. During the period  $T_2$  to  $T_3$ ,  $Q_3$  is only ON and hence,  $V_{s3}$  is present at the output. The output now contains all the input signals separated by a specific time interval, as shown in [Fig. 11.29\(b\)](#).

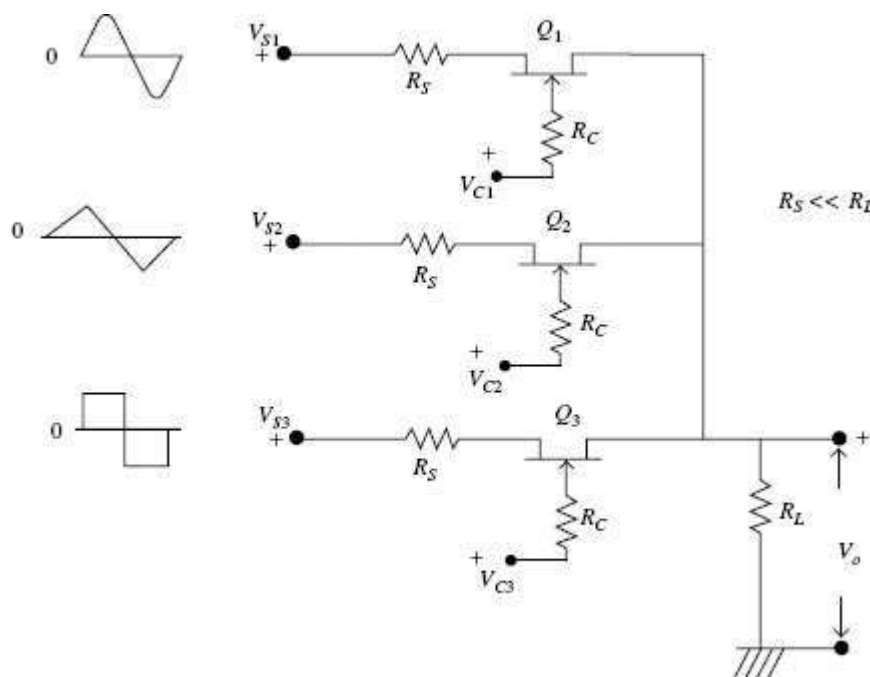

**FIGURE 11.29(a)** The sampling gate used for time division multiplexing

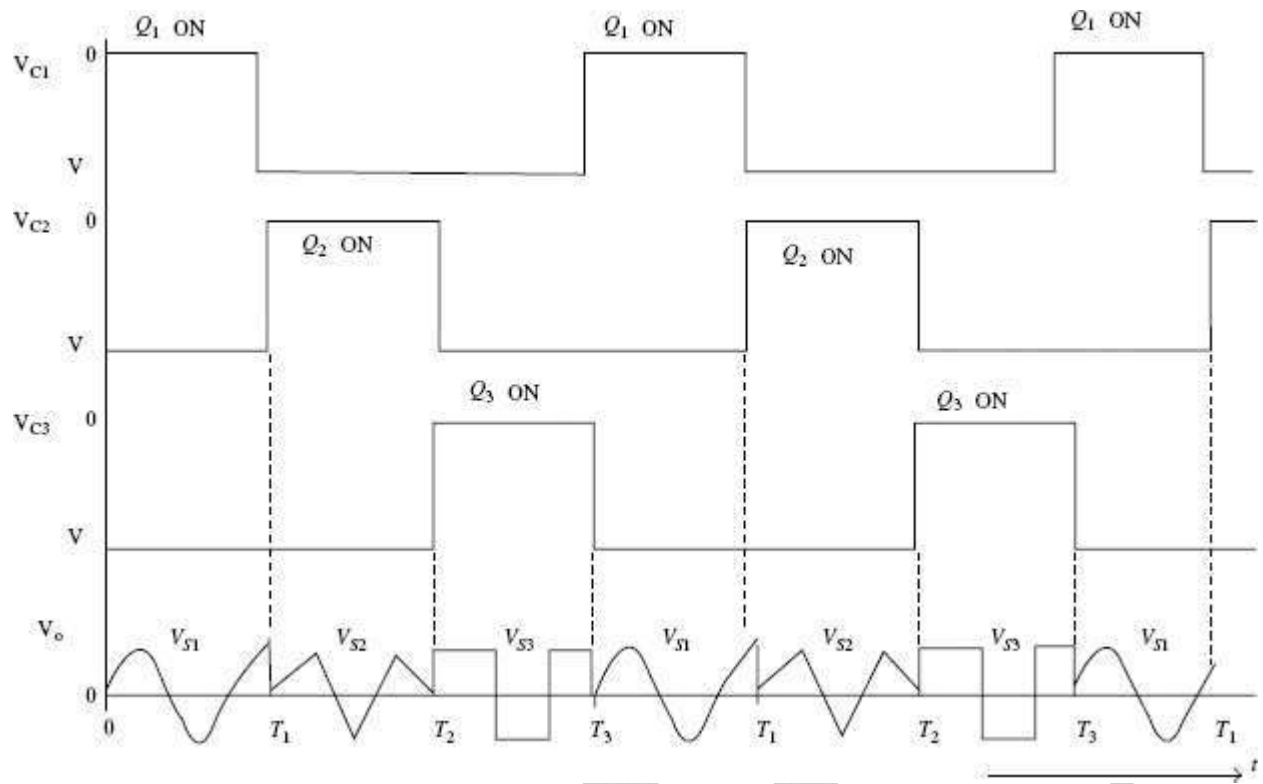

**FIGURE 11.29(b)** The control signals and the output of the multiplexer