

B.Tech I Year II Semester (R15) Regular & Supplementary Examinations May 2018

NETWORK ANALYSIS

(Common to ECE & EIE)

Time: 3 hours

Max. Marks: 70


PART - A
(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
 - (a) Give the properties of Miller and Tellegen's theorem.
 - (b) Define time constant of RL circuit.
 - (c) Define tree and co-tree.
 - (d) Explain maximum power transfer theorem.
 - (e) Write the limitations of super position theorem.
 - (f) Define quality factor and sensitivity of a series RLC circuit.
 - (g) What are the advantages of state variable analysis?
 - (h) What do you mean by external critical frequency?
 - (i) Define Neper.
 - (j) Write the applications of different types of filter.

PART - B
(Answer all five units, 5 X 10 = 50 Marks)


UNIT - I

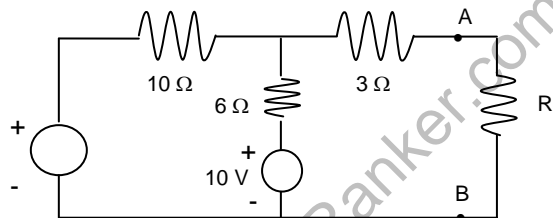- 2 Obtain the Thevenin's equivalent of the network shown in figure below. Then draw the Norton's equivalent network by source transformation.




OR

- 3 Find V and I using mesh analysis.

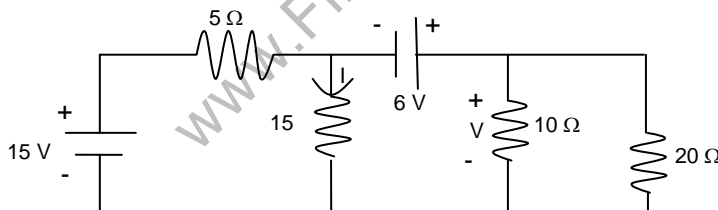

UNIT - II

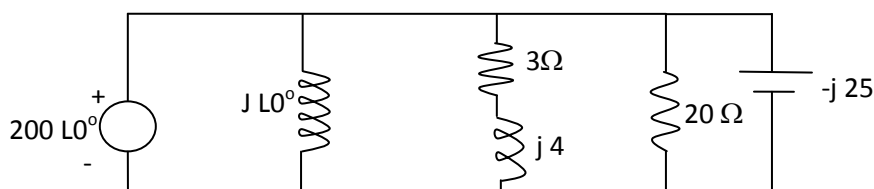- 4 A series RLC circuit with $R = 300 \text{ ohms}$, $L = 1\text{H}$ and $C = 100\mu\text{F}$ has a constant voltage of 50 V applied to it at $t = 0$. Find the maximum current value. Assume zero initial conditions.
- OR**
- 5 Obtain the total current, branch currents and the power consumed by each branch. Draw the phasor diagram for the network shown in figure given below.




Contd. in page 2

Code: 15A04201

R15

UNIT - III

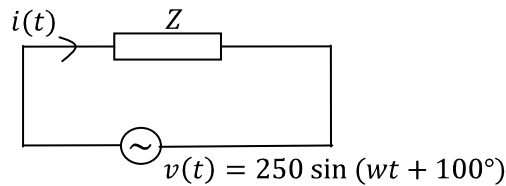- 6 For the circuit shown in the figure below, a voltage $v(t)$ is applied and the resulting current in the circuit $i(t) = 15 \sin(\omega t + 30^\circ)$ A. Determine the active power, reactive power, power factor and the apparent power.



OR

- 7 (a) What is the relation between bandwidth and resonant frequency?
(b) An inductance of 0.5H a resistance of 5Ω and a capacitance of $8 \mu\text{F}$ are in series across a 220 V AC supply. Calculate the frequency at which the circuit resonates. Find the current at resonance bandwidth, half power frequencies and the voltage across capacitance of resonance.

UNIT - IV


- 8 (a) Define self-inductance of a coil, mutual inductance between two coils and coefficient of coupling.
(b) Define the relation between self, mutual inductance and coefficient of coupling.

OR

- 9 (a) Distinguish between reactance, impedance, admittance and susceptance.
(b) Explain image parameters in two port network.

UNIT - V

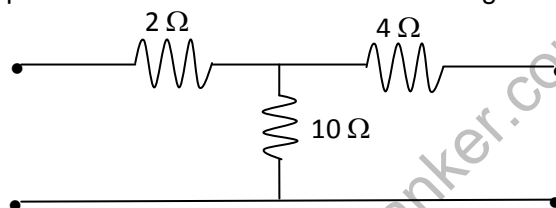- 10 Find the h-parameters for the network shown in figure below.



OR

- 11 Design a constant-K low pass filter, both T and π sections having a cut-off frequency of 2 kHz to operate with a terminated load resistance of 500Ω
