

B.Tech II Year II Semester (R15) Supplementary Examinations December 2018

ELECTRONIC CIRCUIT ANALYSIS

(Common to ECE and EIE)

Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- (a) An amplifier with open loop gain $A_v = 1000 \pm 100$ is available. It is necessary to have an amplifier whose voltage gain values by no more than ± 0.1 percent. Determine the reverse transmission factor (β) of the feedback network used.
 - (b) What is the condition required for sinusoidal oscillations to be sustained. Also write the expression for frequency of oscillations in RC phase shift oscillator.
 - (c) A modern bipolar transistor can have $C_e = 1\text{pF}$. If $g_m = 50\text{ mA/V}$. Determine (f_T) for a common emitter amplifier.
 - (d) What is the relationship between (f_β) and (f_T)?
 - (e) Distinguish between cascade and cascode amplifiers.
 - (f) Explain the effect of bypass capacitor in multistage amplifier.
 - (g) The expression for the efficiency of class B push-pull amplifier is _____ and max efficiency is _____.
 - (h) Write the expression for total harmonic distortion of an amplifier.
 - (i) Define stability of tuned amplifier with relevant expression.
 - (j) What is the effect of Bandwidth in an multistage amplifier?

PART – B

(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- 2 (a) Explain the concept of feedback amplifier using block diagram.
- (b) An amplifier without feedback given a fundamental output of 36 V with 7 percent (7%) second harmonic distortion when the input is 0.028 V. If 1.2% of the output is fed back into the input in a negative voltage series feedback circuit, what is the output voltage?

OR

- 3 (a) Derive an expression for oscillating frequency of Wein bridge oscillator and illustrate its operation.
- (b) A crystal has the following parameters $L = 0.33\text{ H}$, $C = 0.065\text{ pF}$, $C' = 1.0\text{ pF}$ and $R = 5.5\text{ k}\Omega$.
- (i) Find the series resonant frequency.
 - (ii) By what percent does the parallel resonant frequency exceed the series resonant frequency?

UNIT – II

- 4 (a) With the help of hybrid models determine the following high frequency parameters internal of low frequency parameters: (i) Transistor transconductance.
(ii) Input conductance.
(iii) Feedback conductance.
- (b) The following transistor measurements made at room temperature:
 $I_C = 5\text{ mA}$, $V_{CE} = 10\text{ V}$, $h_{fe} = 100$, $h_{ie} = 600\text{ }\Omega$, $C_e = 3\text{ pF}$, $[A_{ie}] = 10$ at 10 MHz. find f_β and f_T .

OR

- 5 Derive an expression for voltage gain, input and output impedances of common drain FET amplifier.

UNIT – III

- 6 Illustrate the concept of Boot-strap emitter follower with expressions.

OR

- 7 Describe the two-stage FET amplifier with neat circuit diagram and relevant expression.

Contd. in page 2

UNIT – IV

- 8 Explain the operation of class-B amplifier with circuit diagram and also derive an expression for maximum efficiency of push-pull class B amplifier.

OR

- 9 (a) Describe the operation of complementary symmetry push-pull amplifier.
(b) A transistor supplies 0.85 W to a 4K-load. The zero signal dc collector current is 31 mA and the dc collector current with signal is 34 mA. Determine the percent second harmonic distortion.

UNIT – V

- 10 With neat circuit diagram, describe the operation of capacitance single tuned amplifier.

OR

- 11 (a) Explain about staggered tuned amplifiers.
(b) Describe briefly the effect of bandwidth of double tuned amplifier, when amplifiers are cascaded.

www.FirstRanker.com