

Code: 15A02601

B.Tech III Year II Semester (R15) Supplementary Examinations December/January 2018/19

**POWER SEMICONDUCTOR DRIVES**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

**PART – A**

(Compulsory Question)

\*\*\*\*\*

- 1 Answer the following: (10 X 02 = 20 Marks)
- (a) Write the basic performance equations of a DC series motor.
  - (b) Name some single phase DC drives.
  - (c) What is plugging?
  - (d) What are the steps to be followed to change the forward motoring mode of operation of DC motor to reverse motoring mode?
  - (e) What is a chopper?
  - (f) Draw the circuit diagram of a two quadrant chopper.
  - (g) List the various methods of speed control of a 3-phase induction motor when fed through semiconductor devices.
  - (h) What are the advantages of slip power recovery scheme?
  - (i) What is a cycloconverter?
  - (j) Mention the features of load commutated CSI fed synchronous motor.

**PART – B**

(Answer all five units, 5 X 10 = 50 Marks)

**UNIT – I**

- 2 Describe with appropriate voltage and current waveforms, the working of a single-phase full-converter fed dc drive. Derive the expression for its input power factor.

**OR**

- 3 The speed of a DC series motor is controlled by a 3-phase semi converter connected to 3- $\phi$ , 400 V, 50 Hz source. The motor constant is 0.4 V.s/A.rad. Total field and armature resistance is 1  $\Omega$ . Assuming continuous and ripple free armature current at a firing angle of 40° and speed of 1000 rpm, determine: (i) Motor current and motor torque. (ii) Power delivered to motor. (iii) Reactive power drawn from the supply.

**UNIT – II**

- 4 With a neat circuit diagram, explain the four quadrant operation of DC motor fed by dual converter?

**OR**

- 5 What is regenerative braking? Describe the regenerative braking of separately excited DC motor fed by a suitable power converter. Draw relevant circuit diagram and waveforms.

**UNIT – III**

- 6 Obtain the speed torque expressions of a chopper fed separately excited DC motor. Also draw and explain the speed torque characteristics.

**OR**

- 7 Explain the working two quadrant chopper fed DC series excited motor. Draw relevant circuit diagram and waveforms.

Contd. in page 2

**UNIT – IV**

- 8 Write short note on the following:
- (a) Vector control principle of induction motor.
  - (b) State rotor resistance control.

**OR**

- 9 (a) Draw neatly the block diagram of closed loop operation of induction motor drive.
- (b) Compare VSI and CSI.

**UNIT – V**

- 10 Elaborately explain about self control of synchronous motor.

**OR**

- 11 A 415 V, 50 Hz, 4-pole star connected synchronous motor has  $X_s = 1.5 \Omega$ . Load torque, proportional to speed is 300 Nm, at synchronous speed the speed of the motor is lowered by keeping v/f constant and maintaining 0.8 p.f leading for the motor operation at 840 rpm, determine:
- (i) Supply voltage.
  - (ii) Armature.
  - (iii) Excitation voltage.
  - (iv) Load angle.
  - (v) Pull-out torque. Neglect rotational losses.

\*\*\*\*\*

www.FirstRanker.com