

B.Tech IV Year I Semester (R15) Regular Examinations November/December 2018

FLEXIBLE AC TRANSMISSION SYSTEMS

(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- (a) Give the classification of FACTS controllers.
 - (b) What is a shunt controller?
 - (c) What are the advantages of using PWM techniques in converters?
 - (d) What are the limitations of using thyristor based converters in FACTS?
 - (e) What are the objectives of shunt compensation?
 - (f) What are hybrid VAR generators?
 - (g) How do prevent the occurrence of resonance in TCSC operation?
 - (h) What is the difference between GCSC and TCSC?
 - (i) What are the multiple functionalities of UPFC?
 - (j) What is IPFC?

PART – B

(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- 2 Discuss in detail about the benefits of FACTS controllers.

OR

- 3 (a) Explain the various stability metrics to the considered in transmission systems.
(b) Write short note on combined shunt and series controllers.

UNIT – II

- 4 With a circuit diagram, explain the 48-pulse operation of the converter. Also explain the transformer connections for 48-pulse operation.

OR

- 5 (a) Distinguish between voltage source and current sourced converters.
(b) Write short notes on PWM converters.

UNIT – III

- 6 Discuss in detail the various methods of controllable VAR generation.

OR

- 7 Discuss the comparison between STATCOM and SVC.

UNIT – IV

- 8 Elaborately explain the various objectives of series compensation.

OR

- 9 Write detailed notes on the following: (i) TSSC. (ii) SSSC.

UNIT – V

- 10 With a neat schematic diagram, explain the real and reactive power control of transmission system using UPFC.

OR

- 11 Explain the basic operating principles and transmission control capabilities of UPFC.
