

Code No: 113AU

**R13****JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B.Tech II Year I Semester Examinations, November - 2015****ELECTRONIC DEVICES AND CIRCUITS****(Common to EEE, ECE, CSE, EIE, BME, IT, MCT, ETM)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

**PART- A****(25 Marks)**

- 1.a) Define Static and Dynamic Resistances. [2M]
- b) Draw V-I characteristics curve of photo diode. [3M]
- c) Explain how PN junction diode acts as a Rectifier. [2M]
- d) Explain the regulation characteristics of Zener diode. [3M]
- e) What is a transistor? Explain about its operation. [2M]
- f) Explain how transistor works as an amplifier. [3M]
- g) Describe the need of biasing. [2M]
- h) Explain thermal Runaway. [3M]
- i) Differences between FET and MOSFET. [2M]
- j) Why we call FET as a Voltage Controlled Device. [3M]

**PART-B****(50 Marks)**

- 2.a) What is Tunnel diode? Explain its characteristics with the help of energy band diagrams.
- b) Derive the expression for transition capacitance of a diode. [5+5]

**OR**

- 3.a) Explain about Avalanche and Zener Breakdowns in PN junction diode.
- b) Draw the equivalent circuit of a varactor diode. [6+4]
- 4.a) A sinusoidal voltage whose  $V_m=24V$  is applied to half-wave rectifier. The diode may be considered to be ideal and  $R_L=1.8K\Omega$  is connected as load. Find out peak value of current, RMS value of Current, DC value of current and Ripple factor.
- b) Compare HWR, FWR and Bridge rectifier. [6+4]

**OR**

- 5.a) Explain the operation of Full Wave Rectifier with necessary graphs and calculate the efficiency and Ripple factor of it.
- b) Explain the necessity of filter circuit after the rectifier circuit. [6+4]
- 6.a) Compare CB, CE and CC Transistor configurations.
- b) Explain the operation of CB Configuration of BJT and its input and output Characteristics briefly. [5+5]

**OR**

- 7.a) A transistor with  $\alpha = 0.985$  has a reverse saturation current of  $2\mu A$  in CB configuration. Calculate the value of leakage current in the CE configuration. Also find the collector current and the emitter current if the value of base current is  $25\mu A$ .
- b) Describe about Early Effect. [7+3]

- 8.a) If the various parameters of a CE amplifier which uses the self bias method are  $V_{CC}=12V$ ,  $R_1=10K\Omega$ ,  $R_2=5K\Omega$ ,  $R_C=1K\Omega$ ,  $R_E=2K\Omega$  and  $\beta=100$ , find:
- i) The coordinates of the operating point and
  - ii) The stability factor, assuming the transistor to be of silicon.
- b) Explain in brief about Thermal stability. [7+3]
- OR**
- 9.a) Draw the circuit diagram of a collector to base bias circuit of CE amplifier and derive expression for Stability factor.
- b) Derive the operating point using AC and DC load lines. [5+5]
- 10.a) Draw the circuit diagram of Common Drain amplifier and derive expressions for voltage gain and input resistance.
- b) Derive the relation between  $g_m$ ,  $\mu$  and  $r_d$ . [5+5]
- OR**
- 11.a) Explain the drain and transfer characteristics of N-channel JFET.
- b) Explain the operation Enhancement mode MOSFET in detail. [5+5]

---ooOoo---