

**R13**

Code No: 114AC

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**

**B.Tech II Year II Semester Examinations, May - 2015**

**NETWORK THEORY**

(Electrical and Electronics Engineering)

**Time: 3 Hours**

**Max. Marks: 75**

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.


Each question carries 10 marks and may have a, b, c as sub questions.

**PART- A**

**(25 Marks)**


- 1.a) Two watt meters connected to a 3-phase motor indicate the total power input to be 12 kW. The power factor is 0.6. Determine the readings of each watt meter. [2M]

- b) If  $V_{ab} = 240 \text{ V} \angle 15^\circ$  for the circuit shown figure 1 below, what is the value of  $I_{ab}$ . [3M]

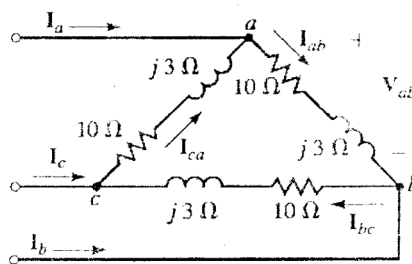


**Figure: 1**

- c) In the circuit shown figure 2, the capacitor voltage just before  $t = 0$  is [2M]

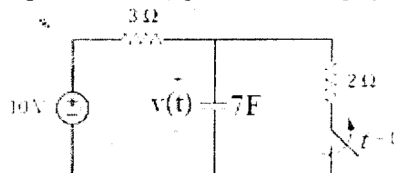

**Figure: 2**

- d) The switch in the figure 3 has been open for a long time. It is open at  $t = 0$ , the value of  $v(\infty)$ . [3M]

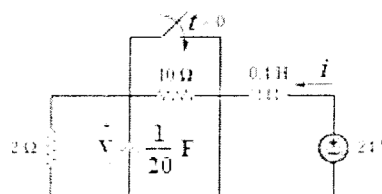

**Figure: 3**

- e) A function is given by  $Z(s) = \frac{2s}{s^2 + 16}$ . Draw its pole-zero plot. [2M]
- f) List the conditions for location of poles and zeros of driving point functions. [3M]
- g) In a two port network, obtain the condition for reciprocity in terms of H parameters. [2M]
- h) A two-port network is described by  $V_1 = I_1 + 2V_2$  and  $I_2 = -2I_1 + 0.4V_2$ . Find the Impedance matrix? [3M]

- i) A voltage source supplies a signal of constant amplitude, from 0 to 40 kHz, to an RC low-pass filter. The load resistor experiences the maximum voltage at which frequency? [2M]
- j) State and explain time duality property of Fourier transform. [3M]


**PART-B**

(50 Marks)

- 2.a) A balanced delta-connected load has a phase current  $I_{AC} = 10\angle -30^\circ$  A:
  - i) Determine the three line currents assuming that the circuit operates in the positive phase sequence.
  - ii) Calculate the load impedance if the line voltage is  $V_{AB} = 110\angle 0^\circ$  V.
- b) A balanced star-connected load absorbs a total power of 5 KW at a leading power factor of 0.6 when connected to a line voltage of 240 V. Find the impedance of each phase and the total complex power of the load. [5+5]


**OR**

- 3.a) The unbalanced  $\Delta$ -load as shown in Figure 4 below is supplied by balanced voltages of 200V in the positive sequence. Find the line currents. Take  $V_{ab}$  as reference.

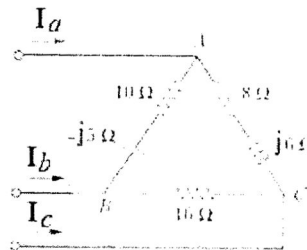


**Figure: 4**

- b) Prove that two watt-meters are sufficient to measure power in three phase system. [6+4]
- 4.a) The switch in the figure 5 has been in position *a* for a long time, At  $t = 4$  s the switch is moved to position *b* and left there. Determine  $v(t)$  at  $t = 10$  s.

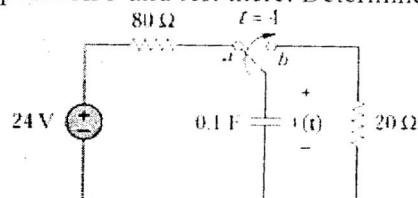

**Figure: 5**

- b) The switch in Figure 6 was open for a long time but closed at  $t = 0$ . Determine: (i)  $i(0+)$ ,  $v(0+)$ , (ii)  $i(\infty)$ ,  $v(\infty)$ . [4+6]

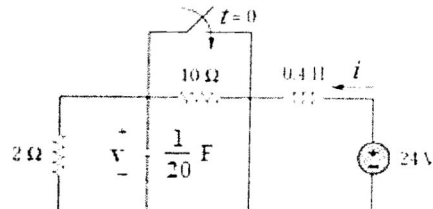

**Figure: 6**

**OR**

- 5.a) The switch in Figure 7 has been in position A for a long time. At  $t = 0$ , the switch moves to B. Determine  $v(t)$  for  $t > 0$  and calculate its value at  $t = 1$  s and 4 s.

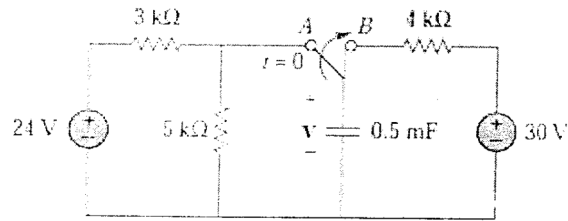


Figure: 7

- b) At  $t = 0$ , switch 1 in Figure 8 is closed, and switch 2 is closed 4 s later. Find  $i(t)$  for  $t > 0$ . Calculate  $i$  for  $t = 2$  s and  $t = 5$  s. [5+5]

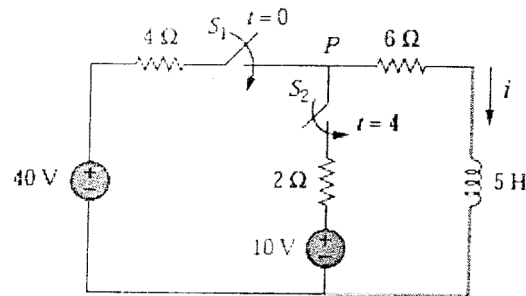


Figure: 8

6. What is the driving point and transfer impedance of the network shown figure 9 below? [10]

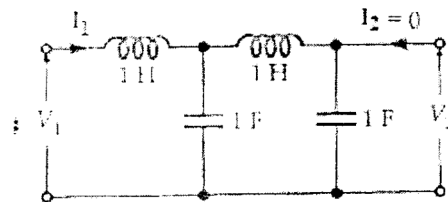


Figure: 9  
OR

- 7.a) Find the expression for voltage transformation ratio for the network shown figure 10 below.

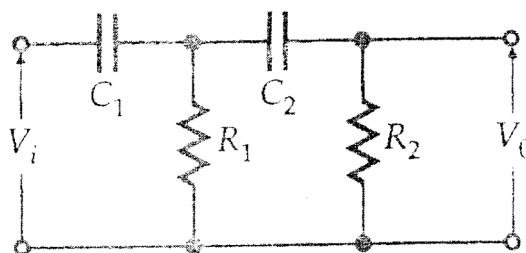


Figure: 10

- b) Find the pole- zero plots of the driving point and transfer impedances of the network shown figure 11 below. [5+5]

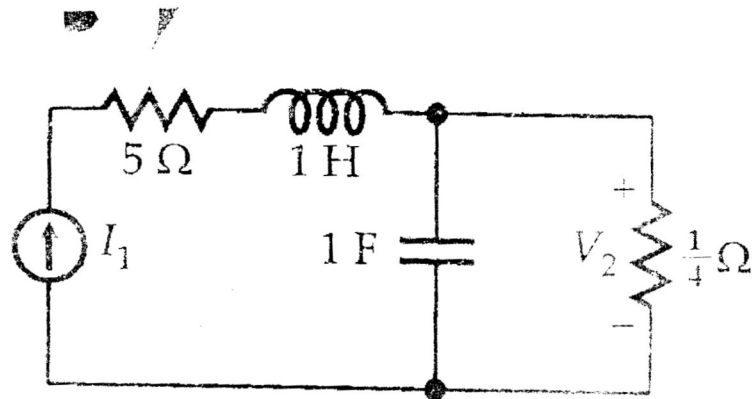


Figure: 11

- 8.a) Determine the  $h$  parameters for the circuit shown figure 12 below.

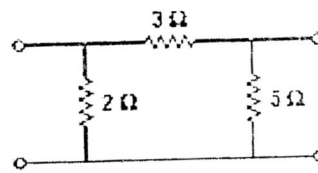


Figure: 12

- b) Determine  $[y]$  and  $[T]$  of a two-port network shown in figure 13 whose  $z$  parameters are  $Z = \begin{bmatrix} 6 & 4 \\ 4 & 6 \end{bmatrix}$ . [5+5]

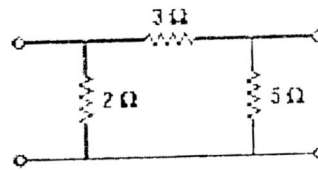


Figure: 13  
OR

- 9.a) Find the  $y$  parameters of the two-port network shown figure 14 below.

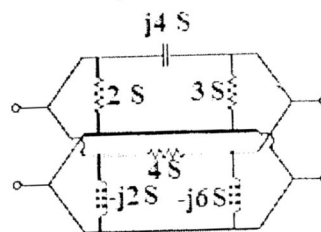


Figure: 14

- b) Find the impedance-parameter equivalent of the circuit shown figure 15 below. [6+4]

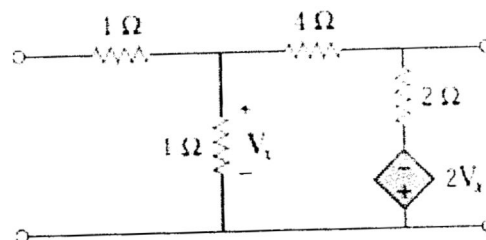


Figure: 15

- 10.a) A filter section is to have a characteristic impedance at zero frequency of  $600 \Omega$  and a cut-off frequency at 5 MHz. Design (a) a low-pass T section filter, and (b) a low-pass  $\pi$  section filter to meet these requirements.
- b) Calculate the Fourier series for the function shown in figure 16 below. [5+5]

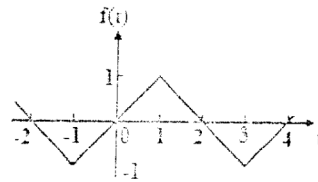


Figure: 16  
OR

- 11.a) A filter is required to pass all frequencies above 25 kHz and to have a nominal impedance of  $600 \Omega$ . Design (i) a high-pass T section filter and (ii) a high-pass  $\pi$  section filter to meet these requirements.
- b) Using the Fourier transform method, find  $i_o(t)$ , when  $i_s(t) = 10 \sin 2t$  A (Figure 17). [5+5]

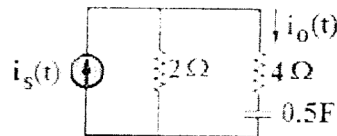


Figure: 17

---ooOoo---