

R13

Code No: 115AH

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B. Tech III Year I Semester Examinations, November - 2015****IC APPLICATIONS****(Electrical and Electronics Engineering)****Time: 3 hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART - A (25 Marks)

- 1.a) Give the characteristics of TTL family. [2]
- b) Draw a CMOS tri state buffer and explain. [3]
- c) What do you mean by voltage regulator? Discuss the types in it. [2]
- d) Discuss the following: input bias current, input off set current and thermal drift. [3]
- e) Design a notch filter to eliminate 120Hz signal. [2]
- f) What are the advantages of active filter over passive filter? [3]
- g) What are the features of 555 timers? [2]
- h) Explain the importance of control voltage pin 5 of the timer 555. [3]
- i) An 8 bit successive approximation type ADC is driven by a 1MHz clock. Find the conversion time. [2]
- j) What are the different sources of errors in DAC? [3]

PART - B (50 Marks)

- 2.a) Explain the operation and use a TTL gate with an open-collector output.
- b) Discuss the logic levels and noise margin with reference to TTL family. [5+5]

OR

- 3.a) Explain the operation of the CMOS gate with open drain output.
- b) Draw a standard two input TTL NAND gate and explain the operation. [5+5]

- 4.a) The input signal V_i to an op amp is $0.04 \sin 1.13 \times 10^5 t$ is to be amplified to the maximum extent. How much maximum gain can be had by using op amp with a slew rate of 0.4V/sec.

- b) Explain how the op amp is used as I-V converter. [5+5]

OR

- 5.a) Explain and draw the output waveforms of the ideal integrator circuit when the input is i) sine wave ii) square wave and iii) step input.
- b) Design a op amp circuit which can give the output as $V_0 = 2V_1 - 3V_2 + 4V_3 - 5V_4$. [5+5]

- 6.a) Design a phase shift oscillator to have output frequency of 500Hz. Use $\pm 12V$ supply.
- b) Draw and analyze the second order low pass Butterworth filter. [5+5]

OR

- 7.a) Explain with the help of the neat diagram and waveforms working of triangular wave generator.
- b) Discuss the applications of VCO. [5+5]

- 8.a) Design a 555 based square wave generator to produce a symmetrical square wave of 1KHz. If $V_{CC}=12V$ draw the voltage across timing capacitor and the output. [5+5]
b) Give the applications of Astable multivibrator. [5+5]

OR

- 9.a) Derive the Lock range and capture range in PLL. [5+5]
b) Explain the PLL as a FM detector. [5+5]

- 10.a) Explain the working of weighted resistor D/A converter and state its features. [5+5]
b) Find the resolution of a 12 bit D/A converter. [5+5]

OR

- 11.a) Explain the working of dual slope A/D converter. [5+5]
b) Draw the IC 1408 DAC pin diagram and explain. [5+5]

---ooOoo---